

EECS150 - Digital Design
Lecture 19 - Combinational Logic
Circuits : A Deep Dive


March 30, 2010
John Wawrzynek

Boolean Algebra I
(Representations of Combinational
Logic Circuits)

Outline

- Review of three representations for combinational logic:
 - truth tables,
 - graphical (logic gates), and
 - algebraic equations
- Relationship among the three
- Adder example
- Laws of Boolean Algebra
- Canonical Forms
- Boolean Simplification

Combinational Logic (CL) Defined

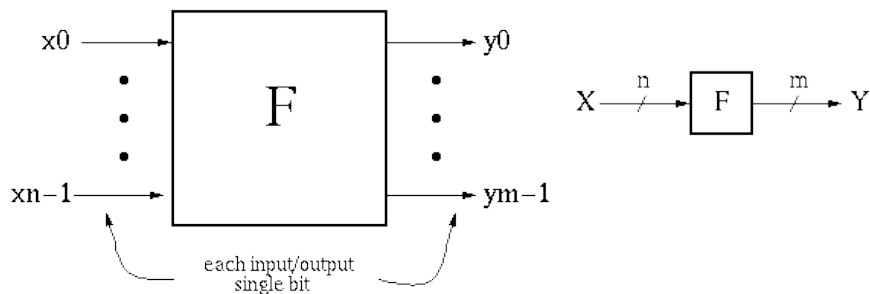


$y_i = f_i(x_0, \dots, x_{n-1})$, where x, y are $\{0,1\}$.

Y is a function of only X .

- If we change X , Y will change immediately (well almost!).
- There is an implementation dependent delay from X to Y .

CL Block Example #1

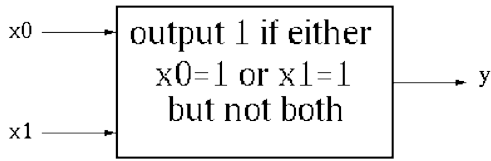


Boolean Equation:

$$y_0 = [x_0 \text{ AND not}\{x_1\}] \\ \text{OR } [\text{not}\{x_0\} \text{ AND } x_1] \\ y_0 = x_0x_1' + x_0'x_1$$

Truth Table Description:

x0	x1	y
0	0	0
0	1	1
1	0	1
1	1	0

Gate Representation:

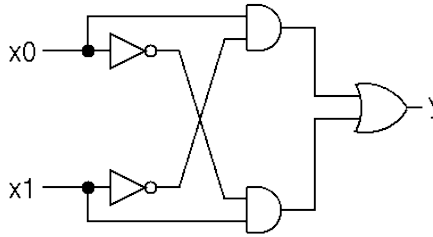

How would we *prove* that all three representations are equivalent?

Boolean Algebra/Logic Circuits

- Why are they called "logic circuits"?
- Logic: The study of the principles of reasoning.
- The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
- His variables took on TRUE, FALSE
- Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits:
- Primitive functions of Boolean Algebra:



a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1



a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1




a	NOT
0	1
1	0



Relationship Among Representations

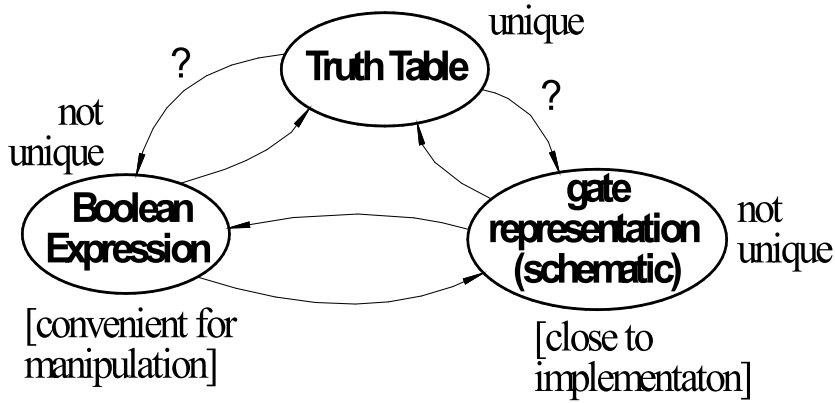
* Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



How do we convert from one to the other?

CL Block Example #2

• 4-bit adder:

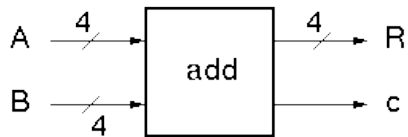

$R = A + B,$
c is carry out

• Truth Table Representation:

a3	a2	a1	a0	b3	b2	b1	b0	r3	r2	r1	r0	c
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	1	0	0	0
⋮												
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	0	0	0	1	1	0	1	0	1	0
⋮												
0	0	0	1	1	1	1	1	0	0	0	0	1

In general: 2^n rows for n inputs.

256 rows!

Is there a more efficient (compact) way to specify this function?

4-bit Adder Example

- Motivate the adder circuit design by hand addition:

$$\begin{array}{r} a_3 \ a_2 \ a_1 \ a_0 \\ + \ b_3 \ b_2 \ b_1 \ b_0 \\ \hline c \ r_3 \ r_2 \ r_1 \ r_0 \end{array}$$

$$\begin{array}{r} a_3 \ a_2 \ a_1 \ a_0 \\ + \ b_3 \ b_2 \ b_1 \ b_0 \\ \hline c \ r_3 \ r_2 \ r_1 \ r_0 \end{array}$$

- Add a_0 and b_0 as follows:

a	b	r	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

carry to next stage

$$r = a \text{ XOR } b = a \oplus b$$

$$c = a \text{ AND } b = ab$$

- Add a_1 and b_1 as follows:

c_i	a	b	r	c_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$r = a \oplus b \oplus c_i$$


$$c_o = ab + ac_i + bc_i$$

4-bit Adder Example

- In general:


$$r_i = a_i \oplus b_i \oplus c_{in}$$
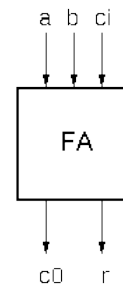
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



“Full adder cell”

- Now, the 4-bit adder:

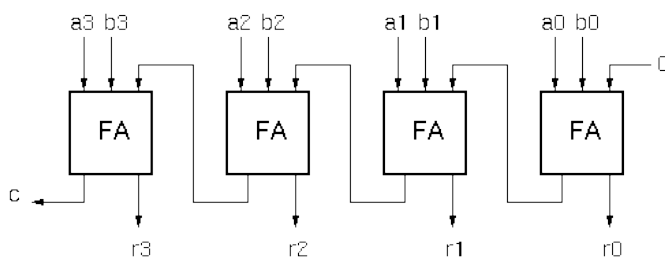


“ripple” adder

4-bit Adder Example

- Graphical Representation of FA-cell

$$r_i = a_i \oplus b_i \oplus c_{in}$$

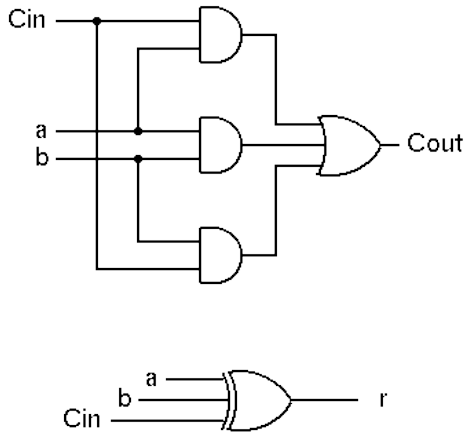
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in}$$



- Alternative Implementation (with 2-input gates):

$$r_i = [a_i \oplus b_i] \oplus c_{in}$$
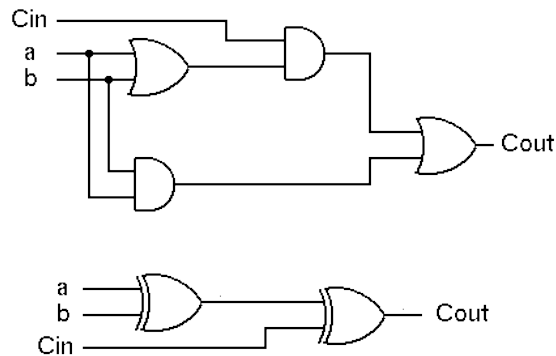
$$c_{out} = c_{in}[a_i + b_i] + a_i b_i$$



Boolean Algebra

Defined as:


Set of elements B , binary operators $\{+, \cdot\}$ unary operation $\{ '\}$ such that the following axioms hold:

- B contains at least two elements a, b such that $a \neq b$.
- Closure: a, b in B ,
 $a + b$ in B , $a \cdot b$ in B , a' in B .
- Commutative laws:
 $a + b = b + a$, $a \cdot b = b \cdot a$.
- Identities: $0, 1$ in B
 $a + 0 = a$, $a \cdot 1 = a$.
- Distributive laws:
 $a + (b \cdot c) = (a + b) \cdot (a + c)$, $a \cdot (b + c) = a \cdot b + a \cdot c$.
- Complement:
 $a + a' = 1$, $a \cdot a' = 0$.

Logic Functions

$B = \{0,1\}$, $+$ = OR, \cdot = AND, $'$ = NOT

is a valid Boolean Algebra.

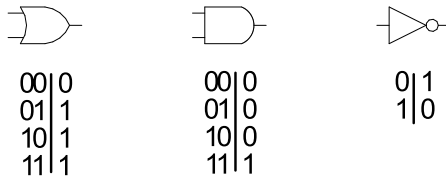


Do the axioms hold?

- Ex: communitive law: $0+1 = 1+0$?



Other logic functions of 2 variables (x,y)


xy	f0	f1													
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0
	0	AND	X	Y	\oplus	OR	NOR	XNOR	NAND						1

Look at NOR and NAND:

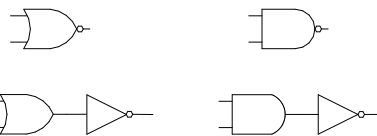

• **Theorem:** Any Boolean function that can be expressed as a truth table can be expressed using NAND and NOR.

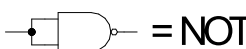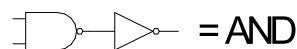- Proof sketch:  = NOT  = AND

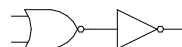 = OR

- How would you show that either NAND or NOR is sufficient?

Laws of Boolean Algebra

Duality: A dual of a Boolean expression is derived by interchanging OR and AND operations, and 0s and 1s (literals are left unchanged).

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)\}$$

Any law that is true for an expression is also true for its dual.

Operations with 0 and 1:

$$\begin{aligned} 1. x + 0 &= x & x \bullet 1 &= x \\ 2. x + 1 &= 1 & x \bullet 0 &= 0 \end{aligned}$$

Idempotent Law:

$$3. x + x = x \quad x \bullet x = x$$

Involution Law:

$$4. [x']' = x$$

Laws of Complementarity:

$$5. x + x' = 1 \quad x \bullet x' = 0$$

Commutative Law:

$$6. x + y = y + x \quad x \bullet y = y \bullet x$$

Laws of Boolean Algebra (cont.)

Associative Laws:

$$(x + y) + z = x + (y + z) \quad x \bullet y \bullet z = x (y \bullet z)$$

Distributive Laws:

$$x (y + z) = (x \bullet y) + (x \bullet z) \quad x + (y \bullet z) = (x + y)(x + z)$$

"Simplification" Theorems:

$$\begin{aligned} x \bullet y + x \bullet y' &= x & (x + y) (x + y') &= x \\ x + x \bullet y &= x & x (x + y) &= x \end{aligned}$$

DeMorgan's Law:

$$(x + y + z + \dots)' = x' y' z' \quad (x \bullet y \bullet z \dots)' = x' + y' + z'$$

Theorem for Multiplying and Factoring:

$$(x + y) (x' + z) = x \bullet z + x' \bullet y$$

Consensus Theorem:

$$\begin{aligned} x \bullet y + y \bullet z + x' \bullet z &= (x + y) (y + z) (x' + z) \\ x \bullet y + x' \bullet z &= (x + y) (x' + z) \end{aligned}$$

Proving Theorems via axioms of Boolean Algebra

Ex: prove the theorem: $x y + x y' = x$

$x y + x y' = x (y + y')$ distributive law

$x (y + y') = x (1)$ complementary law

$x (1) = x$ identity

Ex: prove the theorem: $x + x y = x$

$x + x y = x 1 + x y$ identity


$x 1 + x y = x (1 + y)$ distributive law

$x (1 + y) = x (1)$ identity

$x (1) = x$ identity

DeMorgan's Law


$$(x + y)' = x' y'$$

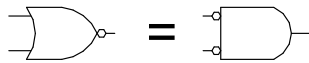

Exhaustive Proof

x	y	x'	y'	(x+y)'	x'y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

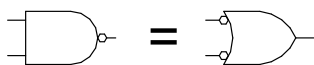


Exhaustive Proof

x	y	x'	y'	(xy)'	x'+y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Relationship Among Representations

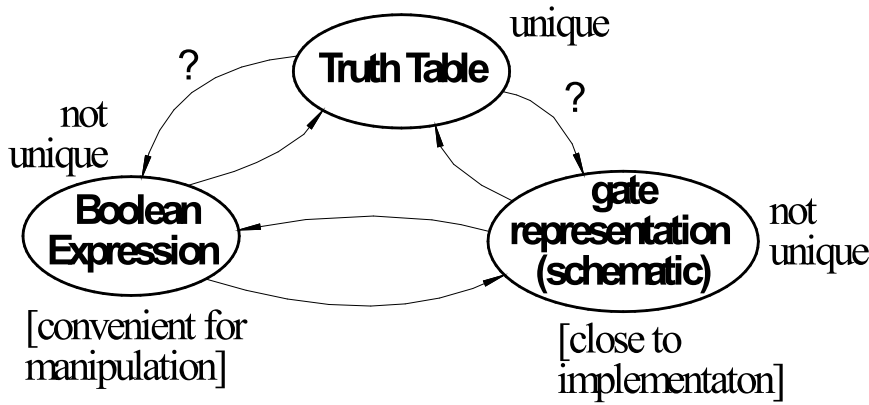- * Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



How do we convert from one to the other?

Canonical Forms

- Standard form for a Boolean expression - unique algebraic expression directly from a true table (TT) description.
- Two Types:
 - * Sum of Products (SOP)
 - * Product of Sums (POS)
- **Sum of Products** (disjunctive normal form, minterm expansion).

Example:

minterms	a b c	f f'
a'b'c'	0 0 0	0 1
a'b'c	0 0 1	0 1
a'bc'	0 1 0	0 1
a'bc	0 1 1	1 0
ab'c'	1 0 0	1 0
ab'c	1 0 1	1 0
abc'	1 1 0	1 0
abc	1 1 1	1 0

One product (**and**) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

Sum of Products (cont.)

Canonical Forms are usually not minimal:

Our Example:

$$\begin{aligned}
 f &= a'bc + ab'c' + ab'c + abc' + abc \quad (xy' + xy = x) \\
 &= a'bc + ab' + ab \\
 &= a'bc + a \quad (x'y + x = y + x) \\
 &= a + bc
 \end{aligned}$$

$$\begin{aligned}
 f' &= a'b'c' + a'b'c + a'bc' \\
 &= a'b' + a'bc' \\
 &= a' (b' + bc') \\
 &= a' (b' + c')
 \end{aligned}$$

Spring 2010

EECS150 - Lec19-cl1

Page 21

Canonical Forms

- **Product of Sums** (conjunctive normal form, maxterm expansion). Example:

maxterms	a	b	c	f	f'
a+b+c	0	0	0	0	1
a+b+c'	0	0	1	0	1
a+b'+c	0	1	0	0	1
a+b'+c'	0	1	1	1	0
a'+b+c	1	0	0	1	0
a'+b+c'	1	0	1	1	0
a'+b'+c	1	1	0	1	0
a'+b'+c'	1	1	1	1	0

One sum (**or**) term for each 0 in f:

$$f = (a+b+c)(a+b+c')(a+b'+c)$$

$$f' = (a+b'+c')(a'+b+c)(a'+b+c')$$

$$(a'+b'+c)(a+b+c')$$

Mapping from SOP to POS (or POS to SOP): Derive truth table then proceed.

Spring 2010

EECS150 - Lec19-cl1

Page 22

Algebraic Simplification Example

Ex: full adder (FA) carry out function (in canonical form):

$$C_{out} = a'bc + ab'c + abc' + abc$$

Algebraic Simplification

$$\begin{aligned} C_{out} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + \mathbf{abc} + \mathbf{abc} \\ &= a'bc + \mathbf{abc} + ab'c + abc' + \mathbf{abc} \\ &= \mathbf{(a' + a)bc} + ab'c + abc' + abc \\ &= \mathbf{(1)bc} + ab'c + abc' + abc \\ &= bc + ab'c + abc' + \mathbf{abc} + \mathbf{abc} \\ &= bc + ab'c + \mathbf{abc} + abc' + \mathbf{abc} \\ &= bc + \mathbf{a(b' + b)c} + abc' + abc \\ &= bc + \mathbf{a(1)c} + abc' + abc \\ &= bc + ac + \mathbf{ab(c' + c)} \\ &= bc + ac + \mathbf{ab(1)} \\ &= bc + ac + ab \end{aligned}$$

Outline for remaining CL Topics

- K-map method of two-level logic simplification
- Multi-level Logic
- NAND/NOR networks
- EXOR revisited

Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

ab	f
00	0
01	0
10	1
11	1

$$f = ab' + ab = a(b' + b) = a$$

b values change within the on-set rows

a values don't change

b is eliminated, a remains

ab	g
00	1
01	0
10	1
11	0

$$g = a'b' + ab' = (a' + a)b' = b'$$

b values stay the same

a values changes

b' remains, a is eliminated


Boolean Cubes

Visual technique for identifying when the Uniting Theorem can be applied


Alternative way to represent boolean functions.

Filled in nodes represent a 1 in the function.

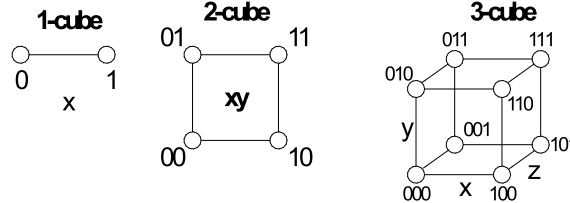Moving between adjacent nodes represents changing only one input.



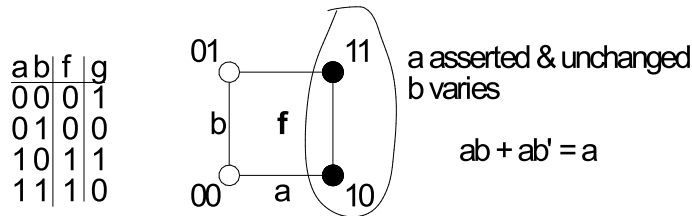
- Sub-cubes of on-nodes can be used for simplification.
 - On-set: filled in nodes, off-set: empty nodes




3-variable cube example

FA carry out:

a	b	c	cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

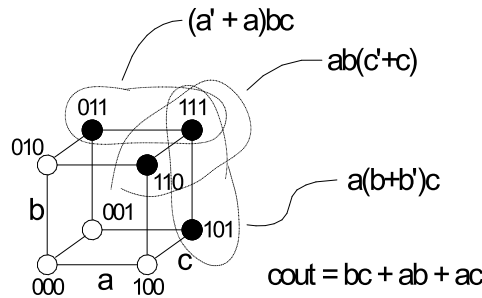

What about larger sub-cubes?

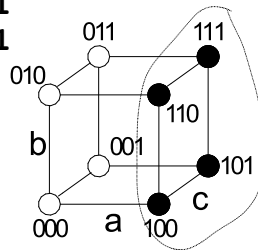


$$ab'c' + ab'c + abc' + abc$$

$$ac' + ac + ab = a + ab = a$$

- Both b & c change, a is asserted & remains constant.


Karnaugh Map Method

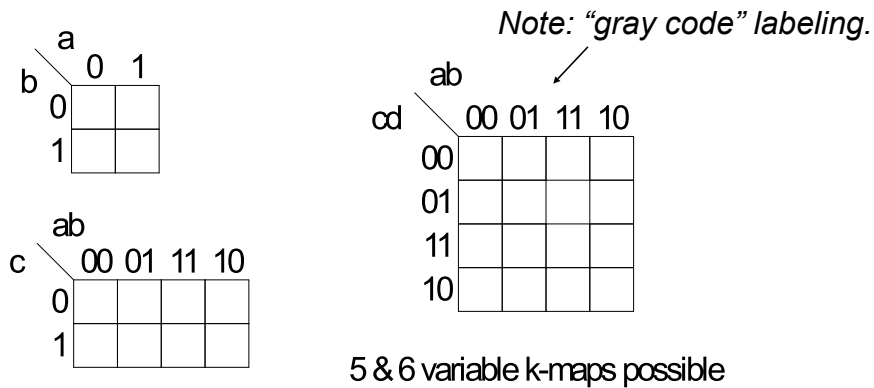- K-map is an alternative method of representing the TT and to help visual the adjacencies.



Karnaugh Map Method

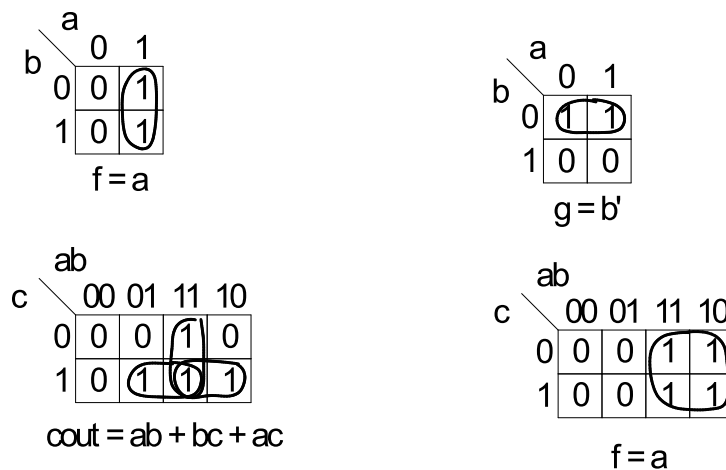- Adjacent groups of 1's represent product terms



K-map Simplification

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
 - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
 - ✓ Form as large as possible groups and as few groups as possible.
 - ✓ Groups can overlap (this helps make larger groups)
 - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

31

K-maps (cont.)

		ab			
		00	01	11	10
c	0	1	0	0	1
	1	0	0	1	1

$$f = b'c' + ac$$

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = c + a'bd + b'd'$$

(bigger groups are better)

Product-of-Sums Version

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.


		ab			
	cd	00	01	11	10
00		1	0	0	1
01		0	1	0	0
11		1	1	1	1
10		1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$

BCD incremter example

Binary Coded Decimal

	a	b	c	d	w	x	y	z
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	0	0	0	0
	1	0	1	0	-	-	-	-
	1	0	1	1	-	-	-	-
	1	1	0	0	-	-	-	-
	1	1	0	1	-	-	-	-
	1	1	1	0	-	-	-	-
	1	1	1	1	-	-	-	-

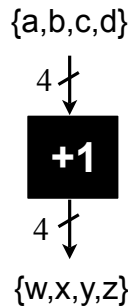

BCD Incrementer Example

- Note one map for each output variable.
- Function includes "don't cares" (shown as "-" in the table).
 - These correspond to places in the function where we don't care about its value, because we don't expect some particular input patterns.
 - We are free to assign either 0 or 1 to each don't care in the function, as a means to increase group sizes.
- In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

BCD incrementer example

	W	X	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 1	0 1 - 0	w =
01	0 0 - 0	0 1 - 0	
11	0 1 - -	1 0 - -	x =
10	0 0 - -	0 1 - -	
			y =
	y	Z	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 0	1 1 - 1	z =
01	1 1 - 0	0 0 - 0	
11	0 0 - -	0 0 - -	
10	1 1 - -	1 1 - -	

BCD Incrementer Example

- Note one map for each output variable.
- Function includes "don't cares" (shown as "-" in the table).
 - These correspond to places in the function where we don't care about its value, because we don't expect some particular input patterns.
 - We are free to assign either 0 or 1 to each don't care in the function, as a means to increase group sizes.
- In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

BCD incrementer example

		W		X	
	ab		ab		
cd	00	01	11	10	
00	0	0	-	1	w =
01	0	0	-	0	
11	0	1	-	-	
10	0	0	-	-	

		y		Z	
	ab		ab		
cd	00	01	11	10	
00	0	0	-	0	y =
01	1	1	-	0	
11	0	0	-	-	
10	1	1	-	-	

	ab		ab		
cd	00	01	11	10	
00	1	1	-	1	z =
01	0	0	-	0	
11	0	0	-	-	
10	1	1	-	-	

Higher Dimensional K-maps

