

EECS150 - Digital Design

Lecture 24 - Arithmetic Blocks,

Part 2 + Shifters


April 15, 2010
John Wawrzynek

Multiplication

		a_3	a_2	a_1	a_0	\leftarrow <i>Multiplicand</i>																						
		b_3	b_2	b_1	b_0	\leftarrow <i>Multiplier</i>																						
<table style="margin-left: auto; margin-right: auto; border-collapse: collapse;"> <tr> <td style="padding-right: 10px;">X</td> <td style="padding-right: 10px;">a_3b_0</td> <td style="padding-right: 10px;">a_2b_0</td> <td style="padding-right: 10px;">a_1b_0</td> <td style="padding-right: 10px;">a_0b_0</td> <td rowspan="4" style="font-size: 3em; vertical-align: middle; padding-left: 10px;">}</td> <td rowspan="4" style="vertical-align: middle;"><i>Partial products</i></td> </tr> <tr> <td></td> <td>a_3b_1</td> <td>a_2b_1</td> <td>a_1b_1</td> <td>a_0b_1</td> </tr> <tr> <td></td> <td>a_3b_2</td> <td>a_2b_2</td> <td>a_1b_2</td> <td>a_0b_2</td> </tr> <tr> <td></td> <td>a_3b_3</td> <td>a_2b_3</td> <td>a_1b_3</td> <td>a_0b_3</td> </tr> </table>							X	a_3b_0	a_2b_0	a_1b_0	a_0b_0	}	<i>Partial products</i>		a_3b_1	a_2b_1	a_1b_1	a_0b_1		a_3b_2	a_2b_2	a_1b_2	a_0b_2		a_3b_3	a_2b_3	a_1b_3	a_0b_3
X	a_3b_0	a_2b_0	a_1b_0	a_0b_0	}	<i>Partial products</i>																						
	a_3b_1	a_2b_1	a_1b_1	a_0b_1																								
	a_3b_2	a_2b_2	a_1b_2	a_0b_2																								
	a_3b_3	a_2b_3	a_1b_3	a_0b_3																								
	\dots	$a_1b_0 + a_0b_1$			a_0b_0	\leftarrow <i>Product</i>																						

*Many different circuits exist for multiplication.
Each one has a different balance between
speed (performance) and amount of logic (cost).*

“Shift and Add” Multiplier

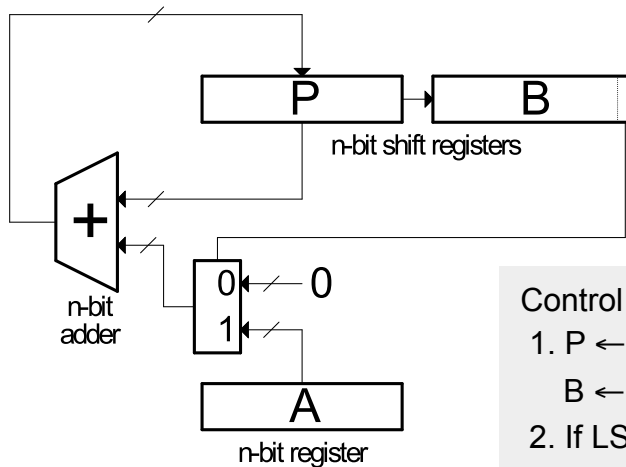

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of A or 0.

Control Algorithm:

1. $P \leftarrow 0$, $A \leftarrow$ multiplicand,
 $B \leftarrow$ multiplier
2. If LSB of $B=1$ then add A to P
else add 0
3. Shift $[P][B]$ right 1
4. Repeat steps 2 and 3 $n-1$ times.
5. $[P][B]$ has product.

- Cost $\propto n$, $T = n$ clock cycles.
- What is the critical path for determining the min clock period?

“Shift and Add” Multiplier

Signed Multiplication:

Remember for 2's complement numbers MSB has negative weight:


$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
 - a) subtract final partial product
 - b) sign-extend partial products
- Modifications to shift & add circuit:
 - a) adder/subtractor
 - b) sign-extender on P shifter register

Bit-serial Multiplier

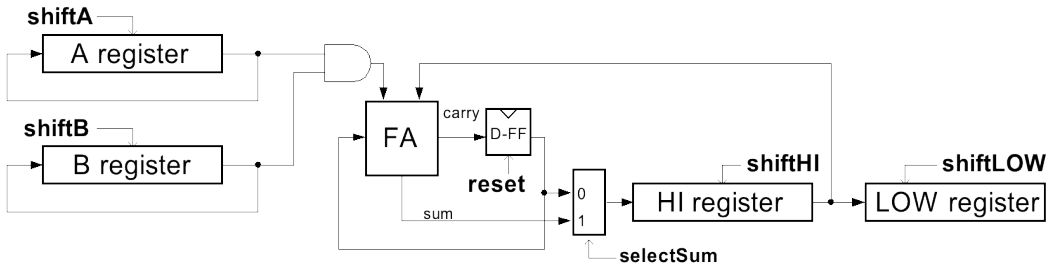- Bit-serial multiplier (n^2 cycles, one bit of result per n cycles):




- Control Algorithm:

```
repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}
```

Note: The occurrence of a control signal x means $x=1$. The absence of x means $x=0$.

Array Multiplier

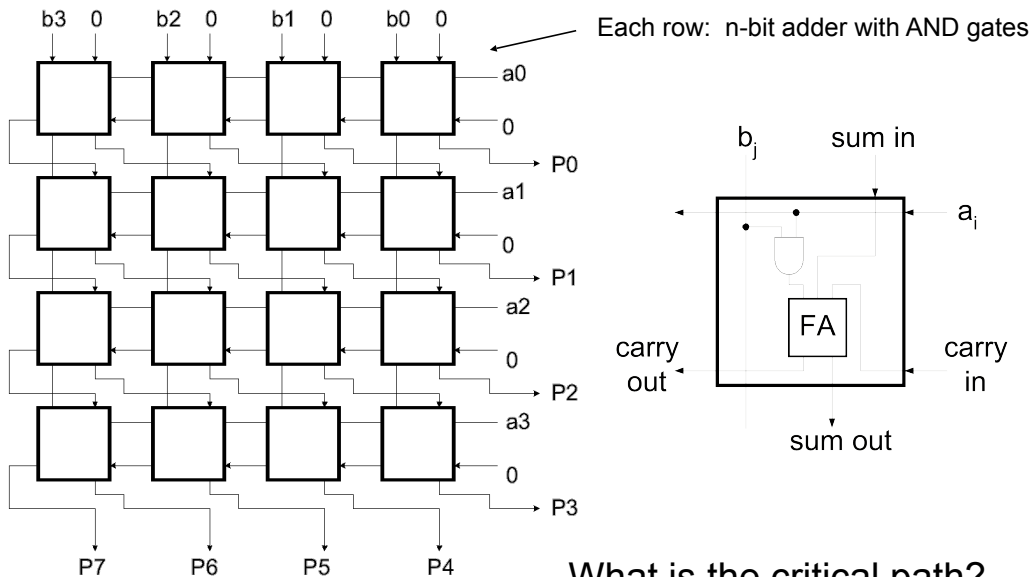Single cycle multiply: Generates all n partial products simultaneously.



What is the critical path?

Carry-Save Addition


- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.

$$\begin{array}{r}
 3_{10} \quad 0011 \\
 + 2_{10} \quad 0010 \\
 \hline
 c \quad 0100 = 4_{10} \\
 s \quad 0001 = 1_{10} \\
 \hline
 3_{10} \quad 0011 \\
 + \quad \quad \quad \\
 \hline
 c \quad 0010 = 2_{10} \\
 s \quad 0110 = 6_{10} \\
 \hline
 1000 = 8_{10}
 \end{array}$$

carry-save add (for the first two additions)
 carry-propagate add (for the final addition)


- In general, *carry-save* addition takes in 3 numbers and produces 2.
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition

Carry-save Circuits

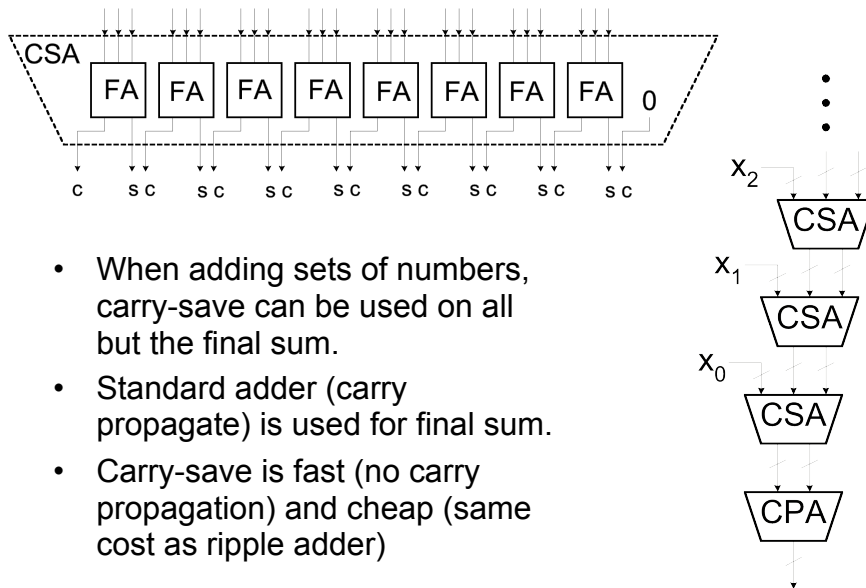

- When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.
- Carry-save is fast (no carry propagation) and cheap (same cost as ripple adder)

 
Array Multiplier using Carry-save Addition



Carry-save Addition

CSA is associative and commutitive. For example:
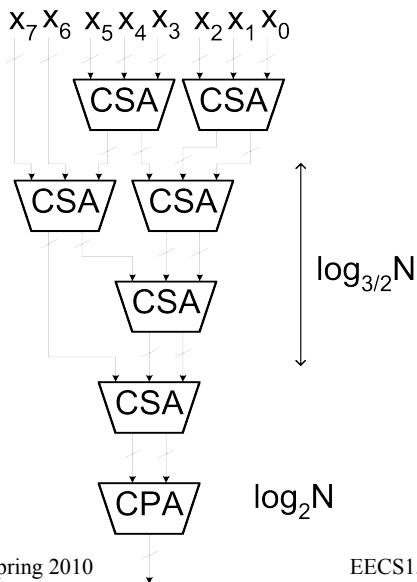
$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay.
- This structure is the basis of the **Wallace Tree Multiplier**.
- Partial products are summed with the CSA tree. Fast CPA (ex: CLA) is used for final sum.
- Multiplier delay $\alpha \log_{3/2} N + \log_2 N$

Constant Multiplication


- Our discussion so far has assumed both the multiplicand (A) and the multiplier (B) can vary at runtime.

- What if one of the two is a constant?

$$Y = C * X$$

- “Constant Coefficient” multiplication comes up often in signal processing and other hardware. Ex:

$$y_i = \alpha y_{i-1} + x_i$$

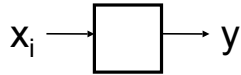


where α is an application dependent constant that is hard-wired into the circuit.

- How do we build an array style (combinational) multiplier that takes advantage of the constancy of one of the operands?

Multiplication by a Constant

 
- If the constant C in $C * X$ is a power of 2, then the multiplication is simply a shift of X.
- Ex: $4 * X$




- What about division?
- What about multiplication by non-powers of 2?

Multiplication by a Constant

 - In general, a combination of fixed shifts and addition:
 - Ex: $6 * X = 0110 * X = (2^2 + 2^1) * X$




– Details:

 

Multiplication by a Constant

 
- Another example: $C = 23_{10} = 010111$



- In general, the number of additions equals the number of 1's in the constant minus one.*
- Using carry-save adders (for all but one of these) helps reduce the delay and cost, but the number of adders is still the number of 1's in C minus 2.
- Is there a way to further reduce the number of adders (and thus the cost and delay)?

Multiplication using Subtraction

 - *Subtraction is ~ the same cost and delay as addition.*
- Consider $C \cdot X$ where C is the constant value $15_{10} = 01111$.
 $C \cdot X$ requires 3 additions.
- We can “recode” 15
 from $01111 = (2^3 + 2^2 + 2^1 + 2^0)$
 to $1000\bar{1} = (2^4 - 2^0)$
 where $\bar{1}$ means negative weight.
- Therefore, $15 \cdot X$ can be implemented with only one subtractor.



Canonic Signed Digit Representation

- CSD represents numbers using 1, $\bar{1}$, & 0 with the least possible number of non-zero digits.
 - Strings of 2 or more non-zero digits are replaced.
 - Leads to a unique representation.
- To form CSD representation might take 2 passes:
 - First pass: replace all occurrences of 2 or more 1's:
 $01..10$ by $10..\bar{1}0$
 - Second pass: same as above, plus replace $0\bar{1}10$ by $00\bar{1}0$
- Examples:

$$011101 = 29$$

$$100\bar{1}01 = 32 - 4 + 1$$

$$0010111 = 23$$

$$001100\bar{1}$$

$$010\bar{1}00\bar{1} = 32 - 8 - 1$$

$$0110110 = 54$$


$$10\bar{1}10\bar{1}0$$

$$100\bar{1}0\bar{1}0 = 64 - 8 - 2$$

- Can we further simplify the multiplier circuits?


“Constant Coefficient Multiplication” (KCM)

 Binary multiplier: $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$




- CSD helps, but the multipliers are limited to shifts followed by adds.

 – CSD multiplier: $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$



- How about shift/add/shift/add ...?

 – KCM multiplier: $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$



- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.


Fixed Shifters / Rotators

- “fixed” shifters “hardwire” the shift amount into the circuit.


- Ex: verilog: `X >> 2`
– (right shift X by 2 places)

- Fixed shift/rotator is nothing but wires!


So what?

 

Logical Shift

 


Rotate

 

Arithmetic Shift

Variable Shifters / Rotators

 
- Example: $X \gg S$, where S is unknown when we synthesize the circuit.
- Uses: shift instruction in processors (ARM includes a shift on every instruction), floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
 - a) Load word, b) shift enable for S cycles, c) read word.




- Worst case delay $O(N)$, not good for processor design.
- Can we do it in $O(\log N)$ time and fit it in one cycle?

Log Shifter / Rotator

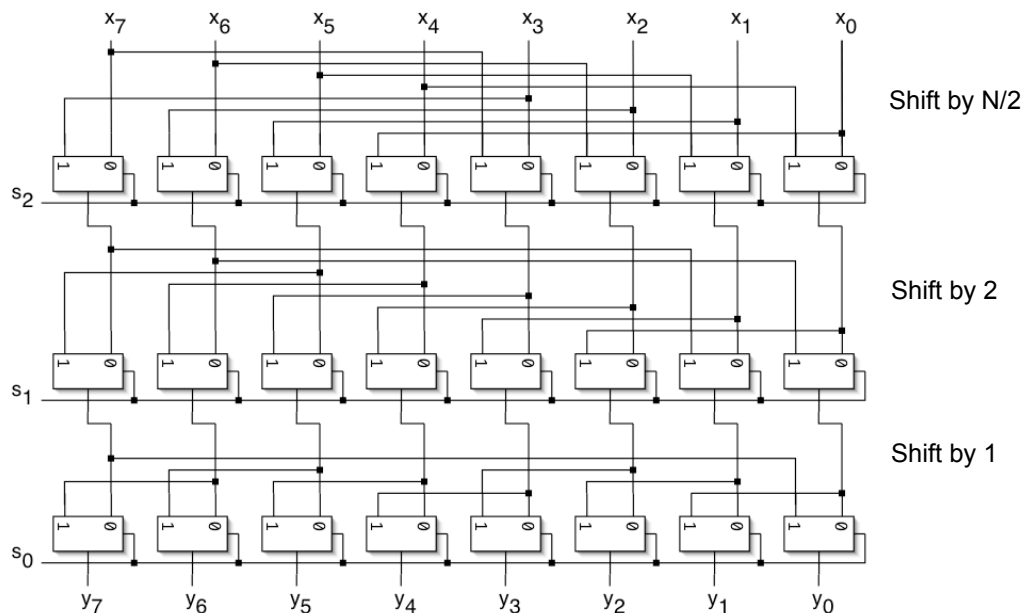- $\log(N)$ stages, each shifts (or not) by a power of 2 places,




LUT Mapping of Log shifter

 


Efficient with 2to1 multiplexors, for instance, 3LUTs.

 Virtex5 has 6LUTs. Naturally makes 4to1 muxes:




Reorganize shifter to use 4to1 muxes.

 


“Improved” Shifter / Rotator

 - How about this approach? Could it lead to even less delay?




- What is the delay of these big muxes?
- Look a transistor-level implementation?

Barrel Shifter

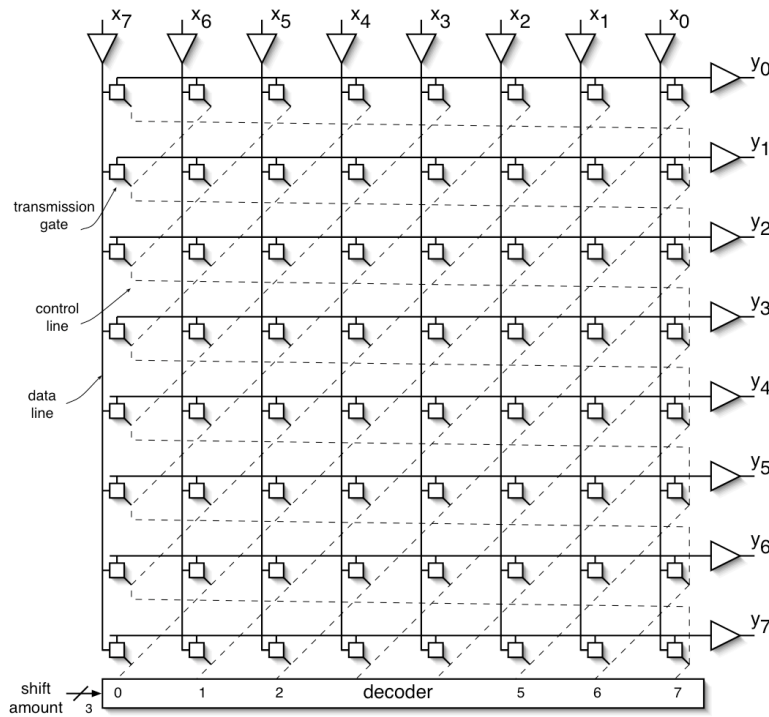

Cost/delay?
- (don't forget the decoder)


Connection Matrix

 

Generally useful structure:

- N^2 control points.
- What other interesting functions can it do?

Cross-bar Switch

 

- $N \log(N)$ control signals.
- Supports all interesting permutations
 - All one-to-one and one-to-many connections.
- Commonly used in communication hardware (switches, routers).