

University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science


EECS150, Spring 2010

Quiz 4: February 19th
Solution

The Verilog in this problem describes an FSM-like circuit with the following truth table:



in	cs	ns
0	0	1
0	1	1
1	0	1
1	1	0

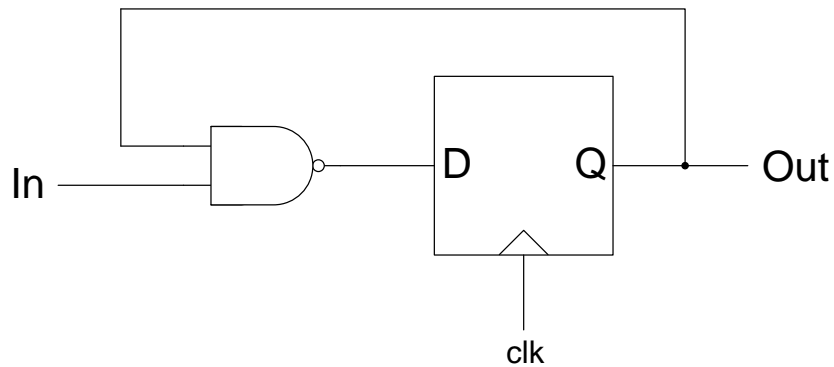Upon examining the truth table, you should see that `ns` can be described using a simple *nand* gate! Thus, in terms of transistors, we need to build the *nand* and a flip-flop (which is, itself, built out of latches, which are, themselves, built out of transmission gates and inverters). The final FSM is shown here:





And the components used to build it are shown (in hierarchal order) on the next page.



NAND Gate

  

Inverter

  

Latch

 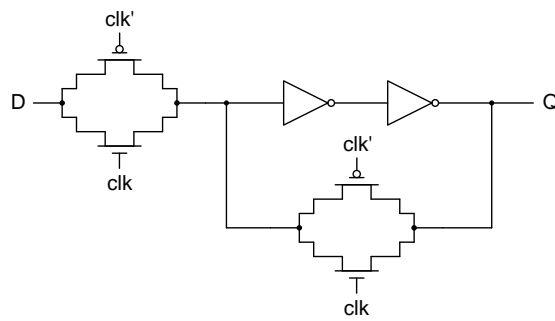

D-Q Flip-flop

