

NAND Gate



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

$$\text{Out} = \overline{A \cdot B}$$

