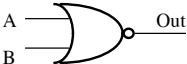


# NOR Gate



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0