
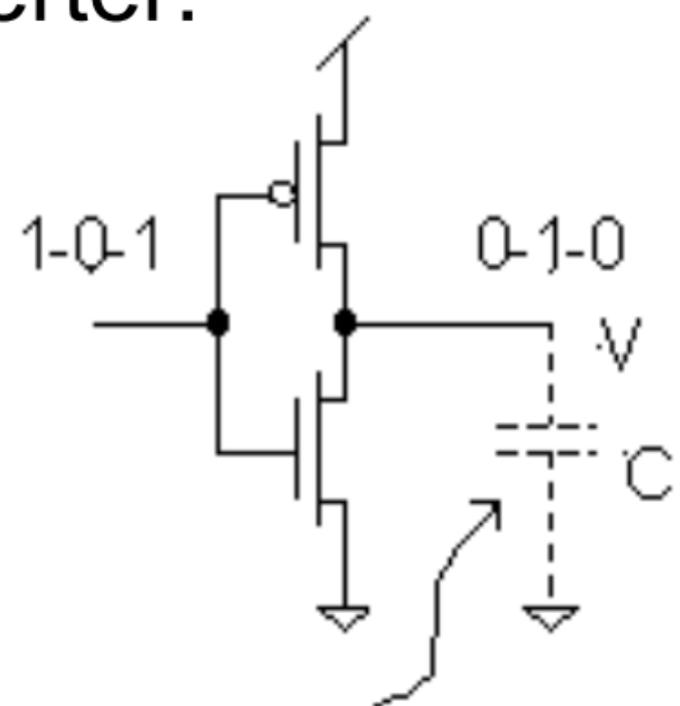


Inverter:

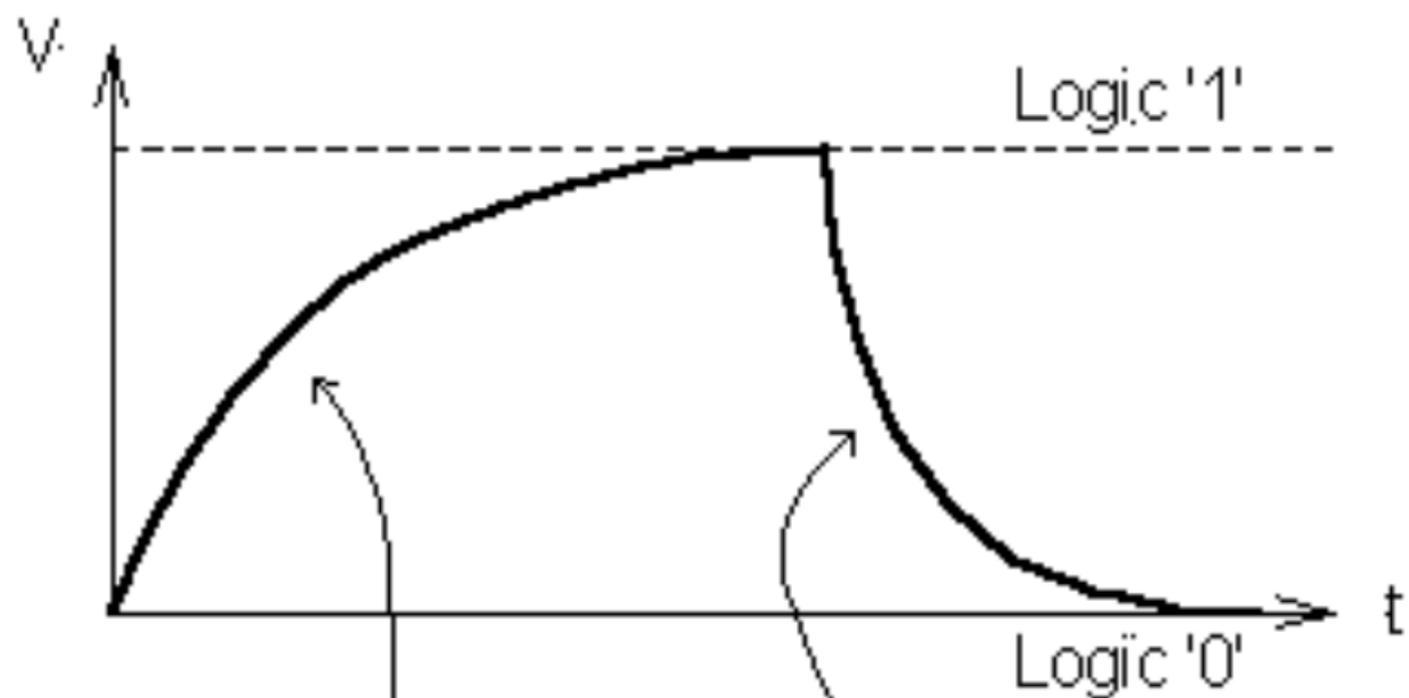

Models inputs to other gates & wire capacitance



rate dependent on pullup strength & C

rate dependent on pulldown strength & C