

inst.eecs.berkeley.edu/~cs61c

# UC Berkeley CS61C : Machine Structures

## Lecture 21 – State Elements : Circuits that Remember



2007-03-07

**“Mocha sipping” TA Valerie Ishida**

inst.eecs.berkeley.edu/~cs61c-td

**161 Exabytes In 2006 ⇒**

In 2006 we created, captured, and replicated 161 exabytes of digital information. The last time anyone tried to estimate global information volume, in 2003, researchers at UC Berkeley came up with 5 exabytes. By 2010 almost a zettabyte!



<http://hardware.slashdot.org/article.pl?sid=07/03/05/2355246>

# Review

---

- **ISA is very important abstraction layer**
  - **Contract between HW and SW**
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types of circuits:**
  - **Stateless Combinational Logic (&,|,~)**
  - **State circuits (e.g., registers)**



# Uses for State Elements

---


- 1. As a place to store values for some indeterminate amount of time:**
  - Register files (like \$1-\$31 on the MIPS)
  - Memory (caches, and main memory)
- 2. Help control the flow of information between combinational logic blocks.**
  - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.


 
# Accumulator Example

---

Why do we need to control the flow of information?



**Want:**

```
S = 0;  
for (i = 0; i < n; i++)  
    S = S + Xi
```


**Assume:**

- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S.



# First try...Does this work?

---

 


**Nope!**

**Reason #1... What is there to control the next iteration of the 'for' loop?**


**Reason #2... How do we say: 's=0'?**



# Second try...How about this?

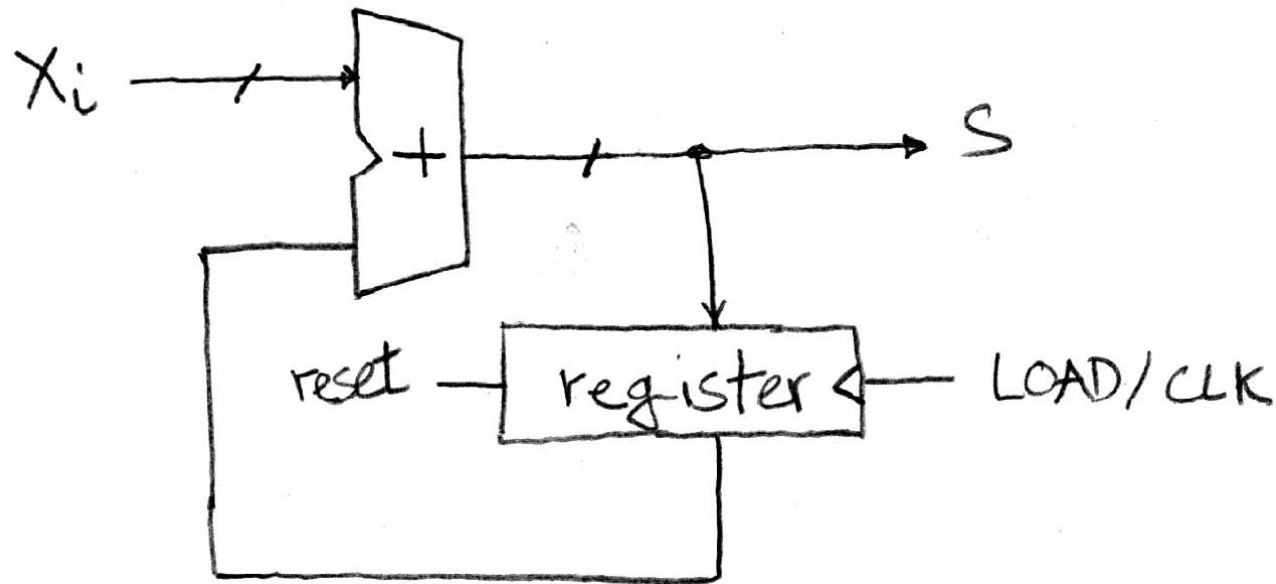


Rough  
timing...

 

Register is used to hold up the transfer of data to adder.



# Register Details...What's inside?

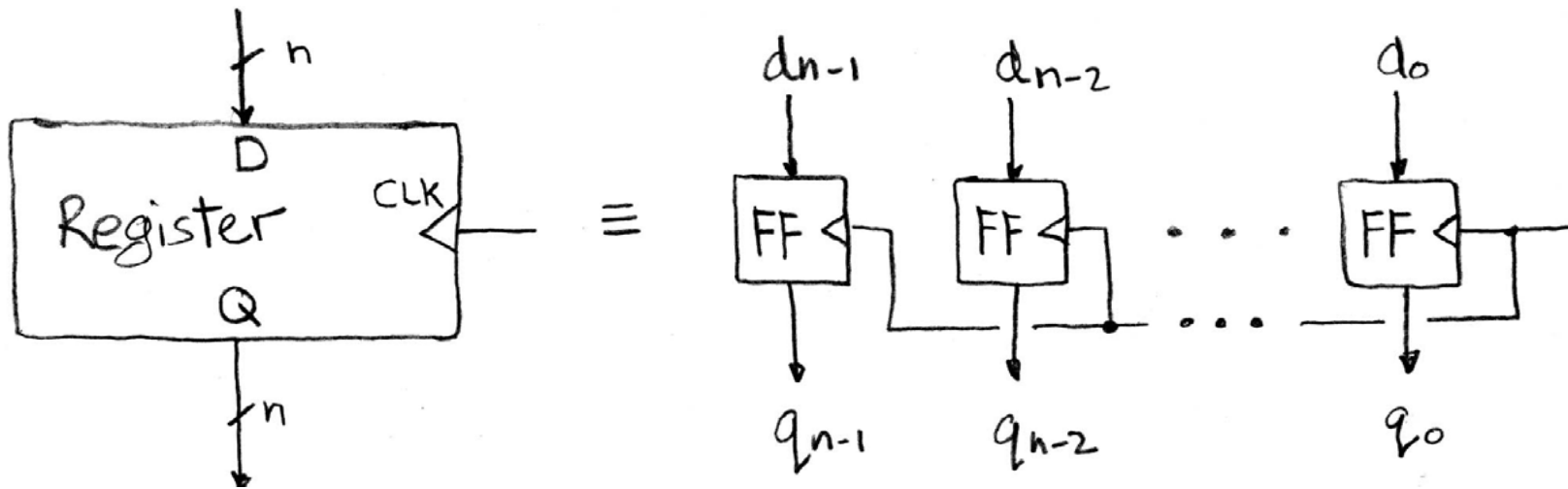

- $n$  instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between 0,1
- $D$  is “data”,  $Q$  is “output”
- Also called “d-type Flip-Flop”



# What's the timing of a Flip-flop? (1/2)



- Edge-triggered d-type flip-flop

- This one is “positive edge-triggered”



- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

- Example waveforms:

 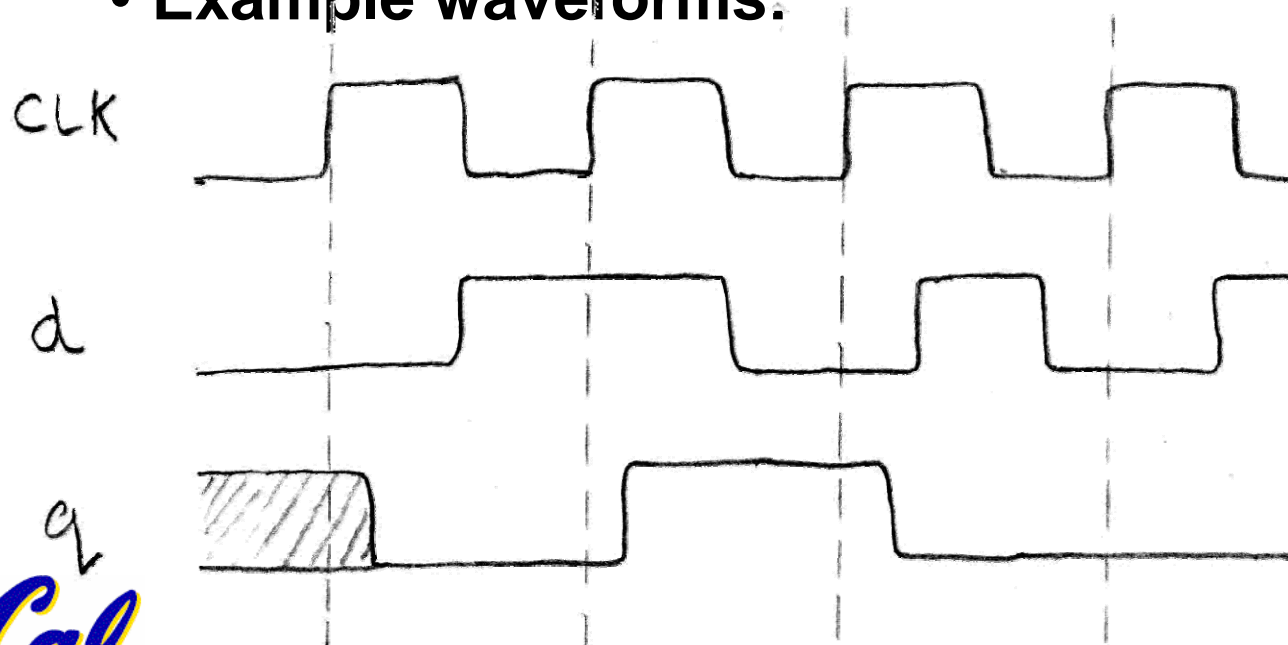



# What's the timing of a Flip-flop? (2/2)



- Edge-triggered d-type flip-flop

- This one is “positive edge-triggered”



- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

- Example waveforms (more detail):

 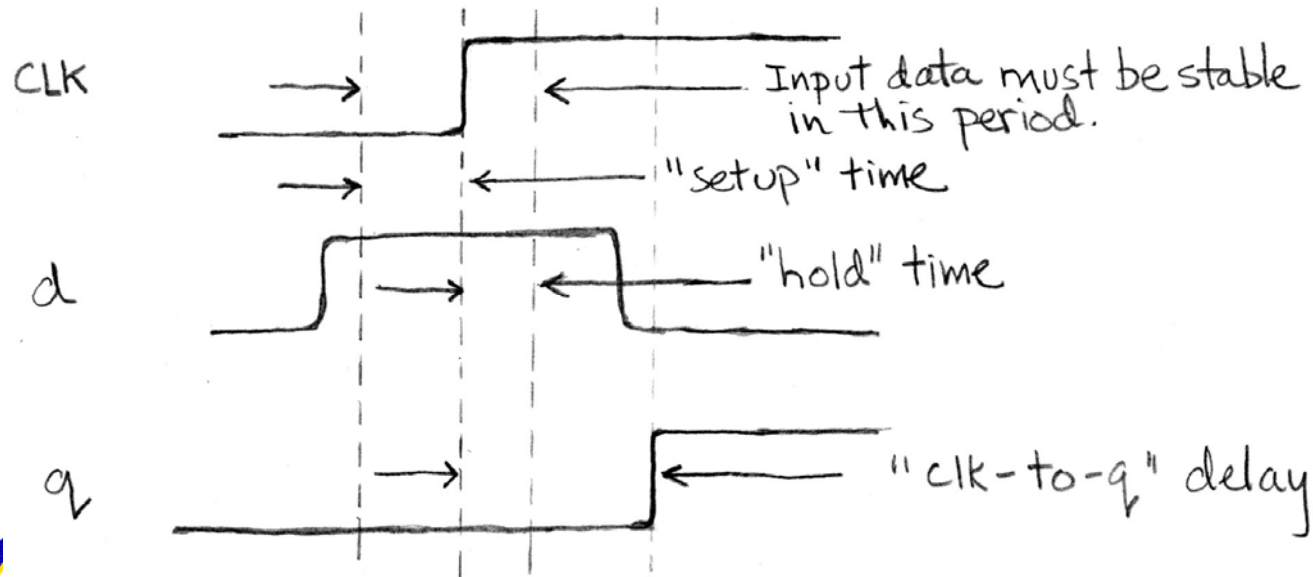


## Administrivia -

---


- **Midterms graded!!**
  - **handed back in Dis/Lab**
  - **TAs and TAsiT graded from 10 PM to 6 AM!**
  - **DO NOT PANIC (remember clobbering)**
  - **You can get a 0 on this midterm and still get the highest overall grade in the class!**



 
# Accumulator Revisited (proper timing 1/2)



 
- Reset input to register is used to force it to all zeros (takes priority over D input).
- $S_{i-1}$  holds the result of the  $i^{\text{th}}-1$  iteration.
- Analyze circuit timing starting at the output of the register.


 
# Accumulator Revisited (proper timing 2/2)




 - reset signal shown.
- Also, in practice  $X$  might not arrive to the adder at the same time as  $S_{i-1}$
- $S_i$  temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.



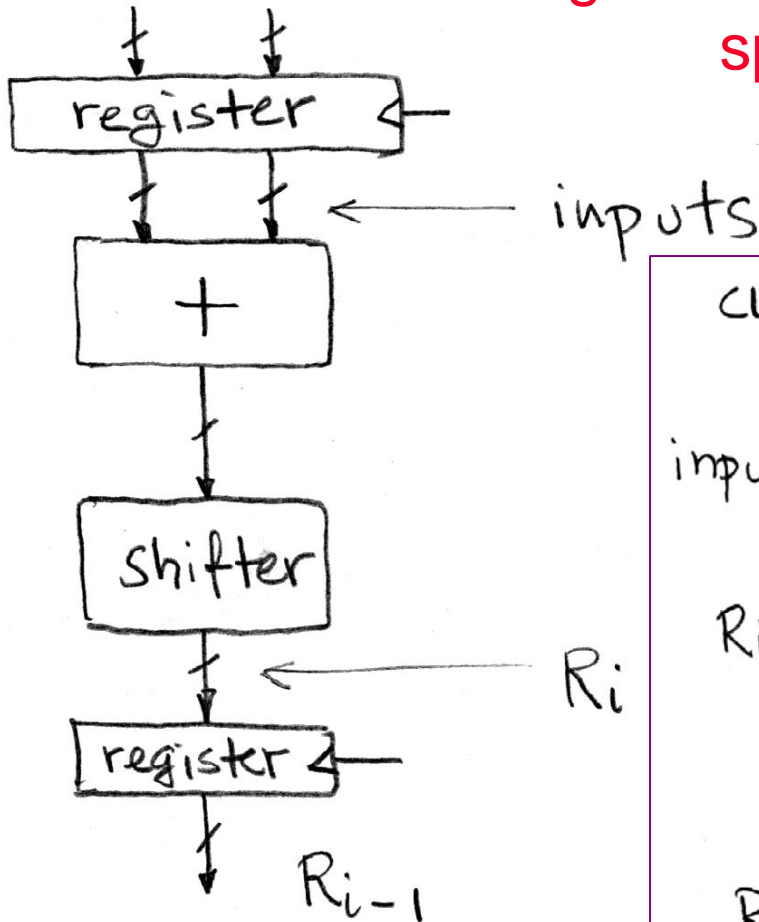
# Pipelining to improve performance (1/2)

Extra Register are often added to help speed up the clock rate.



Timing...

 


Note: delay of 1 clock cycle from input to output.

Clock period limited by propagation delay of adder/shifter.



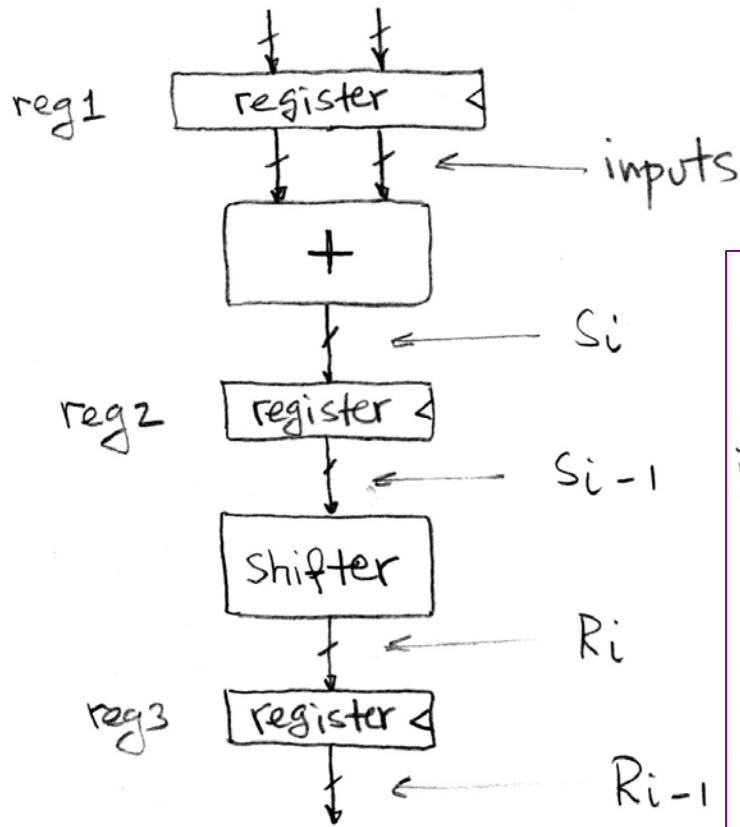
# Pipelining to improve performance (2/2)



- Insertion of register allows higher clock frequency.
- More outputs per second.


**Timing...**

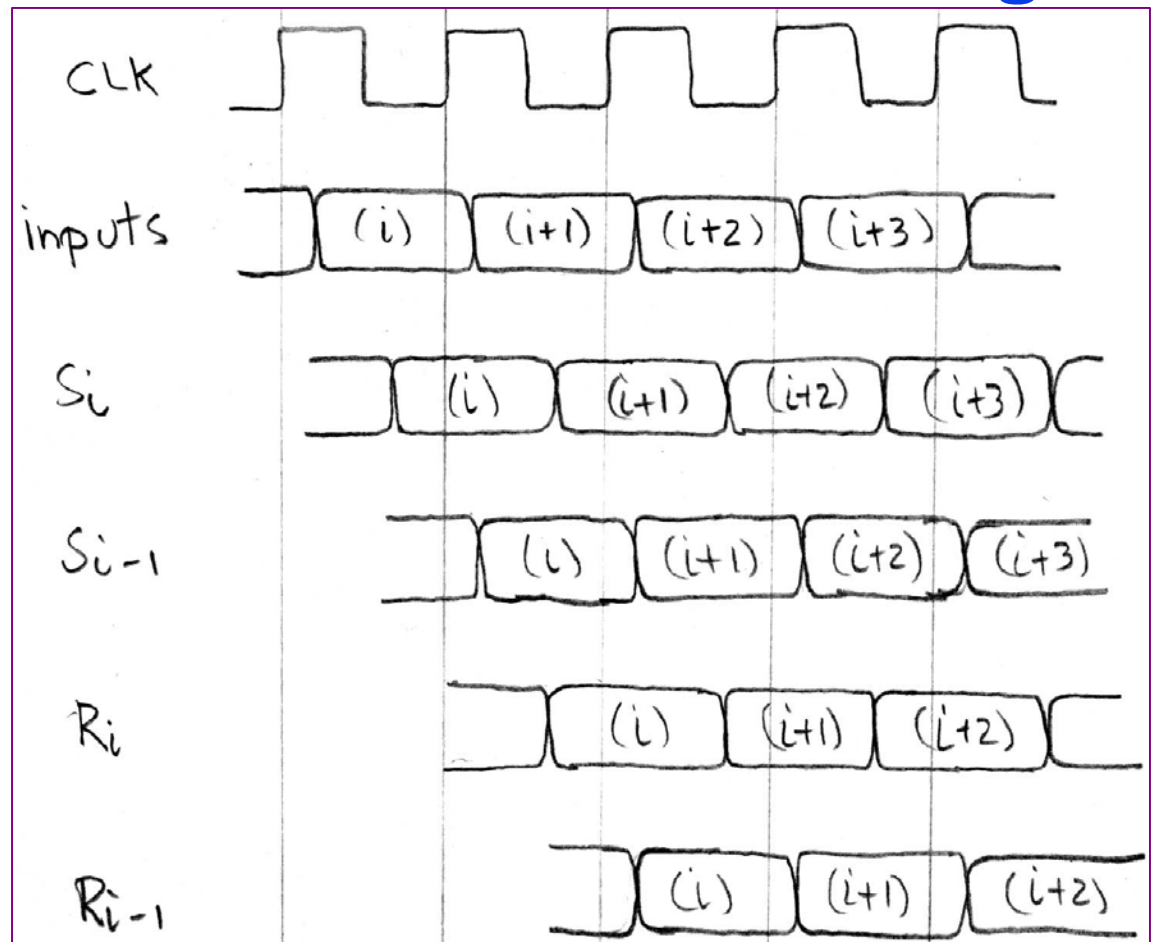
 
# Finite State Machines (FSM) Introduction


---

- You have seen FSMs in other classes.
- Same basic idea.
- The function can be represented with a “state transition diagram”.
- With combinational logic and registers, any FSM can be implemented in hardware.



 
# Finite State Machine Example: 3 ones...

FSM to detect the occurrence of 3 consecutive 1's in the input.



Draw the FSM...

 


Assume state transitions are controlled by the clock:  
on each clock cycle the machine checks the inputs and moves  
to a new state and produces a new output...





 
# Hardware Implementation of FSM


... Therefore a register is needed to hold the a representation of which state the machine is in. Use a unique bit pattern for each state.



+

 

=

 


Combinational logic circuit is used to implement a function maps from *present state and input* to *next state and output*.


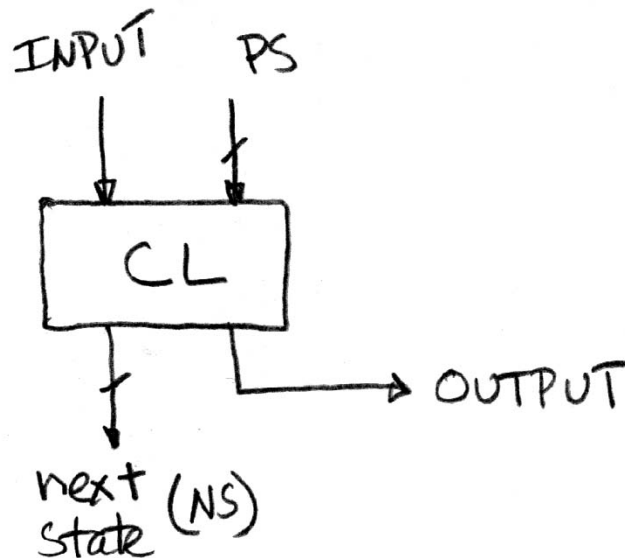
# Hardware for FSM: Combinational Logic


Next lecture we will discuss the detailed implementation, but for now can look at its functional specification, truth table form.



## Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

# General Model for Synchronous Systems

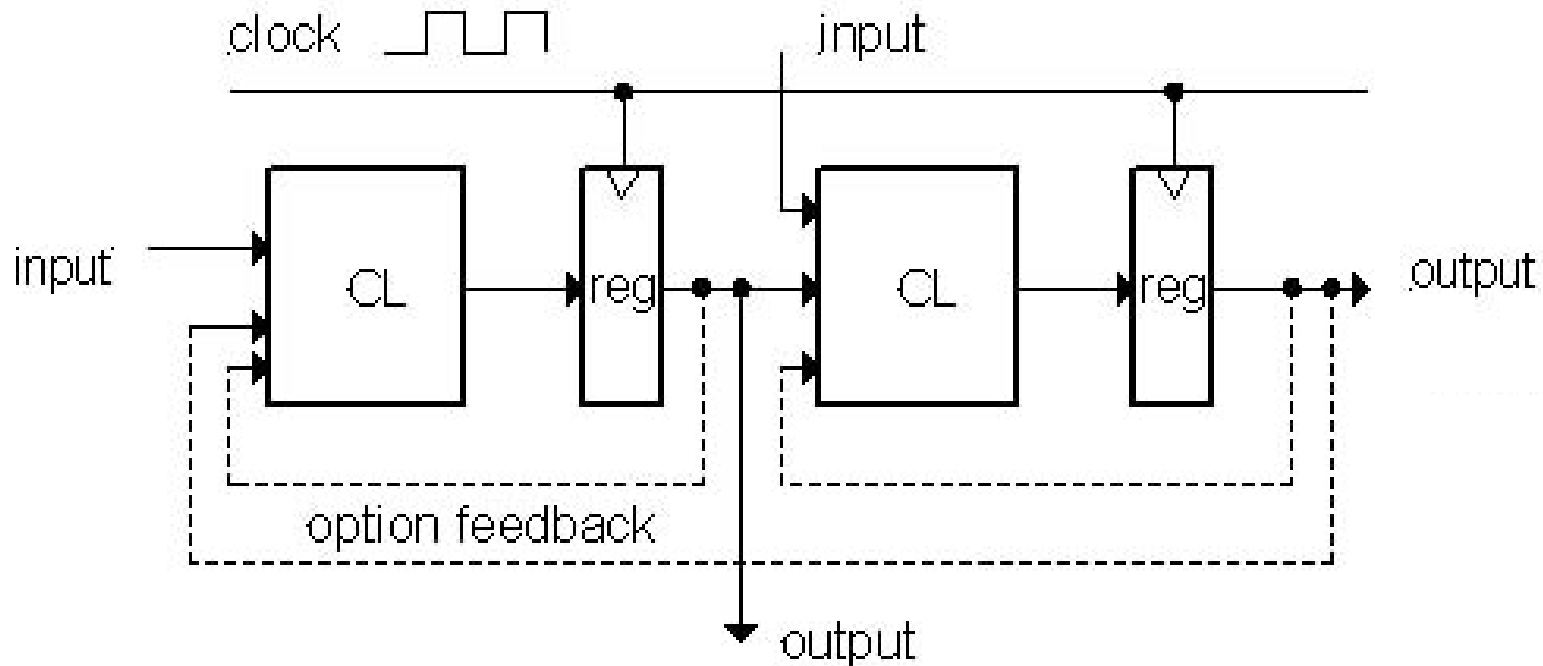

- Collection of CL blocks separated by registers.
- Registers may be back-to-back and CL blocks may be back-to-back.
- Feedback is optional.
- Clock signal(s) connects only to clock input of registers.



# Peer Instruction

---

- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT

# Peer Instruction Answer

A. It needs 'base case' (reg reset), way to step from  $i$  to  $i+1$  (use register + clock).

- True!

B. D-Q has state, CL never has state!

- False!

C. How many states would it have? Say it's  $n$ . How does it know when  $n+1$  bits have been seen?

- False!

**A. HW feedback akin to SW recursion**

**B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**

**C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT

## “And In conclusion...”

---

- **State elements are used to:**
  - **Build memories**
  - **Control the flow of information between other state elements and combinational logic**
- **D-flip-flops used to build registers**
- **Clocks tell us when D-flip-flops change**
  - **Setup and Hold times important**
- **We pipeline long-delay CL for faster clock**
- **Finite State Machines extremely useful**
- **You'll see them again (150,152) & 164**

