

**Lecture 23 – Combinational Logic Blocks**

2007-03-12



Lecturer SOE Dan Garcia

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)


Salamander robot! ⇒

Swiss scientists have built a robot that can both swim and walk. A yard long, it has a “nervous system” based on a lamprey eel.



 **Review**


- Use this table and techniques we learned to transform from 1 to another



**Today**


- Data Multiplexors
- Arithmetic and Logic Unit
- Adder/Subtractor

 **Data Multiplexor (here 2-to-1, n-bit-wide)**



**N instances of 1-bit-wide mux**


How many rows in TT?

 

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$


**How do we build a 1-bit-wide mux?**

$$\bar{s}a + sb$$

 

### 4-to-1 Multiplexor?

How many rows in TT?

 

$$e = \bar{s}_1 \bar{s}_0 a + \bar{s}_1 s_0 b + s_1 \bar{s}_0 c + s_1 s_0 d$$




CS61C L23 Combinational Logic Blocks (7)

Garcia, Spring 2007 © UCB

### Is there any other way to do it?

Hint: NCAA tourney!

 

CS61C L23 Combinational Logic Blocks (8)

Garcia, Spring 2007 © UCB

Ans: Hierarchically!

### Administrivia

- SIGCSE 2007 in Covington, KY
  - Special Interest Group in Computer Science Education conference
  - Great chance to network with like-minded people from around the world!
    - Teaching faculty
    - People interested in Computer Science Education Research
- SIGCSE 2008 is in Portland, OR
  - I'm the "Student Volunteer Coordinator"
  - If you want to go, talk to me!




CS61C L23 Combinational Logic Blocks (9)

Garcia, Spring 2007 © UCB
 
### Arithmetic and Logic Unit

- Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when S=00, R=A+B  
 when S=01, R=A-B  
 when S=10, R=A AND B  
 when S=11, R=A OR B



CS61C L23 Combinational Logic Blocks (10)

Garcia, Spring 2007 © UCB

### Our simple ALU

 

CS61C L23 Combinational Logic Blocks (11)

Garcia, Spring 2007 © UCB

### Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer



CS61C L23 Combinational Logic Blocks (12)

Garcia, Spring 2007 © UCB

### Adder/Subtractor – One-bit adder LSB...

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

$a_0$	$b_0$	$s_0$	$c_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$s_0 =$   
 $c_1 =$



### Adder/Subtractor – One-bit adder (1/2)...


	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

$a_i$	$b_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$s_i =$   
 $c_{i+1} =$



 
### Adder/Subtractor – One-bit adder (2/2)...



$s_i = \text{XOR}(a_i, b_i, c_i)$   
 $c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$


 
### N 1-bit adders $\Rightarrow$ 1 N-bit adder




What about overflow?  
Overflow =  $c_n$ ?


 
### What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



• Highest adder

- $C_1 = \text{Carry-in} = C_{in}$ ,  $C_2 = \text{Carry-out} = C_{out}$
- No  $C_{out}$  or  $C_{in} \Rightarrow$  NO overflow!

What op?


- $C_{in}$ , and  $C_{out} \Rightarrow$  NO overflow!
- $C_{in}$ , but no  $C_{out} \Rightarrow$  A,B both > 0, overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow$  A,B both < 0, overflow!



### What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 


• Overflows when...

- $C_{in}$ , but no  $C_{out} \Rightarrow$  A,B both > 0, overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow$  A,B both < 0, overflow!

overflow =  $c_n \text{ XOR } c_{n-1}$



## Extremely Clever Subtractor

 

CS61C L23 Combinational Logic Blocks (19)

Garcia, Spring 2007 © UCB

## Peer Instruction

- Truth table for mux with 4-bits of signals has  $2^4$  rows
- We could cascade  $N$  1-bit shifters to make 1  $N$ -bit shifter for `sll`, `srl`
- If 1-bit adder delay is  $T$ , the  $N$ -bit adder delay would also be  $T$

	ABC
0:	FFF
1:	FFT
2:	FTF
3:	FTT
4:	TFF
5:	TFT
6:	FTT
7:	TTT

CS61C L23 Combinational Logic Blocks (20)

Garcia, Spring 2007 © UCB

## Peer Instruction Answer



CS61C L23 Combinational Logic Blocks (21)

Garcia, Spring 2007 © UCB

## “And In conclusion...”

- Use muxes to select among input
  - $S$  input bits selects  $2^S$  inputs
  - Each input can be  $n$ -bits wide, indep of  $S$
- Can implement muxes hierarchically
- ALU can be implemented using a mux
  - Coupled with basic block elements
- $N$ -bit adder-subtractor done using  $N$  1-bit adders with XOR gates on input
  - XOR serves as conditional inverter



CS61C L23 Combinational Logic Blocks (22)

Garcia, Spring 2007 © UCB