


inst.eecs.berkeley.edu/~cs61c

UC Berkeley CS61C : Machine Structures

Lecture 23 – Combinational Logic Blocks

2007-03-12

RIP
Richard Jeni
1957-2007

 

Lecturer SOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Salamander robot! ⇒

Swiss scientists have built a robot that can both swim and walk. A yard long, it has a “nervous system” based on a lamprey eel.




www.cnn.com/2007/TECH/03/08/salamander.robot.ap

CS61C L23 Combinational Logic Blocks (1)

Garcia, Spring 2007 © UCB

Review

 - Use this table and techniques we learned to transform from 1 to another




Today

- **Data Multiplexors**
- **Arithmetic and Logic Unit**
- **Adder/Subtractor**




 Data Multiplexor (here 2-to-1, n-bit-wide)



N instances of 1-bit-wide mux

How many rows in TT?

 


$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\ &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\ &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\ &= \bar{s}(a(1) + s((1)b) \\ &= \bar{s}a + sb\end{aligned}$$




How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 

4-to-1 Multiplexor?


How many rows in TT?

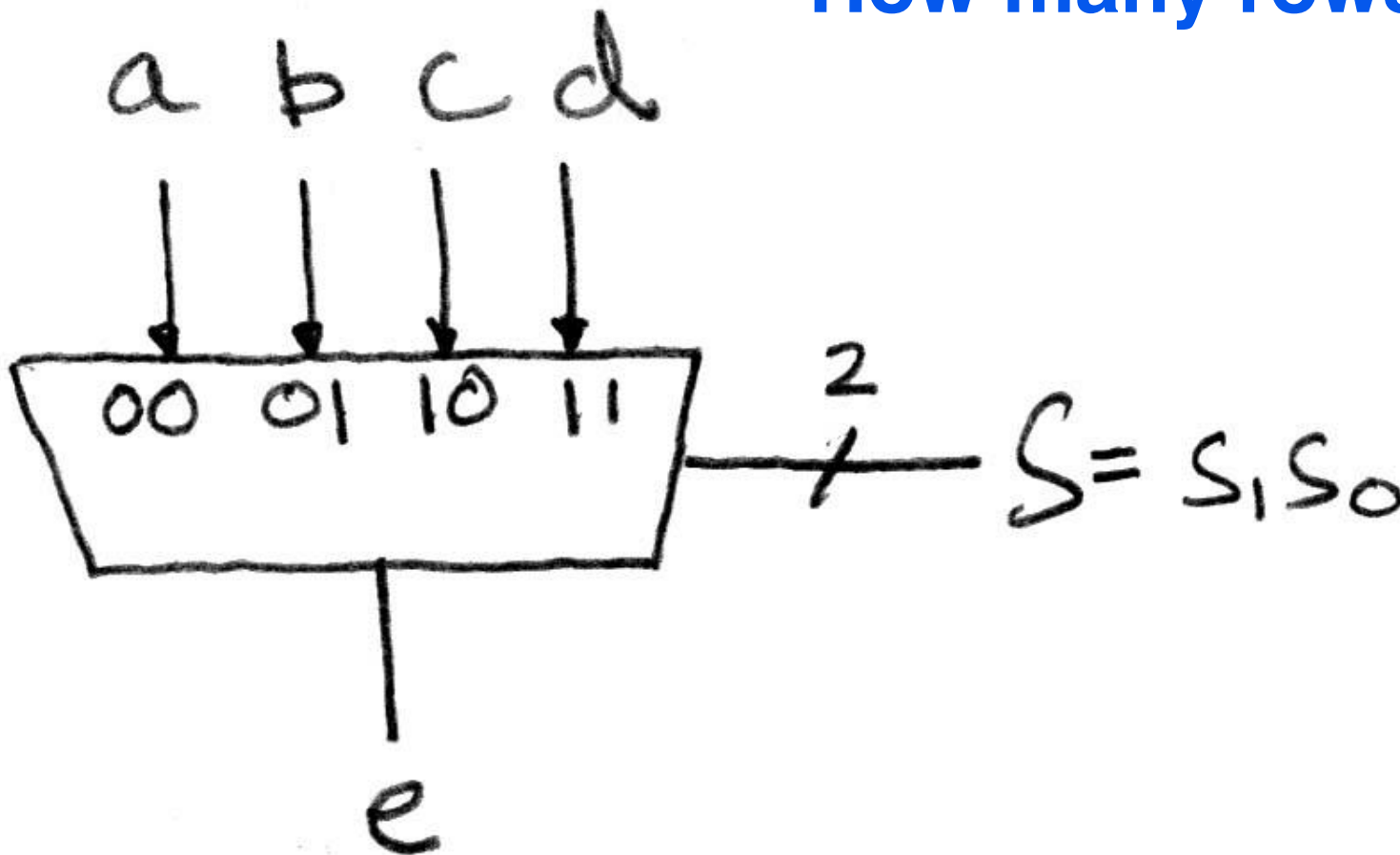

$$e = \bar{s}_1 \bar{s}_0 a + \bar{s}_1 s_0 b + s_1 \bar{s}_0 c + s_1 s_0 d$$

Is there any other way to do it?

Hint: NCAA tourney!

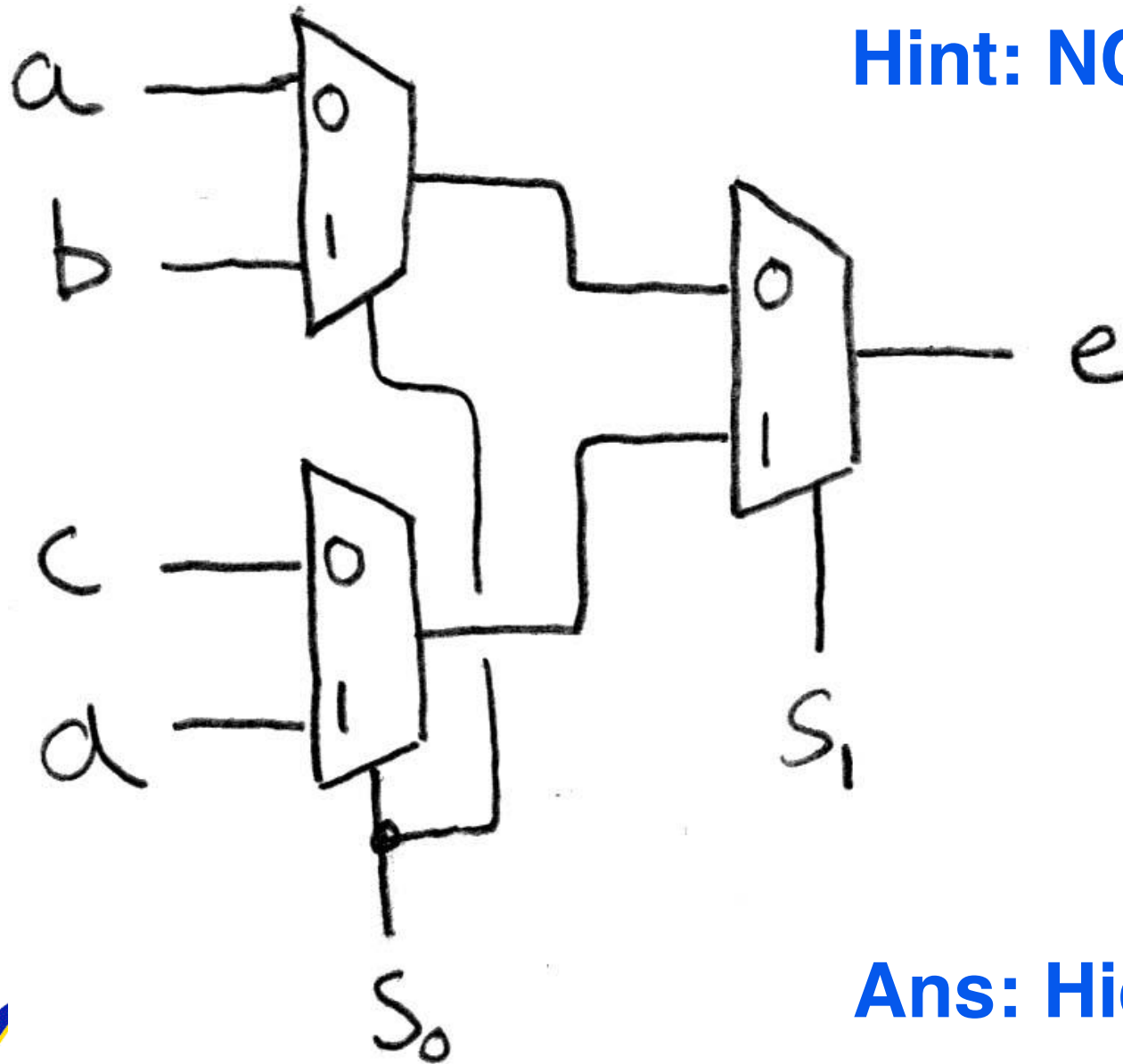

Ans: Hierarchically!




Administrivia

- **SIGCSE 2007 in Covington, KY**
 - **Special Interest Group in Computer Science Education conference**
 - **Great chance to network with like-minded people from around the world!**
 - **Teaching faculty**
 - **People interested in Computer Science Education Research**
- **SIGCSE 2008 is in Portland, OR**
 - **I'm the "Student Volunteer Coordinator"**
 - **If you want to go, talk to me!**



Arithmetic and Logic Unit

 
- Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does **ADD, SUB, bitwise AND, bitwise OR**



when $S=00$, $R=A+B$
when $S=01$, $R=A-B$
when $S=10$, $R=A \text{ AND } B$
when $S=11$, $R=A \text{ OR } B$



Our simple ALU

 

Adder/Subtractor Design -- how?

- **Truth-table, then determine canonical form, then minimize and implement as we've seen before**
- **Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer**



Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 & \end{array}$$

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0



a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$



  
Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

N 1-bit adders \Rightarrow 1 N-bit adder

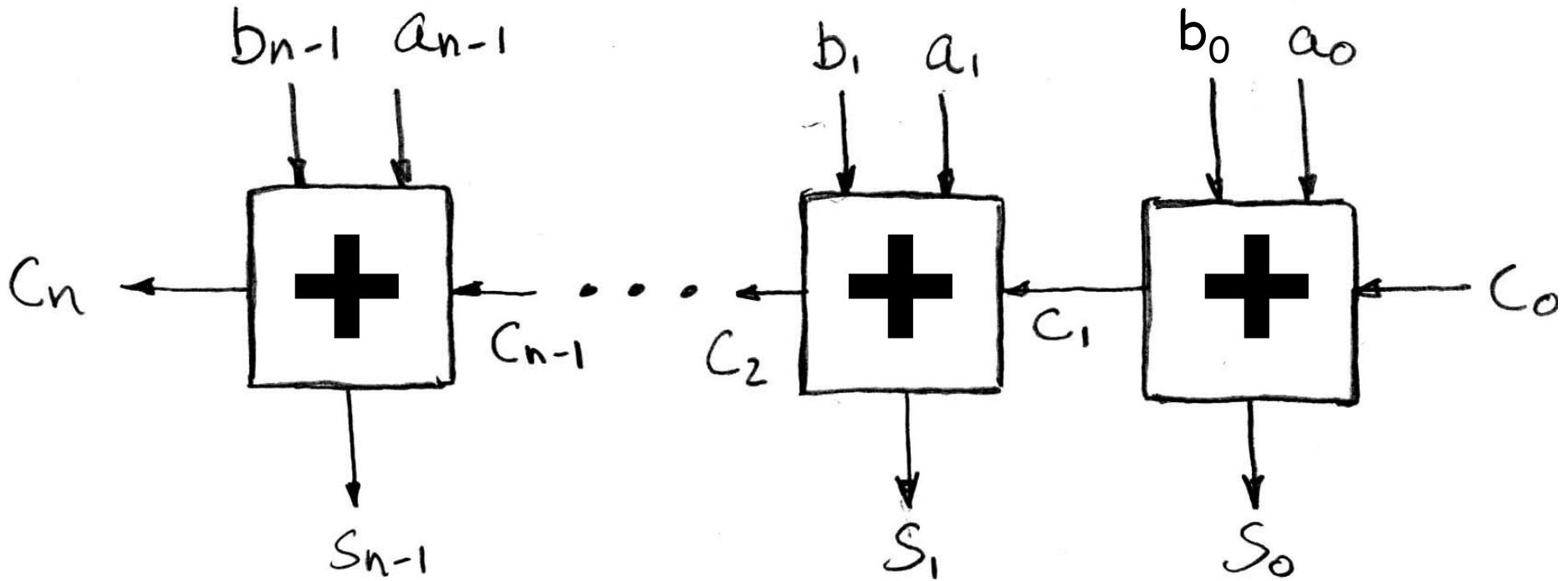


What about overflow?
Overflow = c_n ?

What about overflow?

- Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow \text{NO overflow!}$

What
op?

- C_{in} , and $C_{out} \Rightarrow \text{NO overflow!}$

• C_{in} , but no $C_{out} \Rightarrow A, B \text{ both } > 0, \text{ overflow!}$


• C_{out} , but no $C_{in} \Rightarrow A, B \text{ both } < 0, \text{ overflow!}$



What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2
11 = -1
00 = 0
01 = 1

 


- Overflows when...

- C_{in} , but no $C_{out} \Rightarrow A, B$ both > 0 , overflow!
- C_{out} , but no $C_{in} \Rightarrow A, B$ both < 0 , overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$

Extremely Clever Subtractor

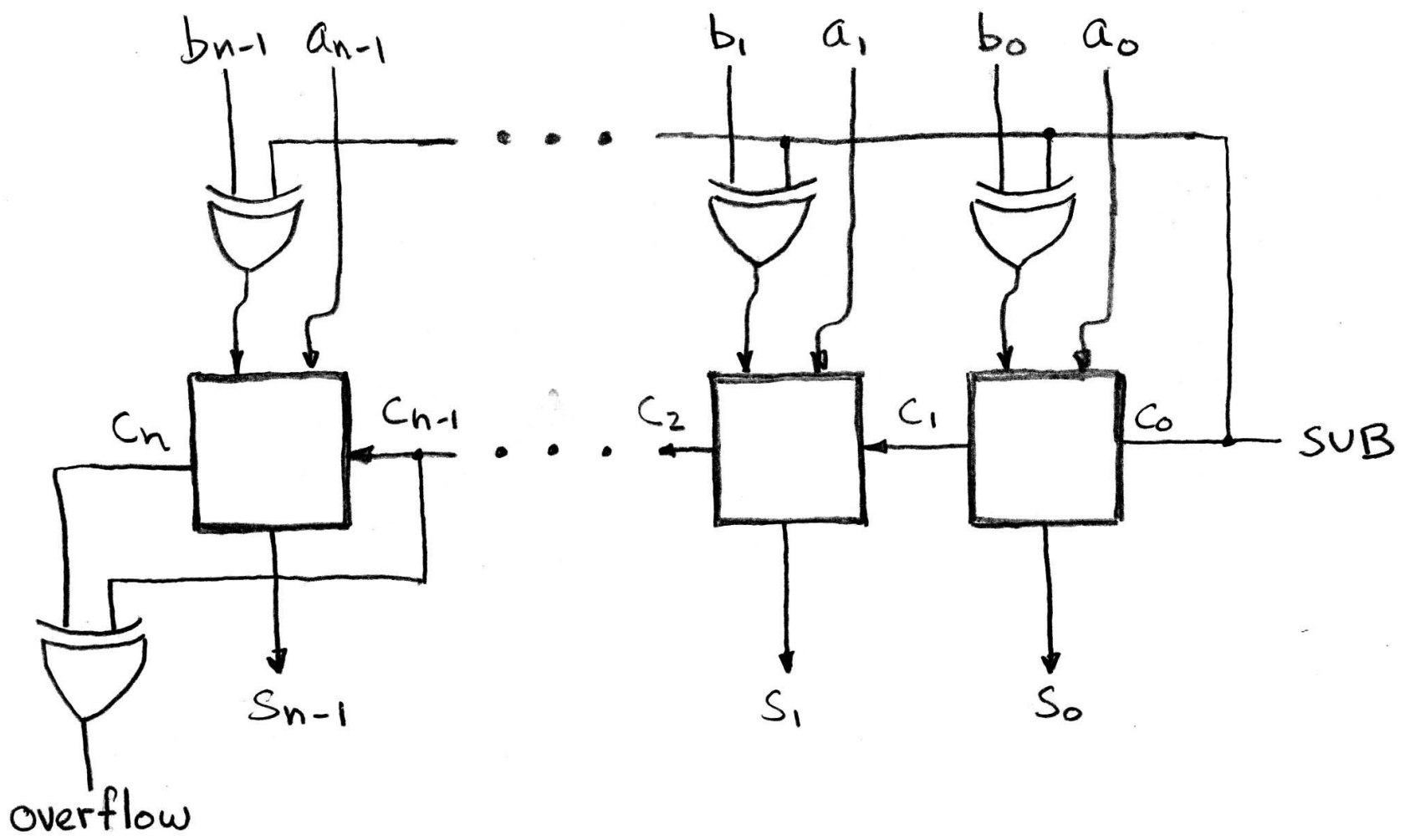

Peer Instruction

- A. Truth table for mux with 4-bits of signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
0:	FFF
1:	FFT
2:	FTF
3:	FTT
4:	TFF
5:	TFT
6:	TF
7:	TTT

Peer Instruction Answer



“And In conclusion...”

- **Use muxes to select among input**
 - **S input bits selects 2^S inputs**
 - **Each input can be n-bits wide, indep of S**
- **Can implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - **Coupled with basic block elements**
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - **XOR serves as conditional inverter**

