


Lecture 24 – Introduction to CPU Design

2007-03-14




Lecturer SOE Dan Garcia
www.cs.berkeley.edu/~ddgarcia

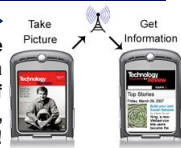Cell pic to web site ⇒
 A new MS app lets people search the web based on a digital cell phone photo (of poster, ad, dvd, magazine, painting, product). Cool!



Five Components of a Computer

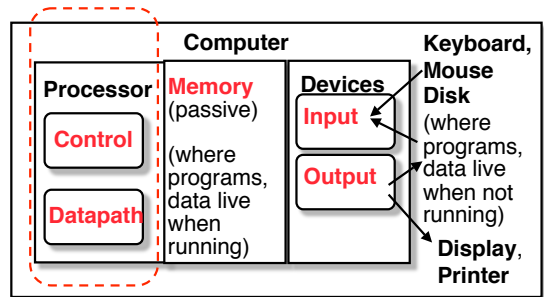

The CPU

- **Processor (CPU):** the active part of the computer, which does all the work (data manipulation and decision-making)
- **Datapath:** portion of the processor which contains hardware necessary to perform operations required by the processor (the brawn)
- **Control:** portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)

Stages of the Datapath : Overview

- **Problem:** a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient
- **Solution:** break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
 - smaller stages are easier to design
 - easy to optimize (change) one stage without touching the others

Stages of the Datapath (1/5)

- There is a *wide* variety of MIPS instructions: so what general steps do they have in common?
- **Stage 1: Instruction Fetch**
 - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we **Increment PC** (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)

Stages of the Datapath (2/5)

- **Stage 2: Instruction Decode**
 - upon fetching the instruction, we next gather data from the fields (*decode* all necessary instruction data)
 - first, read the Opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for `add`, read two registers
 - for `addi`, read one register
 - for `jal`, no reads necessary

Stages of the Datapath (3/5)

• Stage 3: ALU (Arithmetic-Logic Unit)

- the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, !), comparisons (slt)
- what about loads and stores?
 - `lw $t0, 40($t1)`
 - the address we are accessing in memory = the value in `$t1` PLUS the value 40
 - so we do this addition in this stage



Stages of the Datapath (4/5)

• Stage 4: Memory Access

- actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
- since these instructions have a unique step, we need this extra stage to account for them
- as a result of the cache system, this stage is expected to be fast




Stages of the Datapath (5/5)

• Stage 5: Register Write

- most instructions write the result of some computation into a register
- examples: arithmetic, logical, shifts, loads, `slt`
- what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage or skip it all together



Generic Steps of Datapath

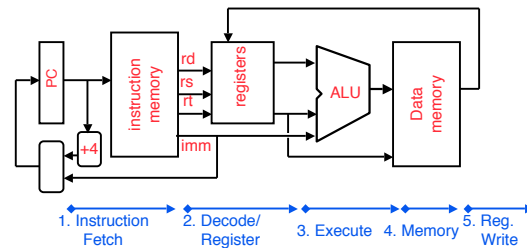


Datapath Walkthroughs (1/3)

- `add $r3, $r1, $r2 # r3 = r1+r2`
- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an add, then read registers `$r1` and `$r2`
- Stage 3: add the two values retrieved in Stage 2
- Stage 4: idle (nothing to write to memory)
- Stage 5: write result of Stage 3 into register `$r3`



Example: add Instruction

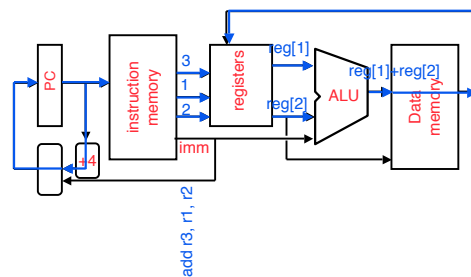

Datapath Walkthroughs (2/3)


- `slti $r3, $r1, 17`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's an `slt`, then read register `$r1`
 - Stage 3: compare value retrieved in Stage 2 with the integer 17
 - Stage 4: idle
 - Stage 5: write the result of Stage 3 in register `$r3`



CS61C L24 Introduction to CPU Design (18)

Garcia, Spring 2007 © UCB

Example: `slt` Instruction

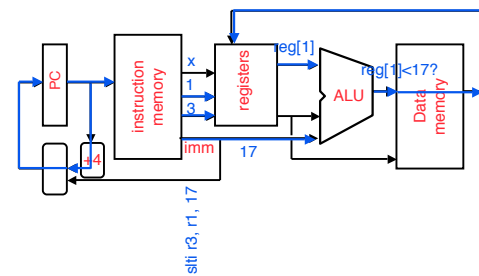

CS61C L24 Introduction to CPU Design (17)

Garcia, Spring 2007 © UCB

Datapath Walkthroughs (3/3)


- `sw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `sw`, then read registers `$r1` and `$r3`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: write value in register `$r3` (retrieved in Stage 2) into memory address computed in Stage 3
 - Stage 5: idle (nothing to write into a register)



CS61C L24 Introduction to CPU Design (19)

Garcia, Spring 2007 © UCB

Example: `sw` Instruction

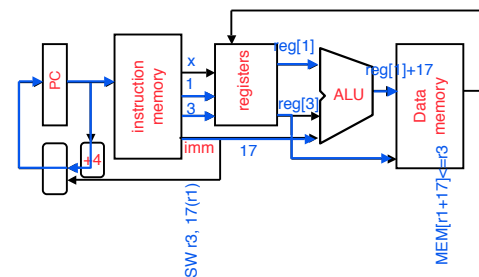

CS61C L24 Introduction to CPU Design (19)

Garcia, Spring 2007 © UCB

Why Five Stages? (1/2)

- Could we have a different number of stages?
 - Yes, and other architectures do
- So why does MIPS have five if instructions tend to idle for at least one stage?
 - The five stages are the union of all the operations needed by all the instructions.
 - There is one instruction that uses all five stages: the load



CS61C L24 Introduction to CPU Design (20)

Garcia, Spring 2007 © UCB

Why Five Stages? (2/2)


- `lw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `lw`, then read register `$r1`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: read value from memory address compute in Stage 3
 - Stage 5: write value found in Stage 4 into register `$r3`



CS61C L24 Introduction to CPU Design (21)

Garcia, Spring 2007 © UCB

Example: `lw` Instruction

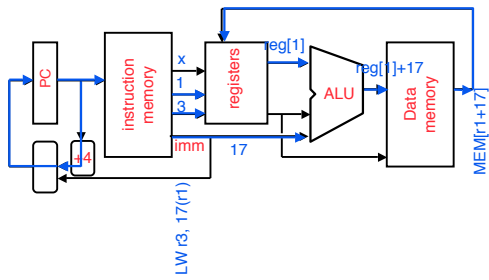


CS61C L24 Introduction to CPU Design (22)

Garcia, Spring 2007 © UCB

Datapath Summary

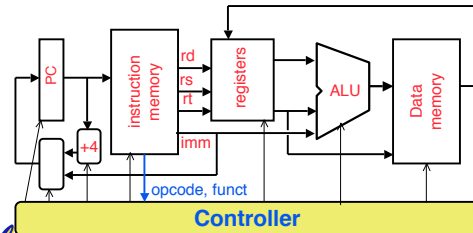- The datapath based on data transfers required to perform instructions
- A *controller* causes the right transfers to happen



CS61C L24 Introduction to CPU Design (23)

Garcia, Spring 2007 © UCB

What Hardware Is Needed? (1/2)

- **PC:** a register which keeps track of memory addr of the next instruction
- **General Purpose Registers**
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- **Memory**
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average



CS61C L24 Introduction to CPU Design (24)

Garcia, Spring 2007 © UCB

What Hardware Is Needed? (2/2)

- **ALU**
 - used in Stage 3
 - something that performs all necessary functions: arithmetic, logicals, etc.
 - we'll design details later
- **Miscellaneous Registers**
 - In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travels from stage to stage.
 - Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the "register file".




CS61C L24 Introduction to CPU Design (25)

Garcia, Spring 2007 © UCB

CPU clocking (1/2)

For each instruction, how do we control the flow of information through the datapath?

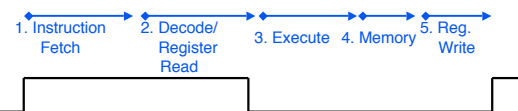- **Single Cycle CPU:** All stages of an instruction are completed within one *long* clock cycle.
 - The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.




CS61C L24 Introduction to CPU Design (26)

Garcia, Spring 2007 © UCB

CPU clocking (2/2)

For each instruction, how do we control the flow of information through the datapath?

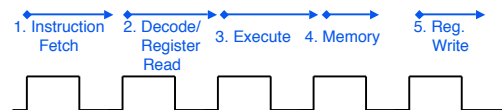- **Multiple-cycle CPU:** Only one stage of instruction per clock cycle.
 - The clock is made as long as the slowest stage.



Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).



CS61C L24 Introduction to CPU Design (27)

Garcia, Spring 2007 © UCB