

inst.eecs.berkeley.edu/~cs61c

UC Berkeley CS61C : Machine Structures

Lecture 25

CPU Design: Designing a Single-cycle CPU



2007-03-16

UC Regents approve 7%
student fee increase!

Lecturer SOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Google Summer of Code ⇒



Student applications are
now open (through 2007-03-24); 131
projects available. Work on wxPython,
PHP, BZFlag, LispNYC, GNU, & more!




Review

- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - **XOR serves as conditional inverter**
- **CPU design involves Datapath, Control**
 - **Datapath in MIPS involves 5 CPU stages**
 - 1) **Instruction Fetch**
 - 2) **Instruction Decode & Register Read**
 - 3) **ALU (Execute)**
 - 4) **Memory**
 - 5) **Register Write**



Datapath Summary

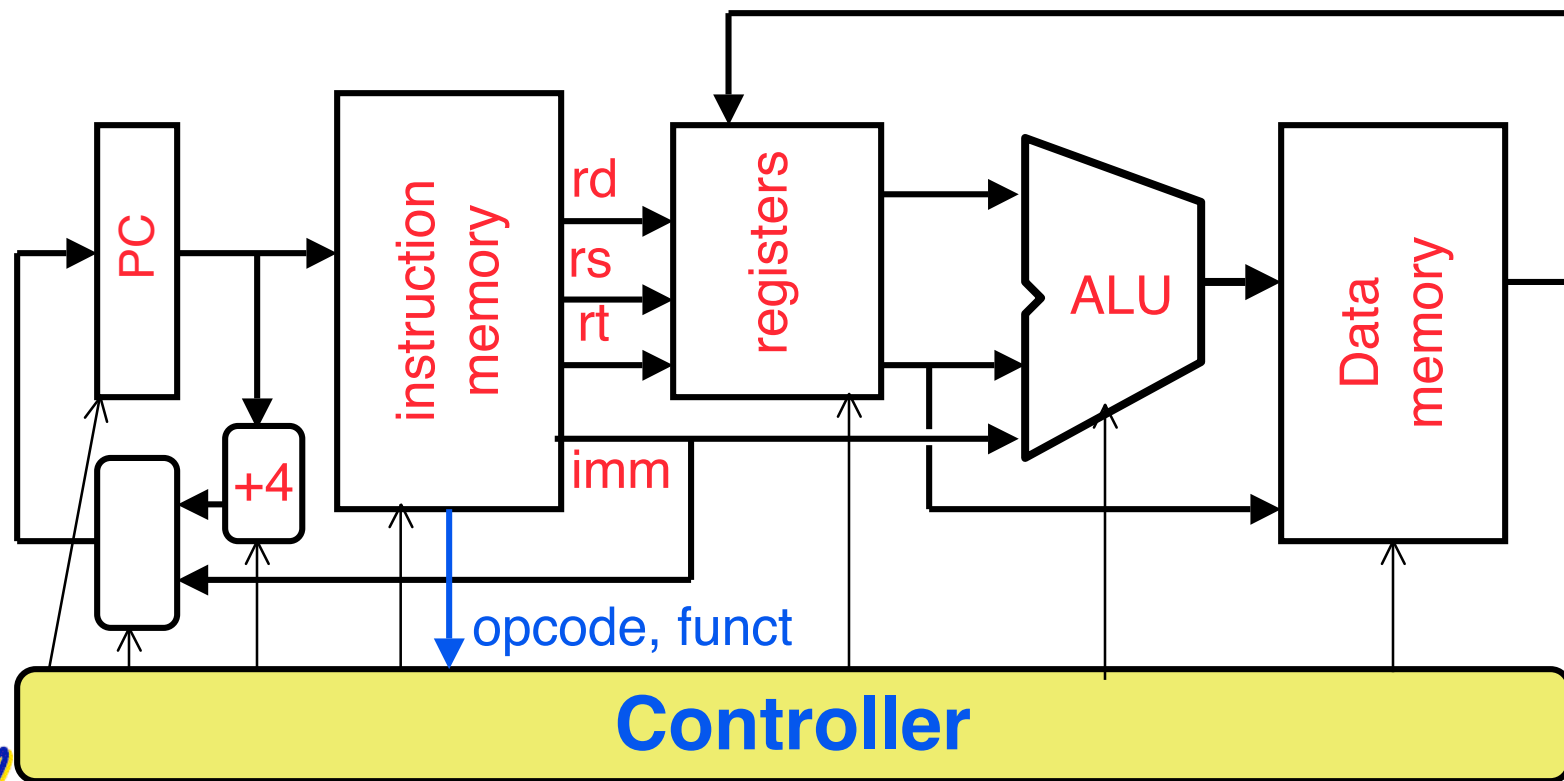
- The datapath based on data transfers required to perform instructions
- A *controller* causes the right transfers to happen



CPU clocking (1/2)

For each instruction, how do we control the flow of information through the datapath?

 
- **Single Cycle CPU:** All stages of an instruction are completed within one *long* clock cycle.
 - The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.



CPU clocking (2/2)

For each instruction, how do we control the flow of information through the datapath?

 - **Multiple-cycle CPU:** Only one stage of instruction per clock cycle.
 - The clock is made as long as the slowest stage.



Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).



How to Design a Processor: step-by-step


- 1. Analyze instruction set architecture (ISA)
⇒ datapath requirements**
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology**
- 3. Assemble datapath meeting requirements**
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- 5. Assemble the control logic**




Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:

- R-type

 

- I-type

 

- J-type



- The different fields are:

- **op**: operation (“opcode”) of the instruction
- **rs, rt, rd**: the source and destination register specifiers
- **shamt**: shift amount
- **funct**: selects the variant of the operation in the “op” field
- **address / immediate**: address offset or immediate value
- **target address**: target address of jump instruction




Step 1a: The MIPS-lite Subset for today

• ADDU and SUBU


• `addu rd,rs,rt`

• `subu rd,rs,rt`

 

• OR Immediate:


• `ori rt,rs,imm16`

 

• LOAD and STORE Word


• `lw rt,rs,imm16`

• `sw rt,rs,imm16`

 

• BRANCH:

• `beq rs,rt,imm16`

 

Register Transfer Language

- RTL gives the meaning of the instructions

$\{op, rs, rt, rd, shamt, funct\} \leftarrow \text{MEM}[PC]$

$\{op, rs, rt, \text{Imm16}\} \leftarrow \text{MEM}[PC]$

- All start by fetching the instruction

inst Register Transfers

ADDU $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

SUBU $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ORI $R[rt] \leftarrow R[rs] | \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rt];$ $PC \leftarrow PC + 4$

BEQ if ($R[rs] == R[rt]$) then
 $PC \leftarrow PC + 4 + (\text{sign_ext}(\text{Imm16}) \parallel 00)$
 else $PC \leftarrow PC + 4$



Step 1: Requirements of the Instruction Set

- **Memory (MEM)**
 - instructions & data (will use one for each)
- **Registers (R: 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender (sign/zero extend)**
- **Add/Sub/OR unit for operation on register(s) or extended immediate**
- **Add 4 or extended immediate to PC**
- **Compare registers?**




Step 2: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology





Combinational Logic Elements (Building Blocks)

• Adder

 

• MUX

  

• ALU

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$

ORI $R[rt] = R[rs] | \text{zero_ext}(\text{Imm16}) \dots$

BEQ $\text{if} (R[rs] == R[rt]) \dots$

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND,
Set Less Than (1 if $A < B$, 0 otherwise)
- ALU follows chap 5



Administrivia

- **Read the book! Important to understand lecture and for project.**
 - **P&H 5.1-5.4**



What Hardware Is Needed? (1/2)

- **PC: a register which keeps track of memory addr of the next instruction**
- **General Purpose Registers**
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- **Memory**
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average



What Hardware Is Needed? (2/2)

- **ALU**

- used in Stage 3
- something that performs all necessary functions: arithmetic, logicals, etc.
- we'll design details later

- **Miscellaneous Registers**

- In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travel from stage to stage.
- Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the “register file”.



Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: **Data In**
- One output bus: **Data Out**

- **Memory word is selected by:**

- **Address** selects the word to put on **Data Out**
- **Write Enable = 1**: address selects the memory word to be written via the **Data In** bus

- **Clock input (CLK)**

 - The **CLK** input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:



- **Address valid \Rightarrow Data Out valid after “access time.”**




Storage Element: Register (Building Block)

- Similar to D Flip Flop except

- N-bit input and output
- Write Enable input

- Write Enable:

 - negated (or deasserted) (0):
Data Out will not change
- asserted (1):
Data Out will become Data In on positive edge of clock



Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:

busA and busB


- One 32-bit input bus: busW

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (clk)

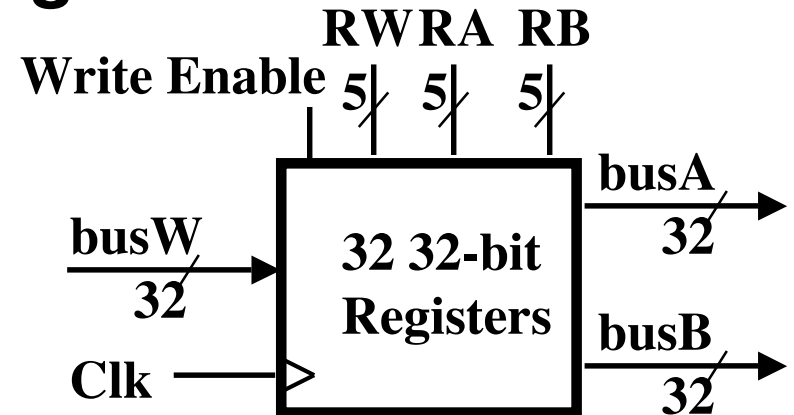- The clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:



- RA or RB valid \Rightarrow busA or busB valid after “access time.”




Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation



3a: Overview of the Instruction Fetch Unit

 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$




3b: Add & Subtract

• $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addU rd,rs,rt`

 • Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields



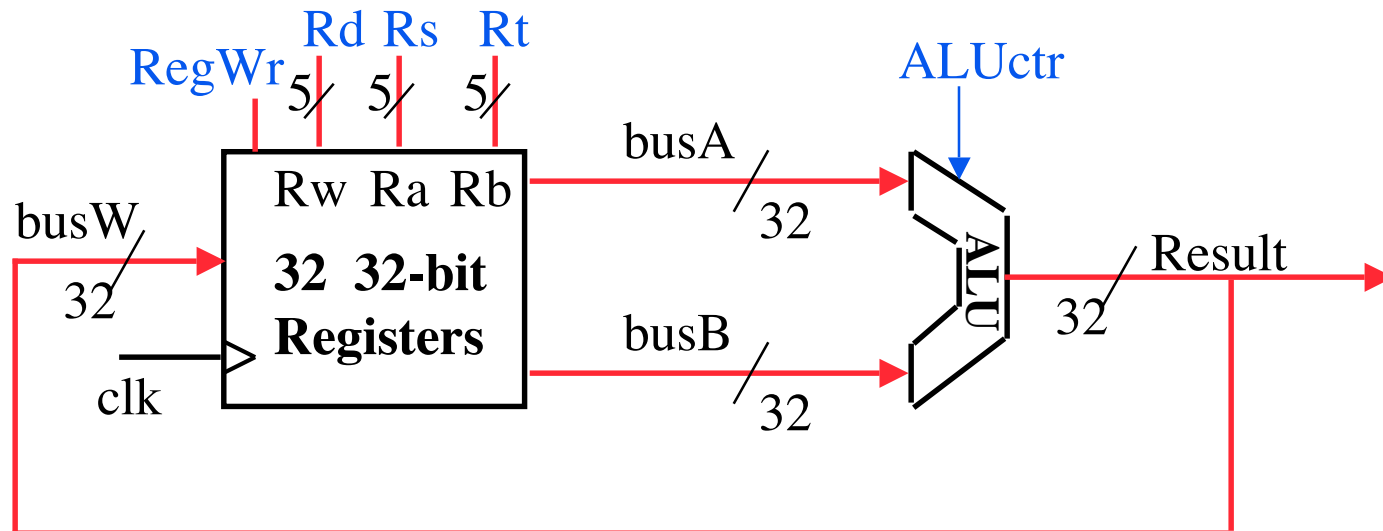• **ALUctr** and **RegWr**: control logic after decoding the instruction



Already defined the register file & ALU

Peer Instruction

- A. Our **ALU** is a synchronous device
- B. We should use the main **ALU** to compute $PC=PC+4$
- C. The **ALU** is inactive for memory reads or writes.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. If the destination reg is the same as the source reg, we **could compute the incorrect value!**
- B. We're going to be able to read 2 registers and write a 3rd in **1 cycle**
- C. Datapath is hard, **Control is easy**

	ABC
0:	FFF
1:	FFT
2:	FTF
3:	FTT
4:	TFF
5:	TFT
6:	TF
7:	TTT

Peer Instruction

- A. Truth table for mux with 4-bits of signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
1 :	FFF
2 :	FFT
3 :	FTF
4 :	FTT
5 :	TFF
6 :	TFT
7 :	TFF
8 :	TTT

Peer Instruction Answer



How to Design a Processor: step-by-step

- **1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic (hard part!)**

