

**Lecture 25 –
 Representations of Combinational Logic Circuits**



Senior Lecturer SOE Dan Garcia
www.cs.berkeley.edu/~ddgarcia

Android Brain on Robots! ⇒
 “Half the weight of some robots is due to on-board computers and the batteries needed to power them. This lightweight robot uses an Android phone as the brain, with the phone’s gyroscope and camera as sensors, with cloud help!”



Truth Tables


a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

How many Fs (4-input devices) @ Radio Shack?

TT Example #1: 1 iff one (not both) a,b=1

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

TT Example #2: 2-bit adder

 

A a ₁ a ₀	B b ₁ b ₀	C c ₂ c ₁ c ₀
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How Many Rows?

TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10


How Many Rows?

TT Example #4: 3-input majority circuit

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Logic Gates (1/2)

AND




ab	c
00	0
01	0
10	0
11	1

OR

 

ab	c
00	0
01	1
10	1
11	1

NOT

 


a	b
0	1
1	0

Cal CS61C L25 Representations of Combinational Logic Circuits (8) Garcia, Spring 2013 © UCB

And vs. Or review – Dan’s mnemonic

AND Gate

Symbol




Definition

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Cal CS61C L25 Representations of Combinational Logic Circuits (9) Garcia, Spring 2013 © UCB


Logic Gates (2/2)

XOR




ab	c
00	0
01	1
10	1
11	0

NAND

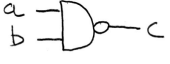

ab	c
00	1
01	1
10	1
11	0

NOR

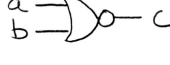

ab	c
00	1
01	0
10	0
11	0

Cal CS61C L25 Representations of Combinational Logic Circuits (10) Garcia, Spring 2013 © UCB

2-input gates extend to n-inputs


- N-input XOR is the only one which isn't so obvious
- It's simple: XOR is a 1 iff the # of 1s at its input is odd ⇒

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Cal CS61C L25 Representations of Combinational Logic Circuits (11) Garcia, Spring 2013 © UCB

Truth Table ⇒ Gates (e.g., majority circ.)


a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

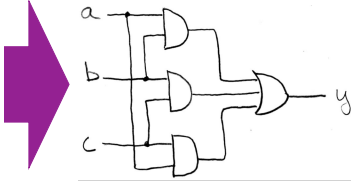


Cal CS61C L25 Representations of Combinational Logic Circuits (12) Garcia, Spring 2013 © UCB

Truth Table ⇒ Gates (e.g., FSM circ.)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 


or equivalently...

 

Cal CS61C L25 Representations of Combinational Logic Circuits (13) Garcia, Spring 2013 © UCB

Boolean Algebra

 
- George Boole, 19th Century mathematician
- Developed a mathematical system (algebra) involving logic
 - later known as “Boolean Algebra”
- Primitive functions: AND, OR and NOT
- The power of BA is there's a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA



+ means OR, · means AND, \bar{x} means NOT



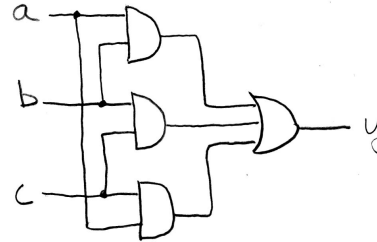Boolean Algebra (e.g., for majority fun.)




$$y = a \cdot b + a \cdot c + b \cdot c$$

$$y = ab + ac + bc$$




Boolean Algebra (e.g., for FSM)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

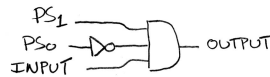


or equivalently...

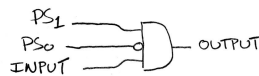

$$y = PS_1 \cdot \overline{PS_0} \cdot INPUT$$



BA: Circuit & Algebraic Simplification

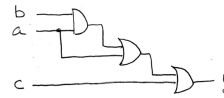

original circuit

$$y = ((ab) + a) + c$$

$$= ab + a + c$$


$$= a(b + 1) + c$$

$$= a(1) + c$$

$$= a + c$$

equation derived from original circuit

algebraic simplification

 

simplified circuit

BA also great for circuit verification
Circ X = Circ Y?
use BA to prove!



Laws of Boolean Algebra

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\bar{x}y + x = x + y$	$(\bar{x} + y)x = xy$	uniting theorem v.2
$\bar{x} \cdot y = \bar{x} + \bar{y}$	$\bar{x} + \bar{y} = \overline{x \cdot y}$	DeMorgan's Law



Boolean Algebraic Simplification Example

$$y = ab + a + c$$

$$= a(b + 1) + c \quad \text{distribution, identity}$$

$$= a(1) + c \quad \text{law of 1's}$$

$$= a + c \quad \text{identity}$$



Canonical forms (1/2)

abc	y	
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0

Sum-of-products (ORs of ANDs)

CS61C L25 Representations of Combinational Logic Circuits (21) Garcia, Spring 2013 © UCB

Canonical forms (2/2)

$$\begin{aligned}
 y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\
 &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) && \text{distribution} \\
 &= \bar{a}\bar{b}(1) + a\bar{c}(1) && \text{complementarity} \\
 &= \bar{a}\bar{b} + a\bar{c} && \text{identity}
 \end{aligned}$$

CS61C L25 Representations of Combinational Logic Circuits (22) Garcia, Spring 2013 © UCB

Peer Instruction

- $(a+b) \cdot (\bar{a}+b) = b$
- N-input gates can be thought of cascaded 2-input gates. I.e., $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$ where Δ is one of AND, OR, XOR, NAND
- You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	123
a:	FFF
a:	FFT
b:	FTF
b:	FTT
c:	TFF
d:	TFT
d:	TTF
e:	TTT

CS61C L25 Representations of Combinational Logic Circuits (23) Garcia, Spring 2013 © UCB

Peer Instruction Answer

- $(a+b) \cdot (\bar{a}+b) = a\bar{a}+ab+b\bar{a}+bb = 0+b(a+\bar{a})+b = b+b = b$ **TRUE**
- (next slide)
- You can use NOR(s) with clever wiring to simulate AND, OR, & NOT.
 $\text{NOR}(a,a) = \bar{a+a} = \bar{a} = \bar{a}$
 Using this NOT, can we make a NOR an OR? An And?
TRUE

- $(a+b) \cdot (\bar{a}+b) = b$
- N-input gates can be thought of cascaded 2-input gates. I.e., $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$ where Δ is one of AND, OR, XOR, NAND
- You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	123
a:	FFF
a:	FFT
b:	FTF
b:	FTT
c:	TFF
d:	TFT
d:	TTF
e:	TTT

CS61C L25 Representations of Combinational Logic Circuits (24) Garcia, Spring 2013 © UCB

Peer Instruction Answer (B)

- N-input gates can be thought of cascaded 2-input gates. I.e., $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$ where Δ is one of AND, OR, XOR, NAND...**FALSE**

Let's confirm!

CORRECT 3-input				
XYZ	AND	OR	XOR	NAND
000	0	0	0	1
001	0	1	1	1
010	0	1	1	1
011	0	1	0	1
100	0	1	1	1
101	0	1	0	1
110	0	1	0	1
111	1	1	1	0

CORRECT 2-input				
YZ	AND	OR	XOR	NAND
00	0	1	0	1
01	0	1	1	1
10	0	1	1	1
11	1	1	0	0

CS61C L25 Representations of Combinational Logic Circuits (25) Garcia, Spring 2013 © UCB

"And In conclusion..."

- Pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You'll see them again in 150, 152 & 164
- Use this table and techniques we learned to transform from 1 to another

CS61C L25 Representations of Combinational Logic Circuits (26) Garcia, Spring 2013 © UCB