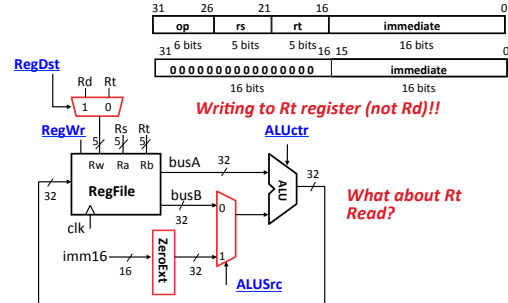


CS 61C: Great Ideas in Computer Architecture (Machine Structures)
 Lecture 30: Single-Cycle CPU
 Datapath Control Part 2

Instructor: Dan Garcia
<http://inst.eecs.berkeley.edu/~cs61c>


3c: Logical Op (or) with Immediate

$R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



3d: Load Operations

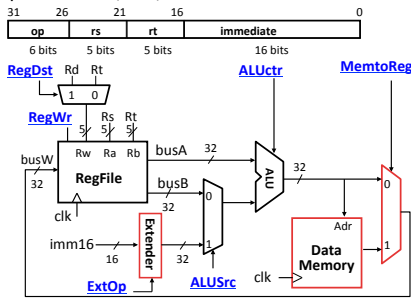
$R[rt] = \text{Mem}[R[rs] + \text{SignExt}[imm16]]$
 Example: lw rt, rs, imm16



3e: Store Operations

$\text{Mem}[R[rs] + \text{SignExt}[imm16]] = R[rt]$


Ex.: sw rt, rs, imm16

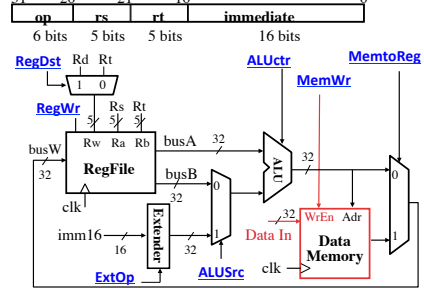

3e: Store Operations

$\text{Mem}[R[rs] + \text{SignExt}[imm16]] = R[rt]$







Ex.: sw rt, rs, imm16



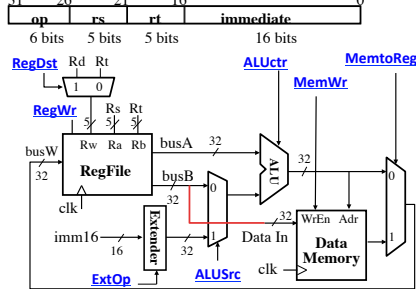


3f: The Branch Instruction

beq rs, rt, imm16

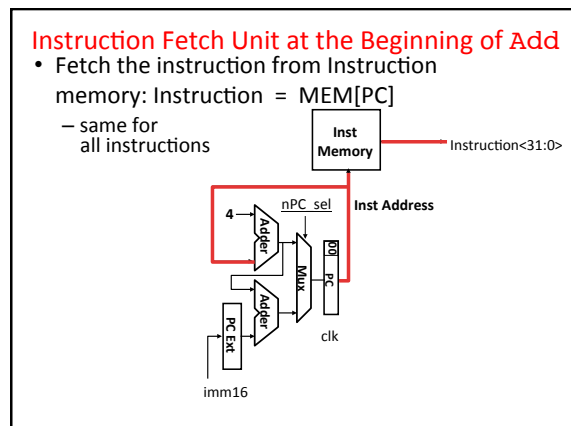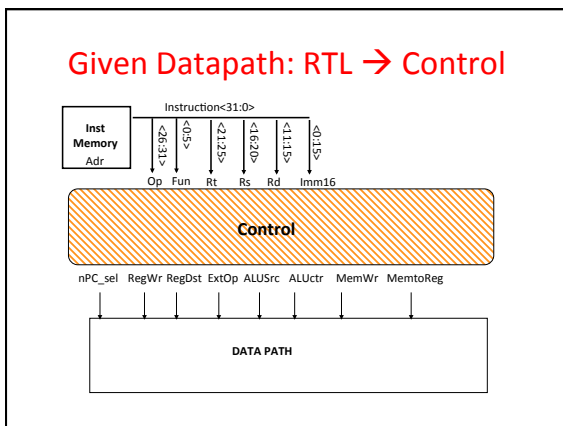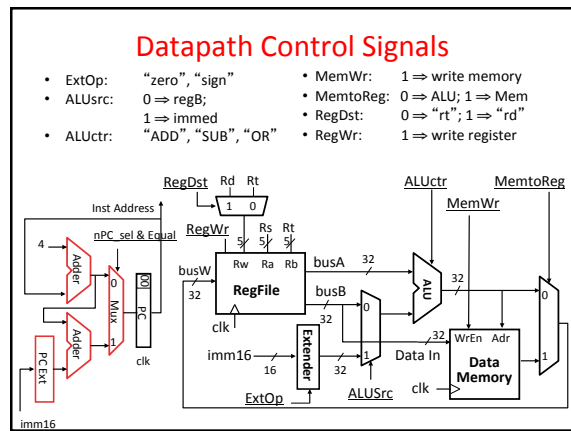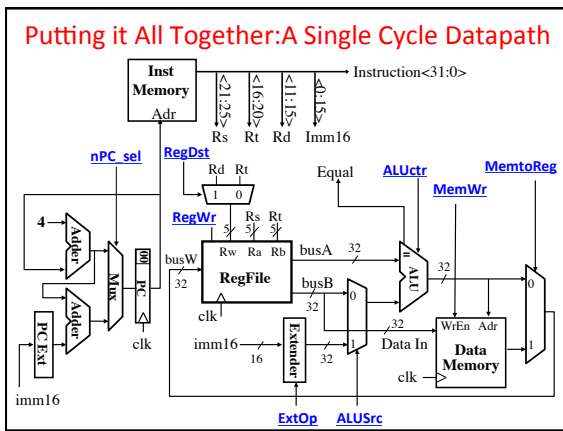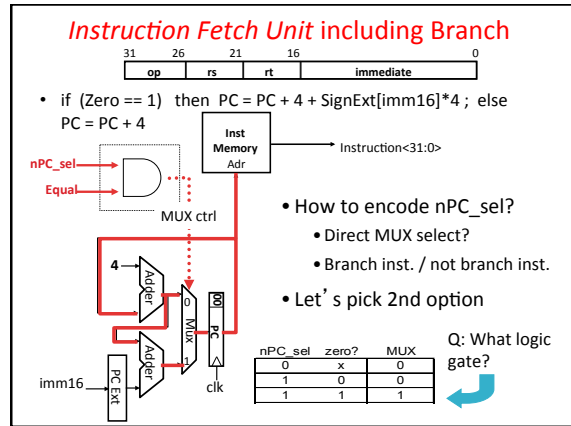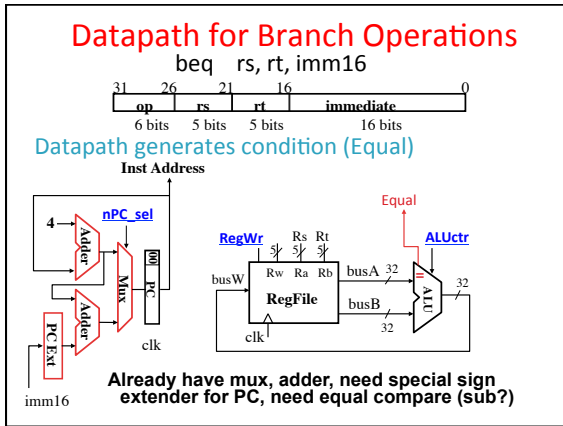- mem[PC] Fetch the instruction from memory
- Equal = $R[rs] == R[rt]$ Calculate branch condition
- if (Equal) Calculate the next instruction's address
 - $PC = PC + 4 + (\text{SignExt}(imm16) \times 4)$
- else
 - $PC = PC + 4$



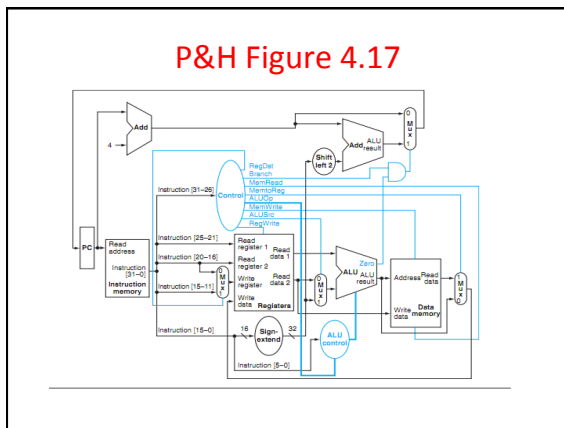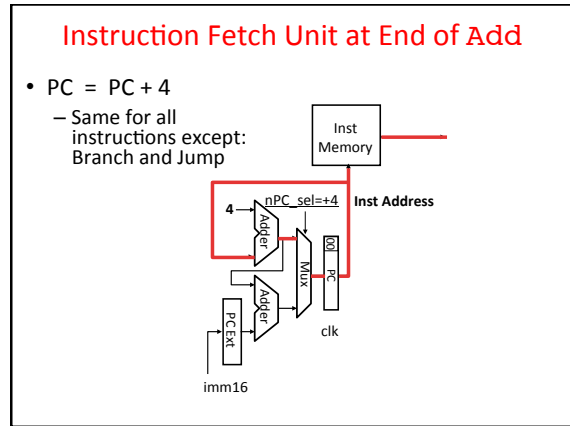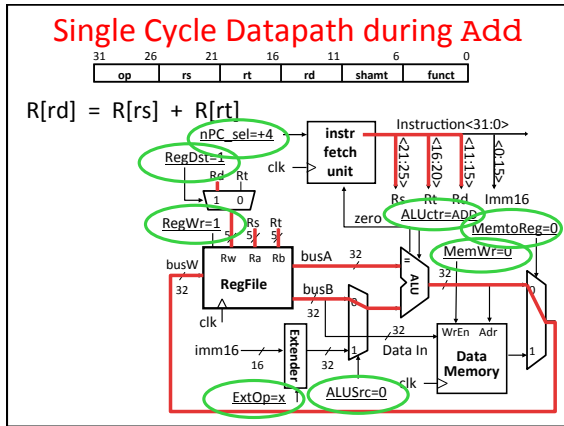

Summary of the Control Signals (1/2)

inst Register Transfer

```

add  R[rd] ← R[rs] + R[rt]; PC ← PC + 4
     ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"

sub  R[rd] ← R[rs] - R[rt]; PC ← PC + 4
     ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"

ori  R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
     ALUSrc=Im, Extop="z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"

lw   R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
     ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
     nPC_sel = "+4"

sw   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rs]; PC ← PC + 4
     ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq  if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00
     else PC ← PC + 4
     nPC_sel = "br", ALUctr = "SUB"
    
```

Summary of the Control Signals (2/2)

See Appendix A

func	10 0000	10 0010	We Don't Care :-)				
op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

R-type	op	rs	rt	rd	shamt	funct	add, sub
I-type	op	rs	rt	immediate			ori, lw, sw, beq
J-type	op	target address					jump

Boolean Expressions for Controller

```

RegDst  = add + sub
ALUSrc  = ori + lw + sw
MemtoReg = lw
RegWrite = add + sub + ori + lw
MemWrite = sw
nPCsel  = beq
Jump    = jump
ExtOp   = lw + sw
ALUctr[0] = sub + beq  (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1] = or
    
```

Where:


```

rtype = ~op3 * ~op2 * ~op1 * ~op0 * ~op0
ori   = ~op3 * ~op2 * op1 * op0 * ~op0 * op0
lw    = op3 * ~op1 * ~op2 * ~op2 * op1 * op0
sw    = op3 * ~op1 * op2 * ~op2 * op1 * op0
beq   = ~op3 * ~op1 * ~op2 * op2 * ~op1 * ~op0
jump  = ~op3 * ~op1 * ~op2 * ~op2 * op1 * ~op0
    
```

add = rtype * func₃ * ~func₄ * ~func₃ * ~func₂ * ~func₁ * ~func₀
sub = rtype * func₃ * ~func₄ * ~func₃ * ~func₂ * func₁ * ~func₀

How do we implement this in gates?


Controller Implementation

 


Summary: Single-cycle Processor

• Five steps to design a processor:

 
1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - Formulate Logic Equations
 - Design Circuits
5. Assemble the control logic




Single Cycle Datapath during Jump

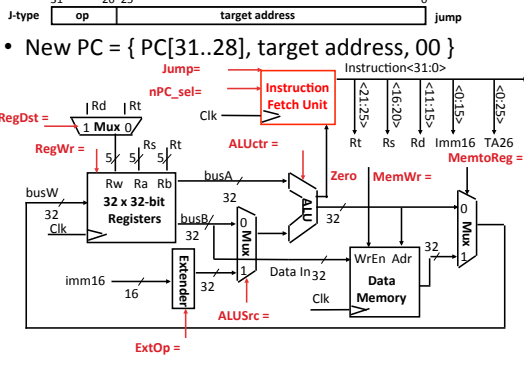

Single Cycle Datapath during Jump

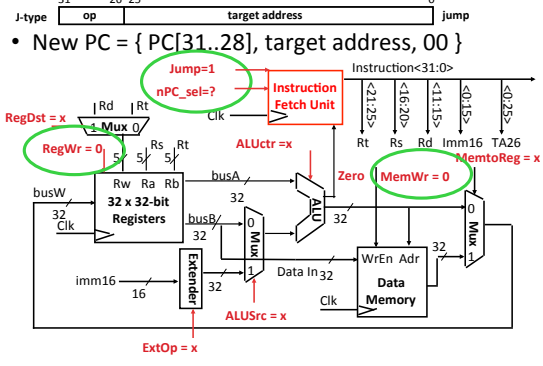

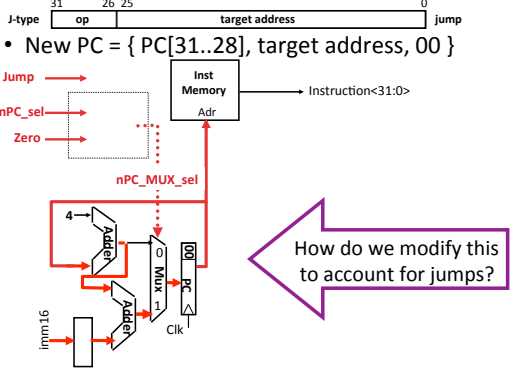Instruction Fetch Unit at the End of Jump



Instruction Fetch Unit at the End of Jump

