

Lecture #14
Introduction to Synchronous Digital Systems


2007-7-18




Scott Beamer, Instructor



Review

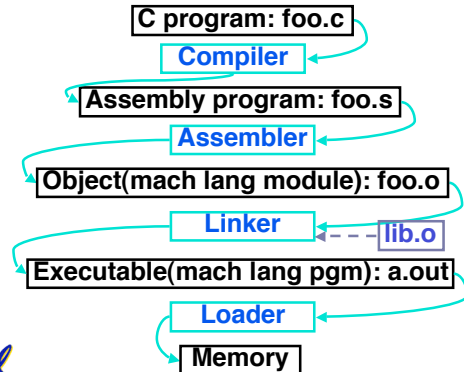

What are "Machine Structures"?

 

Coordination of many *levels of abstraction*

We'll investigate lower abstraction layers!
(contract between HW & SW)



Below the Program


• High-level language program (in C)

```
swap int v[], int k){
    int temp;
    temp = v[k];
    v[k] = v[k+1];
    v[k+1] = temp;
}
```



• Assembly language program (for MIPS)
 
```
swap: sll $2, $5, 2
      add $2, $4, $2
      lw $15, 0($2)
      lw $16, 4($2)
      sw $16, 0($2)
      sw $15, 4($2)
      jr $31
```



• Machine (object) code (for MIPS)

```
000000 00000 00101 00010000010000000
000000 00100 00010 00010000000100000 . . .
```



Synchronous Digital Systems

The hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System

Synchronous:

- Means all operations are coordinated by a central **clock**.
- It keeps the "heartbeat" of the system!

Digital:

- Mean all values are represented by discrete values
- Electrical signals are treated as 1's and 0's and grouped together to form words.



Logic Design

- Next 2 weeks: we'll study how a modern processor is built; starting with basic elements as building blocks.
- Why study hardware design?
 - Understand capabilities and limitations of hardware in general and processors in particular.
 - What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
 - Background for more detailed hardware courses (CS 150, CS 152)
 - There is just so much you can do with processors. At some point you may need to design your own custom hardware.




Logic Gates

- Basic building blocks are logic *gates*.
 - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
 - Can build gates with transistors and resistors
- Then found theoretical basis for design
 - Can represent and reason about gates with truth tables and Boolean algebra
 - Assume know some truth tables and Boolean algebra from a math or circuits course.
 - Section B.2 in the textbook has a review



Physical Hardware

 

Let's look closer...

PowerPC




Transistors 101

MOSFET

- Metal-Oxide-Semiconductor Field-Effect Transistor
- Come in two types:
 - n-type NMOSFET
 - p-type PMOSFET


For n-type (p-type opposite)

 - If voltage not enough between G & S, transistor turns "off" (cut-off) and Drain-Source NOT connected
- If the G & S voltage is high enough, transistor turns "on" (saturation) and Drain-Source ARE connected



Transistor Circuit Rep. vs. Block diagram

 - Chips is composed of nothing but transistors and wires.
- Small groups of transistors form useful building blocks.




a	b	c
0	0	1
0	1	1
1	0	1
1	1	0


- Block are organized in a hierarchy to build higher-level blocks: ex: adders.




Signals and Waveforms: Clocks

 

Signals and Waveforms: Adders

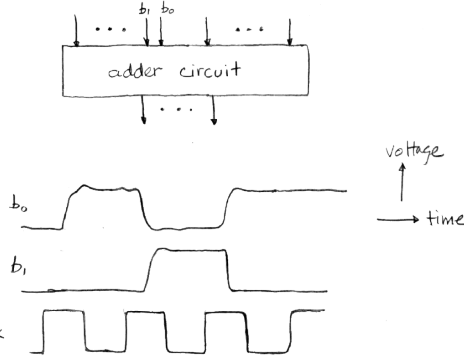


Signals and Waveforms: Grouping

 

Bus - more than one signal treated as a unit

Signals and Waveforms: Circuit Delay

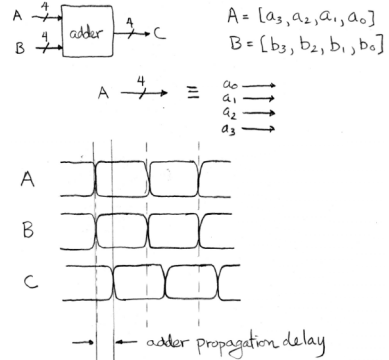


adder propagation delay

Type of Circuits

- Synchronous Digital Systems are made up of two basic types of circuits:
 - **Combinational Logic (CL) circuits**
 - Our previous adder circuit is an example.
 - **Output is a function of the inputs only.**
 - Similar to a pure function in mathematics, $y = f(x)$. (No way to store information from one invocation to the next. No side effects)
 - **State Elements:** circuits that store information.

Cal

Circuits with STATE (e.g., register)

 

Cal

Peer Instruction

- SW can peek at HW (past ISA abstraction boundary) for optimizations
- SW can depend on particular HW implementation of ISA
- Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TFF
8:	TTT

Cal

And in semi conclusion...

- ISA is very important abstraction layer
 - Contract between HW and SW
- Basic building blocks are logic **gates**
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
 - Stateless Combinational Logic (&, |, ~)
 - State circuits (e.g., registers)

Cal


Administrivia

- Proj2 due Friday
- Midterm 7-10p on Monday in 10 Evans
- Midterm Review 11-2 on Friday, probably in 10 or 60 Evans
- Scott is not holding OH on Monday, but is holding extra OH on Friday 3-5



Accumulator Example

 Why do we need to control the flow of information?




Want: $S=0;$
for $(i=0; i<n; i++)$
 $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S.



First try...Does this work?

 



Nope!

Reason #1... What is there to control the next iteration of the 'for' loop?

Reason #2... How do we say: 's=0'?




Second try...How about this?

  

Register is used to hold up the transfer of data to adder.



Register Details...What's inside?

 


- n instances of a "Flip-Flop"
- Flip-flop name because the output flips and flops between and 0,1
- D is "data", Q is "output"
- Also called "d-type Flip-Flop"




What's the timing of a Flip-flop? (1/2)

- Edge-triggered d-type flip-flop
 - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."

Example waveforms:

 

What's the timing of a Flip-flop? (2/2)

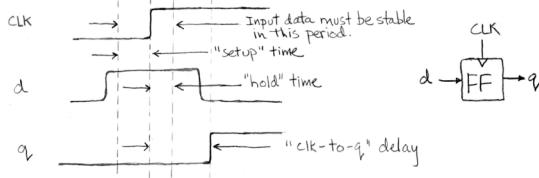

• Edge-triggered d-type flip-flop

- This one is "positive edge-triggered"

• "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."




Recap of Timing Terms


- **Clock (CLK)** - steady square wave that synchronizes system
- **Setup Time** - when the input must be stable before the rising edge of the CLK
- **Hold Time** - when the input must be stable after the rising edge of the CLK
- **"CLK-to-Q" Delay** - how long it takes the output to change, measured from the rising edge
- **Flip-flop** - one bit of state that samples every rising edge of the CLK
- **Register** - several bits of state that samples on rising edge of CLK or on LOAD



 
Accumulator Revisited (proper timing 1/2)



 
- Reset input to register is used to force it to all zeros (takes priority over D input).
- S_{i-1} holds the result of the $i^{th}-1$ iteration.
- Analyze circuit timing starting at the output of the register.



 Accumulator Revisited (proper timing 2/2)



 - reset signal shown.
- Also, in practice X might not arrive to the adder at the same time as S_{i-1}
- S_i temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.



Peer Instruction

- CLK-to-Q delays propagate in a synchronized circuit
- The hold time should be less than the CLK-to-Q delay
- The minimum period of a usable synchronous circuit is at least the CLK-to-Q delay

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TFB
8:	TTT



"And In conclusion..."

- We use feedback to maintain state
- Register files used to build memories
- D Flip-Flops used to build Register files
- Clocks tell us when D Flip-Flops change
 - Setup and Hold times important

