

inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

Lecture #14
Introduction to Synchronous Digital Systems


2007-7-18




Scott Beamer, Instructor



Review

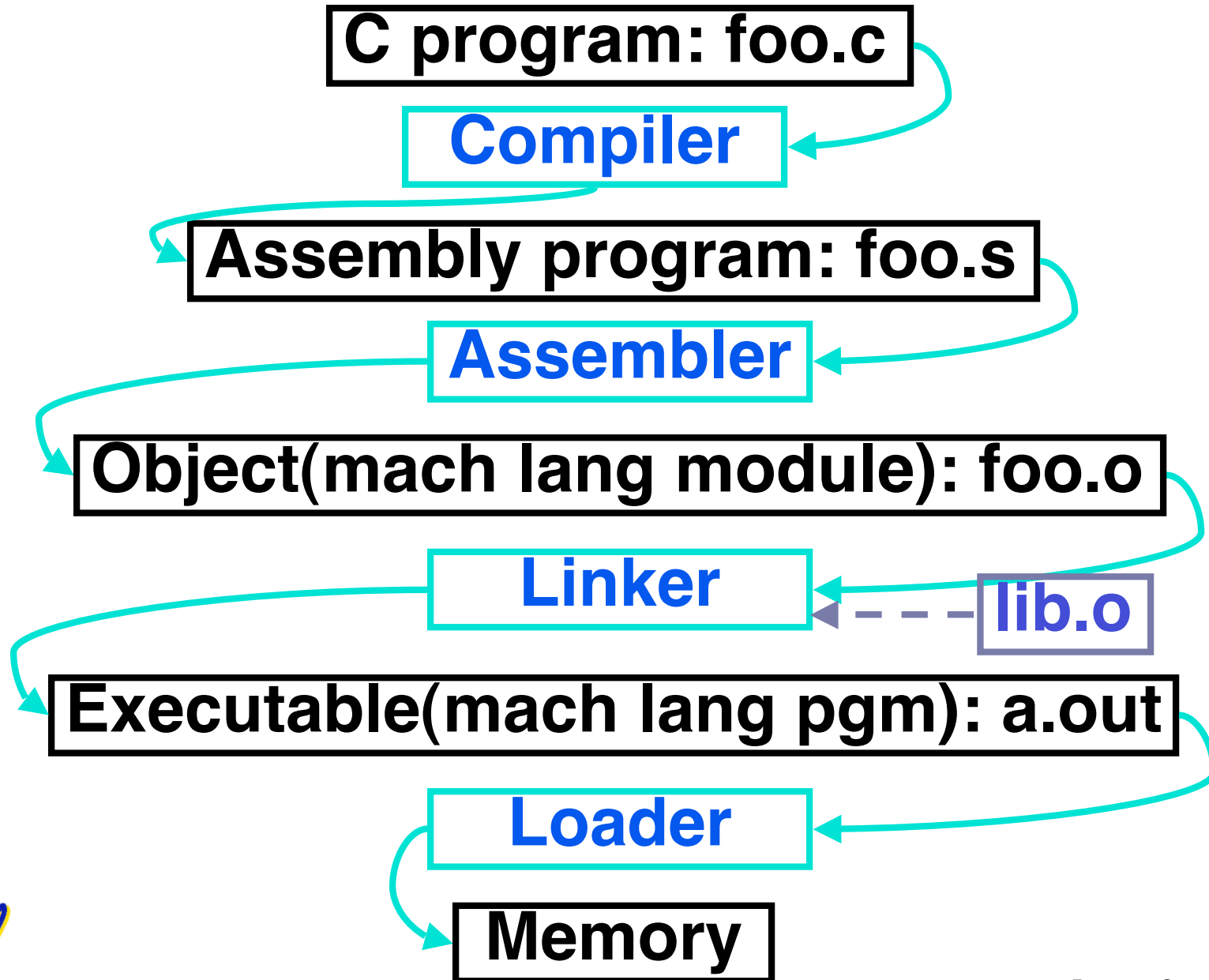

What are “Machine Structures”?

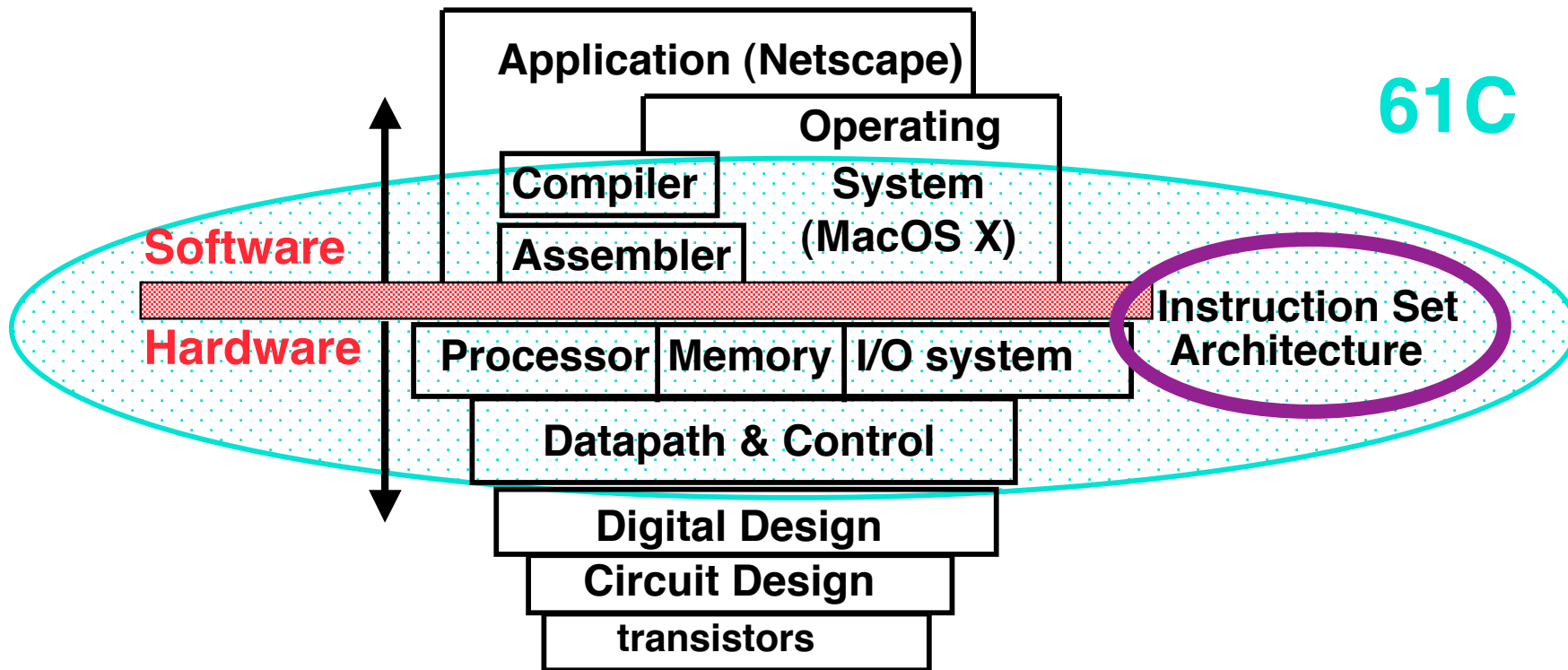

Coordination of many *levels of abstraction*


We'll investigate lower abstraction layers!
(contract between HW & SW)



Below the Program


- High-level language program (in C)
 
```
swap int v[], int k){  
    int temp;  
    temp = v[k];  
    v[k] = v[k+1];  
    v[k+1] = temp;  
}
```




- Assembly language program (for MIPS)
 
```
swap: sll    $2, $5, 2  
      add    $2, $4, $2  
      lw     $15, 0($2)  
      lw     $16, 4($2)  
      sw     $16, 0($2)  
      sw     $15, 4($2)  
      jr     $31
```



- Machine (object) code (for MIPS)
 
```
000000 00000 00101 0001000010000000  
000000 00100 00010 0001000000100000 . . .
```



Synchronous Digital Systems

The hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System

Synchronous:

- Means all operations are coordinated by a central **clock**.
 - It keeps the “heartbeat” of the system!

Digital:

- Mean all values are represented by discrete values
- Electrical signals are treated as 1's and 0's and grouped together to form words.



Logic Design

- **Next 2 weeks: we'll study how a modern processor is built; starting with basic elements as building blocks.**
- **Why study hardware design?**
 - **Understand capabilities and limitations of hardware in general and processors in particular.**
 - **What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
 - **Background for more detailed hardware courses (CS 150, CS 152)**
 - **There is just so much you can do with processors. At some point you may need to design your own custom hardware.**




Logic Gates

- **Basic building blocks are logic *gates*.**
 - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
 - Can build gates with transistors and resistors
- **Then found theoretical basis for design**
 - Can represent and reason about gates with truth tables and Boolean algebra
 - Assume know some truth tables and Boolean algebra from a math or circuits course.
 - Section B.2 in the textbook has a review



Physical Hardware

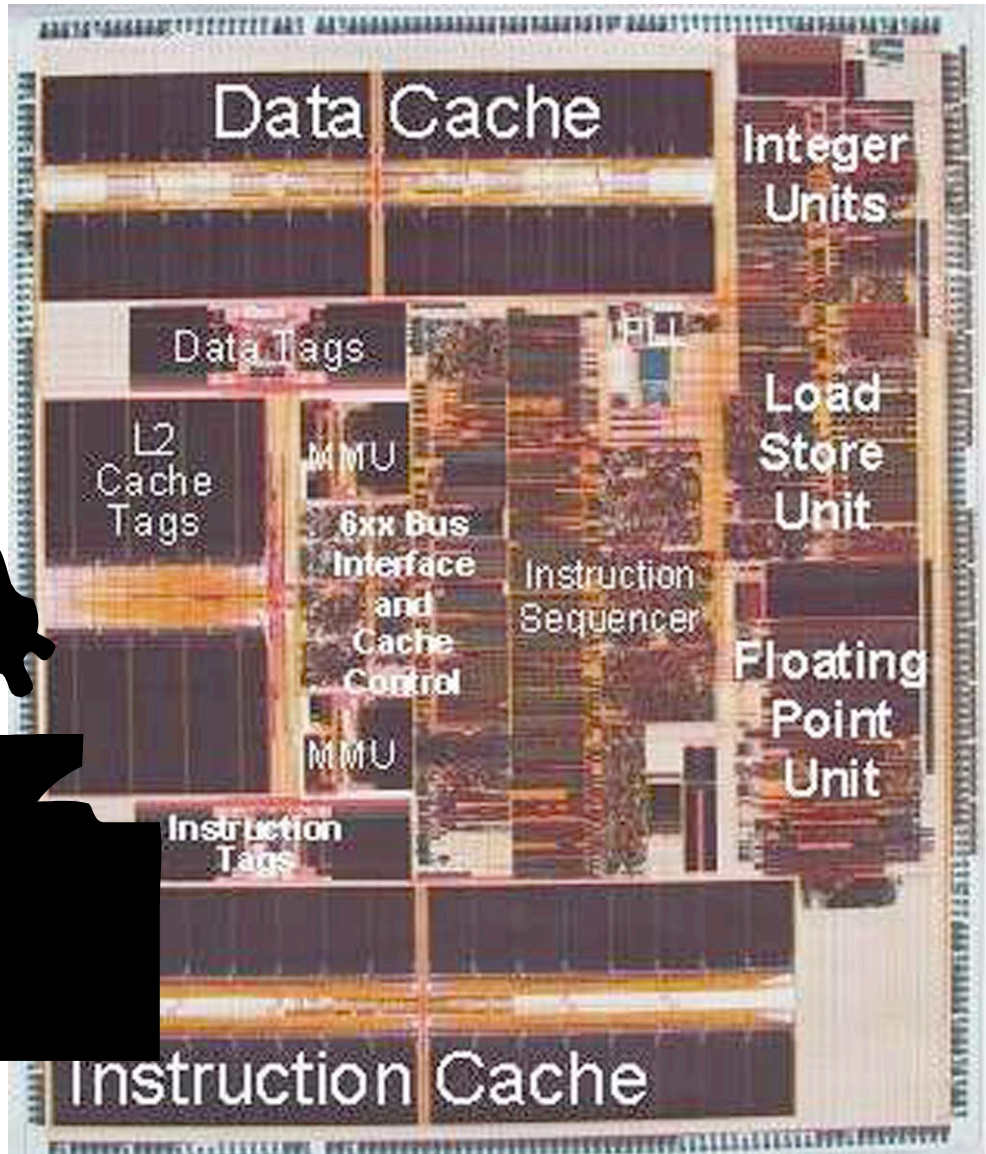

Let's look closer...



Transistors 101

- **MOSFET**

- **Metal-Oxide-Semiconductor Field-Effect Transistor**



- **Come in two types:**

- **n-type** NMOSFET
- **p-type** PMOSFET

- **For n-type (p-type opposite)**

- **If voltage not enough between G & S, transistor turns “off” (cut-off) and Drain-Source NOT connected**

  - **If the G & S voltage is high enough, transistor turns “on” (saturation) and Drain-Source ARE connected**




Side view



www.wikipedia.org/wiki/Mosfet

Transistor Circuit Rep. vs. Block diagram

 
- Chips is composed of nothing but transistors and wires.
- Small groups of transistors form useful building blocks.





a	b	c
0	0	1
0	1	1
1	0	1
1	1	0

- Block are organized in a hierarchy to build higher-level blocks: ex: adders.


Signals and Waveforms: Clocks

 

Signals and Waveforms: Adders

  

Signals and Waveforms: Grouping

 



Bus - more than one signal treated as a unit

Signals and Waveforms: Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

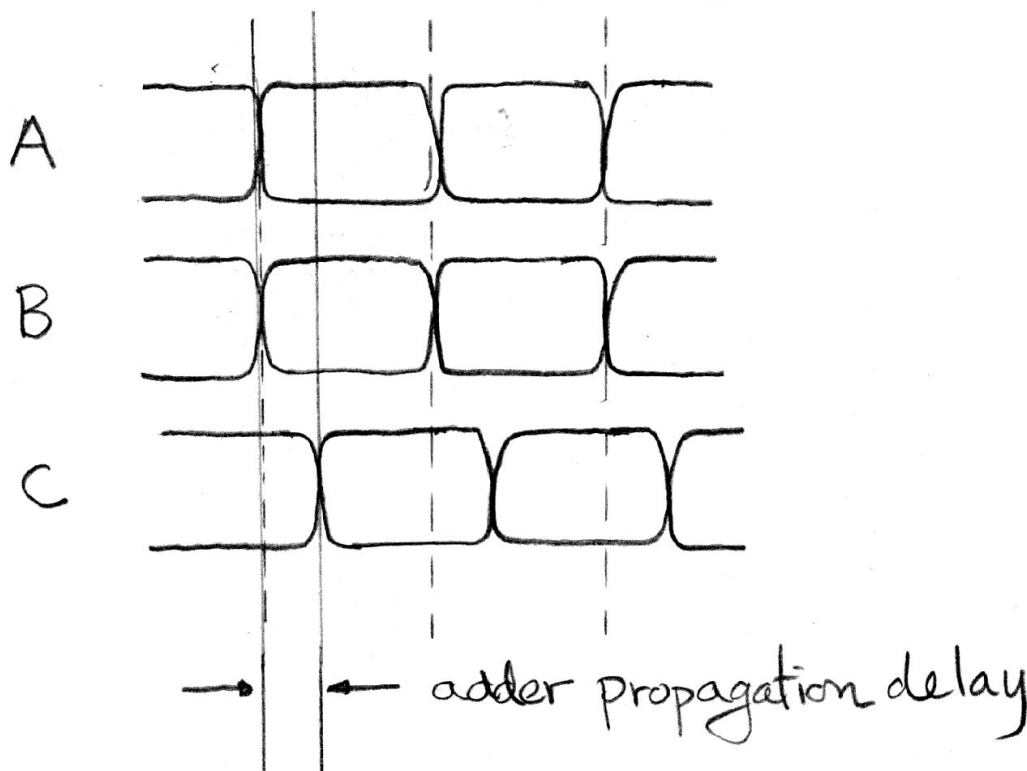 


Type of Circuits

- Synchronous Digital Systems are made up of two basic types of circuits:
- Combinational Logic (CL) circuits
 - Our previous adder circuit is an example.
 - Output is a function of the inputs only.
 - Similar to a pure function in mathematics, $y = f(x)$. (No way to store information from one invocation to the next. No side effects)
- State Elements: circuits that store information.



Circuits with STATE (e.g., register)

 


Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Sample Debugging Waveform

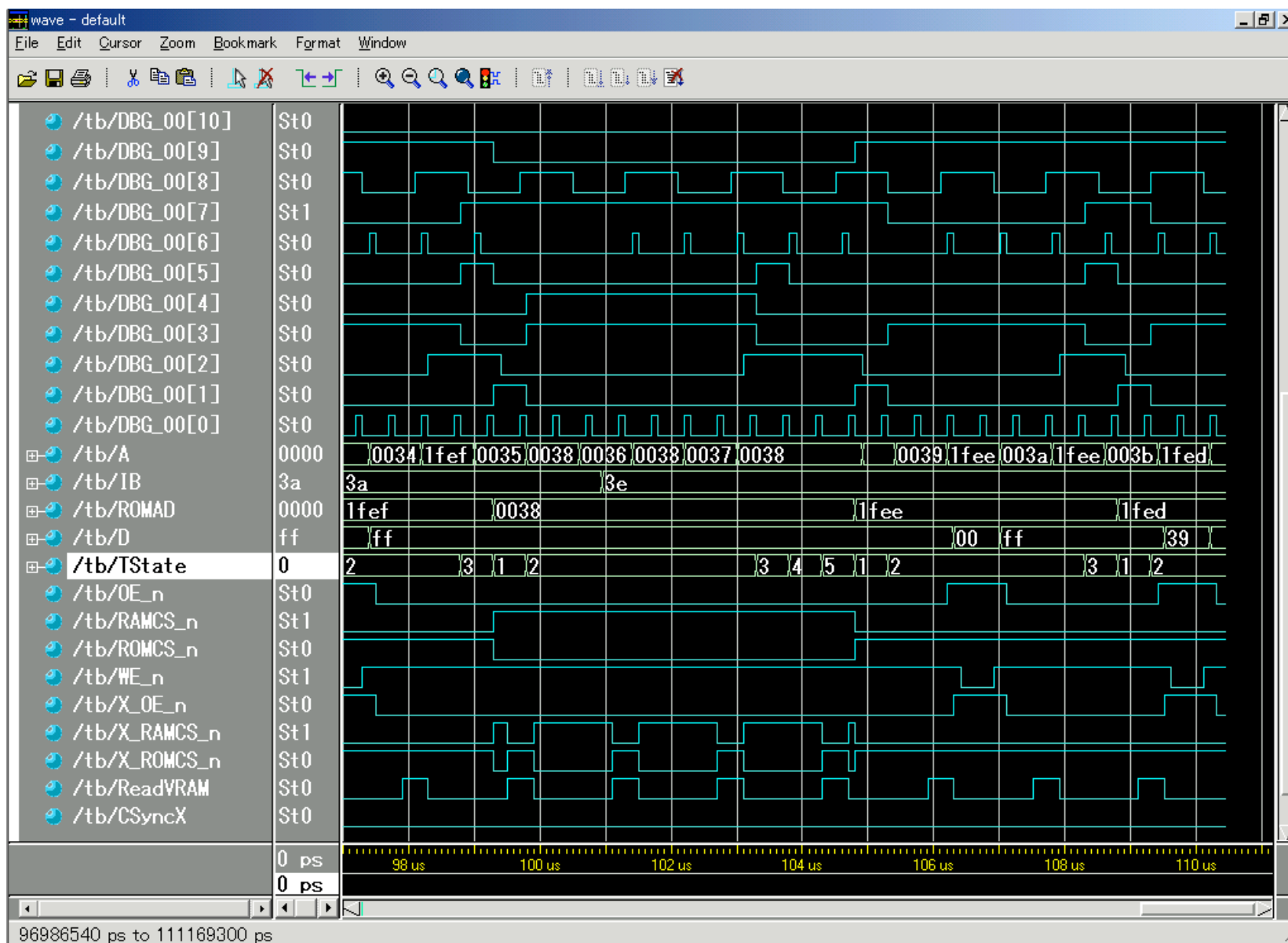

And in semi conclusion...

- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
 - **Stateless Combinational Logic (&,!,~)**
 - **State circuits (e.g., registers)**




Administrivia

- **Proj2** due Friday
- **Midterm** 7-10p on Monday in 10 Evans
- **Midterm Review** 11-2 on Friday, probably in 10 or 60 Evans
- **Scott** is not holding OH on Monday, but is holding **extra OH** on Friday 3-5



Accumulator Example

 Why do we need to control the flow of information?



Want:


```
S=0;
for (i=0; i<n; i++)
    S = S + Xi
```

Assume:

- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S.



First try...Does this work?

 


Nope!

Reason #1... What is there to control the next iteration of the 'for' loop?


Reason #2... How do we say: 's=0'?



Second try...How about this?

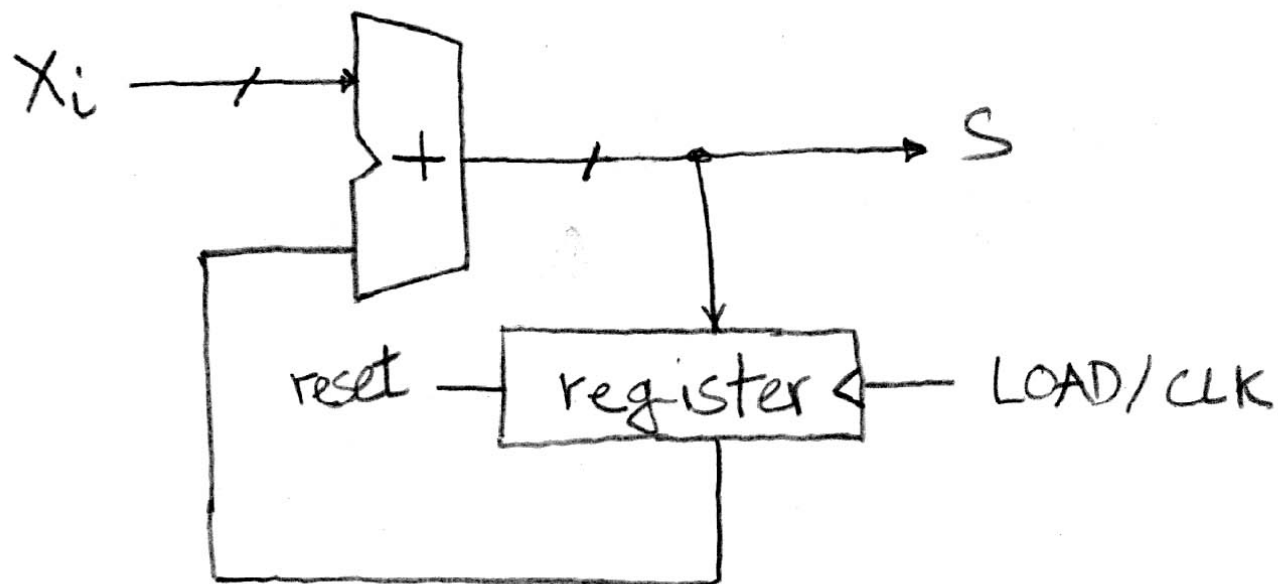


Rough
timing...

 

Register is used to hold up the transfer of data to adder.



Register Details...What's inside?

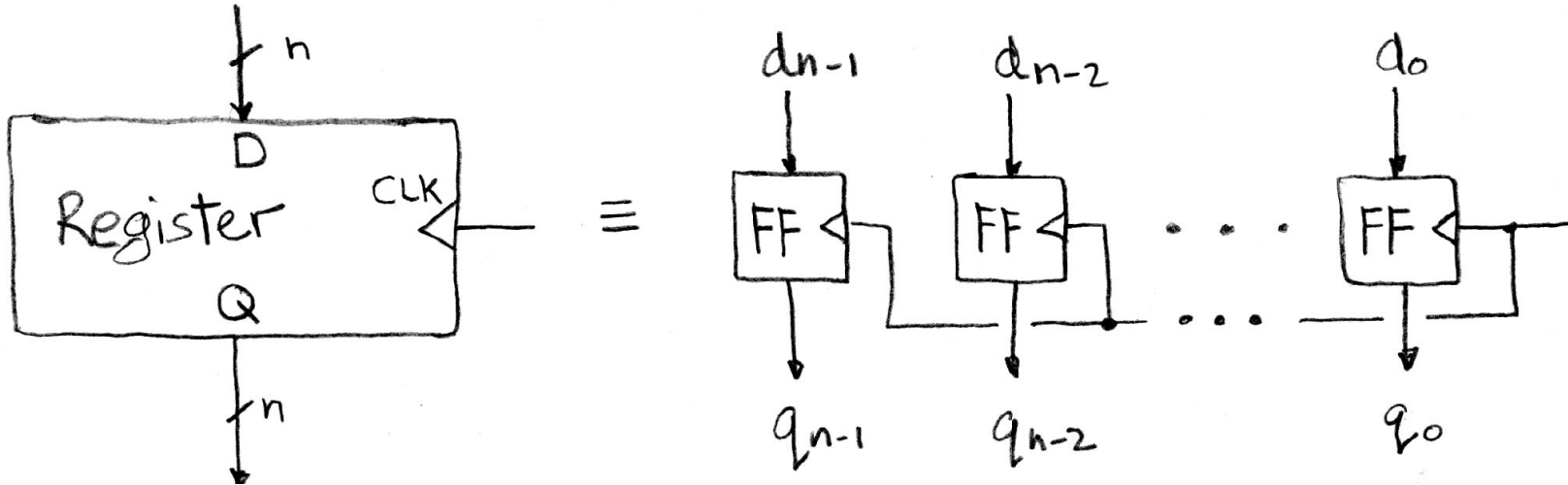

- n instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between 0,1
- D is “data”, Q is “output”
- Also called “d-type Flip-Flop”



What's the timing of a Flip-flop? (1/2)



- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”




- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

- **Example waveforms:**

  


What's the timing of a Flip-flop? (2/2)

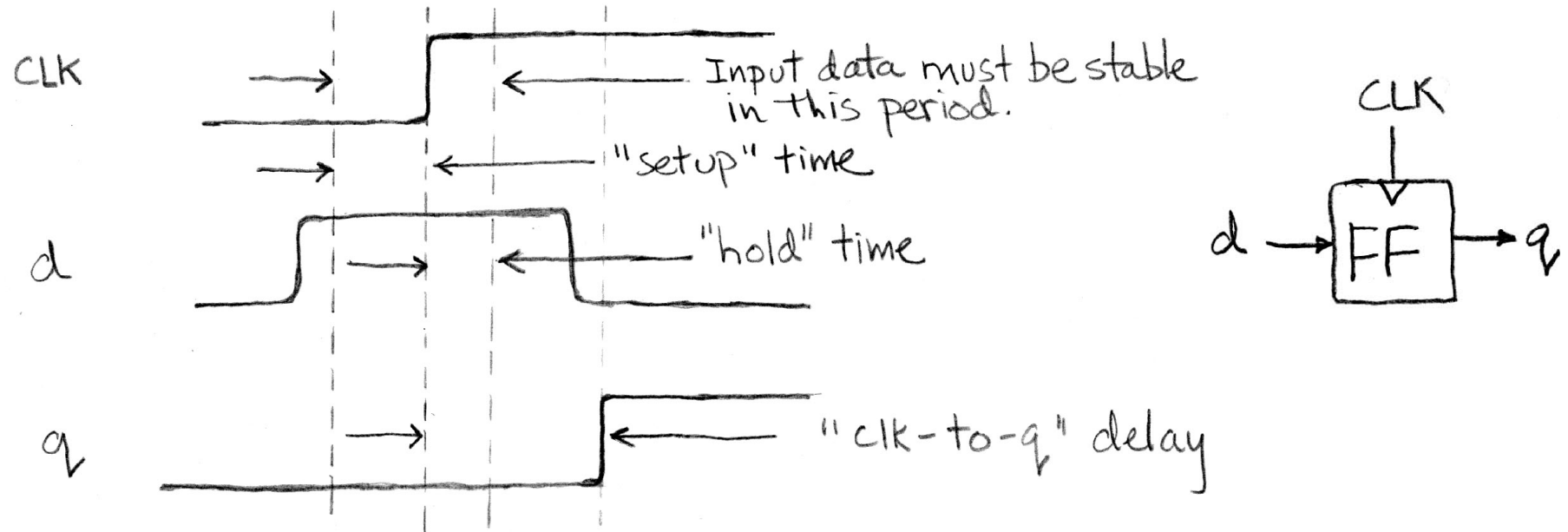

- **Edge-triggered d-type flip-flop**

- This one is "positive edge-triggered"

 


- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."

Recap of Timing Terms


- **Clock (CLK)** - steady square wave that synchronizes system
- **Setup Time** - when the input must be stable before the rising edge of the CLK
- **Hold Time** - when the input must be stable after the rising edge of the CLK
- **“CLK-to-Q” Delay** - how long it takes the output to change, measured from the rising edge
- **Flip-flop** - one bit of state that samples every rising edge of the CLK
- **Register** - several bits of state that samples on rising edge of CLK or on LOAD



 
Accumulator Revisited (proper timing 1/2)



 
- Reset input to register is used to force it to all zeros (takes priority over D input).
- S_{i-1} holds the result of the $i^{\text{th}}-1$ iteration.
- Analyze circuit timing starting at the output of the register.



 Accumulator Revisited (proper timing 2/2)



 - reset signal shown.
- Also, in practice X might not arrive to the adder at the same time as S_{i-1}
- S_i temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.



Peer Instruction

- A. CLK-to-Q delays **propagate** in a synchronized circuit
- B. The **hold time should** be less than the **CLK-to-Q delay**
- C. The minimum period of a **usable synchronous circuit** is at least the CLK-to-Q delay

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



“And In conclusion...”

- We use **feedback** to maintain **state**
- Register files used to build memories
- D Flip-Flops used to build Register files
- Clocks tell us when D Flip-Flops change
 - Setup and Hold times important

