

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

**Lecture #15**  
**Synchronous Digital Systems II**

**2007-7-19**



**Scott Beamer, Instructor**



# Review of SDS

---

**Synchronous** - Means all operations are coordinated by a central **clock**.

**Digital** - Means all values are represented by discrete values


- Electrical signals are treated as 1's and 0's and grouped together to form words.

**Combinational Logic** - functional block built only from logic gates

**State Element** - anything capable of storing data (ie registers, flip-flops...)



# What are “Machine Structures”?

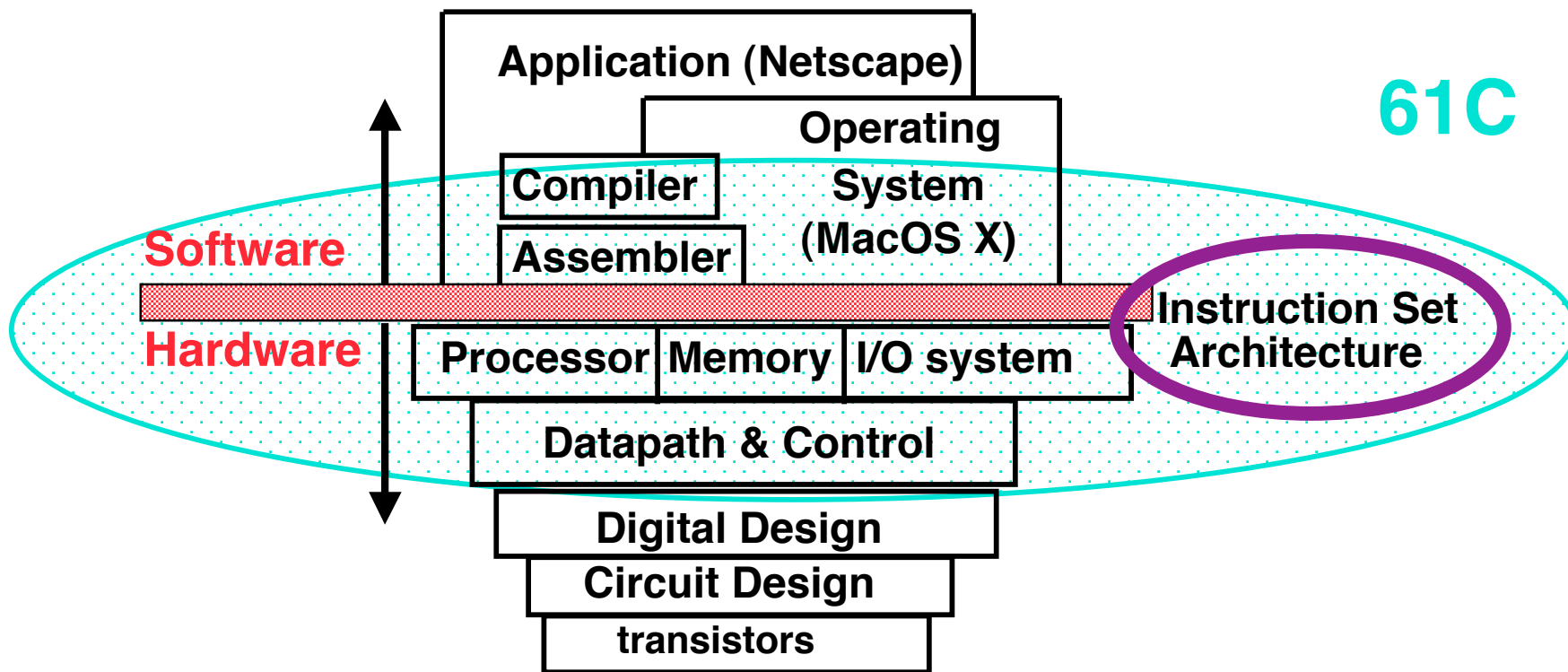


Coordination of many *levels of abstraction*

We'll investigate lower abstraction layers!  
(contract between HW & SW)



# Signals and Waveforms: Clocks

 


## • Signals

- When **digital** (this class) is only treated as 1 or 0
- Is transmitted over wires continuously
- Transmission is effectively instant
  - Implies that any wire only contains 1 value at a time



# Signals and Waveforms: Grouping

 



**Bus** - more than one signal treated as a unit

# Signals and Waveforms: Circuit Delay




$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

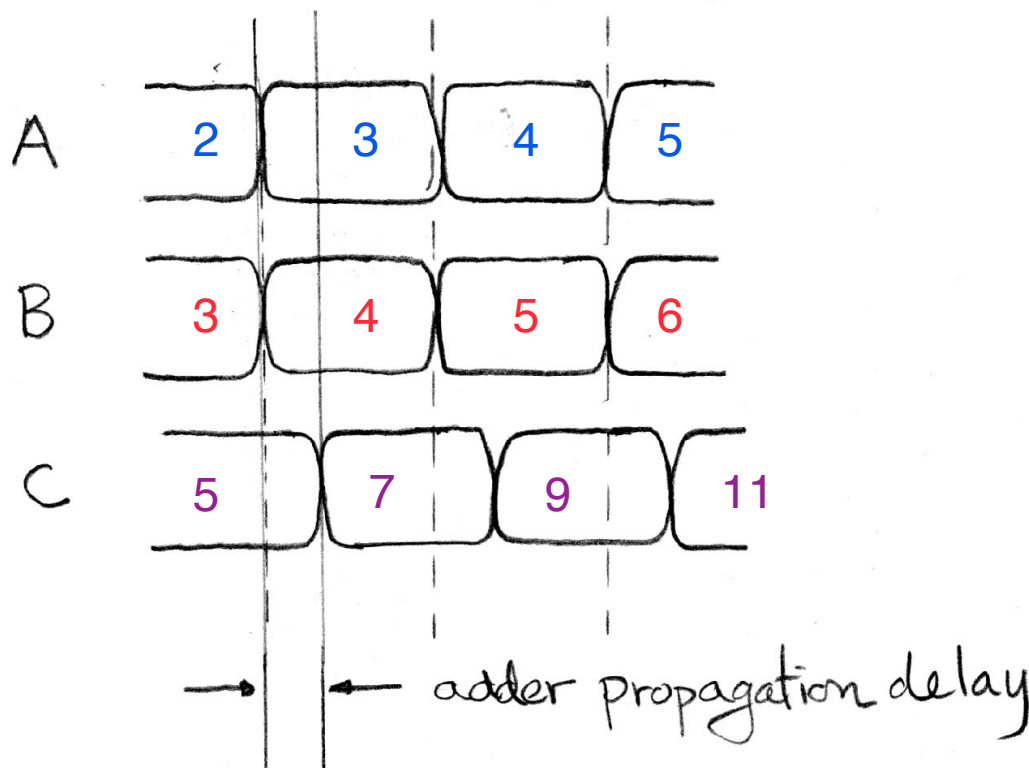 

# Circuits with STATE (e.g., register)


---

 
 
# Accumulator Example

---

Why do we need to control the flow of information?



**Want:**

```
S=0;  
for (i=0; i<n; i++)  
    S = S + Xi
```

**Assume:**


- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S.





# First try...Does this work?

---

 


**Nope!**

**Reason #1... What is there to control the next iteration of the 'for' loop?**


**Reason #2... How do we say: 's=0'?**



# Second try...How about this?

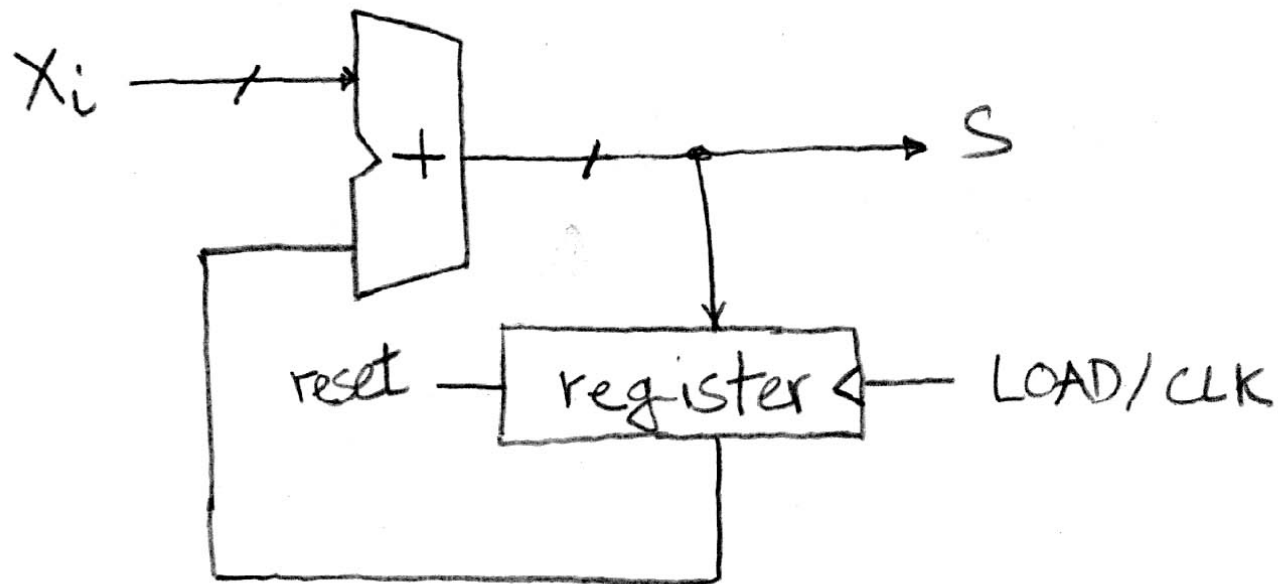


Rough timing...

 

Register is used to hold up the transfer of data to adder.



# Register Details...What's inside?

 


- $n$  instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between 0,1
- $D$  is “data”,  $Q$  is “output”
- Also called “d-type Flip-Flop”



# What's the timing of a Flip-flop? (1/2)



- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”

 


- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

- **Example waveforms:**

 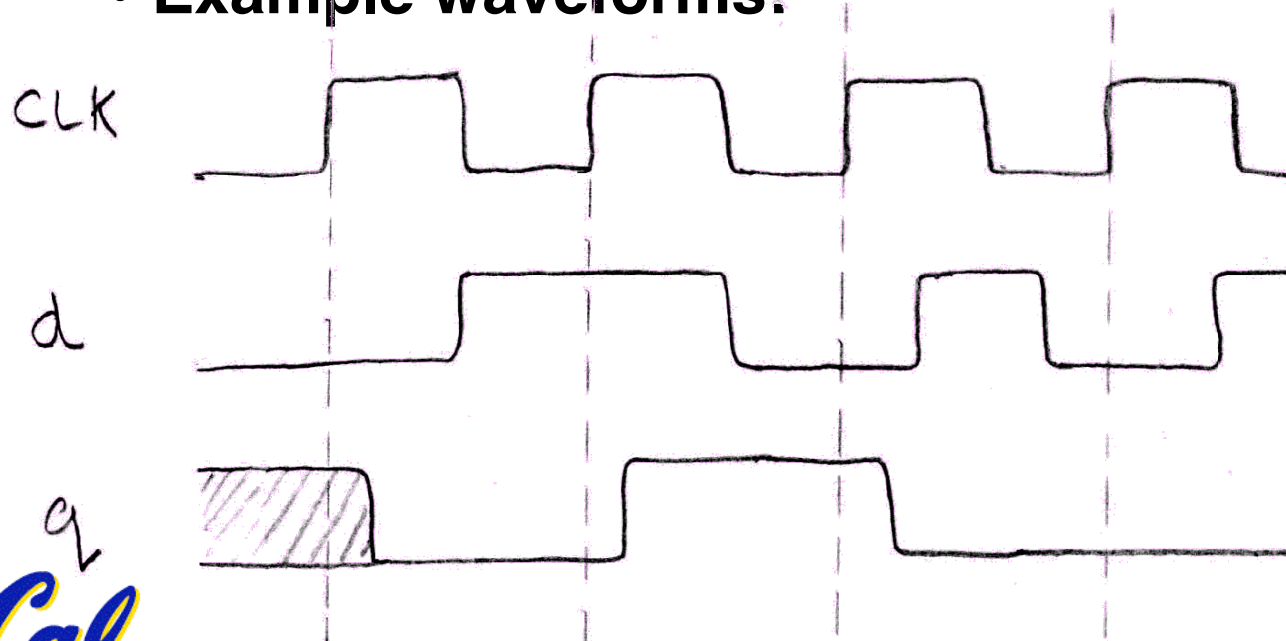

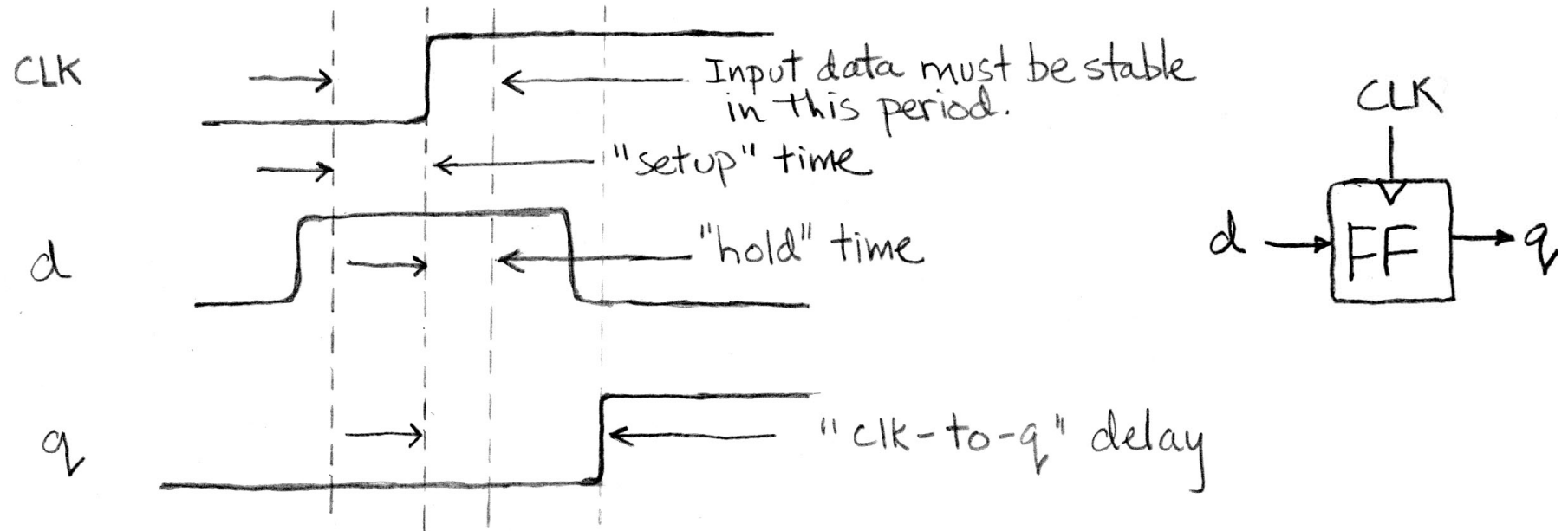
# What's the timing of a Flip-flop? (2/2)




- **Edge-triggered d-type flip-flop**

- This one is "positive edge-triggered"

 


- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."

 
# Accumulator Revisited (proper timing 1/2)



 
- Reset input to register is used to force it to all zeros (takes priority over D input).
- $S_{i-1}$  holds the result of the  $i^{\text{th}}-1$  iteration.
- Analyze circuit timing starting at the output of the register.


 
# Accumulator Revisited (proper timing 2/2)



 - reset signal shown.
- Also, in practice  $X$  might not arrive to the adder at the same time as  $S_{i-1}$
- $S_i$  temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.



# Administrivia

---

- **Proj2** due Friday
- **Midterm** 7-10p on Monday in 10 Evans
- **Midterm Review** 11-2 on Friday, probably in 10 or 60 Evans
- **Scott** is not holding OH on Monday, but is holding **extra OH** on Friday 3-5
- **Reading**: For what the textbook lacks, there are handouts on the website





 
# Finite State Machines (FSM) Introduction


---

- You have seen FSMs in other classes.
- Same basic idea.
- The function can be represented with a “state transition diagram”.
- With combinational logic and registers, any FSM can be implemented in hardware.



 
# Finite State Machine Example: 3 ones...

FSM to detect the occurrence of 3 consecutive 1's in the input.



Draw the FSM...

 


Assume state transitions are controlled by the clock:  
on each clock cycle the machine checks the inputs and moves  
to a new state and produces a new output...



 
# Hardware Implementation of FSM


... Therefore a register is needed to hold the a representation of which state the machine is in. Use a unique bit pattern for each state.



+

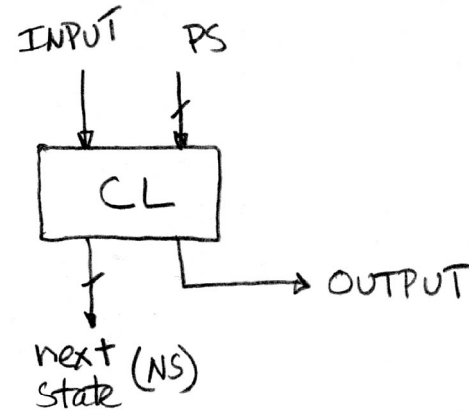


=

 

Combinational logic circuit is used to implement a function maps from *present state and input* to *next state and output*.
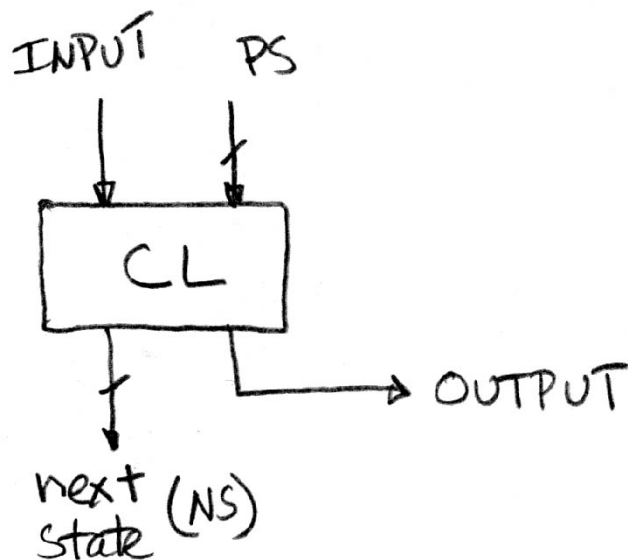
# Hardware for FSM: Combinational Logic

Next lecture we will discuss the detailed implementation, but for now can look at its functional specification, truth table form.




## Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

# Maximum Clock Frequency

---

 

**Hint...**  
**Frequency = 1/Period**


- **What is the maximum frequency of this circuit?**

$$\text{Max Delay} = \text{Setup Time} + \text{CLK-to-Q Delay} + \text{CL Delay}$$



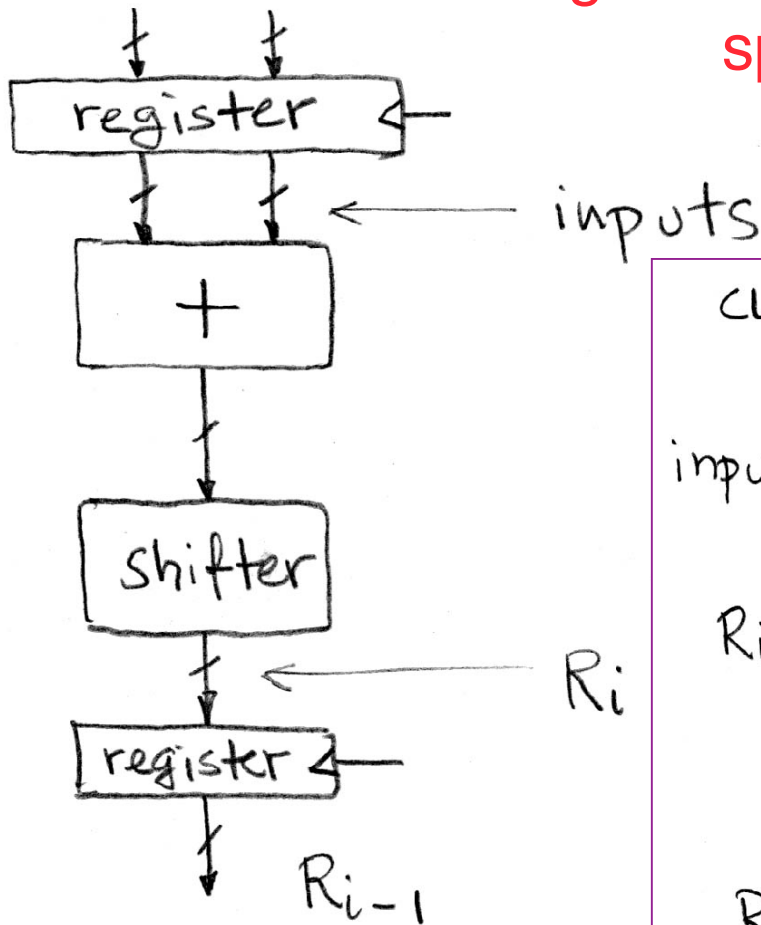
# Pipelining to improve performance (1/2)

Extra Register are often added to help speed up the clock rate.




## Timing...

 

Note: delay of 1 clock cycle from input to output.


Clock period limited by propagation delay of adder/shifter.
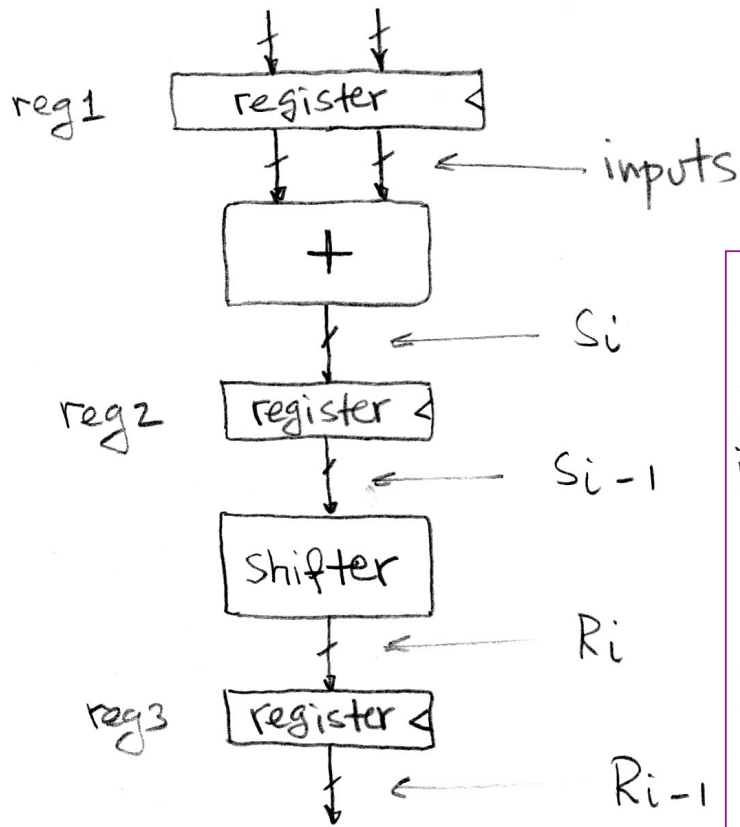
# Pipelining to improve performance (2/2)



- Insertion of register allows higher clock frequency.
- More outputs per second.

**Timing...**

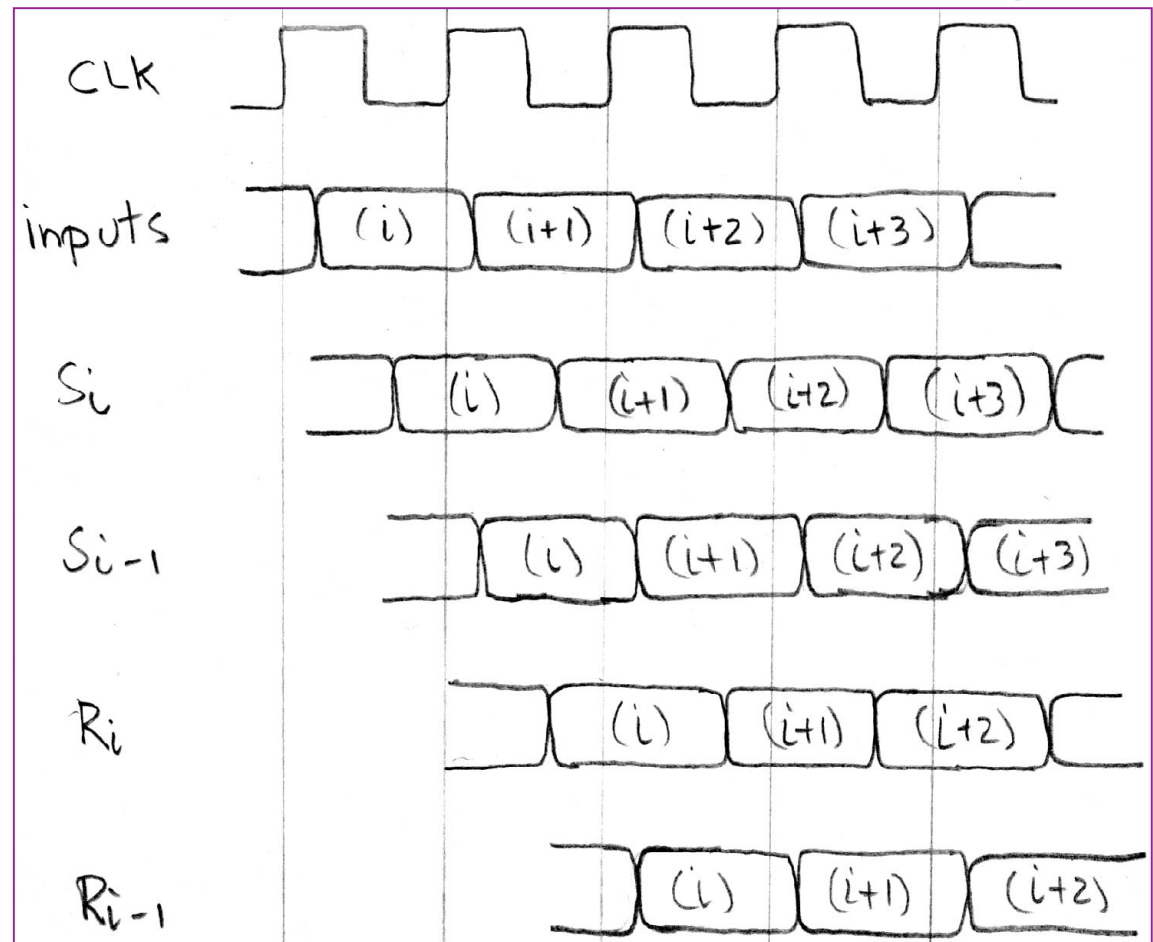

# Peer

## Instruction

---

- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT




# Peer Instruction

- A. It needs 'base case' (reg reset), way to step from  $i$  to  $i+1$  (use register + clock).
- True!
- B. D-Q has state, CL never has state!
- False!
- C. How many states would it have? Say it's  $n$ . How does it know when  $n+1$  bits have been seen?
- False!
- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1 :	FFF
2 :	FFT
3 :	FTF
4 :	FTT
5 :	TFF
6 :	TFT
7 :	TTF
8 :	TTT

# General Model for Synchronous Systems

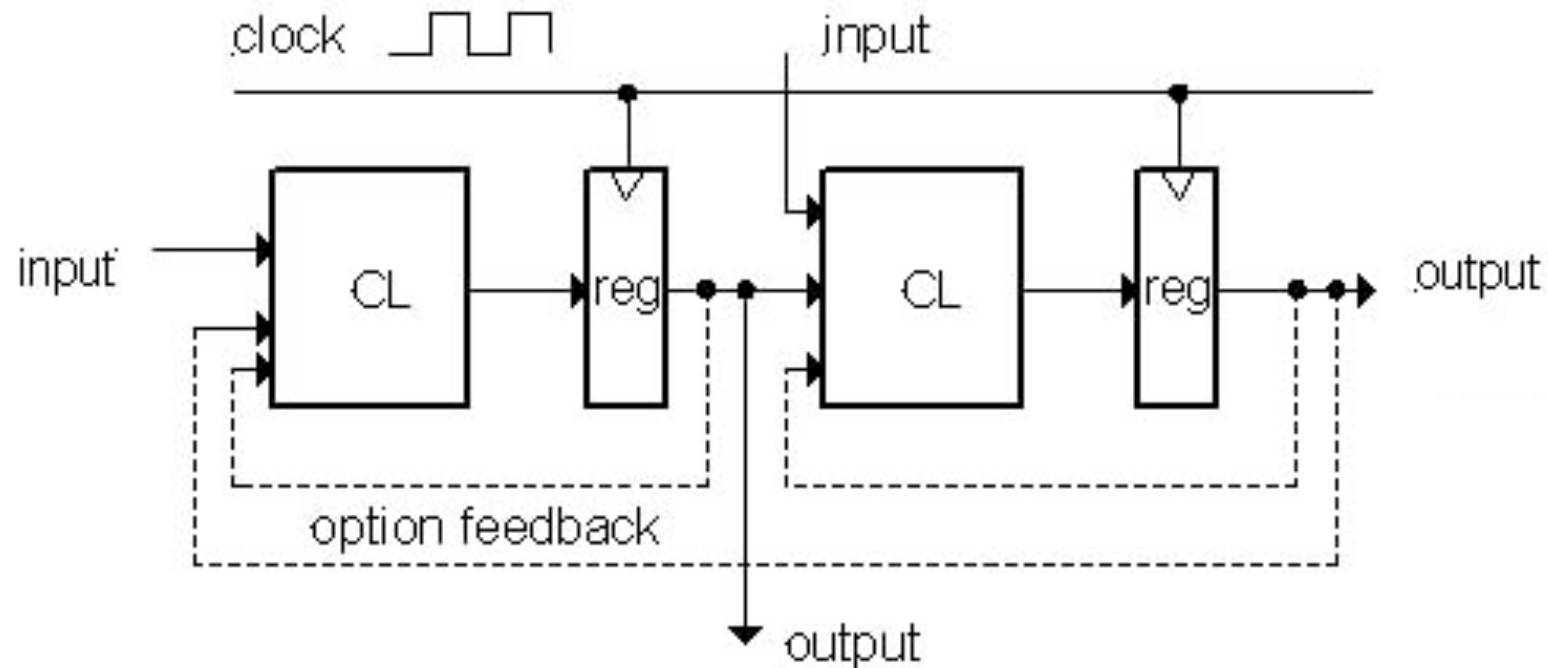

- Collection of CL blocks separated by registers.
- Registers may be back-to-back and CL blocks may be back-to-back.
- Feedback is optional.
- Clock signal(s) connects only to clock input of registers.



## “And In conclusion...”

---

- **State elements are used to:**
  - **Build memories**
  - **Control the flow of information between other state elements and combinational logic**
- **D-flip-flops used to build registers**
- **Clocks tell us when D-flip-flops change**
  - **Setup and Hold times important**
- **We pipeline long-delay CL for faster clock**
- **Finite State Machines extremely useful**
- **You'll see them again (150,152) & 164**

