

Lecture #16 – Representations of Combinatorial Logic Circuits



2007-7-23

Scott Beamer

Instructor

Plug-in Hybrid
 Upgrades
 Available




Review

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
 - Setup and Hold times important
- **TODAY**
 - Representation of CL Circuits
 - Truth Tables
 - Logic Gates
 - Boolean Algebra



Truth Tables

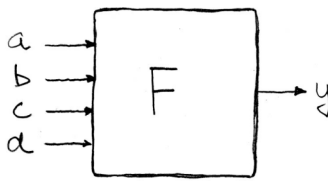

a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)




TT Example #1: 1 iff one (not both) a,b=1

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



TT Example #2: 2-bit adder

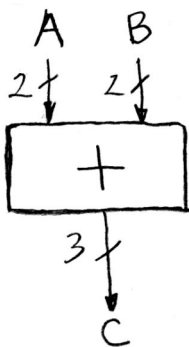

A	B	C
a_1a_0	b_1b_0	$c_2c_1c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How Many Rows?



TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

How Many Rows?




TT Example #3: 3-input majority circuit


a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1




Logic Gates (1/2)

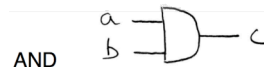

ab	c
00	0
01	0
10	0
11	1

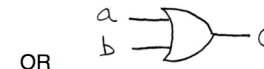

ab	c
00	0
01	1
10	1
11	1

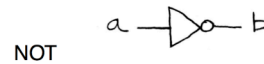


a	b
0	1
1	0



And vs. Or review – Dan's mnemonic

AND Gate

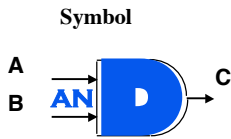


Definition


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1




Logic Gates (2/2)

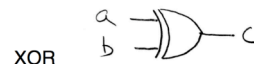

ab	c
00	0
01	1
10	1
11	0

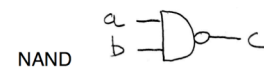

ab	c
00	1
01	1
10	1
11	0

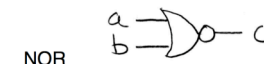

ab	c
00	1
01	0
10	0
11	0



2-input gates extend to n-inputs

• N-input XOR is the only one which isn't so obvious

• It's simple: XOR is a 1 iff the # of 1s at its input is odd ⇒

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Administrivia

• **Midterm TONIGHT 7-10pm in 10 Evans**

• Bring

- Pencils/pens
- One 8.5"x11" sheet of notes
- Green Sheet (or copy of it)

• Don't bring calculators (or other large electronics)


• **Assignments**

- HW5 due 7/26 (up today)
- HW6 due 7/29




Truth Table ⇒ Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

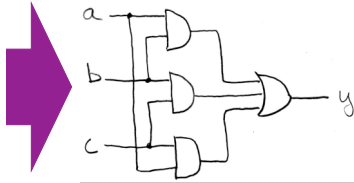

Truth Table ⇒ Gates (e.g., FSM circ.)


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

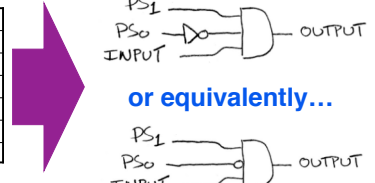

or equivalently...


Boolean Algebra

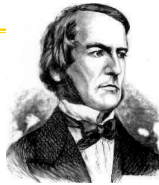- George Boole, 19th Century mathematician
- Developed a mathematical system (algebra) involving logic
 - later known as “Boolean Algebra”
- Primitive functions: AND, OR and NOT
- The power of BA is there's a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA



+ means OR, · means AND, \bar{x} means NOT

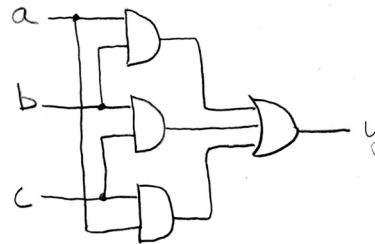Boolean Algebra (e.g., for majority fun.)




$$y = a \cdot b + a \cdot c + b \cdot c$$

$$y = ab + ac + bc$$

Boolean Algebra (e.g., for FSM)


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

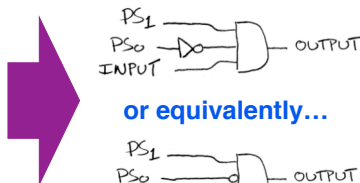

or equivalently...

$$y = PS_1 \cdot \overline{PS_0} \cdot INPUT$$

BA: Circuit & Algebraic Simplification

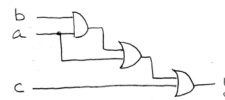


original circuit

$$\begin{aligned}
 y &= ((ab) + a) + c \\
 &= ab + a + c \\
 &= a(b+1) + c \\
 &= a(1) + c \\
 &= a + c
 \end{aligned}$$

equation derived from original circuit

algebraic simplification

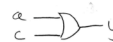

simplified circuit

BA also great for circuit verification
Circ X = Circ Y?
use BA to prove!

Laws of Boolean Algebra

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\bar{x} \cdot \bar{y} = \overline{x + y}$	$\overline{(x + y)} = \bar{x} \cdot \bar{y}$	DeMorgan's Law



CS61C L16 Representations of Combinatorial Logic Circuits (19)

Beamer, Summer 2007 © UCB

Boolean Algebraic Simplification Example

$$\begin{aligned}
 y &= ab + a + c \\
 &= a(b + 1) + c && \text{distribution, identity} \\
 &= a(1) + c && \text{law of 1's} \\
 &= a + c && \text{identity}
 \end{aligned}$$



CS61C L16 Representations of Combinatorial Logic Circuits (20)

Beamer, Summer 2007 © UCB

Canonical forms (1/2)

	abc	y
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0

Sum-of-products
(ORs of ANDs)




CS61C L16 Representations of Combinatorial Logic Circuits (21)

Beamer, Summer 2007 © UCB

Canonical forms (2/2)
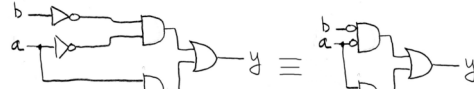
$$\begin{aligned}
 y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\
 &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) && \text{distribution} \\
 &= \bar{a}\bar{b}(1) + a\bar{c}(1) && \text{complementarity} \\
 &= \bar{a}\bar{b} + a\bar{c} && \text{identity}
 \end{aligned}$$



CS61C L16 Representations of Combinatorial Logic Circuits (22)

Beamer, Summer 2007 © UCB

Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e., $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$ where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	FTF
8:	FTT




CS61C L16 Representations of Combinatorial Logic Circuits (23)

Beamer, Summer 2007 © UCB

"And In conclusion..."

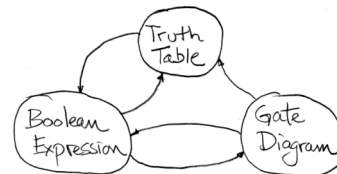- Pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You'll see them again in 150, 152 & 164
- Use this table and techniques we learned to transform from 1 to another



CS61C L16 Representations of Combinatorial Logic Circuits (26)

Beamer, Summer 2007 © UCB