 


Lecture #16 – Representations of Combinatorial Logic Circuits

2007-7-23



Scott Beamer

Instructor

**Plug-in Hybrid
Upgrades
Available**



Chronicle / Lance Jackson



Chronicle / Chris Stewart




sfgate.com

Review

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
 - Setup and Hold times important
- **TODAY**
 - Representation of CL Circuits
 - Truth Tables
 - Logic Gates
 - Boolean Algebra



Truth Tables

 


a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

TT Example #1: 1 iff one (not both) a,b=1

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



TT Example #2: 2-bit adder

 

A	B	C
a_1a_0	b_1b_0	$c_2c_1c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How
Many
Rows?



TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

**How
Many
Rows?**




TT Example #3: 3-input majority circuit

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1




Logic Gates (1/2)

AND

 


ab	c
00	0
01	0
10	0
11	1

OR

 

ab	c
00	0
01	1
10	1
11	1

NOT

 


a	b
0	1
1	0



And vs. Or review – Dan’s mnemonic

AND Gate

Symbol

 

Definition

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Logic Gates (2/2)

XOR



NAND



NOR



ab	c
00	0
01	1
10	1
11	0

ab	c
00	1
01	1
10	1
11	0

ab	c
00	1
01	0
10	0
11	0

2-input gates extend to n-inputs

- **N-input XOR is the only one which isn't so obvious**
- **It's simple: XOR is a 1 iff the # of 1s at its input is odd \Rightarrow**

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




Administrivia

- **Midterm TONIGHT 7-10pm in 10 Evans**
 - **Bring**
 - Pencils/pens
 - One 8.5"x11" sheet of notes
 - Green Sheet (or copy of it)
 - **Don't bring calculators (or other large electronics)**
- **Assignments**
 - **HW5** due 7/26 (up today)
 - **HW6** due 7/29




Truth Table \Rightarrow Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


Truth Table \Rightarrow Gates (e.g., FSM circ.)


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 

or equivalently...

 


Boolean Algebra

 

- **George Boole, 19th Century mathematician**
 - **Developed a mathematical system (algebra) involving logic**
 - later known as “Boolean Algebra”
 - **Primitive functions: AND, OR and NOT**
 - **The power of BA is there’s a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA**
- + means OR, • means AND, \bar{x} means NOT**



 Boolean Algebra (e.g., for majority fun.)




$$y = a \cdot b + a \cdot c + b \cdot c$$


$$y = ab + ac + bc$$

Boolean Algebra (e.g., for FSM)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 


or equivalently...

 

$$y = PS_1 \cdot \overline{PS_0} \cdot INPUT$$

BA: Circuit & Algebraic Simplification

 


original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

 

simplified circuit

**BA also great for
circuit verification
Circ X = Circ Y?
use BA to prove!**

Laws of Boolean Algebra

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

complementarity
laws of 0's and 1's
identities
idempotent law
commutativity
associativity
distribution
uniting theorem
DeMorgan's Law



Boolean Algebraic Simplification Example

$$\begin{aligned}y &= ab + a + c \\ &= a(b + 1) + c && \text{distribution, identity} \\ &= a(1) + c && \text{law of 1's} \\ &= a + c && \text{identity}\end{aligned}$$



Canonical forms (1/2)

	abc	y
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0




**Sum-of-products
(ORs of ANDs)**

Canonical forms (2/2)

$$\begin{aligned}y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\ &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) \\ &= \bar{a}\bar{b}(1) + a\bar{c}(1) \\ &= \bar{a}\bar{b} + a\bar{c}\end{aligned}$$

distribution
complementarity
identity

 

Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

Peer Instruction Answer

A. $(a+b) \cdot (\bar{a}+b) = b$

B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND

C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

Peer Instruction Answer (B)



“And In conclusion...”

- **Pipeline big-delay CL for faster clock**
- **Finite State Machines extremely useful**
 - You'll see them again in 150, 152 & 164
- **Use this table and techniques we learned to transform from 1 to another**

