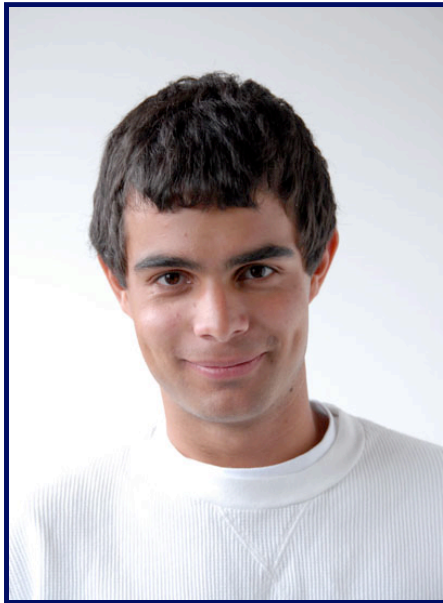


`inst.eecs.berkeley.edu/~cs61c`  
**CS61C : Machine Structures**

## **Lecture #17 Combinatorial Logic Blocks**

**2007-7-24**




**Scott Beamer, Instructor**


 
# Review


---

- **Pipeline big-delay CL for faster clock**
- **Finite State Machines extremely useful**
  - You'll see them again in 150, 152 & 164
- **Use this table and techniques we learned to transform from 1 to another**




# Review: Logic Gates (1/2)

AND

 


ab	c
00	0
01	0
10	0
11	1

OR

 

ab	c
00	0
01	1
10	1
11	1

NOT

 

a	b
0	1
1	0



# Review: Logic Gates (2/2)


XOR



NAND



NOR

 

ab	c
00	0
01	1
10	1
11	0

ab	c
00	1
01	1
10	1
11	0

ab	c
00	1
01	0
10	0
11	0

# Laws of Boolean Algebra

---

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

complementarity  
laws of 0's and 1's  
identities  
idempotent law  
commutativity  
associativity  
distribution  
uniting theorem  
DeMorgan's Law




# Today

---

- **Data Multiplexors**
- **Arithmetic and Logic Unit**
- **Adder/Subtractor**
- **Programmable Logic Arrays**


 
# Data Multiplexor (here 2-to-1, n-bit-wide)




Truth table

<b>S</b>	<b>C</b>
<b>0</b>	<b>A</b>
<b>1</b>	<b>B</b>

# N instances of 1-bit-wide mux

How many rows in TT?

 

$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\ &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\ &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\ &= \bar{s}(a(1) + s((1)b) \\ &= \bar{s}a + sb\end{aligned}$$






# How do we build a 1-bit-wide mux?


---

$$\bar{s}a + sb$$

 

# 4-to-1 Multiplexor?

How many rows in TT?

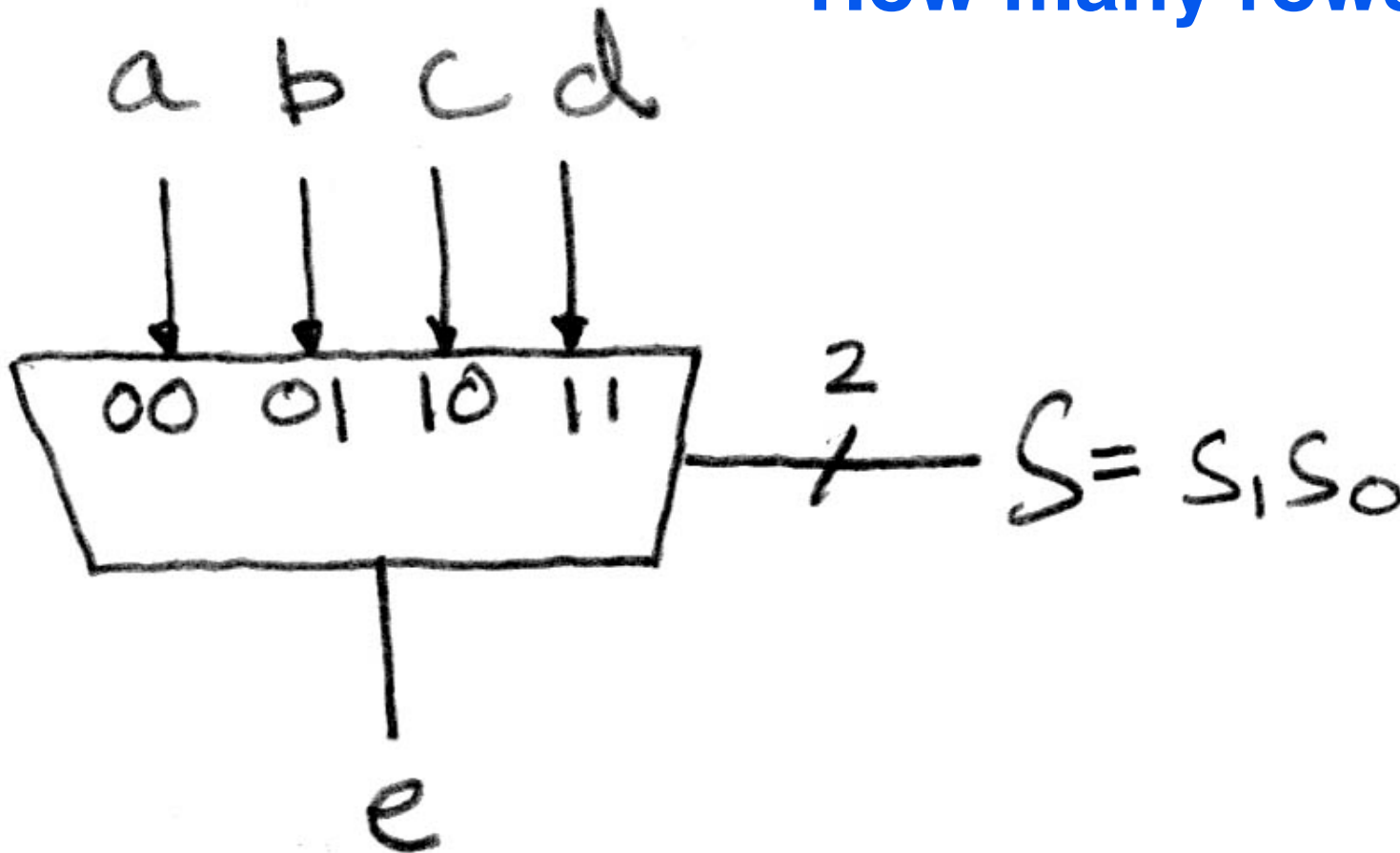


$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$

# Is there any other way to do it?

---

Hint: NCAA tourney!

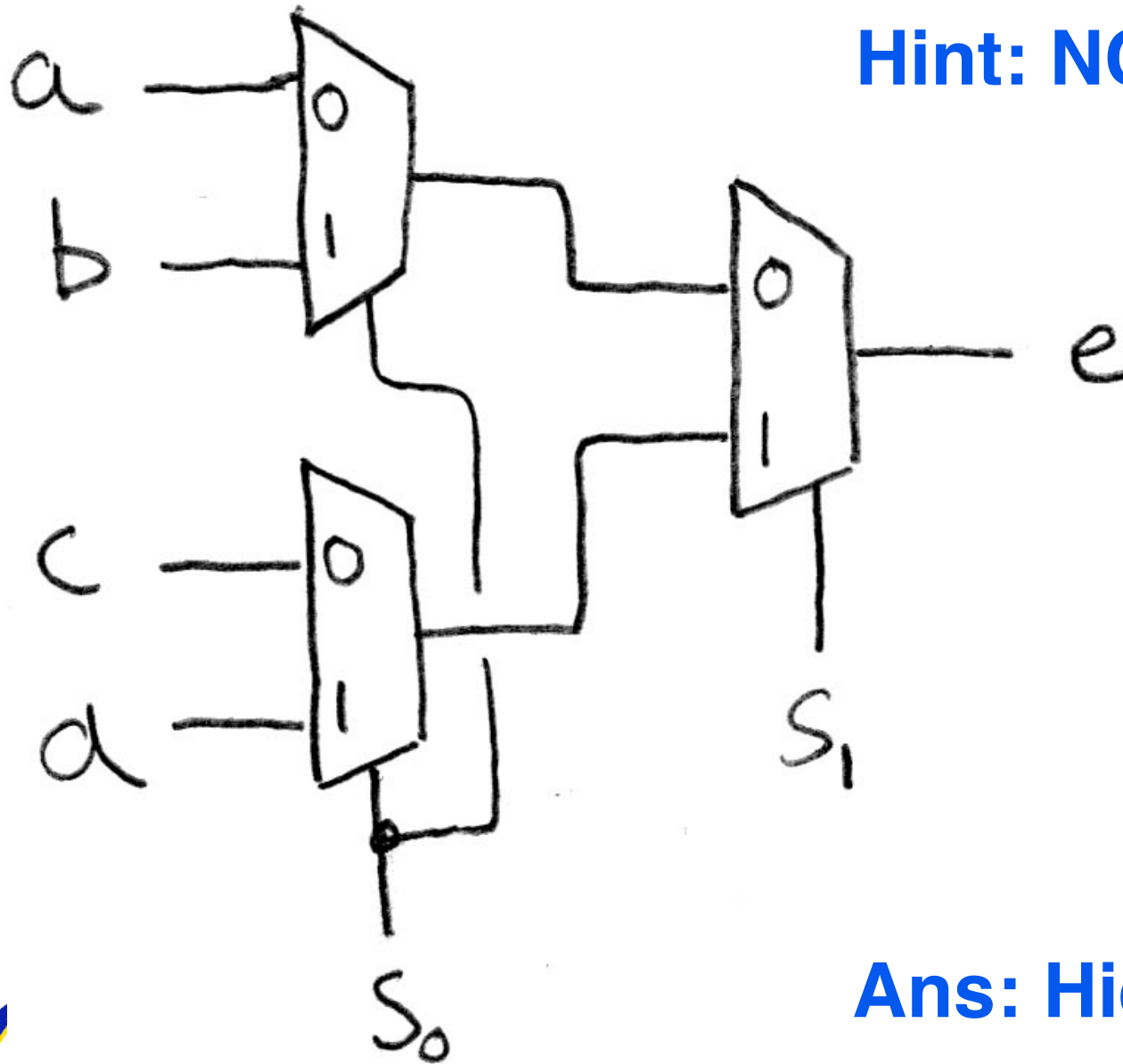


Ans: Hierarchically!



# Do you really understand NORs?

- If one input is 1, what is a NOR?
- If one input is 0, what is a NOR?

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

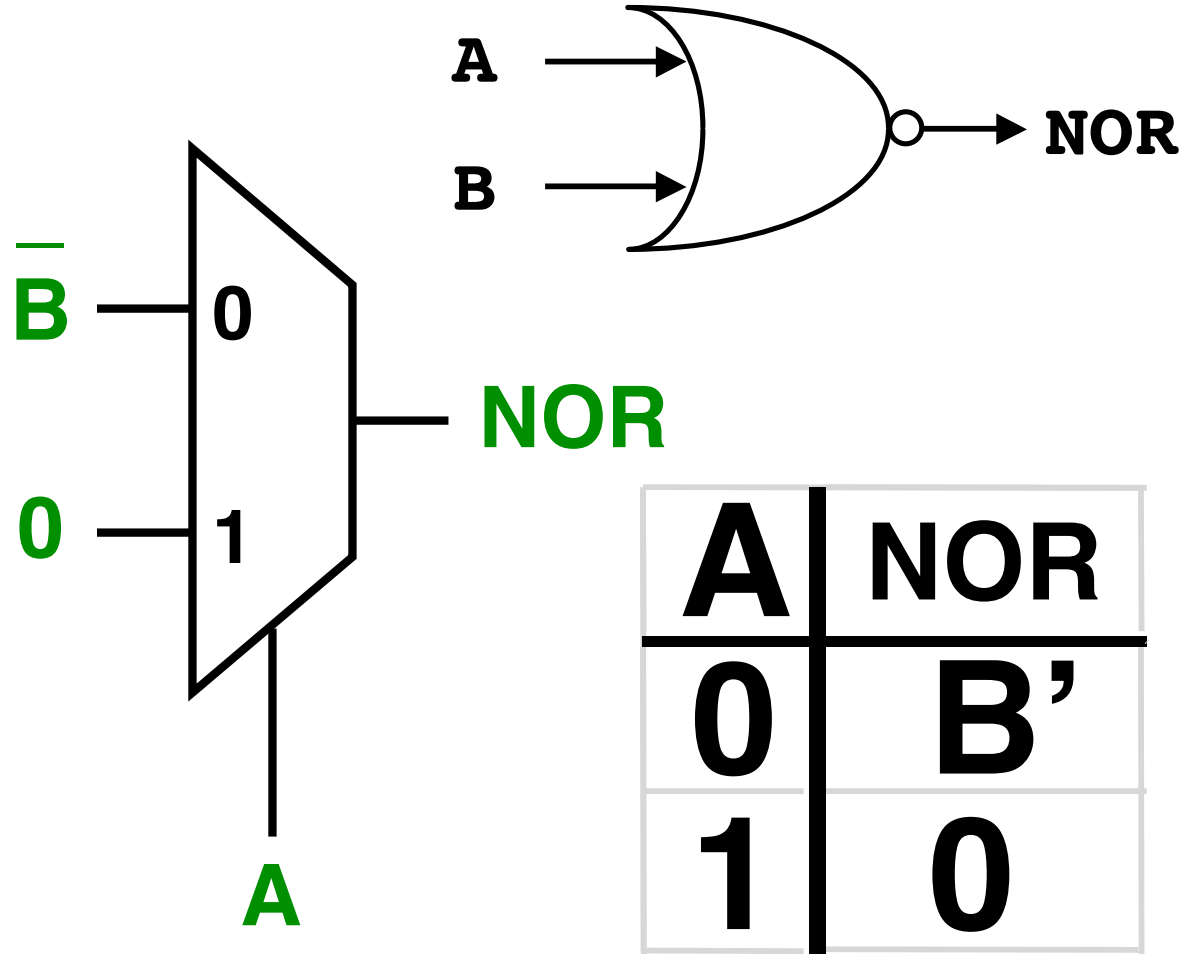


A	NOR
0	$B'$
1	0

# Do you really understand NANDs?

- If one input is 1, what is a NAND?
- If one input is 0, what is a NAND?

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

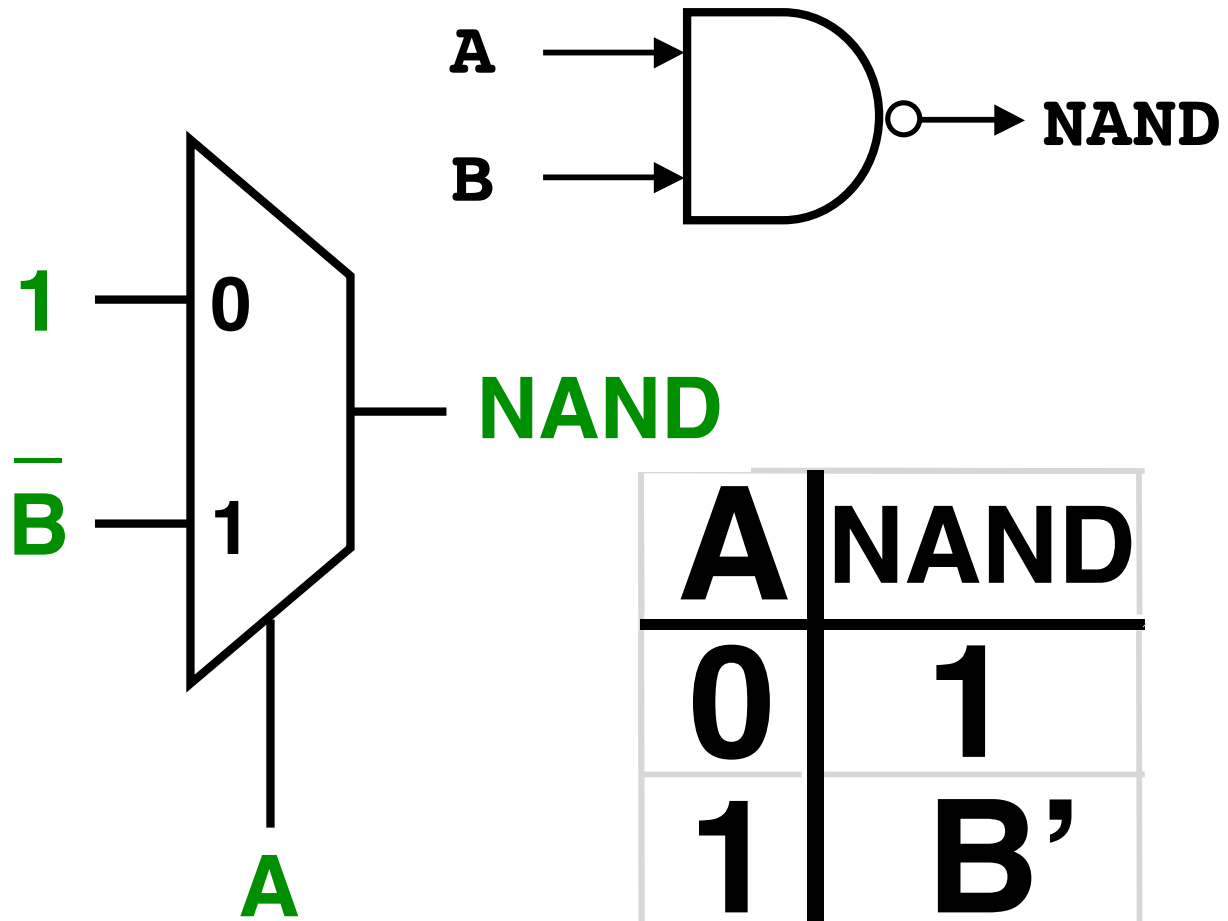

A	NAND
0	1
1	$B'$

# Administrivia

---

- **Assignments**

- **HW5** due 7/26
- **HW6** due 7/29

- **Midterm Regrade Policy**

- **What you do...**

- On paper, explain what was graded incorrectly
- Staple to front of exam and give to TA or Scott by **8/1**

- **What we do...**

- Regrade the entire exam blind
- Then look at what you wrote, discuss as staff, and regrade
- **Warning: your grade can go down**



# What does it mean to “clobber” midterm?

---


- You **STILL** have to take the final even if you aced the midterm!
- The final will contain midterm-material Qs and new, post-midterm Qs
- They will be graded separately
- If you do “**better**” on the midterm-material, we will **clobber your midterm with the “new” score!** **If you do worse, midterm unchanged.**
- What does “**better**” mean?
  - Better w.r.t. Standard Deviations around mean
- What does “**new**” mean?
  - Score based on remapping St. Dev. score on final midterm-material to midterm score St. Dev.


 
# Arithmetic and Logic Unit

---

- Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does **ADD, SUB, bitwise AND, bitwise OR**



when  $S=00$ ,  $R=A+B$

when  $S=01$ ,  $R=A-B$


when  $S=10$ ,  $R=A \text{ AND } B$

when  $S=11$ ,  $R=A \text{ OR } B$





# Our simple ALU

 

# Adder/Subtractor Design -- how?

---

- **Truth-table, then determine canonical form, then minimize and implement as we've seen before**
- **Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer**



# Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 & \end{array}$$

$a_0$	$b_0$	$s_0$	$c_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



# Adder/Subtractor – One-bit adder (1/2)...

$$\begin{array}{rcccc}
 & a_3 & a_2 & a_1 & a_0 \\
 + & b_3 & b_2 & b_1 & b_0 \\
 \hline
 s_3 & s_2 & s_1 & s_0 & 
 \end{array}$$



$a_i$	$b_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$


  
# Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

# N 1-bit adders $\Rightarrow$ 1 N-bit adder

---

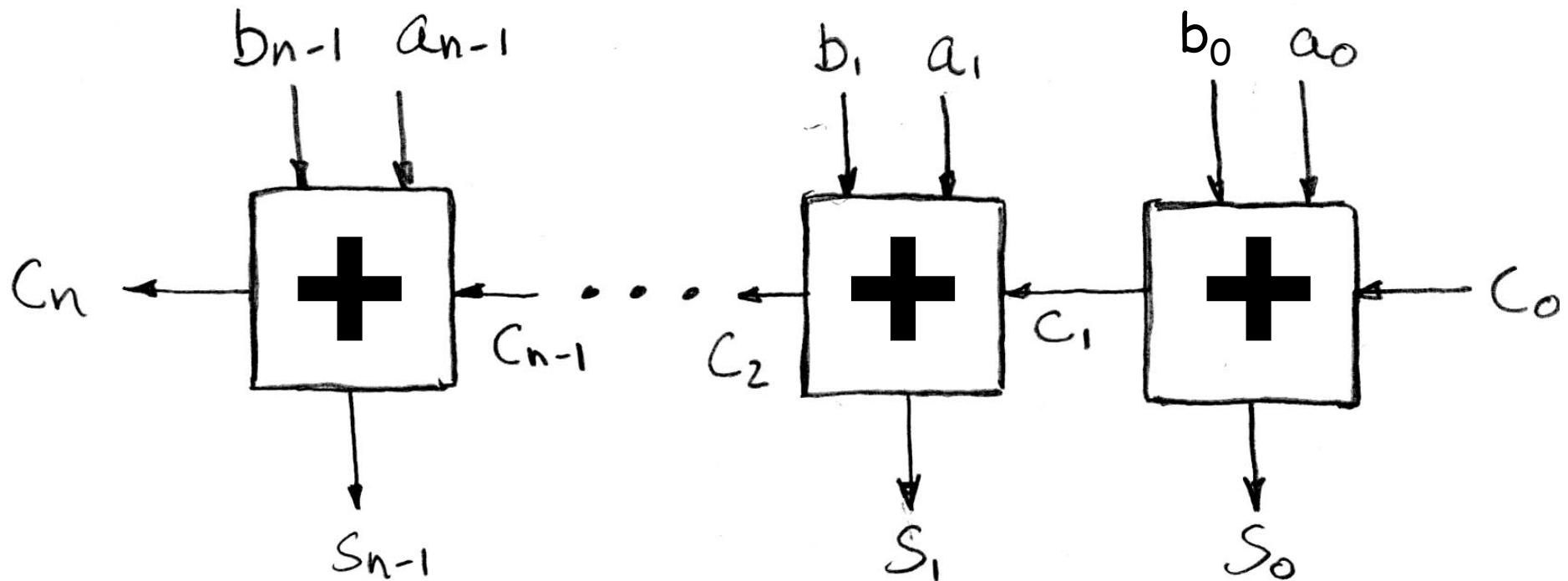


**What about overflow?  
Overflow =  $c_n$ ?**
 
# What about overflow?

- Consider a 2-bit signed # & overflow:

- 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$ ,  $C_2 = \text{Carry-out} = C_{out}$
- No  $C_{out}$  or  $C_{in} \Rightarrow \text{NO overflow!}$

What  
op?

- $C_{in}$ , and  $C_{out} \Rightarrow \text{NO overflow!}$

•  $C_{in}$ , but no  $C_{out} \Rightarrow A, B \text{ both } > 0, \text{ overflow!}$


•  $C_{out}$ , but no  $C_{in} \Rightarrow A, B \text{ both } < 0, \text{ overflow!}$



# What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2  
11 = -1  
00 = 0  
01 = 1

 


- Overflows when...

- $C_{in}$ , but no  $C_{out} \Rightarrow A, B$  both  $> 0$ , overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow A, B$  both  $< 0$ , overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$





# Extremely Clever Subtractor

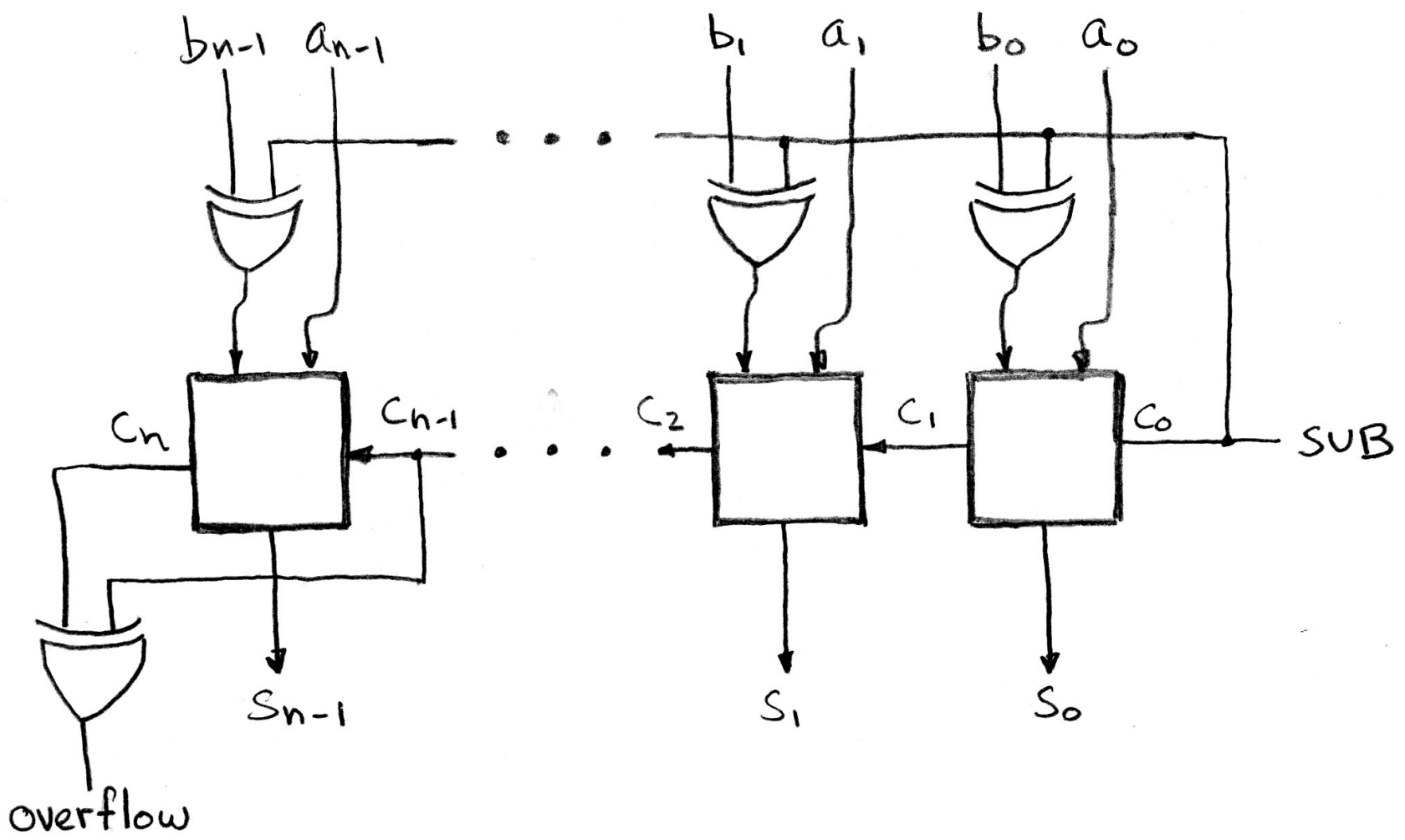
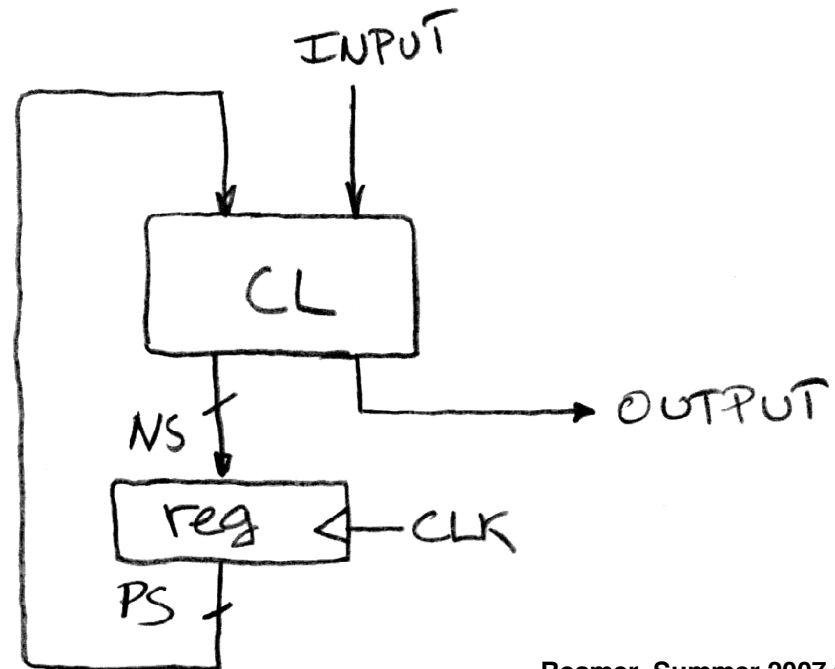 
# Review: Finite State Machine (FSM)

- **States** represent possible output values.
- **Transitions** represent changes between states based on inputs.
- **Implement** with CL and clocked register feedback.



# Finite State Machines extremely useful!

---

- They define
  - How **output signals** respond to input signals and previous state.
  - How we **change states** depending on input signals and previous state
- We could implement very detailed FSMs w/ **Programmable Logic Arrays**



# Taking advantage of sum-of-products


---

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is **Programmable Logic Arrays (PLAs)**
- Designed so that can select (program) ands, ors, complements after you get the chip
  - Late in design process, fix errors, figure out what to do later, ...


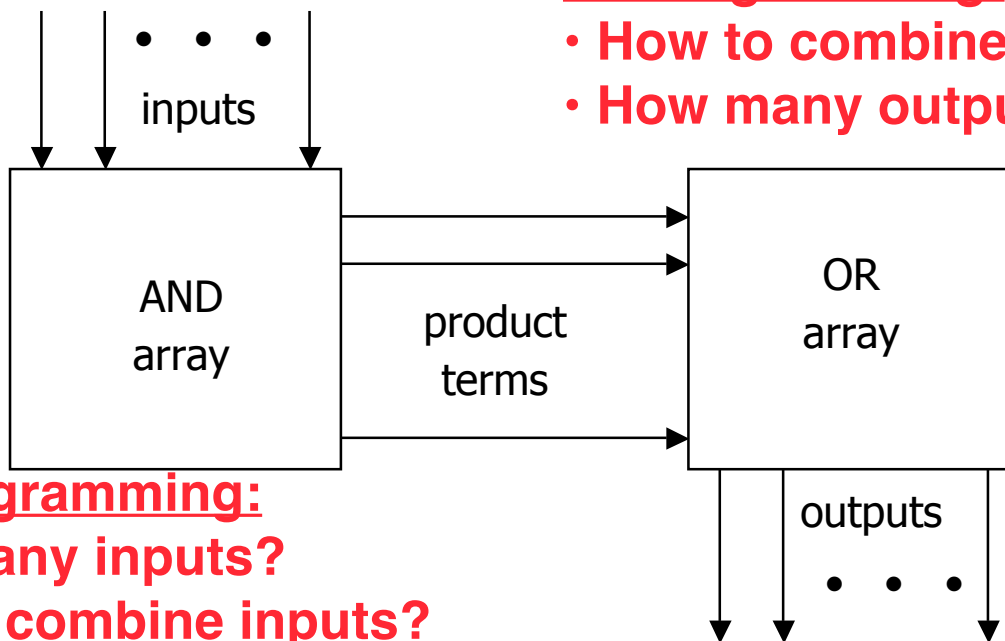
# Programmable Logic Arrays

- Pre-fabricated building block of many AND/OR gates
  - “Programmed” or “Personalized” by making or breaking connections among gates
  - Programmable array block diagram for sum of products form



## Or Programming:

- How to combine product terms?
- How many outputs?

## And Programming:

- How many inputs?
- How to combine inputs?
- How many product terms?



# Enabling Concept

- Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

input side: 3 inputs

1 = uncomplemented in term  
 0 = complemented in term  
 - = does not participate

## personality matrix

Product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

output side: 4 outputs

1 = term connected to output  
 0 = no connection to output


reuse of terms;  
 5 product terms


 
# Before Programming


---

- All possible connections available before “programming”


 
# After Programming

- Unwanted connections are "blown"
  - Fuse (normally connected, break unwanted ones)
  - Anti-fuse (normally disconnected, make wanted connections)







# Alternate Representation

- Short-hand notation--don't have to draw all the wires
  - X Signifies a connection is present and perpendicular signal is an input to gate

notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

  

## “And In conclusion...”

---

- **Use muxes to select among input**
  - S input bits selects  $2^S$  inputs
  - Each input can be n-bits wide, indep of S
- **Implement muxes hierarchically**
- **ALU can be implemented using a mux**
  - Coupled with basic block elements
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
  - XOR serves as conditional inverter
- **Programmable Logic Arrays** are often used to implement our CL



# Peer Instruction

---

- A. Truth table for mux with 4-bits of signals has  $2^4$  rows**
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl**
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T**

	ABC
1 :	<b>FFF</b>
2 :	<b>FFT</b>
3 :	<b>FTF</b>
4 :	<b>FTT</b>
5 :	<b>TFF</b>
6 :	<b>TFT</b>
7 :	<b>TF</b> <b>F</b>
8 :	<b>TTT</b>

# Peer Instruction Answer

---

