

REVIEW PROBLEMS FOR THE FINAL

I. Introduction

1. There are a total of 14 problems in this review handout. Problems 1 through 3 serve as review of basic material. The final exam is going to concentrate on problems 4 through 14. Some information about the exam:
 - i. The exam is on Saturday, December 18th 2004, from 8:00 AM to 11:00 AM in 234 Hearst Gym.
 - ii. You may use a calculator.
 - iii. The exam has 5 questions. They each have different parts. The important concepts covered on each question are:
 1. Op-amp analysis
 2. Oscillators
 3. Flip-flops
 4. Op-amp frequency analysis
 5. Diode Driving-point characteristics

Understanding the concepts in these review problems should help you do really well on the exam. Please do not waste time trying to memorize these problems – that is not going to help you on the final. **You should also understand the flip-flop problem (question 5) in homework 9 (PLEASE DO THIS, I DO NOT HAVE A FLIP-FLOP PROBLEM IN THIS REVIEW PACKET) and the driving point characteristic problem in homework 7 (problem 3). The solutions are available in 140AB Cory (the EE100 lab). You may browse them anytime a TA is in there – BUT, do NOT take them out of the lab. Finally, UNDERSTAND section 9.6 in the book (pp. 495 – 499), this will help with problem 5 on the final exam.**

2. There is a review session scheduled on Saturday, December 11th 2004, 9:00 AM – 11:00 AM, location: TBA. I will try to answer any questions you have on these review problems and other material from class. I will hand out solutions to these review problems.
3. Here are my extra office hours for the final: Thursday (12/16): 6:00 pm – 12:00 AM (midnight), Friday (12/17): 3:00 pm – 9:00 pm. All office hours are going to be held in the Free Speech Cafe next to the Moffit library since Cory hall is a pain in the a** to get in after-hours. 204B Cory (the location of my Sunday office hours) is unavailable during those days. I DO NOT have office hours on Sunday and Wednesday anymore.

**IN CONCLUSION, ON THE FINAL: READ THE QUESTION, THINK,
THEN ANSWER!**

- Ref.: 1. Nilsson and Riedel, *Electric Circuits*, 6th Edition, McGraw-Hill.
2. Chua, Desoer and Kuh. *Linear and Nonlinear Circuits*. McGraw-Hill.

(1) Figure 1 below shows a model for the MOS transistor. Using this model in the circuit below, find v_o and V_{DS} .

 


Figure 1. Transistor model and circuit for problem 1

(2) Find the equivalent resistance as seen at terminals ab in the circuit in figure 2.

 


Figure 2. Circuit for problem 2

(3) Find the thevenin equivalent at terminals ab in the circuit below.

 


Figure 3. Circuit for problem 3

- (4) In the figure 4 (a), assume the open loop gain of the op-amp is really big (say 10^6). Assume $E_{\text{sat}} = 12 \text{ V}$.
- Sketch the transfer characteristic when $E = 5 \text{ V}$.
 - Sketch the transfer characteristic when $E = -5 \text{ V}$.
 - Sketch $v_o(t)$ for the $v_{\text{in}}(t)$ shown in figure 4 (b). ASSUME: $E = 0 \text{ V}$ and the maximum and minimum value of v_{in} is 5 V and -5 V respectively.

 


Figure 4 (a). The comparator

 


Figure 4 (b). Sample input voltage for figure 4 (a).

(5) Find v_o as a function of v_1 and v_2 in the circuit below. Assume op-amp is operating in the linear region.

 


Figure 5. Circuit for problem 5.

(6) In the circuit in figure 6, find $\frac{v_o(j\omega)}{v_i(j\omega)}$. Assume op-amp is operating in the linear region. Give your answer in the form $\frac{a + jb}{c + jd} = \mathbf{H}(j\omega)$.

 


Figure 6. Circuit for problem 6.

(7) In the circuit in figure 7, find $\frac{v_o(j\omega)}{v_i(j\omega)}$. Assume op-amp is operating in the linear region. Give your answer in the form $\frac{a + jb}{c + jd} = \mathbf{H}(j\omega)$.

 


Figure 7. Circuit for problem 7.

- (8) Consider the circuit shown in figure P6.20 (a) where N is described by the i - v characteristic shown in figure P6.20 (b).
- Indicate the dynamic route. Label all equilibrium points and state whether they are stable or unstable.
 - Suppose $v_c(0) = 15$ V. Find and sketch $v_c(t)$ and $i_c(t)$ for $t \geq 0$. Indicate all pertinent information on the sketches.

 


Figure P6.20

- (9) Consider the circuit shown in figure P6.21 (a) where N is described by the i - v characteristic shown in figure P6.21 (b).
- Indicate the dynamic route. Label all equilibrium points and state whether they are stable or unstable.
 - Suppose $i_L(0) = -20$ mA; calculate and sketch $i(t)$ and $v(t)$ for $t \geq 0$.

 
 


Figure P6.21

- (10) For the circuit in figure P6.22 (a) with the nonlinear resistor i - v characteristic as shown in figure P6.22 (b), find all equilibrium states and classify each as stable or unstable:
- when switch S is in position 1.
 - when switch S is in position 2.

 
 


Figure P6.22

- (11) Consider the circuit shown in figure P6.23 (a) where N is described by the i - v characteristic shown in figure P6.23 (b).
- Sketch the dynamic route.
 - If $v_c(0) = 2$ V and $i_c(0) = -2$ mA; calculate and sketch $i(t)$ and $v(t)$ for $t \geq 0$.

 


Figure P6.23

- (12) Consider the circuit in figure P6.21 (a) along with the i - v characteristic shown in figure P6.24.
- Sketch the dynamic route.
 - For what range of initial condition $i_L(0)$ does this circuit exhibit oscillation?


 


Figure P6.24

 - (13) Consider the circuit shown in figure P6.25 (a) where the one-port is described by the i - v characteristic in figure P6.25 (b).
- Sketch the dynamic route.
 - If $i_L(0) = -15$ mA, find and sketch $i(t)$ and $v(t)$ for $t \geq 0$
 - Determine all switching times.
 - Calculate the period of oscillation.



(14) Plot the driving-point characteristics of the one-ports shown in figure P2.4. You can use graphic series and parallel addition or any other method of your choosing. Assume all diodes are ideal.

 


Figure P2.4