
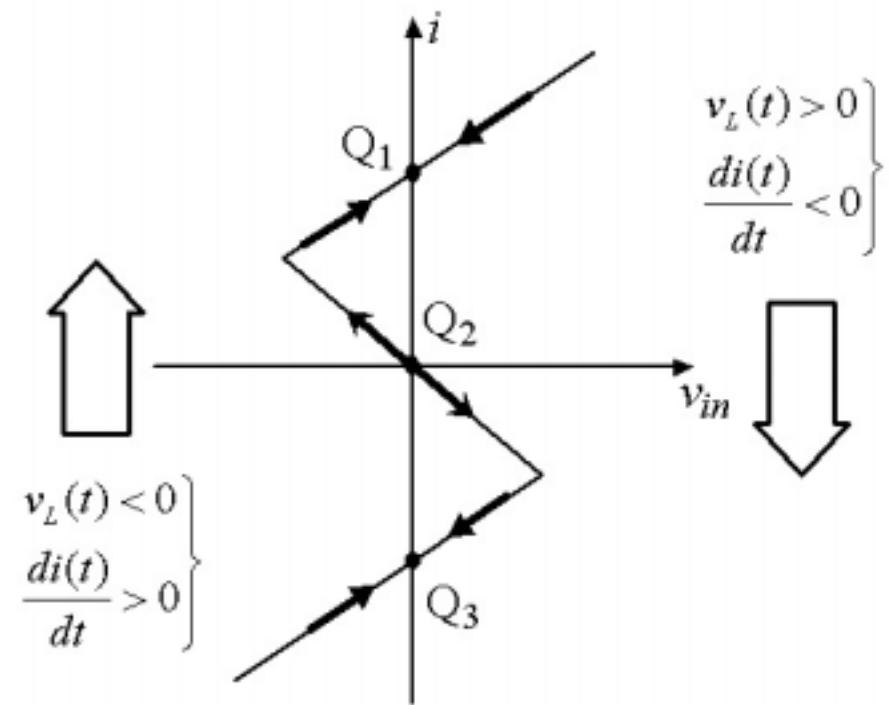


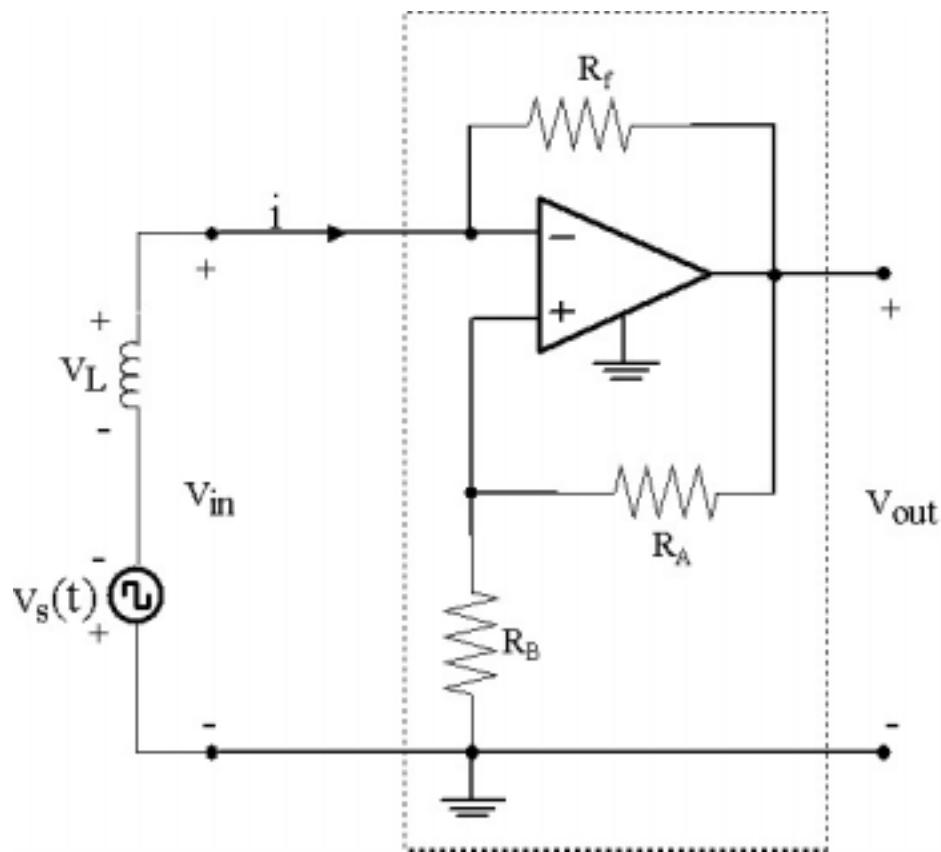A Bi-stable op-amp Circuit and its Driving Point Characteristic



Jump Rule

Capacitor Current Jump Rule




Upon reaching an **impasse point** Q at $t = t_k^-$ in an **RC circuit**, the **dynamic route jumps abruptly** to a point on the v - i curve at $t = t_k^+$ such that

$$v_C(t_k^+) = v_C(t_k^-)$$




Inductor Voltage Jump Rule

Upon reaching an **impasse point** Q at $t = t_k^-$ in an **RL circuit**, the **dynamic route jumps abruptly** to a point on the v - i curve at $t = t_k^+$ such that





$$i_L(t_k^+) = i_L(t_k^-)$$


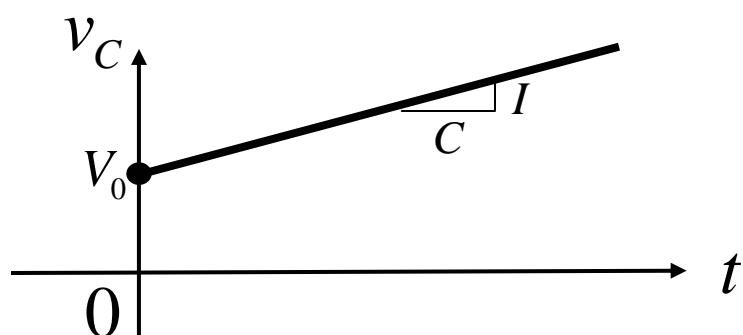
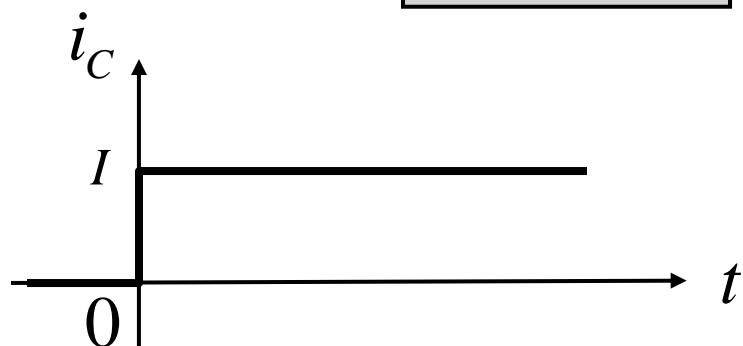
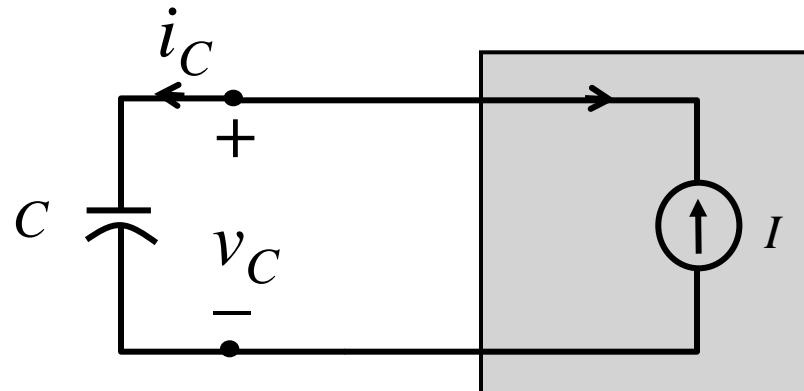

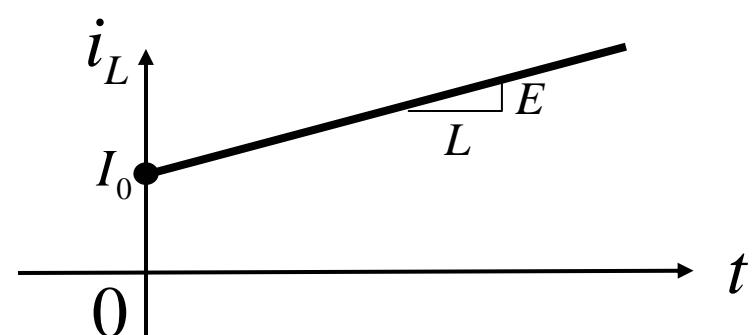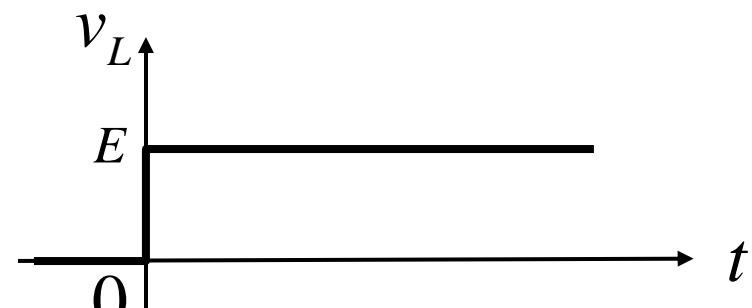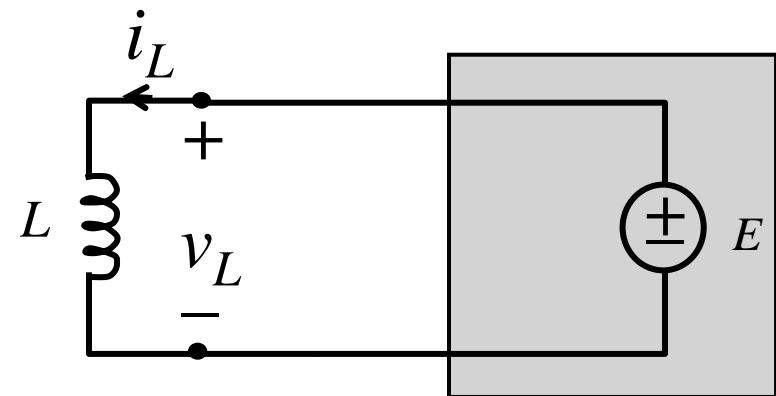
$$\begin{aligned}v_C(t) &= v_C(t_0) + \int_{t_0}^t i_C(\tau) d\tau \\&= V_0 + \frac{I}{C} t\end{aligned}$$


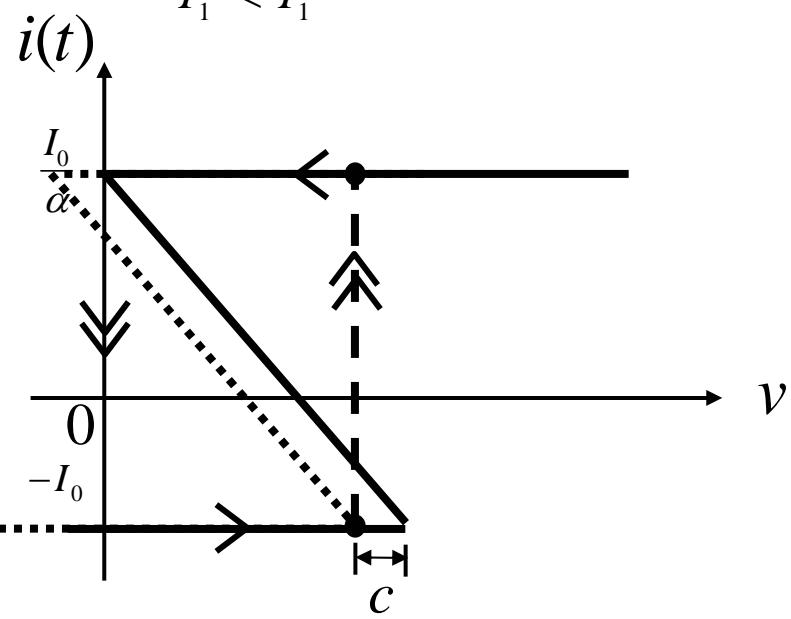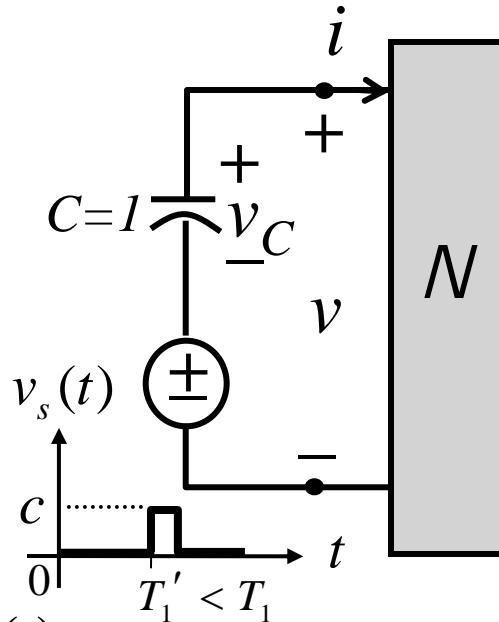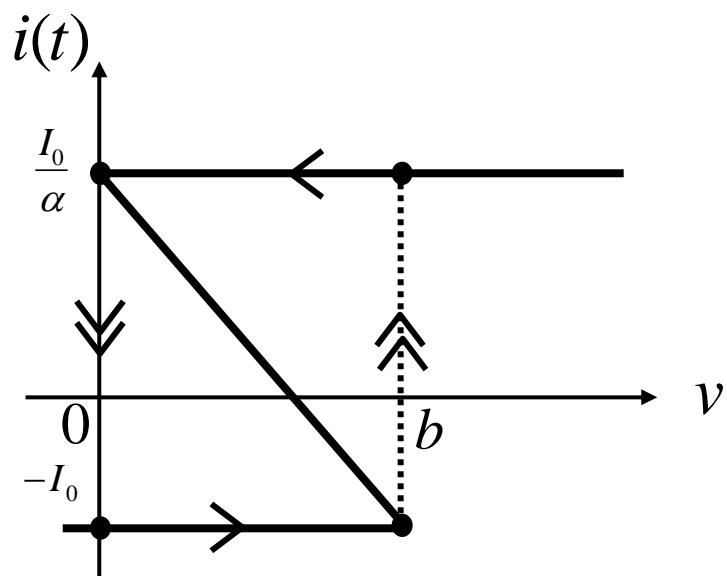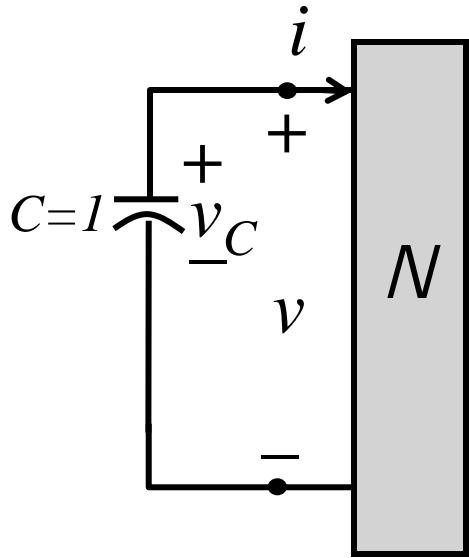
$$\begin{aligned}i_L(t) &= i_L(t_0) + \int_{t_0}^t v_L(\tau) d\tau \\&= I_0 + \frac{E}{L} t\end{aligned}$$



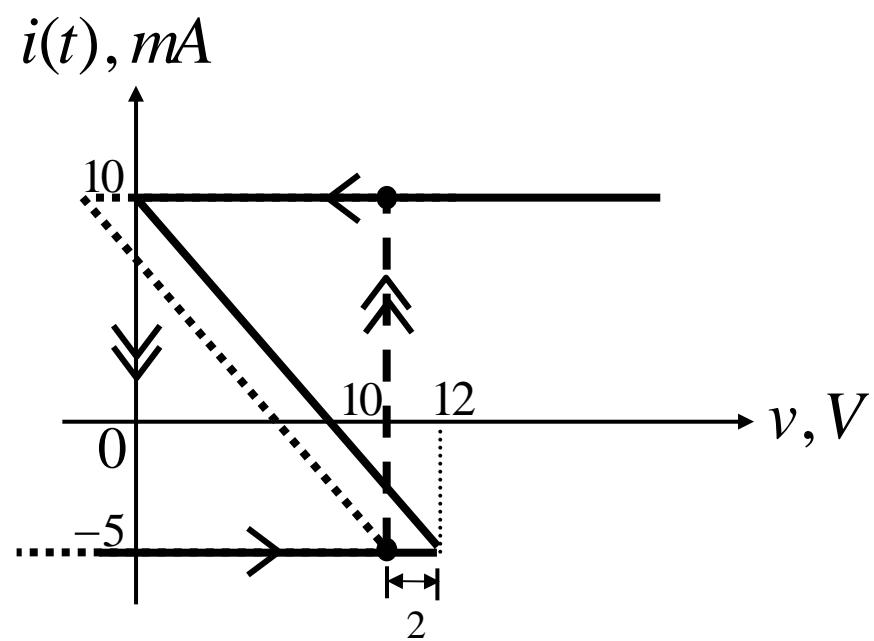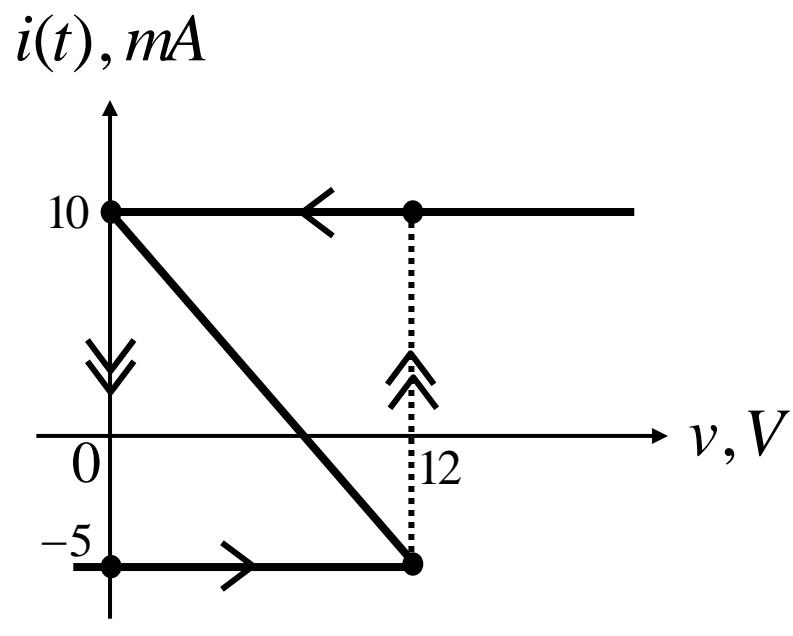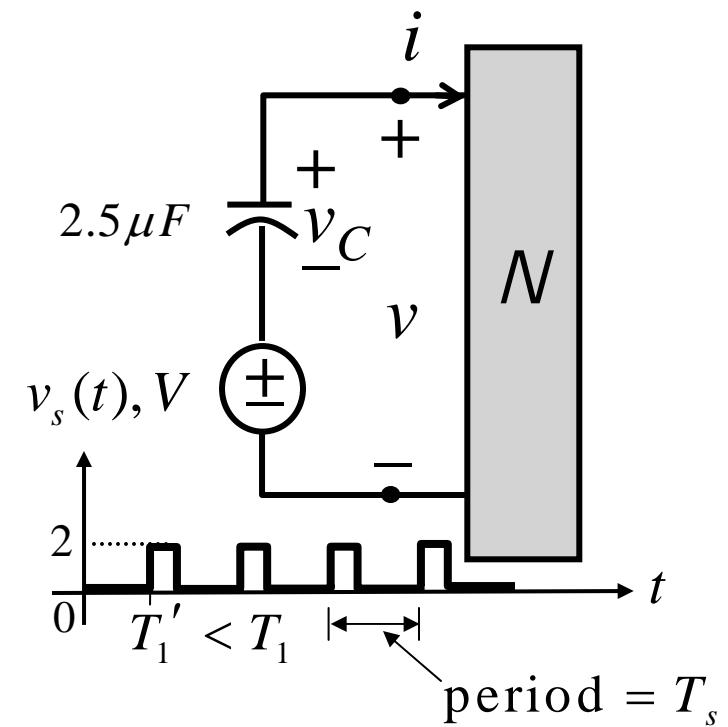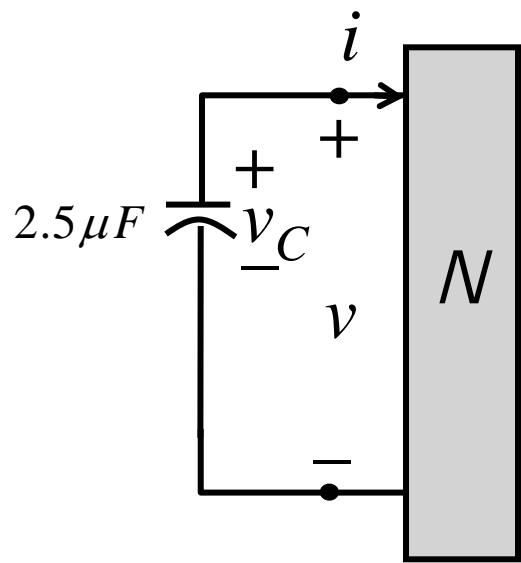

Proof.

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$\Rightarrow v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

$$v_C(t_k^- + \Delta t) = \underbrace{\frac{1}{C} \int_{-\infty}^{t_k^-} i_C(\tau) d\tau}_{v_C(t_k^-)} + \underbrace{\frac{1}{C} \int_{t_k^-}^{t_k^- + \Delta t} i_C(\tau) d\tau}_{A_\Delta}$$

$$= v_C(t_k^-) + \frac{1}{C} (A_\Delta)$$


as $\Delta t \rightarrow 0$,


$t_k^- + \Delta t \rightarrow t_k^+$ and

$A_\Delta \rightarrow 0$

(provided $i_C(t_k) \neq \pm\infty$)
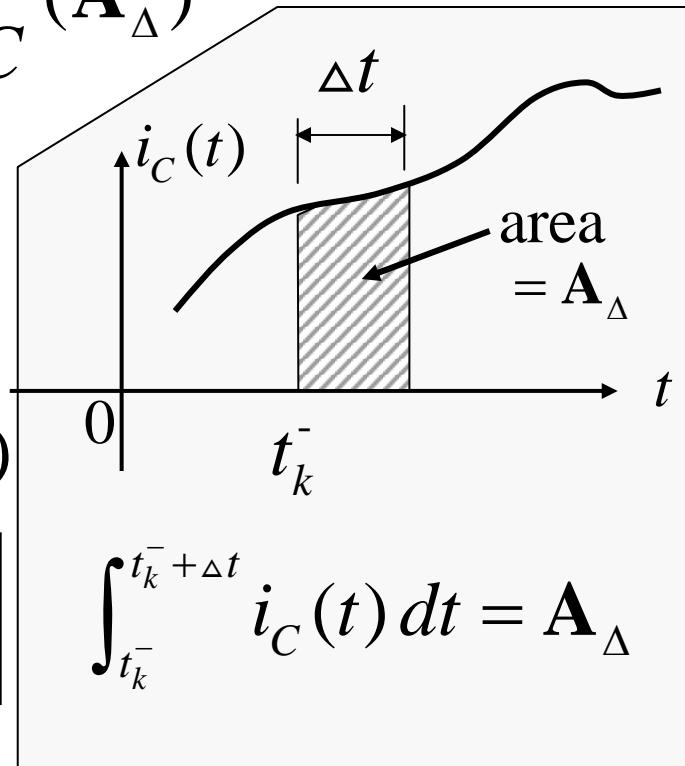
$$\therefore \boxed{v_C(t_k^+) = v_C(t_k^-)}$$



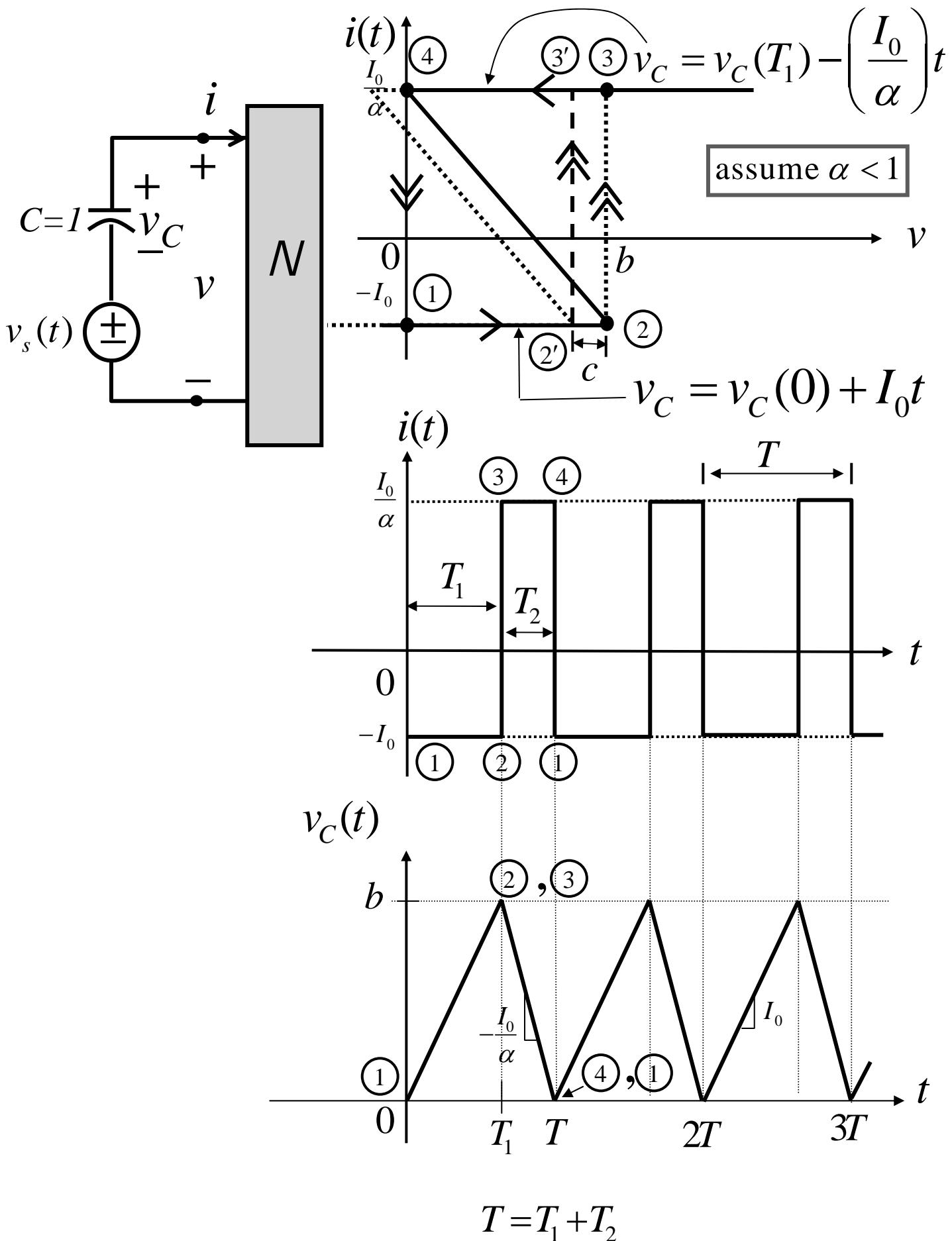

Dynamic Route of the Bi-stable op-amp Circuit Corresponding to a Square Pulse Triggering Signal

