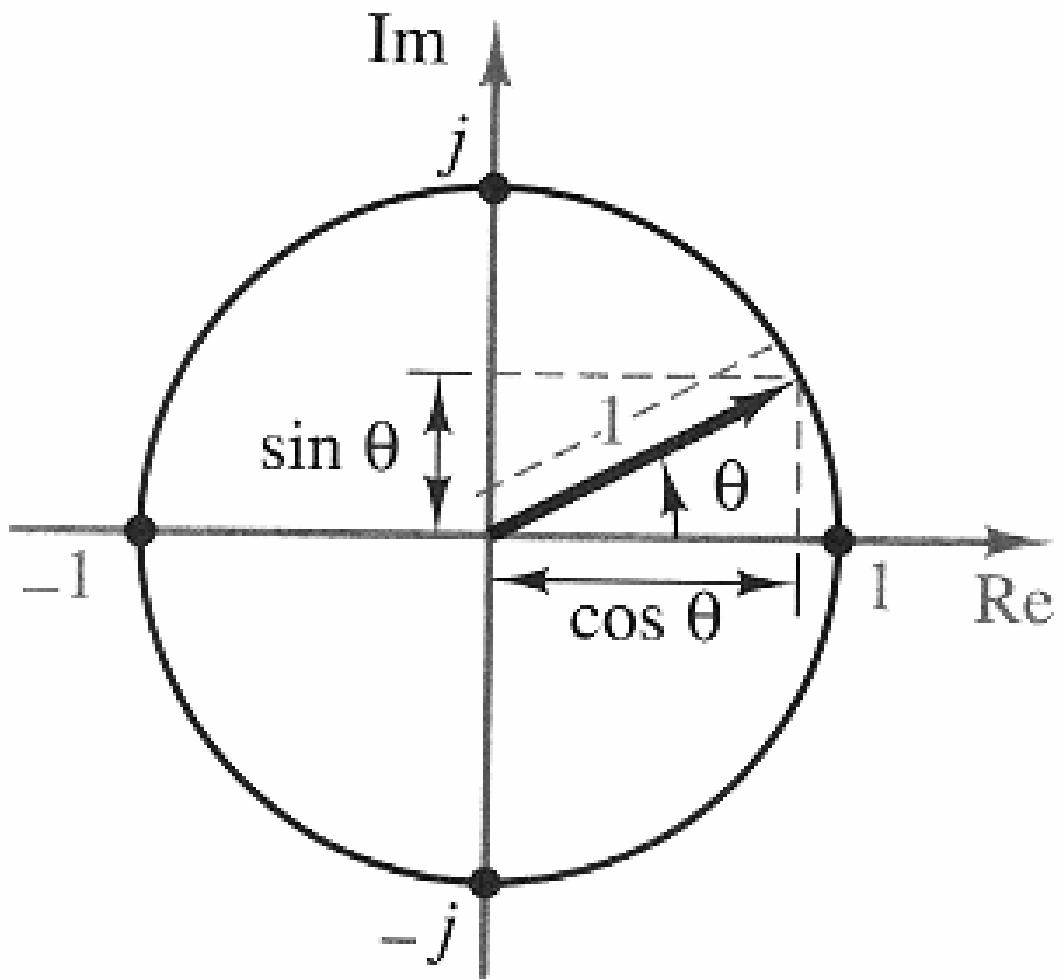


# Euler's Identity

$$e^{j\theta} = \cos \theta + j \sin \theta$$



# Euler's Identity

Substituting

$\theta = \pi$  in Euler's Identity,  
we obtain :

$$\begin{aligned} e^{j\pi} &= \cos \pi + j \sin \pi \\ &= -1 + j 0 \end{aligned}$$

$$e^{j\pi} + 1 = 0$$

⇒ Most beautiful relationship  
in Number theory

# Real Exponentials

$$x(t) = x(t_{\infty}) + [x(t_0) - x(t_{\infty})] e^{\frac{-(t-t_0)}{\tau}}$$

- A **real exponentials** is **uniquely** identified by 3 parameters:  
 $\tau$ ,  $x(t_0)$ , and  $x(t_{\infty})$
- Sum of 2 or more **real exponentials** of the same **time constant**  $\tau$  results in another **real exponential** with **time constant**  $\tau$ .

$$\sum_{i=0}^n k_i e^{-\frac{t}{\tau}} = \left( \sum_{i=0}^n k_i \right) e^{-\frac{t}{\tau}}$$

# Complex Exponentials



$$\begin{aligned}x(t) &= Ae^{j(\omega t + \theta)} \\&= A \cos(\omega t + \theta) + jA \sin(\omega t + \theta)\end{aligned}$$

- A **complex exponentials** is **uniquely** identified by 3 parameters:  
 $\omega$ ,  $A$ , and  $\theta$
- Sum of 2 or more **complex exponentials** (sinusoids) of the same **frequency**  $\omega$  results in another **complex exponential** (sinusoids) with **frequency**  $\omega$ .


$$\begin{aligned}\sum_{i=0}^n A_i e^{j(\omega t + \theta_i)} &= \underbrace{\left( \sum_{i=0}^n A_i e^{j\theta_i} \right)}_{\left( Ae^{j\theta} \right)} e^{j\omega t} \\&= [A \cos(\omega t + \theta)] + j[A \sin(\omega t + \theta)]\end{aligned}$$

# Phasor Diagram


$$|I|\cos(\omega t + \theta)$$

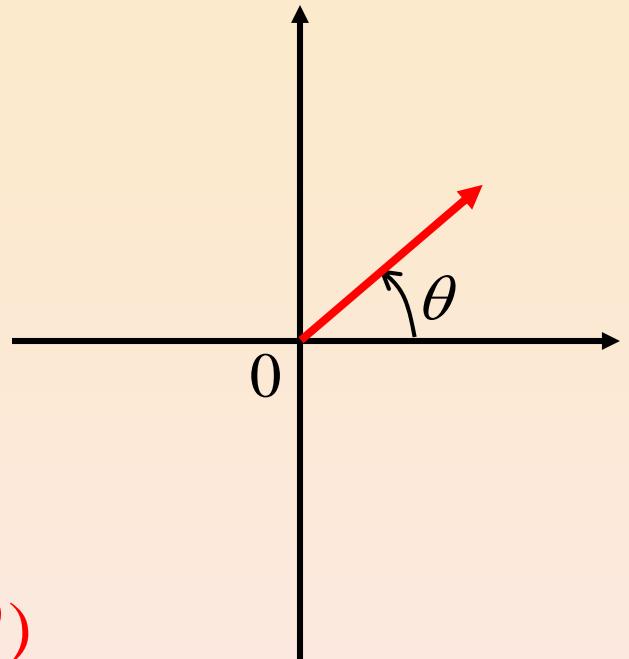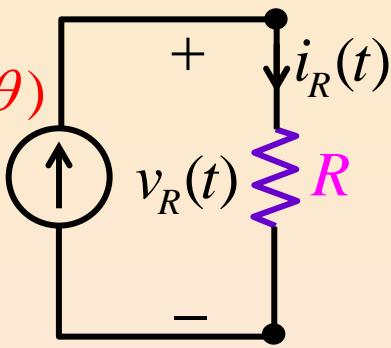

$$v_R(t) = R |I| \cos(\omega t + \theta)$$


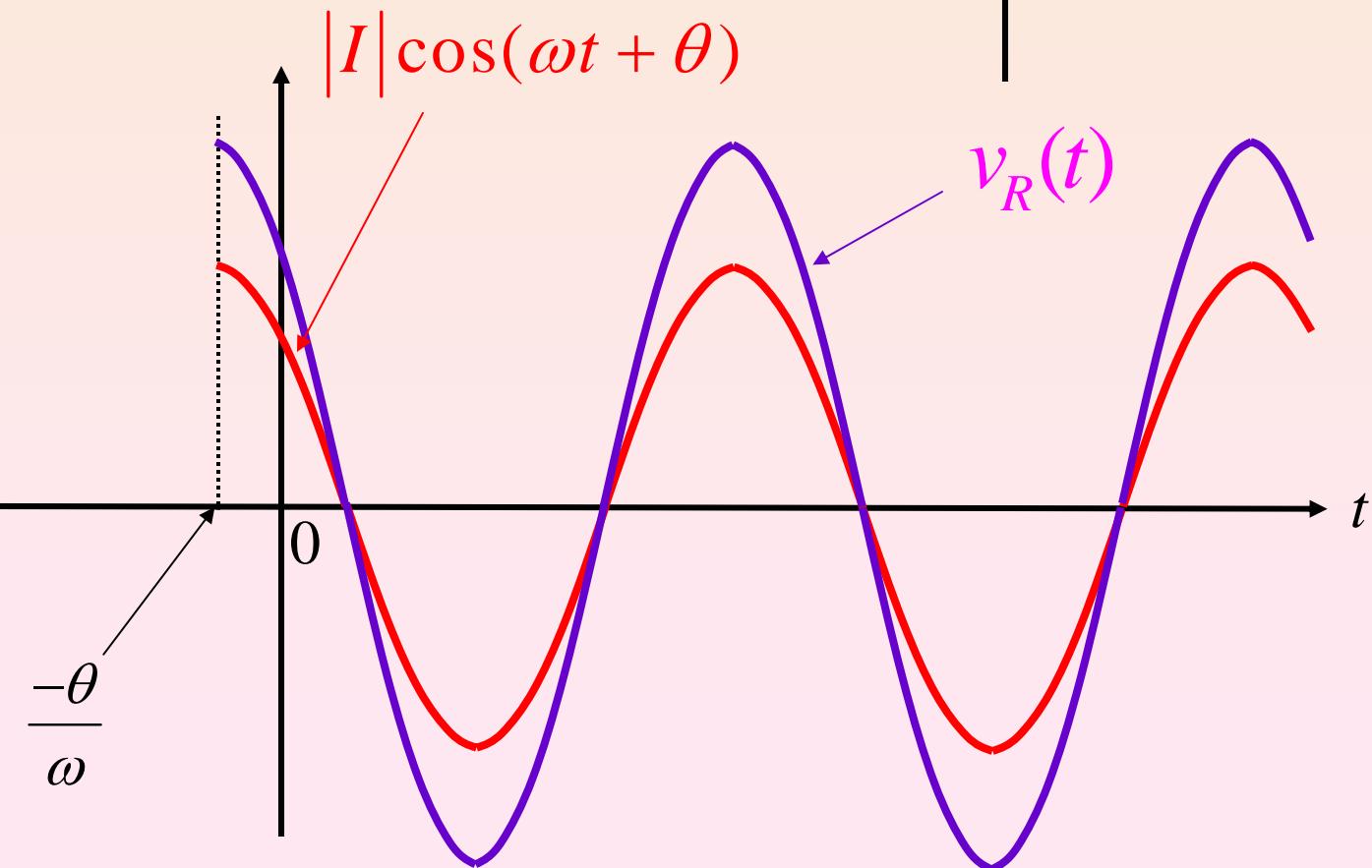


# Phasor Diagram


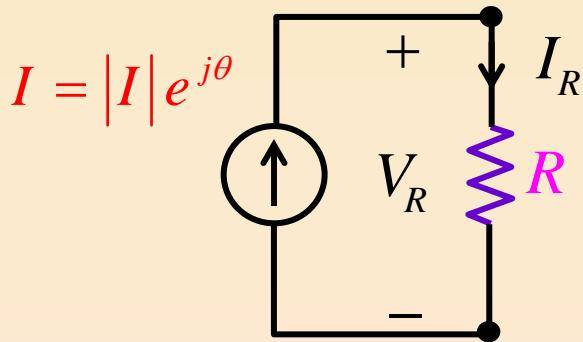


$$V_R = RI_R = R|I|e^{j\theta}$$

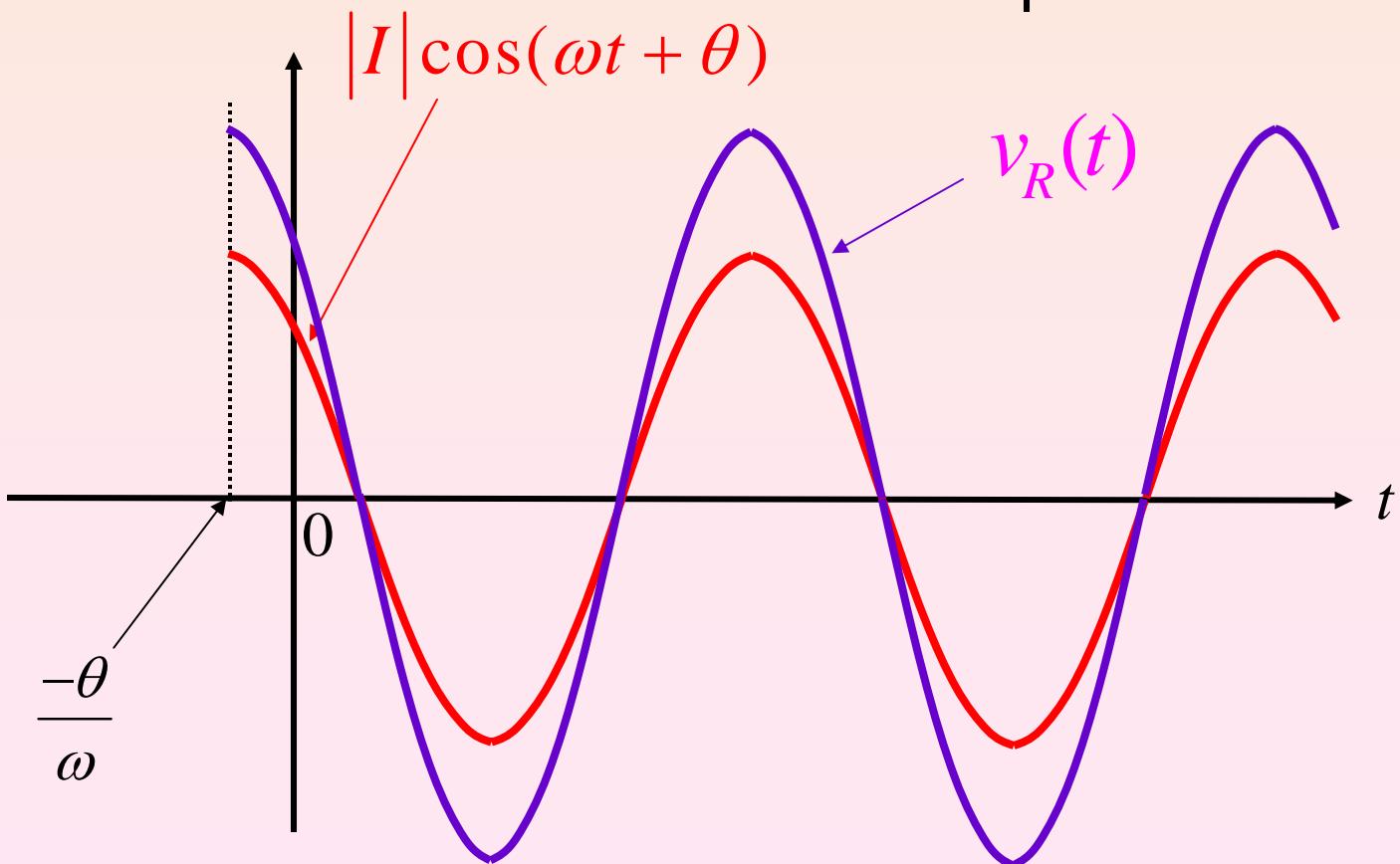
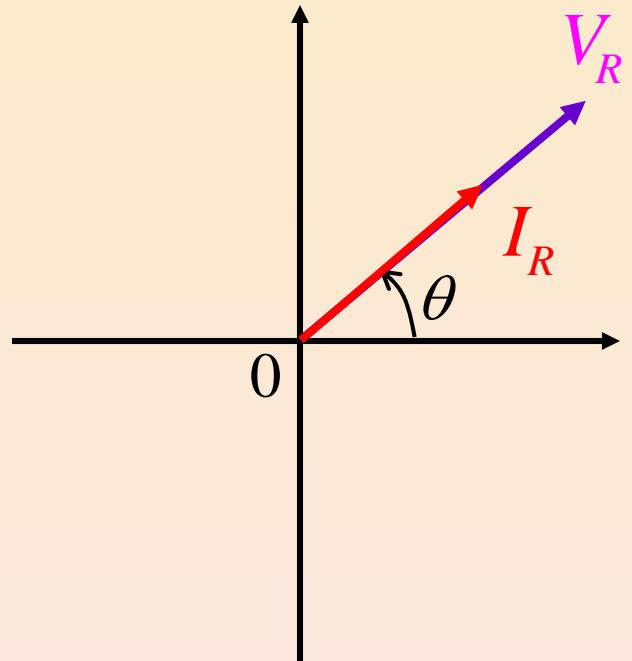
$\therefore$  Resistor Current is  
**in phase** with  
Resistor Voltage.




# Phasor Diagram

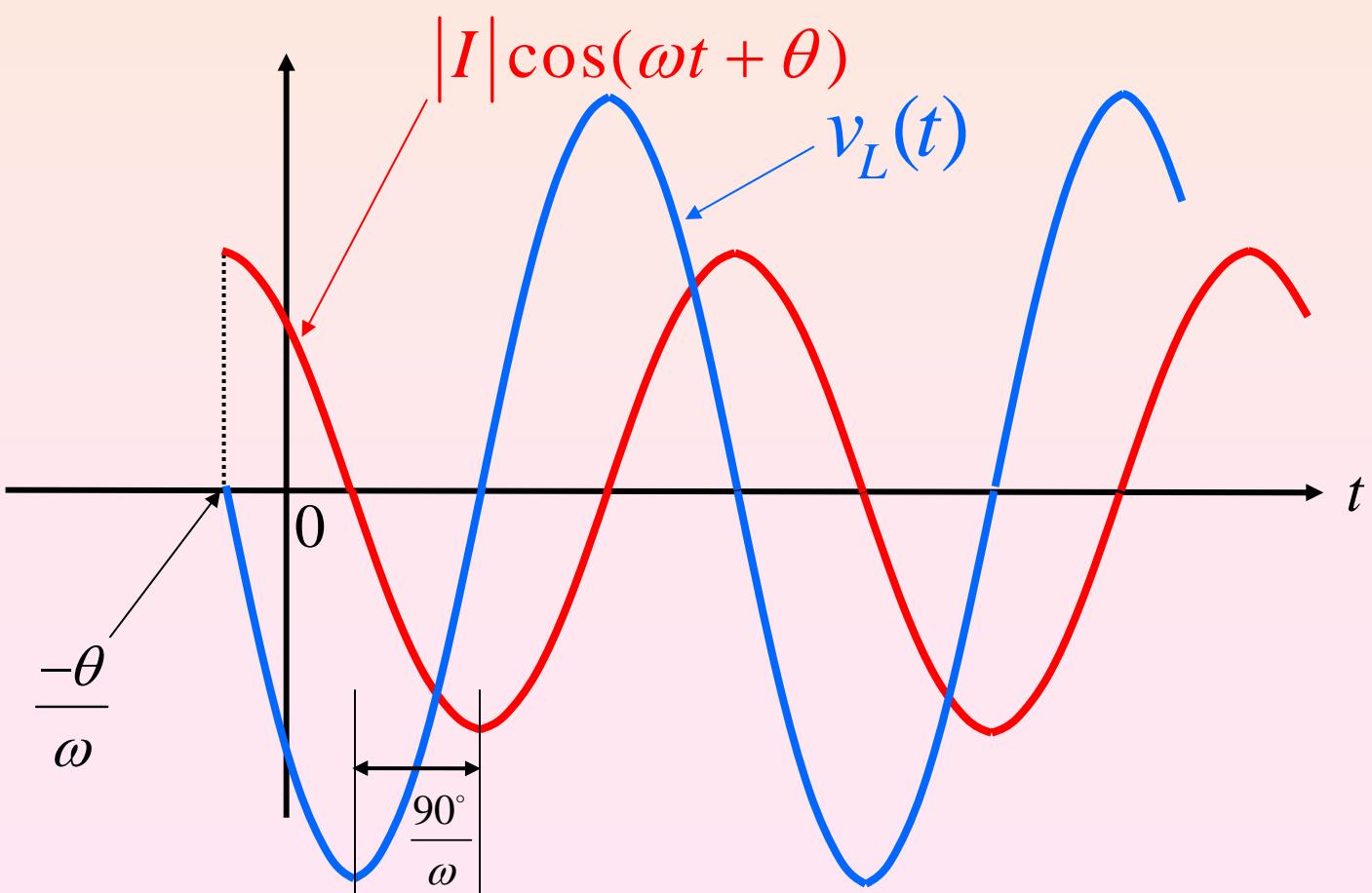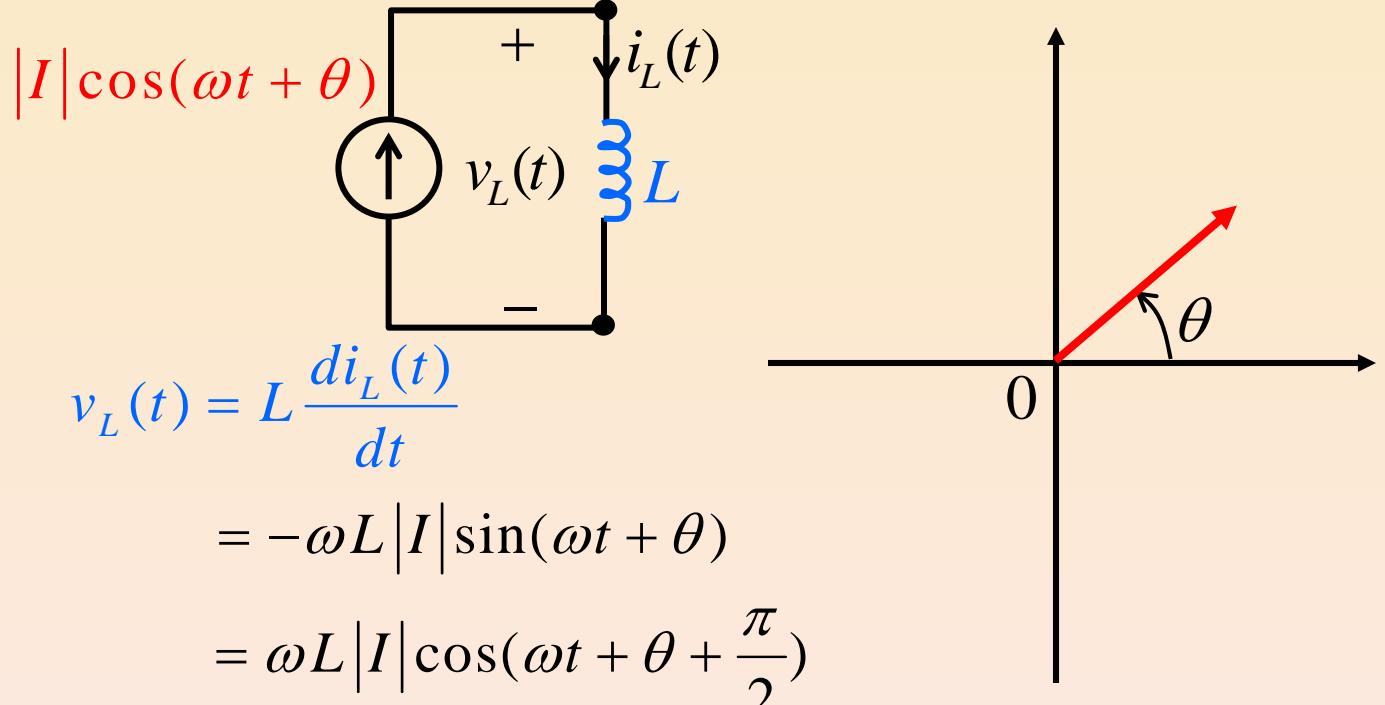

# Phasor Diagram

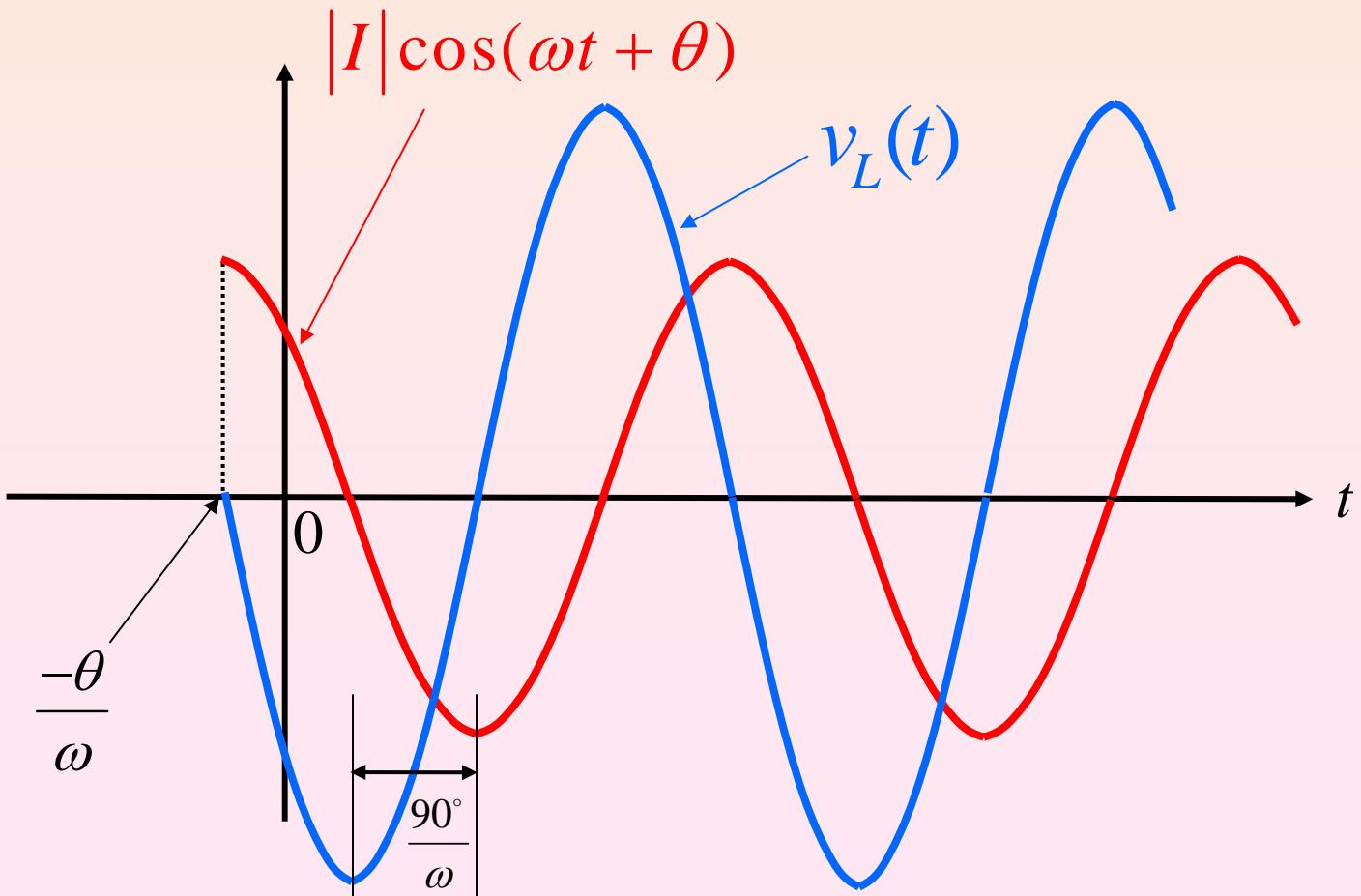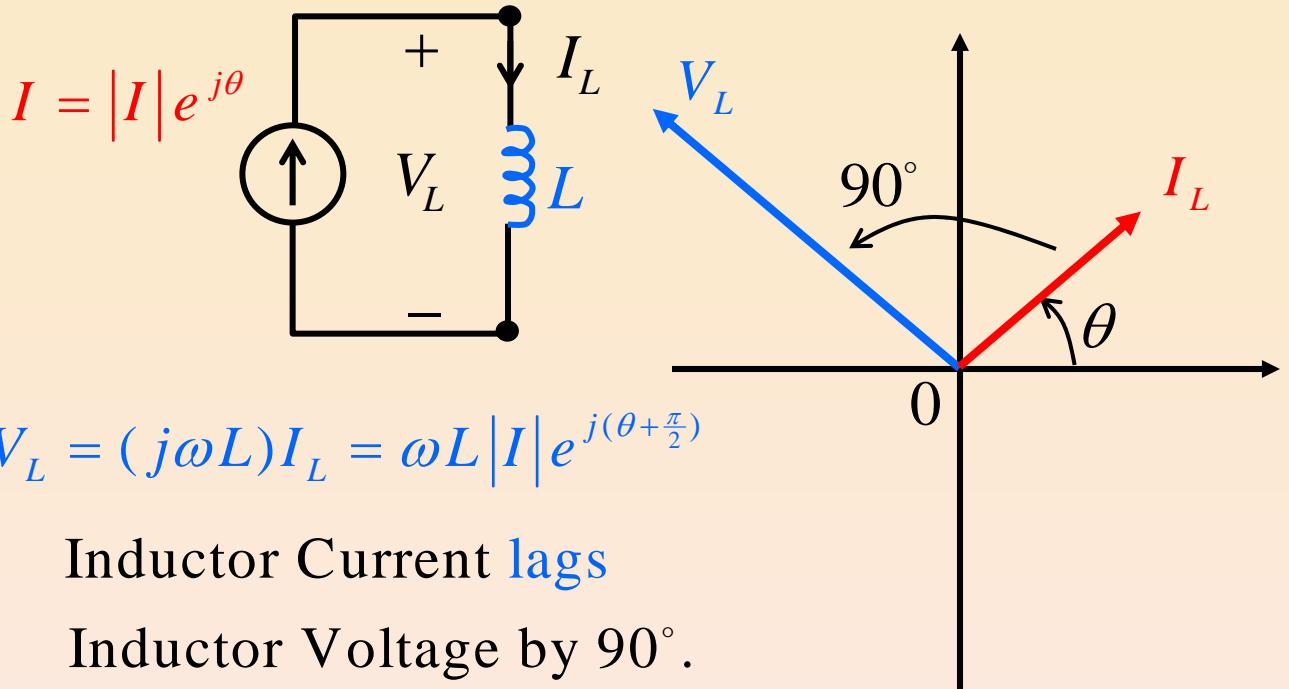



# Phasor Diagram

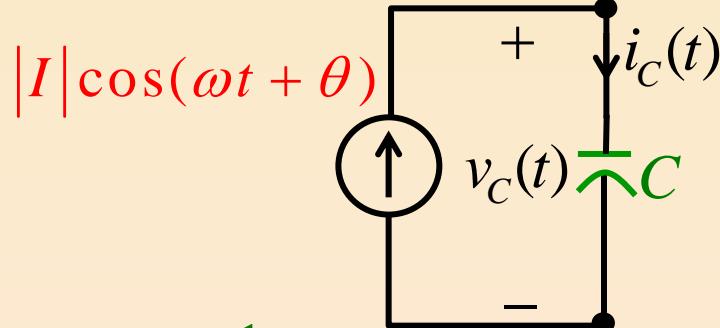

$$v_C(t) = \frac{1}{C} \int i_C(t) dt$$


$$= \frac{|I|}{\omega C} \sin(\omega t + \theta)$$

$$= \frac{|I|}{\omega C} \cos(\omega t + \theta - \frac{\pi}{2})$$

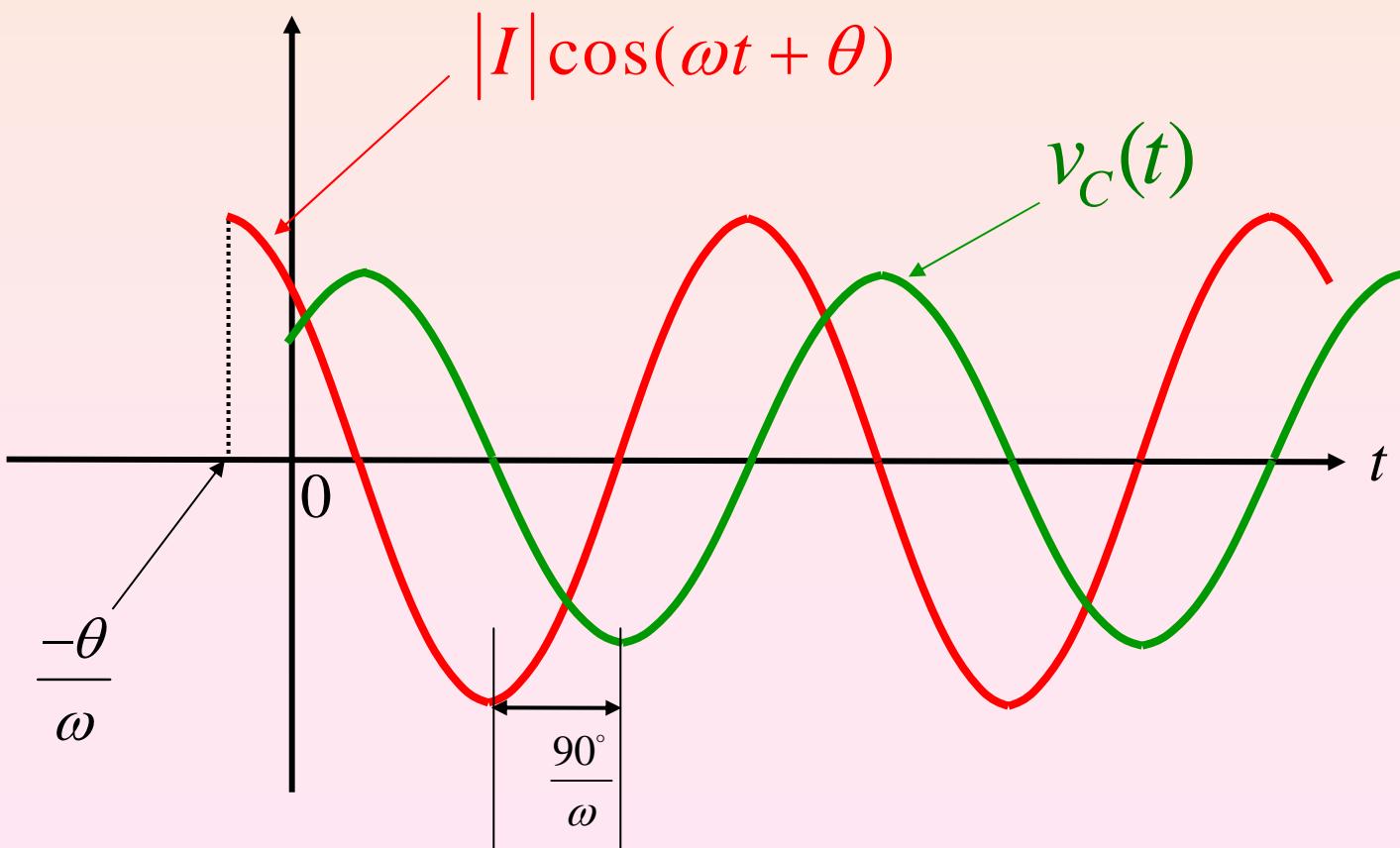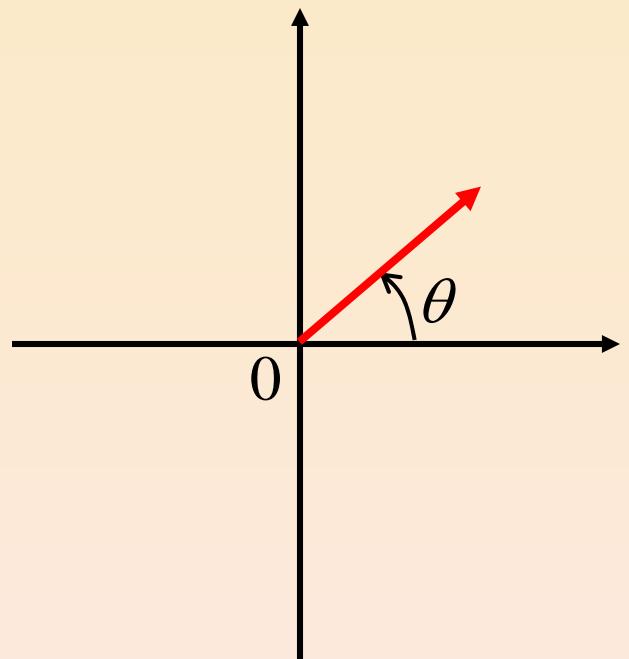


# Phasor Diagram

$$I = |I| e^{j\theta}$$

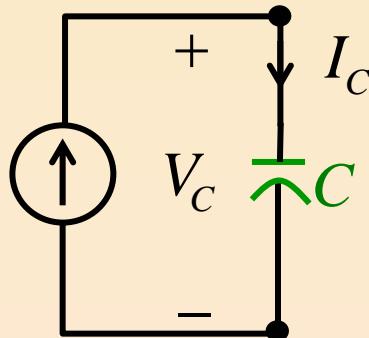


$$V_C = \left( -\frac{1}{j\omega C} \right) I_C = \frac{|I|}{\omega C} e^{j(\theta - \frac{\pi}{2})}$$

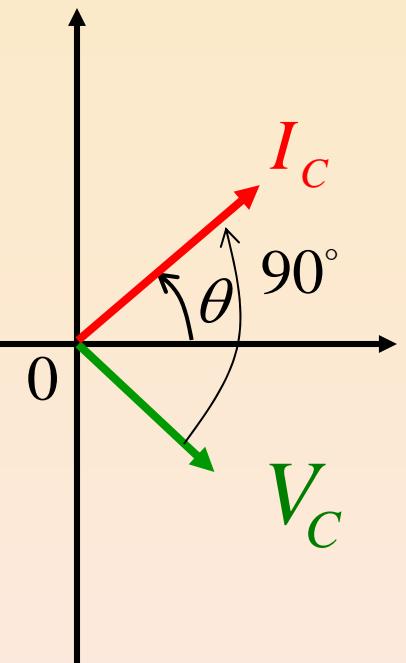


$\therefore$  Capacitor Current leads


Capacitor Voltage  $90^\circ$ .

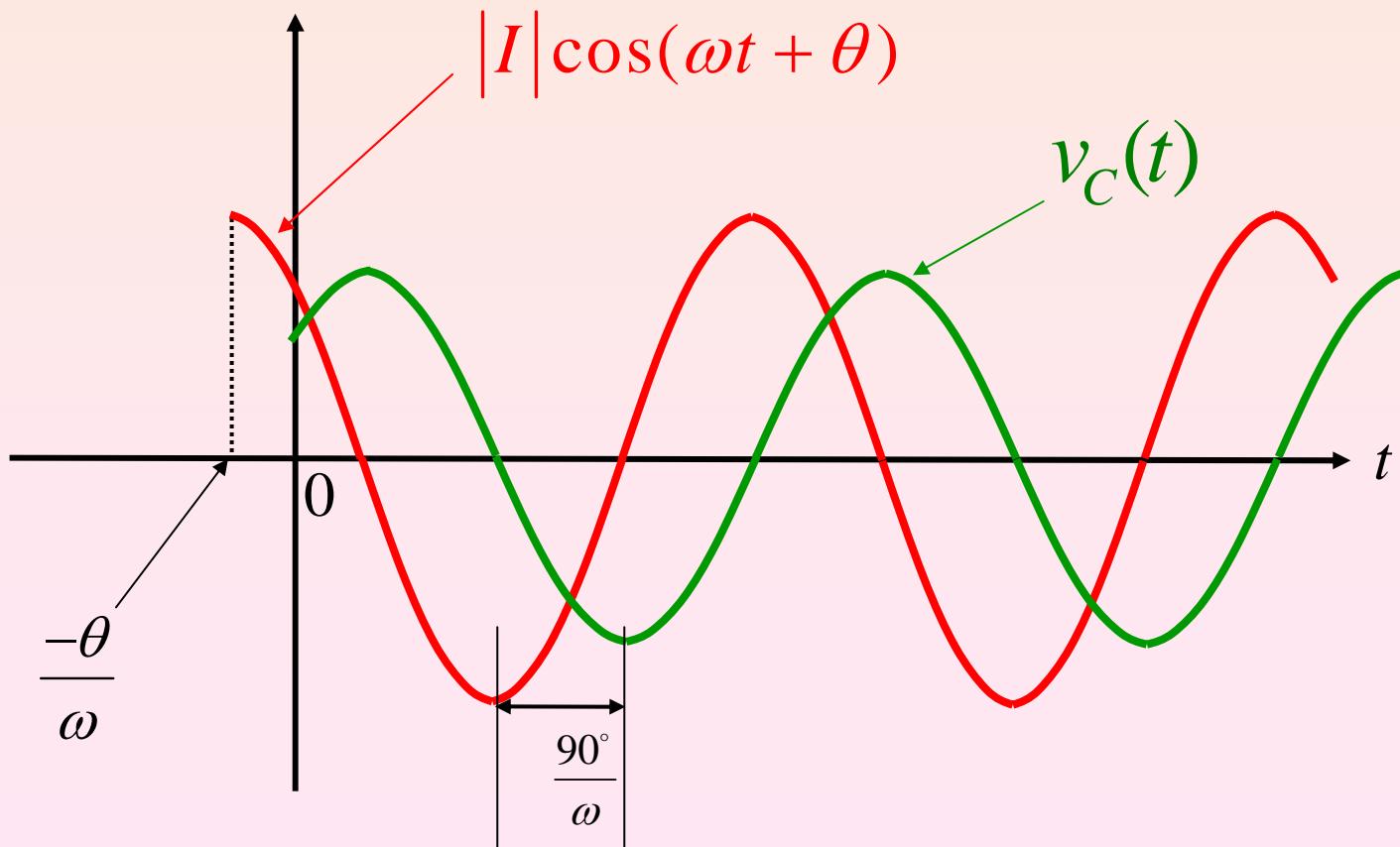

# Phasor Diagram

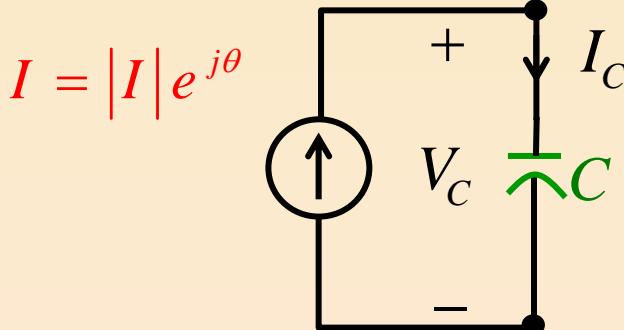


$$V_C = \left( -\frac{1}{j\omega C} \right) I_C = \frac{|I|}{\omega C} e^{j(\theta - \frac{\pi}{2})}$$


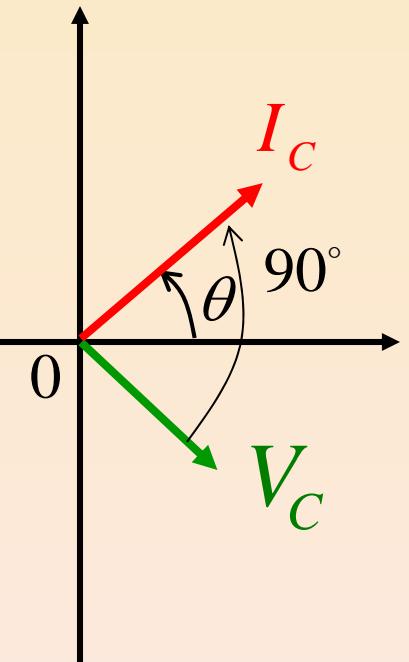


$\therefore$  Capacitor Current leads  
Capacitor Voltage  $90^\circ$ .

Instantaneous Power
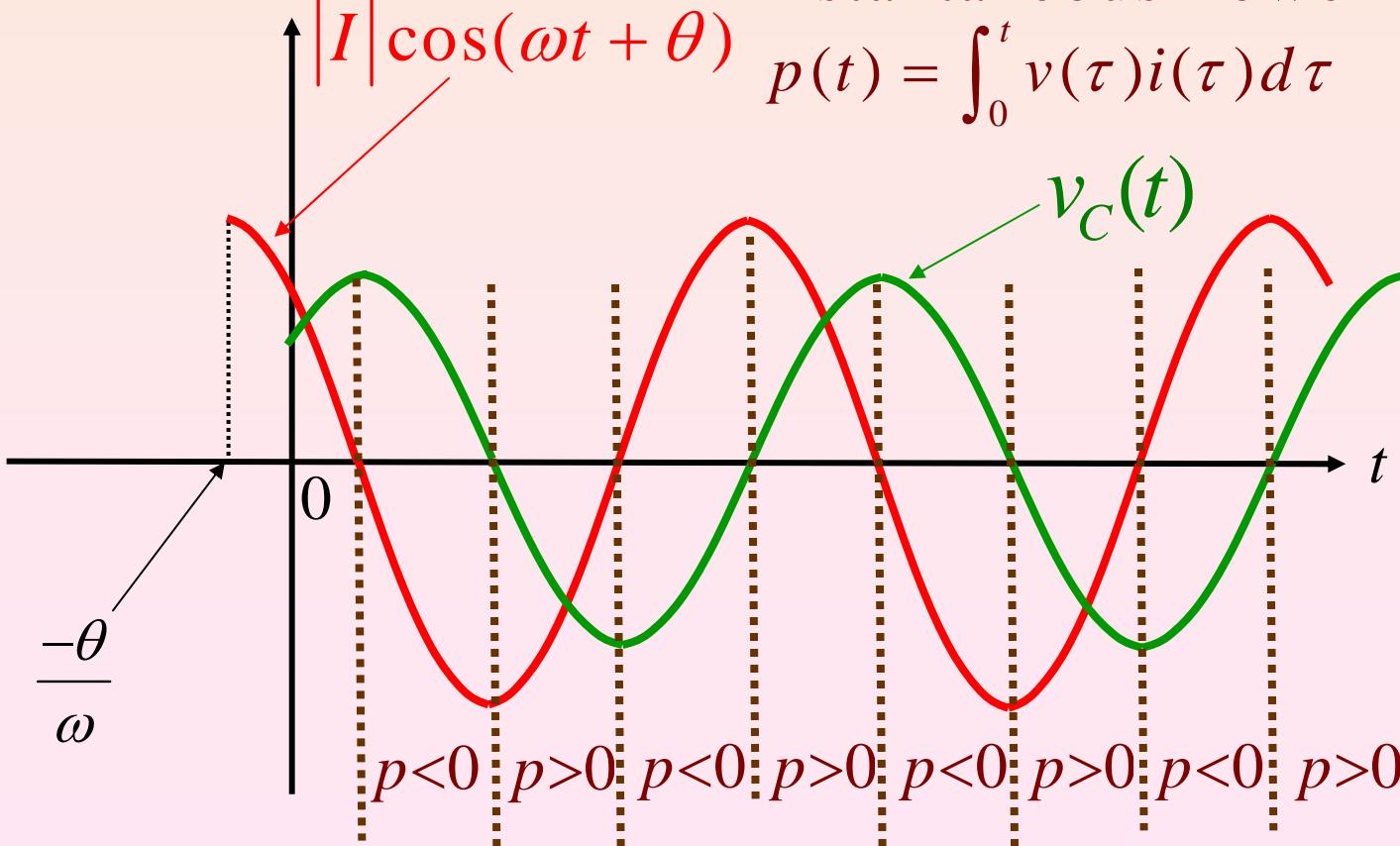
$$p(t) = \int_0^t v(\tau) i(\tau) d\tau$$



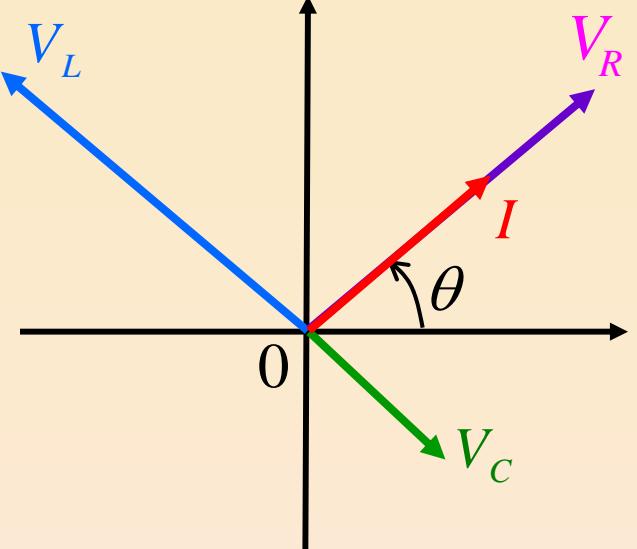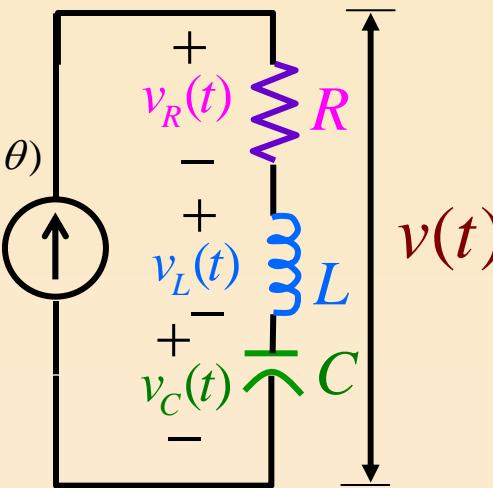




$$v(t) = R |I| \cos(\omega t + \theta)$$

$$+ \omega L |I| \cos(\omega t + \theta + \frac{\pi}{2})$$


$$+ \frac{|I|}{\omega C} \cos(\omega t + \theta - \frac{\pi}{2})$$



$v_R(t) = R |I| \cos(\omega t + \theta)$   
 $v_L(t) = \omega L |I| \cos(\omega t + \theta + \frac{\pi}{2})$   
 $v_C(t) = \frac{|I|}{\omega C} \cos(\omega t + \theta - \frac{\pi}{2})$

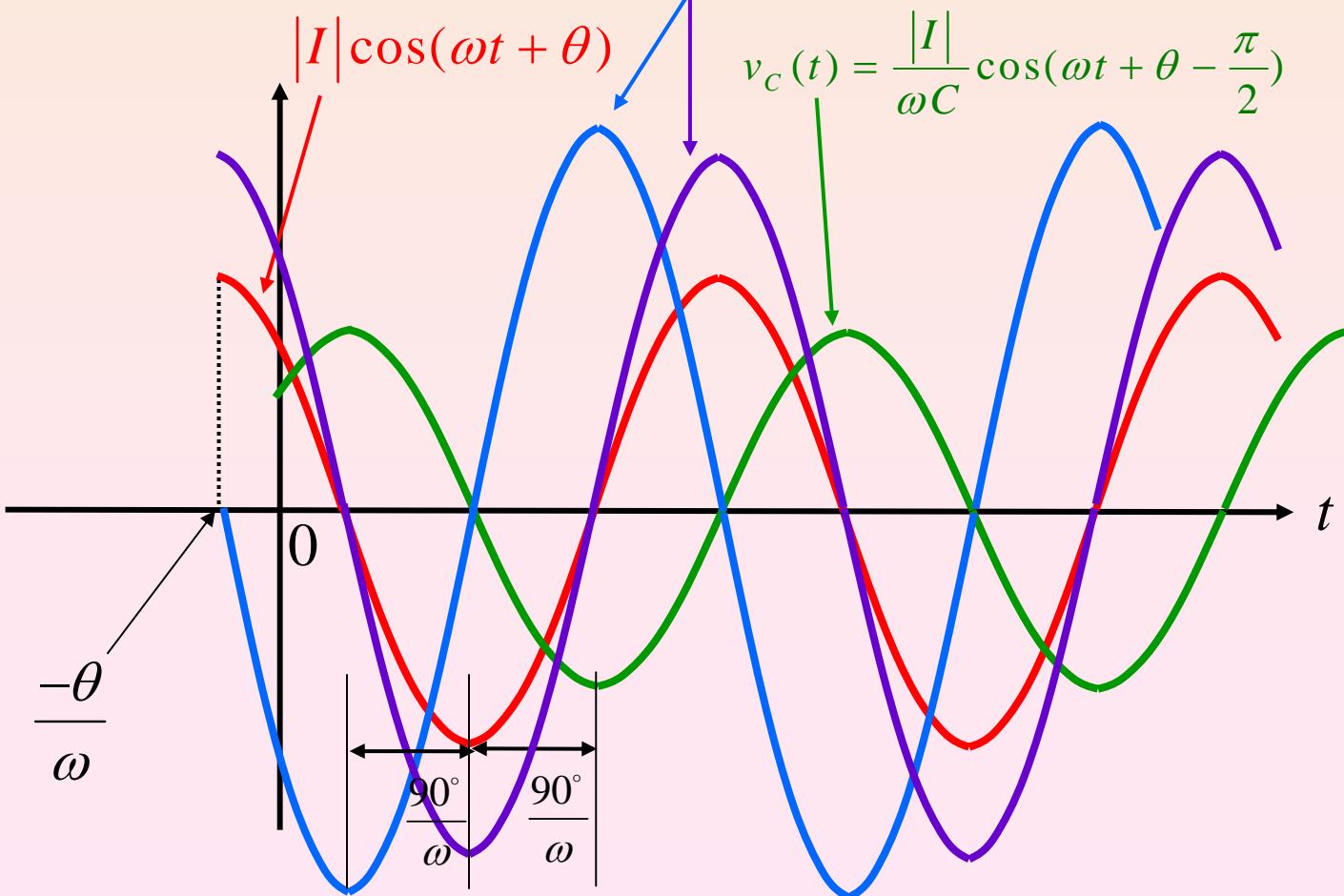

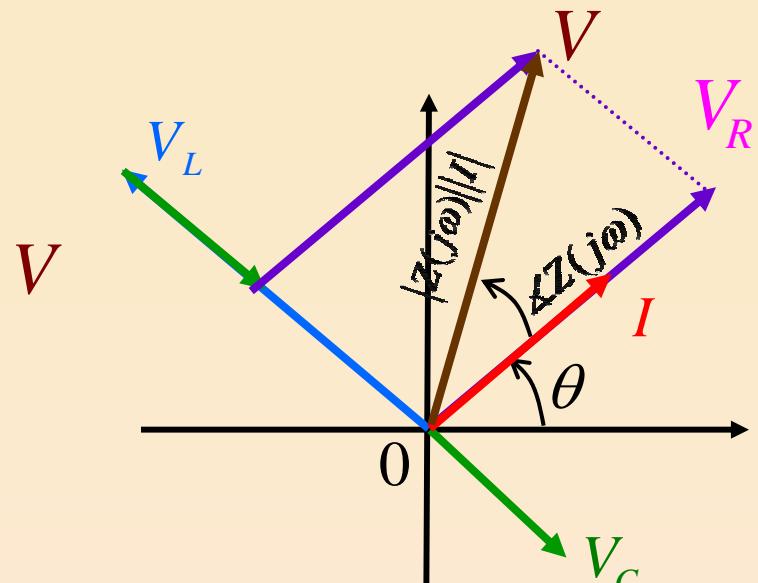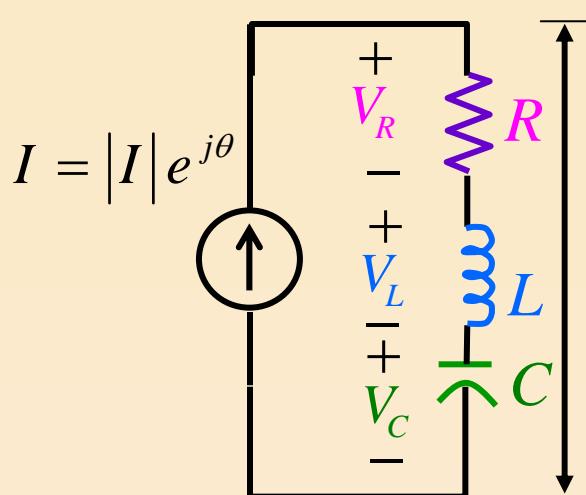

$$V = V_R + V_L + V_C = Z(j\omega)I$$

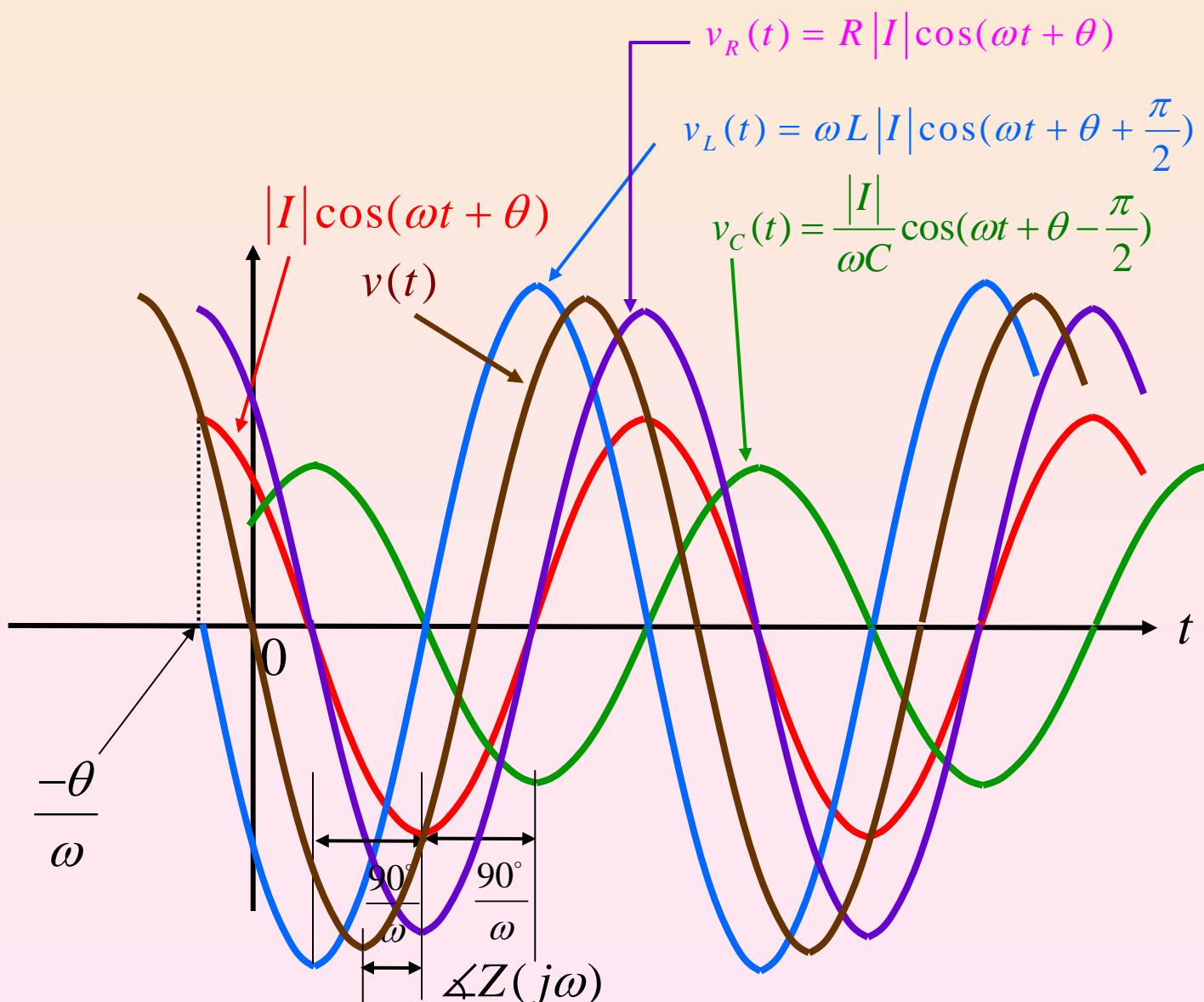

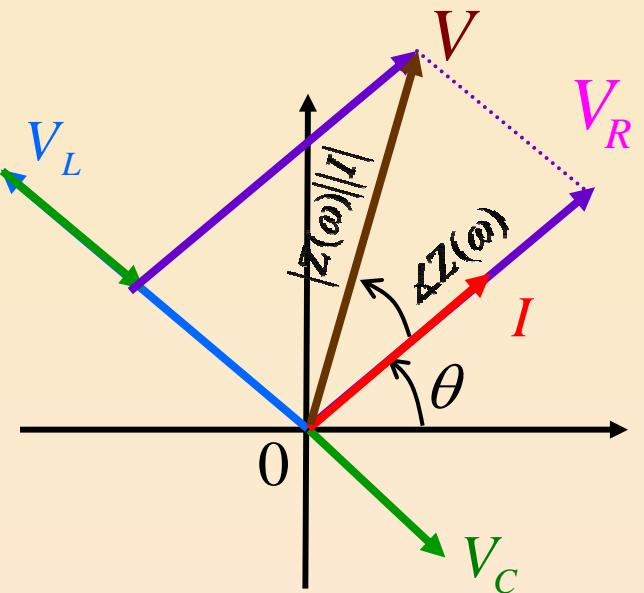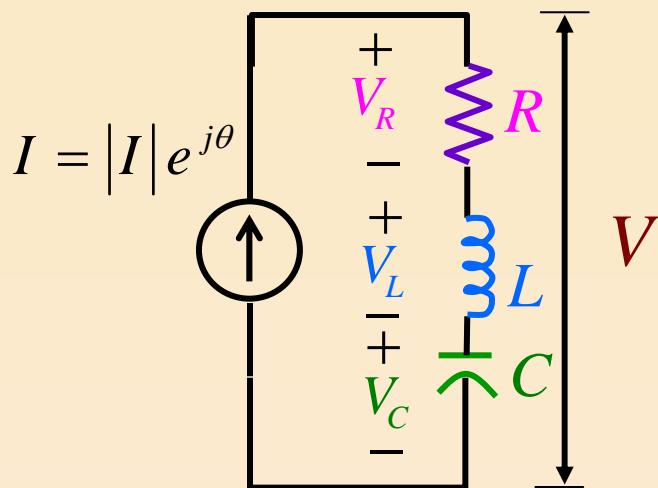

$$V = V_R + V_L + V_C$$

$$= \left( R + j\omega L + \frac{1}{j\omega C} \right) I$$

$$= \underbrace{Z(j\omega)}_{\text{Impedance}} I$$

**Impedance**