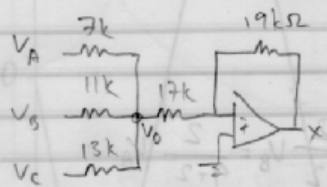


EE100 Midterm Review Problems Solutions

1. $V_A = 10V$ (Voltage Follower)

$V_B = (1 + \frac{2}{3})10V = 16.7V$ (Non-inverting amp)

$V_C = -\frac{7k}{25k} \cdot 10V = -2.8V$ (Inverting amp)



$$\frac{V_A - V_O}{7k} + \frac{V_B - V_O}{11k} + \frac{V_C - V_O}{13k} = \frac{V_O}{17k}$$

$$\frac{V_A}{7k} + \frac{V_B}{11k} + \frac{V_C}{13k} = V_O \left(\frac{1}{17k} + \frac{1}{7k} + \frac{1}{11k} + \frac{1}{13k} \right)$$

$$= \frac{V_O}{2.7k} \Rightarrow V_O = 7.4V$$

$$\frac{V_O - 0}{17k} = \frac{0 - V_x}{19k\Omega} \Rightarrow V_x = -\frac{19k}{17k} V_O$$

$$\boxed{V_x = -8.3V}$$

Non


2. Inverting Amp: $V_O = (1 + \frac{R_F}{5k}) \cdot 10V$

$$\left(1 + \frac{R_F}{5k}\right) \cdot 10 > 16 \Rightarrow \boxed{R_F > 3k\Omega}$$


$\left(1 + \frac{R_F}{5k}\right) \cdot 10 < -16$ will never occur with $R_F > 0$.

(b) Non-inverting amp: $V_o = (1 + \frac{6}{4}) \cdot 8 = 20V$
 saturated at 16V.

equiv ckt.

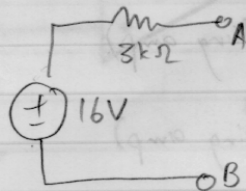

3. (a) ideal op-amp, $V_B = V_{IN}$.

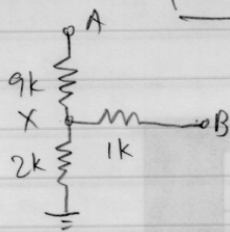

$$V_x = \frac{2}{1+2} V_B = \frac{2}{3} V_B$$

$$V_A = \frac{11}{3} V_B$$

$$V_A = \frac{11}{3} V_{IN}$$

(b) Same as (a) because input voltages are equal in an ideal op-amp.

4. Prob. 5.36: $V_p = \frac{1.5(-18V)}{9.0} = -3V = V_n$

The i-v graph of the non-linear resistor is shown below. $v(0) = 0V$.

$$\frac{-18 - (V_n)}{1.6k} = \frac{V_n - V_o}{R_f} \Rightarrow V_o = \frac{R_f}{1.6k} (15) - 3$$

(a) Find the equilibrium point and dynamic route.

(b) Sketch the dynamic route. Switching times on the graph(s).



$R_f > 0$: +ve Sat's limit.

$$9 = \frac{R_f}{1.6k} 15 - 3$$

$$\hookrightarrow R_f = 1.28k\Omega$$

5. Prob. 5.47:

Inverting amp: $V_o = -\frac{120k}{7.5k} V_{in} = -16 V_{in}$
 clips when $|V_{in}| = 0.03125 V$.

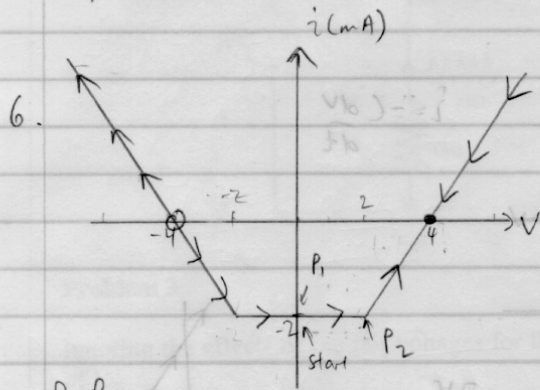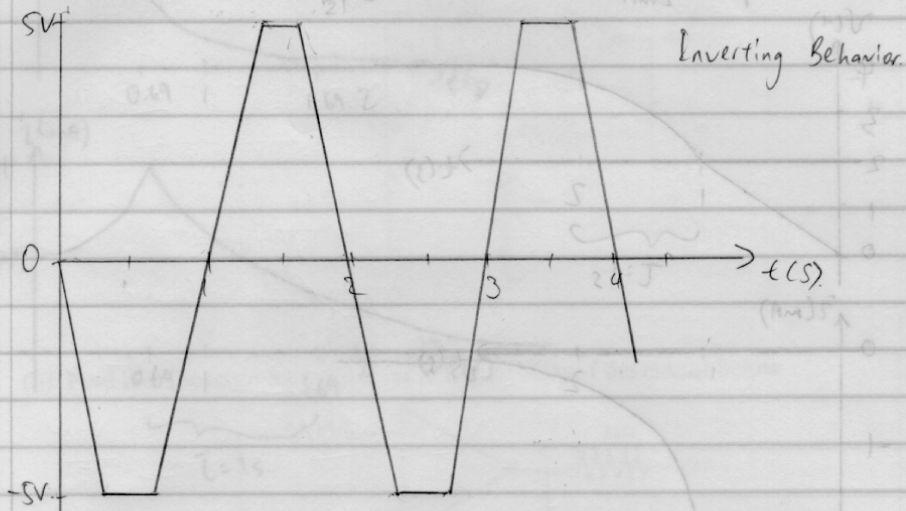

$P_1 - P_2$
 $V_i = 0 V$ $V_f = 2 V$ $i = \text{constant} = -C \frac{dv}{dt} \Rightarrow V$ is linear.

$\frac{dv}{dt} = \frac{+2 mA}{1 mF} = +2 \Rightarrow V(t) = 2t + C$


$V(0) = 2(0) + C = 0 \Rightarrow C = 0$

$V(t) = 2 \cdot 1 = 2 \Rightarrow t = 1 s$


P_2 onwards.

$V_i = 2V$ $V_{final} = 4V$.

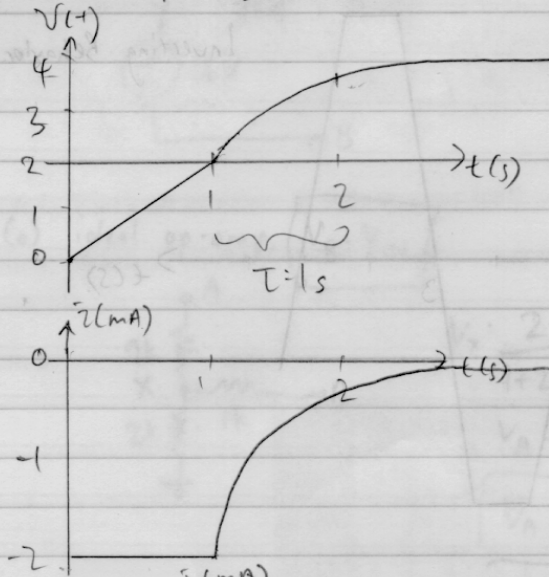$R = \frac{1}{\text{slope}} = \frac{2V}{2mA} = 1k\Omega$ $\tau = RC = 1k \cdot 1m = 1s$.



7.

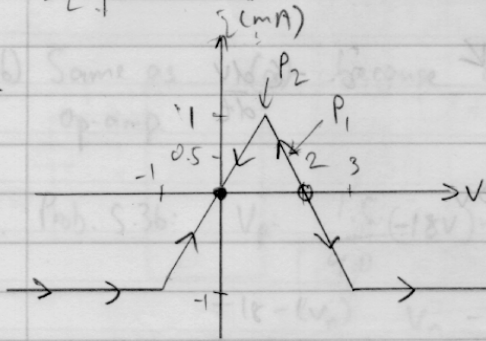

$i = -C \frac{dV}{dt}$

$P_1 - P_2$ $V_{initial} = 1.5V$ $V_{final} = 2V$

$R = \frac{1}{\text{slope}} = \frac{-1V}{1mA} = -1k\Omega$ $\tau = -1s$.

$V(t) = V_{final} - (V_{final} - V_{initial}) e^{\frac{t}{\tau}}$
 $= 2 - 0.5 e^{\frac{t}{-1}} V$

$V(t) = 1V = 2 - 0.5 e^{\frac{t}{-1}} \Rightarrow t = 0.69s = \text{arrive at } P_2 (+1V)$

P_2 onwards: $\tau = 1s$ $V_{final} = 0V$.

