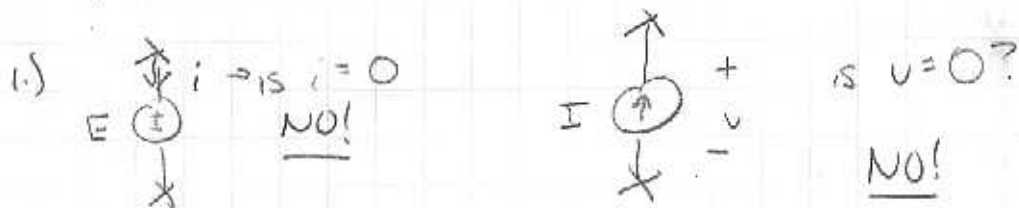


# FINAL REVIEW

Review Notes:



2.) Final is 4 Problems

(1) Nodal Analysis  $\rightarrow$  Set up, don't solve  
 $\rightarrow$  Review Problem 4 of Midterm 1

Undecided Yet {

(2) Op-Amp or RC/RL circuit (not sure yet)  
 $\rightarrow$  Review HW Problems

(3) Diodes or another Op-Amp (not sure yet)  
 $\rightarrow$   $\Sigma$  diode  $\rightarrow$  just review HW  
 $\rightarrow$   $\Sigma$  op-amps  $\rightarrow$  review Problems 1 & 4 from Midterm 2

(4) Graphical Method & Load Line Method  
 $\rightarrow$  Review my lecture notes & last HW  
 $\rightarrow$  Know how to Thevenize Circuits

3.) For RC/RL circuits, remember

a)  $v_C = \frac{1}{C} \int i_C dt$

$i_C = C \frac{dv_C}{dt}$

b)  $v_L = L \frac{di_L}{dt}$

$i_L = \frac{1}{L} \int v_L dt$

c)  $x(t) = x_{\infty} + (x_0 - x_{\infty}) \exp[-(t-t_0)/\tau]$

d)  $\tau = RC$  or  $L/R$

4.) All diodes will be ideal. Not necessarily true of op-amps.

5.) Make sure to go over all of Chapter 7 for RC/RL circuits.  
" " " " " " " Chapter 5 for op-amps.

6.) All circuits to be thevenized do not require "Test Source Method"

i.e. Just find  $V_{oc}$  &  $I_{sc} \rightarrow R_{Th} = \frac{V_{oc}}{I_{sc}}$

7.) When/how to assume if a diode is on.

if  $i \rightarrow \nabla$  ~~—|~~ Assume on  
 if  $i \rightarrow \nabla$  ~~—|~~ Assume off


8.) For multiple switches in RC/RL circuits.

$\tau$  could change after each switch.

9.) Op-Amps. Can't assume ideal?

Then  $v_{out} = A(v^+ - v^-)$  ALWAYS TRUE


10.) Remember for diodes,

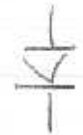$D_1$    $v_D$  IF you assume  $D_1$  is off & you calculate  $v_D > 0$ , ASSUMPTION IS WRONG.


$v_D < 0$  for diode off &  $v_D > 0$  for diode on

11.) Graphical Method


Series:

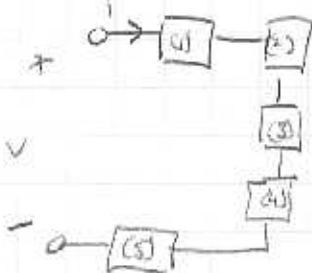

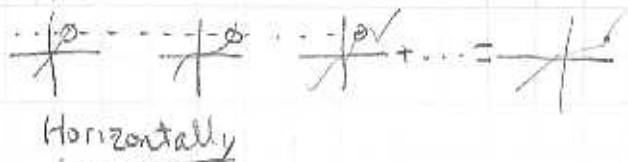$i$  is same, but  $v_1 + v_2 + v_3 + \dots = v$   
 For a given  $i$ , add all  $v$ 's.




Parallel

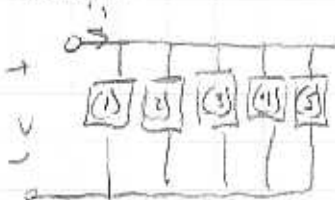

$v$  is same for all, but  $i = i_1 + i_2 + i_3 + \dots$   
 For a given  $v$ , add all  $i$ 's




Example 1

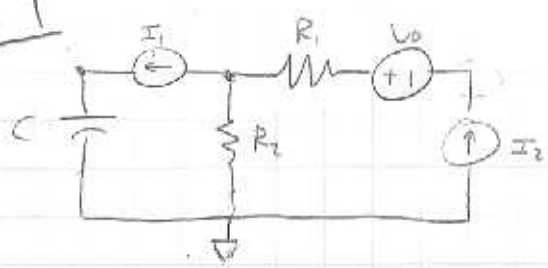


Write 3 nodal Equations

Soln

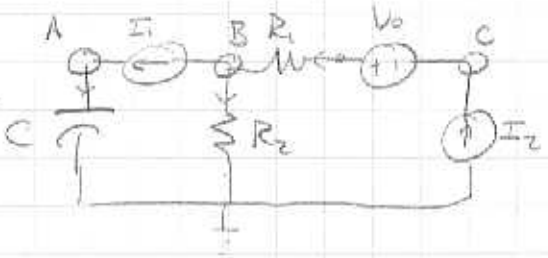


(A)  $I_1 = C \frac{dV_A}{dt}$  ✓  
 (B)  $I_{in} = I_{out}$   
 $I_2 = \frac{V_B}{R_2} + I_1$  ✓  
 (C)  $\frac{V_C + V_0 - V_B}{R_1} = I_2$  ✓

Example 2

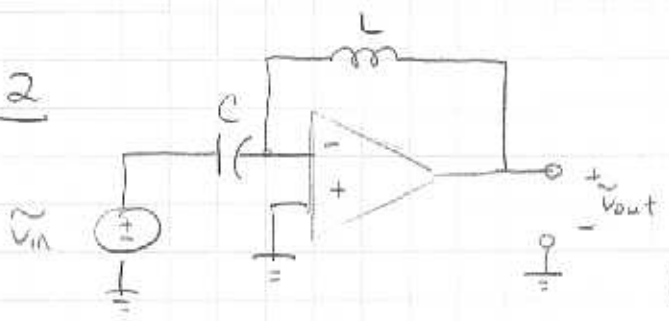

$\tilde{V}_{in} = \sin(\omega t)$   
 $\omega = 1000 \text{ rad/sec}$   
 $L = 1 \text{ mH}$   
 $C = 1 \text{ mF}$   
 Find  $v_{out}/v_{in}$

Soln

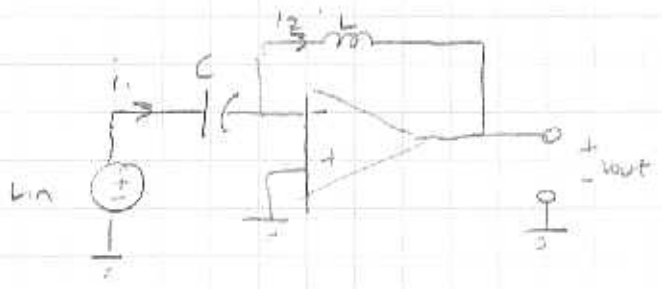

$i_1 = i_2$

$i_1 = C \frac{dv_{in}}{dt}$        $i_2 = \frac{v_{out} - v_{in}}{L}$        $v = 0 - v_{out} = L \frac{di_2}{dt} = L \frac{di_1}{dt}$

So:  $i_1 = C \frac{dv_{in}}{dt}$        $v_{out} = -L \frac{di_1}{dt}$

$v_{out} = -L \frac{d}{dt} \left[ C \frac{dv_{in}}{dt} \right] = -LC \frac{d^2 v_{in}}{dt^2}$

$\frac{d^2 v_{in}}{dt^2} = \frac{d}{dt} \left[ \frac{d}{dt} (\sin \omega t) \right] = \frac{d}{dt} [\omega \cos \omega t] = -\omega^2 \sin \omega t = -\omega^2 v_{in}$


$v_{out} = -LC (-\omega^2 v_{in}) \Rightarrow \frac{v_{out}}{v_{in}} = LC \omega^2$

$\frac{v_{out}}{v_{in}} = (0.001 \text{ H})(0.001 \text{ F})(1000 \text{ sec}^{-1})^2 \Rightarrow \frac{v_{out}}{v_{in}} = 1$

### Example 3
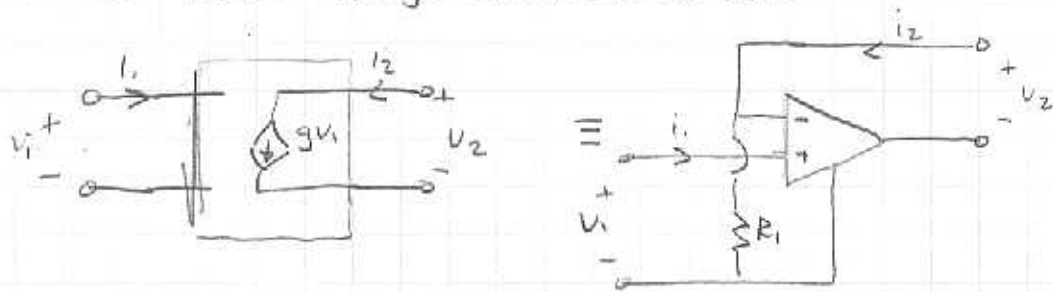
### Controlled Sources modeled by Amplifiers:

① VCCS: Voltage Controlled Current Source



$$i_2 = g v_1$$

What is "g"?

$$V^+ = V^- = V_1, \quad i_1 = 0$$

$$\frac{V_1 - 0}{R_1} = i_2 \Rightarrow i_2 = \frac{V_1}{R_1} = g v_1 \Rightarrow \boxed{g = \frac{1}{R_1}}$$

② CCVS: Current Controlled Voltage Source



$$v_2 = r i_1$$

What is "r"?

$$V_1 = V^- = V^+ = 0, \quad i_1 = \frac{0 - v_2}{R} \Rightarrow v_2 = -R i_1 = r i_1 \Rightarrow \boxed{r = -R}$$

③ VCVS: Voltage Controlled Voltage Source



$$v_2 = \mu v_1$$

What is "mu"?


$$i_1 = 0, \quad V_1 = V^- = V^+$$

$$\frac{v_2 - v_1}{R_2} = \frac{v_1 - 0}{R_1} \Rightarrow v_2 = R_2 v_1 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$v_2 = v_1 \left[ 1 + \frac{R_2}{R_1} \right] = \mu v_1 \Rightarrow \boxed{\mu = 1 + \frac{R_2}{R_1}}$$
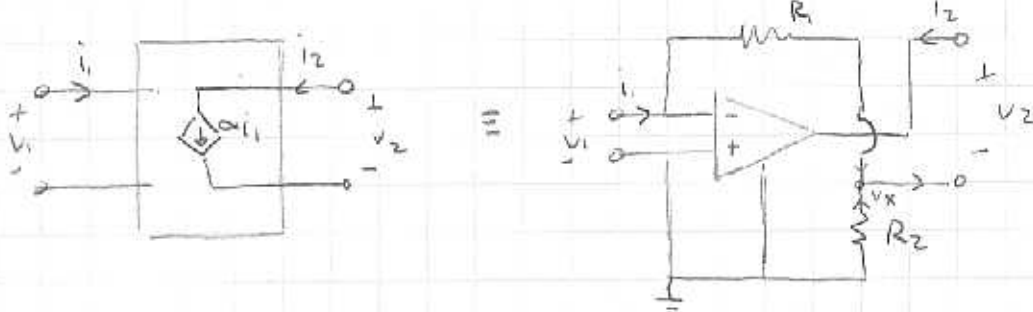
### Example 3 Continued

④ CCCS : Current Controlled Current Source



$i_2 = \alpha i_1$   
What is "alpha"?


$$v_1 = 0 \quad v^- = v^+ = 0 \quad v_x = 0 - i_1 R_1$$

$$\frac{0 - v_x}{R_2} + i_1 = i_2 = i_1 \frac{-(-i_1 R_1)}{R_2} = i_1 \left[ 1 + \frac{R_1}{R_2} \right] = \alpha i_1$$

$$\alpha = 1 + \frac{R_1}{R_2}$$

### Example 4

$$v_s(t) = 10 \sin(2000\pi t)$$

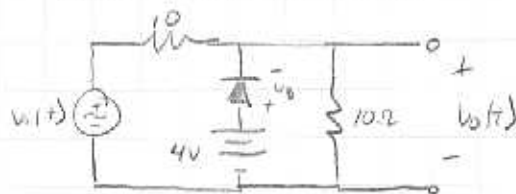

a) Find  $v_o(t)$  vs.  $t$

b) Find Transfer Characteristic:  $v_o(t)$  vs  $v_s(t)$



Case 1: Diode is on:  
 $v_s \geq 0$



$$v_s = 0$$

$$v_{out} = 4V$$

Case 2: Diode is off:

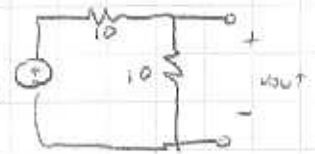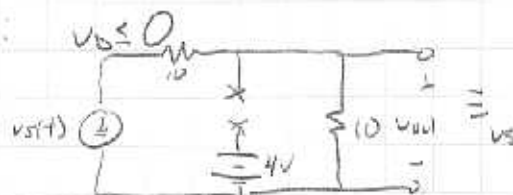

Voltage Divider:

$$v_{out} = \left( \frac{10}{10+10} \right) v_s \Rightarrow v_{out} = \frac{v_s}{2}$$

When valid:

$$4 - v_D = v_{out}$$

$$4 - v_{out} = v_D$$

$$\text{Diode off} \Rightarrow 4 - v_{out} \leq 0$$



$$v_{out} \geq 4 \Rightarrow \frac{v_s}{2} \geq 4 \Rightarrow v_s \geq 8$$

$$\text{Diode on} \Rightarrow 4 - v_{out} \geq 0$$


$$v_{out} \leq 4 \Rightarrow \frac{v_s}{2} \leq 4 \Rightarrow v_s \leq 8$$

$$v_o(t) = \begin{cases} 4V, & \text{if } v_s \leq 8V \\ \frac{v_s}{2}, & \text{if } v_s \geq 8V \end{cases}$$

### Ex 4 Cont

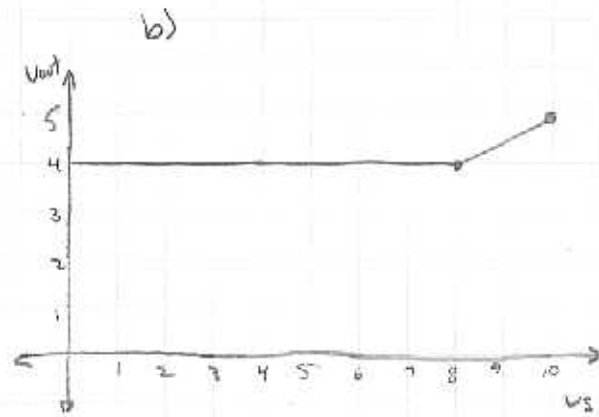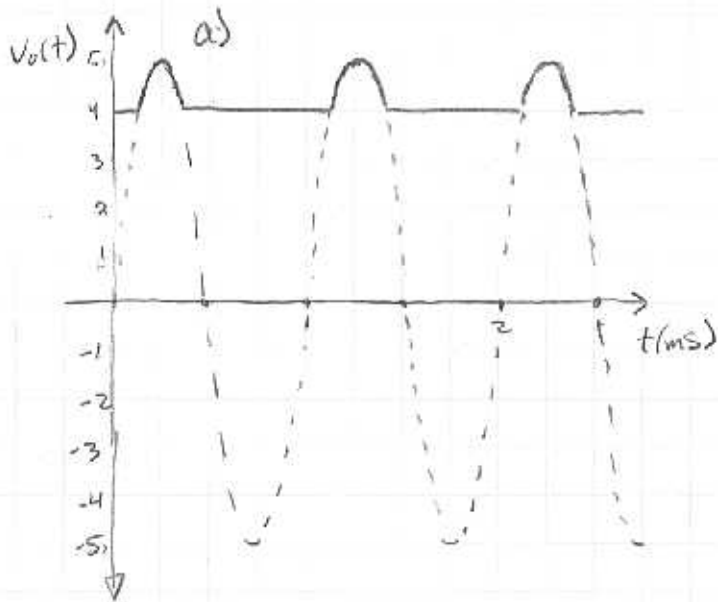

### Example 5 Bridge Rectifier

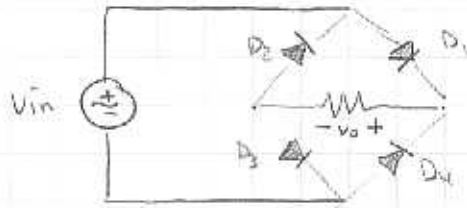


$$v_{in} = 10 \sin(2\pi 60 t)$$

All diodes ideal

Plot  $v_o(t)$


→ Analyse path of current for varying  $v_{in}$ .
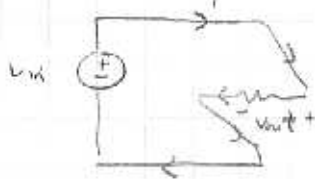
$$v_{in} > 0 \Rightarrow D_1, D_3 \text{ on, } D_2 \text{ \& D}_4 \text{ off}$$





$$v_{in} = v_{out}$$
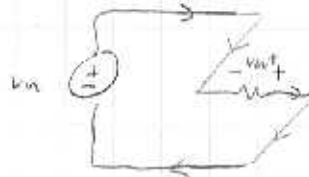
$$v_{in} < 0 \Rightarrow D_1, D_3 \text{ off, } D_2 \text{ \& D}_4 \text{ on}$$




$$v_{in} = -v_{out}$$

Ex. 5 Cont

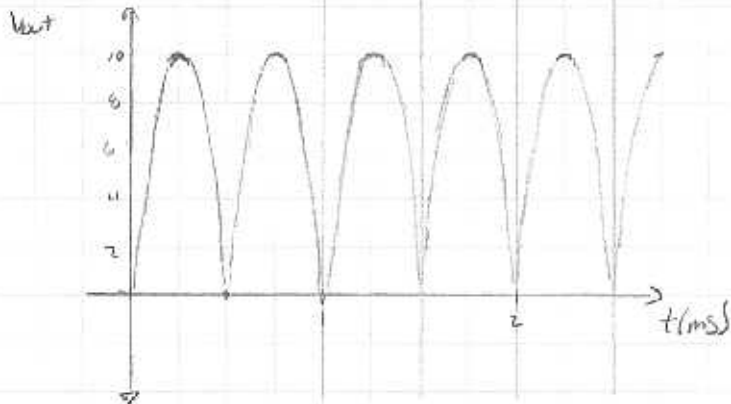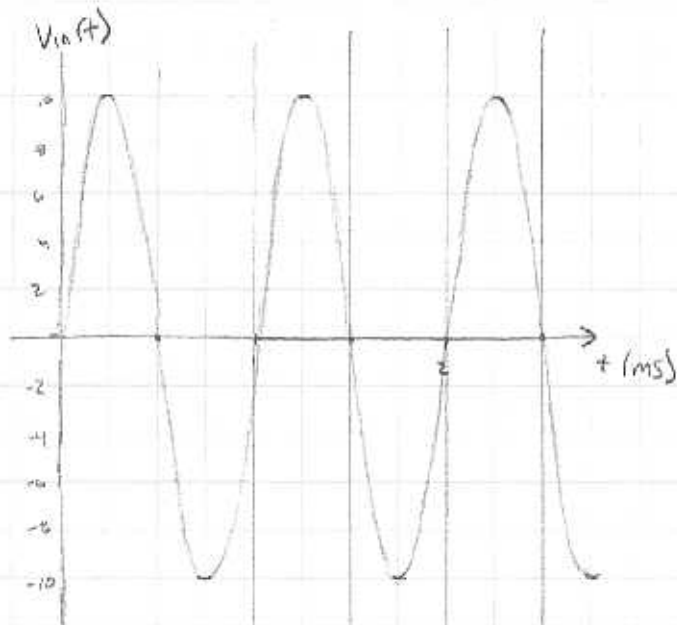

Ex. 6

Problem 485

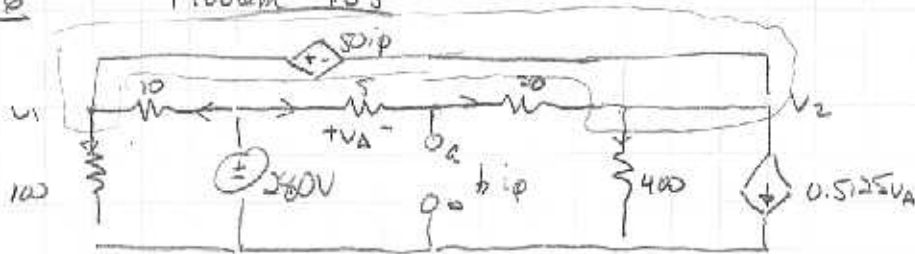

Find Thevenin Equivalent

$$V_{oc}: i_{\phi} = 0 \quad 50i_{\phi} = 0 \quad v_1 = v_2$$

$$\textcircled{1} \quad \frac{280 - v_1}{10} + \frac{280 - v_1}{25} = \frac{v_1}{100} + \frac{v_1}{400} + 0.5125v_A$$

$$\textcircled{2} \quad \text{Voltage Divider: } v_A = \frac{5}{25} (280 - v_1) = 56 - 0.2v_1$$

Solve:  $v_1 = 210V \quad v_A = 14$   
 $V_{TH} = 280 - v_A = 266V$


$$I_{sc}: v_A = 280 \quad v_1 - v_2 = 50i_{\phi}$$

$$\frac{280 - v_1}{10} + \frac{0 - v_2}{20} = \frac{v_1}{100} + \frac{v_2}{400} + 0.5125v_A$$

$$i_{\phi} = \frac{280 - 0}{5} - \left[ \frac{0 - v_2}{20} \right] \Rightarrow i_{\phi} = 56 + 0.05v_2$$



Solve:  $i_{\phi} = I_{sc} = 7.6A$

$$R_{TH}: \frac{V_{TH}}{I_{sc}} = \frac{266V}{7.6A} = 35\Omega$$

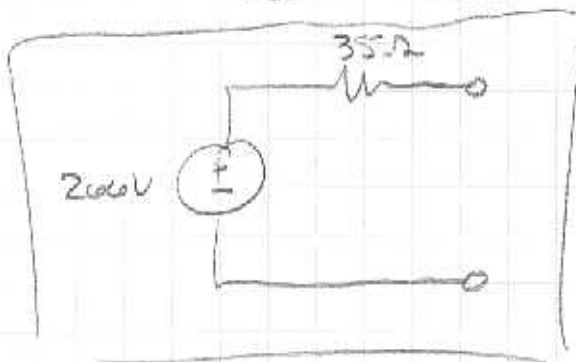




Example 7

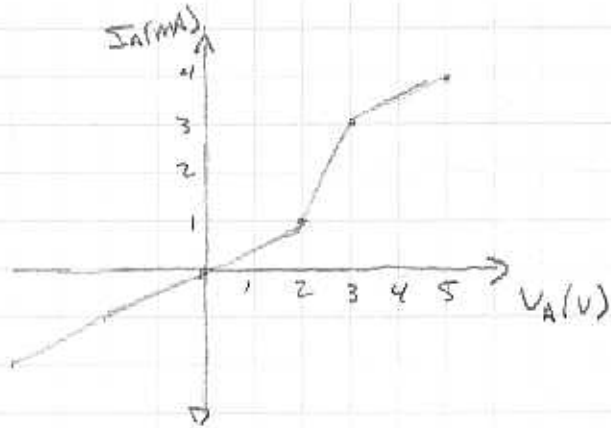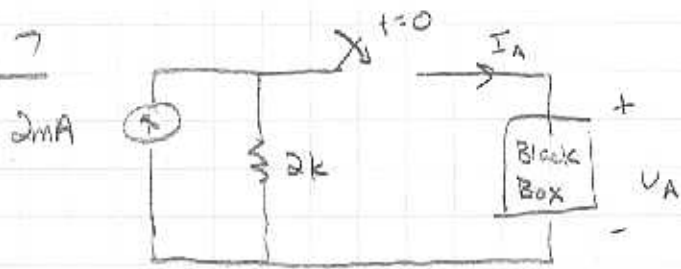

What is the operating pt. of this circuit?

Load-Line Method!

Side-Note:

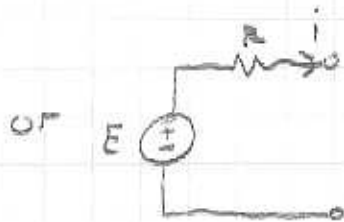

KVL:


$$E - iR = V$$

$$i = F(V) = \frac{1}{R} [E - V]$$

KCL:  $I = i + i_R$ ,  $i_R = V/R$

$$\rightarrow i = F(V) = I - \frac{V}{R}$$

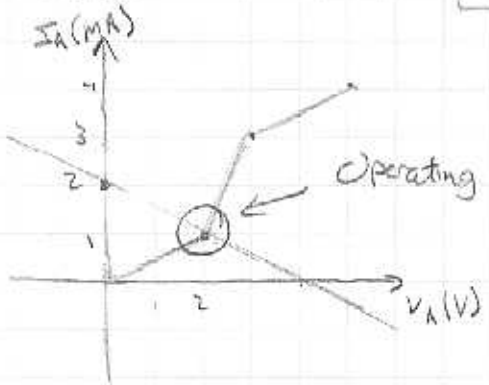Back to circuit:  $i = I - V/R \Rightarrow i \text{ (mA)} = 2 - V/2$



$$\begin{matrix} V_A = 2V \\ I_A = 2mA \end{matrix}$$