





Tricks for non-linear circuits


(1) v_{oc}, i_{sc} Capacitors: $-i = \frac{dv}{dt}$ i_{sc} always 0Inductors: $-v = \frac{di}{dt}$ v_{oc} always 0(2) Always use $-\frac{i}{C} = \frac{dv}{dt}$ for Cap. $-\frac{v}{L} = \frac{di}{dt}$ for Ind.↳ so general soln: $x(t) = x_{\infty} + (x_0 - x_{\infty}) \exp[-(t-t_0)/\tau]$ (3) (i) If you're not at eq or you're not heading towards stable equilibrium, determine a switching time.(ii) If headed to stable eq. don't find a switching time.

- (4) (i) In a negative slope region if x is increasing? Draw 
- (ii) In a " " " " " decreasing? Draw 
- (iii) In a positive " " " " " increasing? Draw 
- (iv) In " " " " " decreasing? Draw 


(5) Easy way to find shape of curves? → See Problem 3

Tricks for Op-amps

(1) Ideal? → Does not saturate → Ignore railings

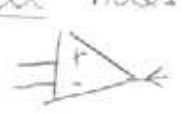(2) Nonideal → ~~Can~~ Can saturate → Accounts for railings → $V_n \neq V_p$ (3) Do nodal analysis at all nodes you see
EXCEPT v_{out} .  Current can flow into output of op-amp

From the Summer:

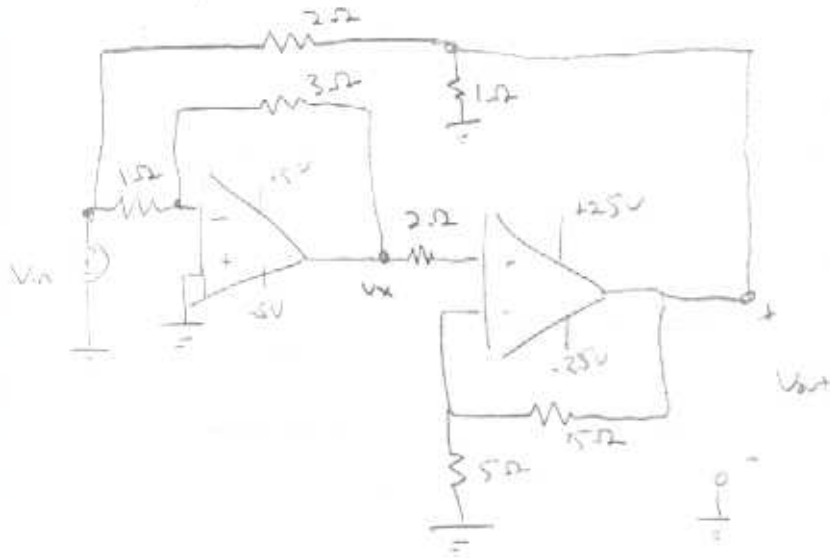

- a) Find type of amplifier
- b) Find v_x/v_{in} (Ideal)
- c) Find v_{out}/v_{in} (Ideal)
- d) $v_{in} = 3V$, $v_{out} = ?$
- e) $v_{in} = -4V$, $v_{out} = ?$
- f) $v_{in} = 1V$, $v_{out} = ?$

Soln

a) Inverting + Non-inverting = Inverting

b) Inverting op-amp:
$$\frac{v_{in} \cdot 0}{1} = \frac{0 \cdot v_x}{3} \Rightarrow \frac{v_x}{v_{in}} = -3$$

c) Non-inverting op-amp:
$$\frac{v_{out} - v_x}{15} = \frac{v_x - 0}{5} \Rightarrow \frac{v_{out}}{v_x} = 4$$

$$\left(\frac{v_{out}}{v_x} \right) \left(\frac{v_x}{v_{in}} \right) = \frac{v_{out}}{v_{in}} = -12$$


d) $v_{in} = 3$: 1st op-amp: $v_x = -9 \rightarrow \text{Saturates} \Rightarrow v_x = -5$
 2nd op-amp: $v_{out} = -20V$

e) $v_{in} = -4$: 1st op-amp: $v_x = 12 \rightarrow \text{Saturates} \Rightarrow v_x = +5$
 2nd op-amp: $v_{out} = +20V$

f) $v_{in} = 1$: 1st op-amp: $v_x = -3V$
 2nd op-amp: $v_{out} = -12V$

Pg. 3

Problem 2:

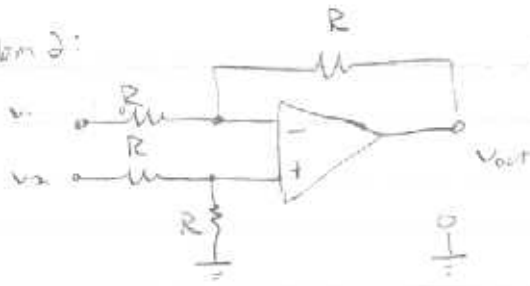

a) Find $v_{out} = f(v_{in1}, v_{in2})$
Weighting factors of v_1 & v_2 ?

Soln: $V_{in} = V_p = V_n$

$$a) \frac{v_2 - v_x}{R} = \frac{v_x}{R} \Rightarrow v_2 = R \left[\frac{2v_x}{R} \right] \Rightarrow v_x = \frac{v_2}{2}$$

$$v_1 - \frac{v_2}{2} = \frac{v_2/2 - v_{out}}{R} \Rightarrow v_1 = \frac{v_2 - v_{out}}{R}$$



$v_{out} = v_2 - v_1$

b) Weighting Factors

$$\alpha = -1 \quad \beta = 1$$

$$v_{out} = \alpha v_1 + \beta v_2$$

Problem 3

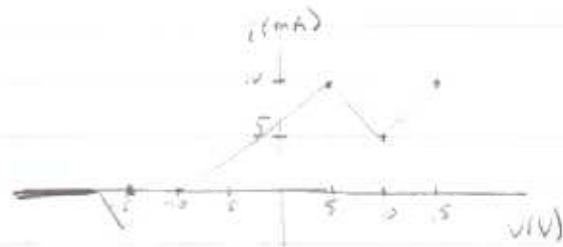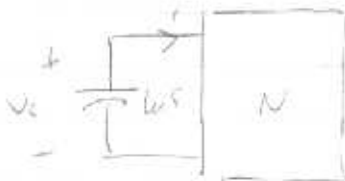


(i) Indicate Dynamic Range, Eg. PDS & Stability

(ii) $v_s(0) = 15V$ Find $v_L(t)$, $i_L(t)$ for $t \geq 0$

See Soln on Pg 3

Pg 4

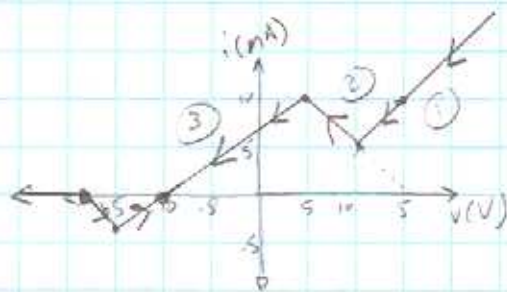

$$i = -C \frac{dv}{dt} \Rightarrow \frac{-i}{C} = \frac{dv}{dt} \quad \text{Eg: } \frac{dv}{dt} = 0 \Rightarrow i = 0 \quad 2 \text{ eq. pts.}$$

$$i > 0 \Rightarrow \frac{dv}{dt} < 0 \quad i < 0 \Rightarrow \frac{dv}{dt} > 0 \quad v = -10 \rightarrow \text{Stable} \\ v \leq -10 \rightarrow \text{Unstable}$$

Start ③ $v_c(0) = 15V$

Region 1: Need 4 pieces of info:

Kr ⑧:

$v_0 = 15V$	$v_{\infty} = 5V$	$R = 1000\Omega$	$\tau = .001s$
$i_0 = 10mA$	$i_{\infty} = 0mA$	$C = 1 \times 10^{-6}C$	$t_0 = 0$

$$v(t) = 5 + 10e^{-1000t} \quad (V)$$

$$i(t) = 10e^{-1000t} \quad (mA)$$

For $0 < t < t_1$

4th piece of info: Switching time $t_1 \rightarrow$ time to get to (10V, 5mA)

Use i because simpler $5 = 10e^{-1000t} \rightarrow t_1 = \ln 2 / 1000 = .69ms$

Region 2:

$v_0 = 10V$	$v_{\infty} = 15$	$R = -1000\Omega$	$\tau = -1 \times 10^{-3}$
$i_0 = 5mA$	$i_{\infty} = 0$	$C = 1 \times 10^{-6}C$	$t_1 = \ln 2 / 1000$

$$v(t) = 15 - 5 \exp[+1000(t - t_1)] \quad \text{for } t_1 < t < t_2$$

$$i(t) = 5 \exp[+1000(t - t_1)]$$

$$t_2 \text{ is } \textcircled{2} (15V, 10mA) \rightarrow t_2 = t_1 + \ln 2 / 1000 = \ln 4 / 1000 = 1.38ms$$

Region 3: To Stable Eg

$v_0 = 5V$	$v_{\infty} = -10$	$R = 1500\Omega$	$\tau = 0.0015s$
$i_0 = 10mA$	$i_{\infty} = 0$	$C = 1 \times 10^{-6}C$	$t_2 = \ln 4 / 1000$

$$v(t) = -10 + 15 \exp[-667(t - t_2)] \quad \text{for } t > t_2$$

$$i(t) = 10 \exp[-667(t - t_2)]$$


pg 5

Now to graph.
 We could just graph what we got, but here's an easy way to eyeball the plots.

Good if running out of time & don't want to write out equations.

For $i(t)$, use "i-Draw Approach"

For $v(t)$, use "Invert & Draw Approach"

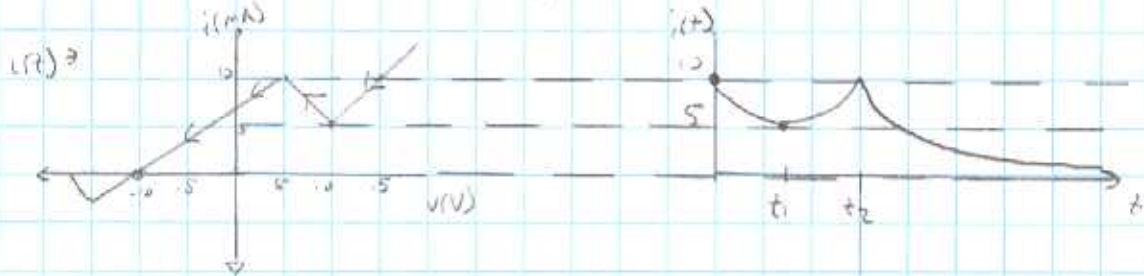


Extrapolate all essential values ($i = 5, 10$ mA)

Start at 10 \rightarrow decrease to 5 @ t_1

\rightarrow increase back to 10 @ t_2 \rightarrow decrease to 0 asymptotically



First: Invert $i-v$ graph, Then repeat the above for v

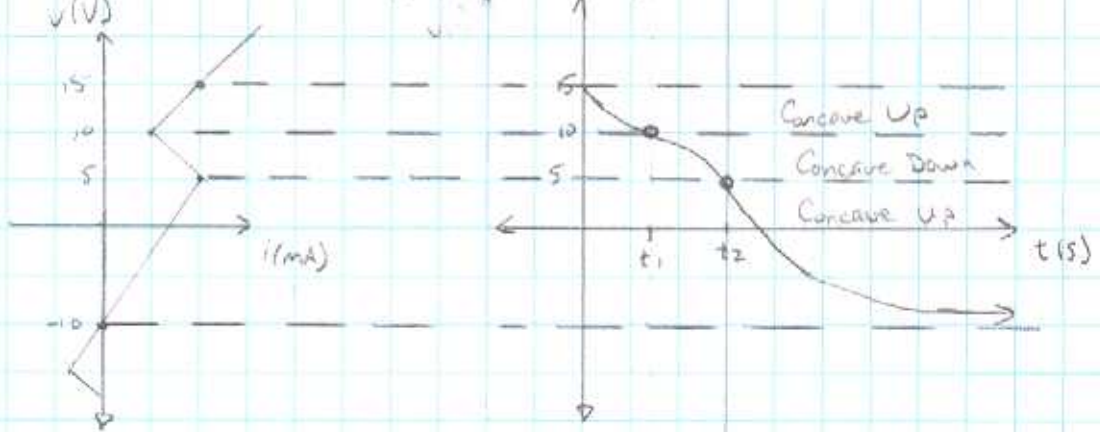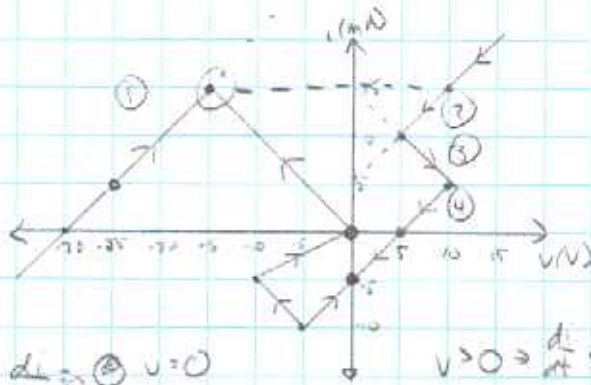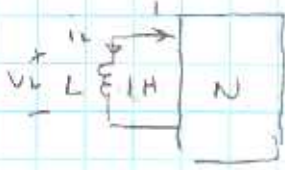

Pg 6

Problem 4

The "Justin is a Crazy Bastard" (JCB) Problem

Find $v(t)$ & $i(t)$
for $t \geq 0$ Start @ $v_L(0) = -25V$

$$-v = L \frac{di}{dt}$$

$$\text{Eg: } \frac{di}{dt} \circledast v = 0$$

$$v > 0 \Rightarrow \frac{di}{dt} < 0$$

$$v < 0 \Rightarrow \frac{di}{dt} > 0$$

Impossible Pt $\textcircled{2}$ $(-10V, 15mA) \Rightarrow$ jumps to $(10V, 15mA)$

$$\tau = L/R$$

4 Regions

$$\text{Region I: } v_0 = -25V \quad v_{oc} = 0 \quad R = 1000\Omega \quad \tau = 0.001s$$

$$i_0 = 5mA \quad i_{oc} = 30mA \quad L = 1H \quad t_0 = 0$$

$$v(t) = -25 \exp[-1000t] \quad \text{for } 0 \leq t \leq t_1$$

$$i(t) = 30 - 25 \exp[-1000t]$$

$$t_1 \textcircled{2} v = -5 \Rightarrow t_1 = \ln 6 / 1000$$

$$\text{Region II: } v_0 = 10 \quad v_{oc} = 0 \quad R = 1000\Omega \quad \tau = 0.001s$$

$$i_0 = 5 \quad i_{oc} = 5 \quad L = 1H \quad t_1 = \ln 6 / 1000$$

$$v(t) = 10 \exp[-1000(t-t_1)] \quad \text{for } t_1 \leq t \leq t_2$$

$$i(t) = 5 + 0 \exp[-1000(t-t_1)]$$

$$t_2 \textcircled{2} v = 5 \quad t_2 = t_1 + \ln 2 / 1000 = \ln 12 / 1000$$

$$\text{Region III: } v_0 = 5 \quad v_{oc} = 0 \quad R = -1000\Omega \quad \tau = -0.001s$$

$$i_0 = 10 \quad i_{oc} = 15 \quad L = 1H \quad t_2 = \ln 12 / 1000$$

$$v(t) = 5 \exp[1000(t-t_2)] \quad \text{for } t_2 \leq t \leq t_3$$

$$i(t) = 15 - 5 \exp[1000(t-t_2)]$$

$$t_3 \textcircled{2} v = 10 \Rightarrow t_3 = t_2 + \ln 2 / 1000 = \ln 24 / 1000$$

$$\text{Region IV: } v_0 = 10 \quad v_{oc} = 0 \quad R = 1000\Omega \quad \tau = 0.001s$$



$$i_0 = 5 \quad i_{oc} = -5 \quad L = 1H \quad t_3 = \ln 24 / 1000$$

$$v(t) = 10 \exp[-1000(t-t_3)] \quad \text{for } t \geq t_3$$

$$i(t) = -5 + 10 \exp[-1000(t-t_3)]$$


Q97

Plots of $v(t)$ & $i(t)$

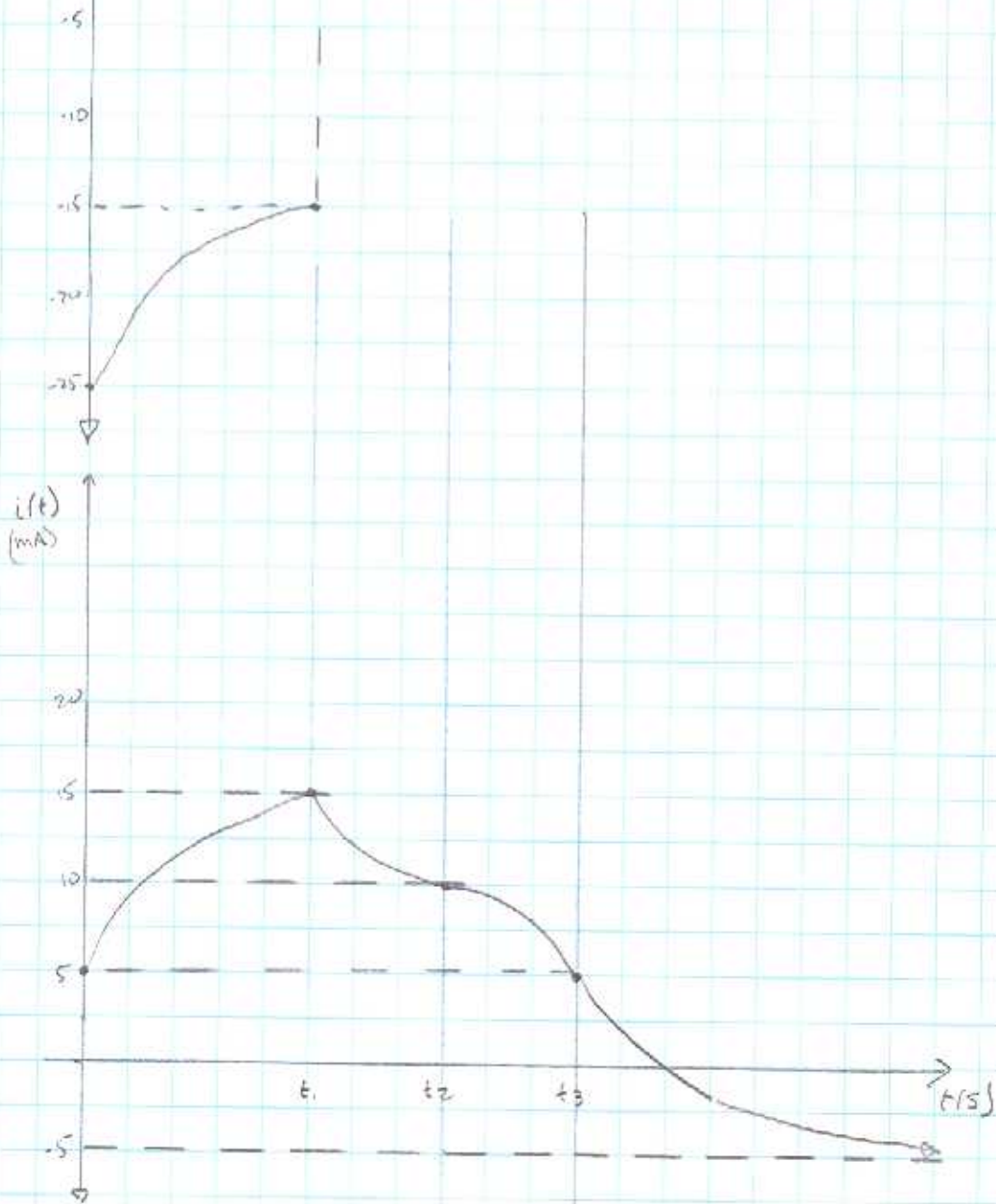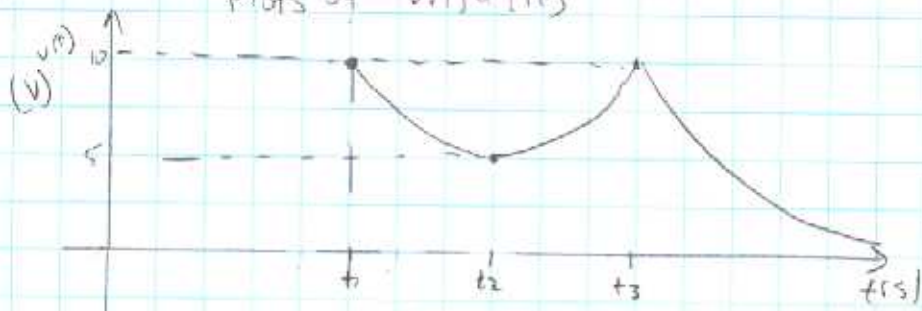

Problem 5: Flip-Flops


Fig 1

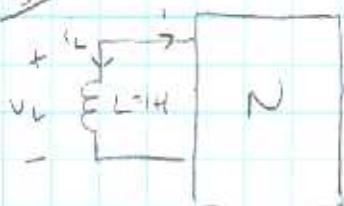

$$\frac{v}{L} = \frac{di}{dt} \quad \frac{di}{dt} \text{ @ } v=0$$

$$v > 0 \Rightarrow \frac{di}{dt} < 0$$

$$v < 0 \Rightarrow \frac{di}{dt} > 0$$

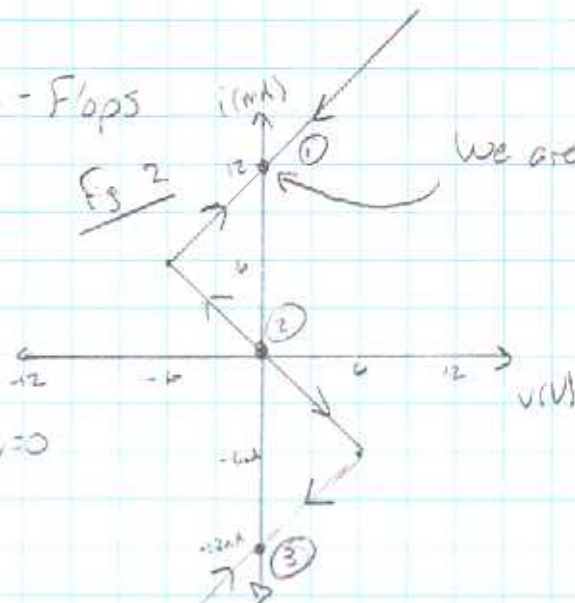


2 Stable Eq & 1 unstable

2 Possible Questions:

- a) Min voltage you must add in Fig 3 to flip from 1 eg pt to another $1 \rightarrow 3$
- b) Time to flip from one to another. $1 \rightarrow 3$

Fig 3

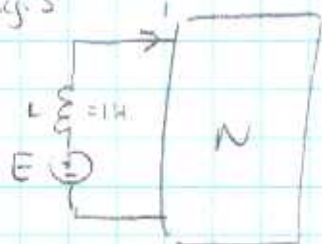


a) IF symmetric: always difference between $V(\text{unstable eq})$ & $V(\text{cusp})$
 $\Rightarrow E = 0 - (-6) = \boxed{+6V}$

b) IF $E = 12V$, what is min time for E to be "on" to get from 1 to 3?

Hint: Use dynamic route.

Trick: IF we can get to pt 2 & turn off E , dynamic route will take us to 3

Pg 9

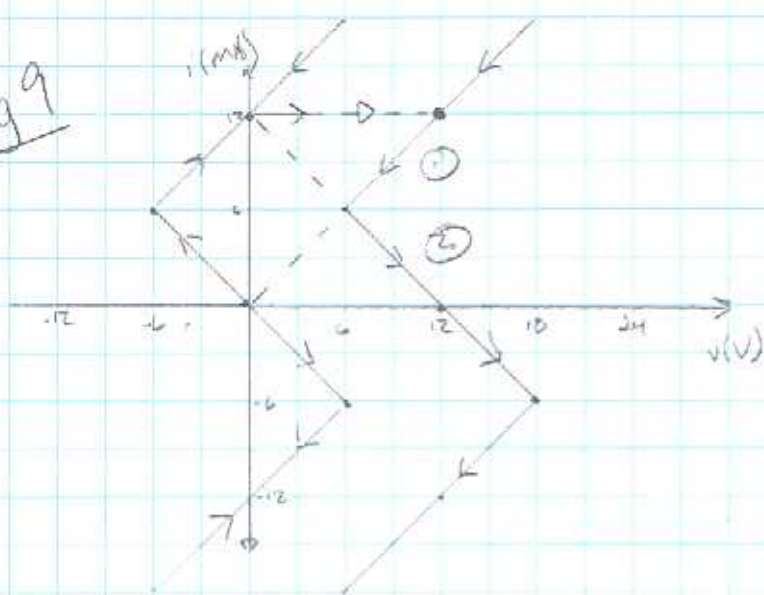

- ① Shift from $(0, 12\text{mA}) \rightarrow (12\text{V}, 12\text{mA})$
- ② Draw new dynamic rate
- ③ Find t_1 & t_2 $t_2 = t_{\min}$

Region ①

$$v_0 = 12 \quad v_{\infty} = 0 \quad R = 1000 \quad \tau = .001$$

$$i_0 = 12 \quad i_{\infty} = 0 \quad L = 1\text{H} \quad t_0 = 0$$

Only need $\rightarrow v(t) = 12 \exp(-1000t)$
 $\rightarrow i(t) = 12 \exp(-1000t)$

$$t_1 \text{ ① } v = 6 \quad \rightarrow t_1 = \ln 2 / 1000$$

Region ②

$$v_0 = 6 \quad v_{\infty} = 0 \quad R = -1000 \quad \tau = -.001$$

$$i_0 = 6 \quad i_{\infty} = 12 \quad L = 1 \quad t_1 = \ln 2 / 1000$$

Only need $\rightarrow v(t) = 6 \exp[1000(t - t_1)]$
 $\rightarrow i(t) = 12 - 6 \exp[1000(t - t_1)]$

$$t_2 \text{ ② } v = 12 \quad t_2 = \ln 2 / 1000 + t_1 \quad t_2 = \ln 4 / 1000$$

$$t_{\min} = t_2 = \ln 4 / 1000$$

THAT'S ALL THERE IS TO FLIP-FLOPS