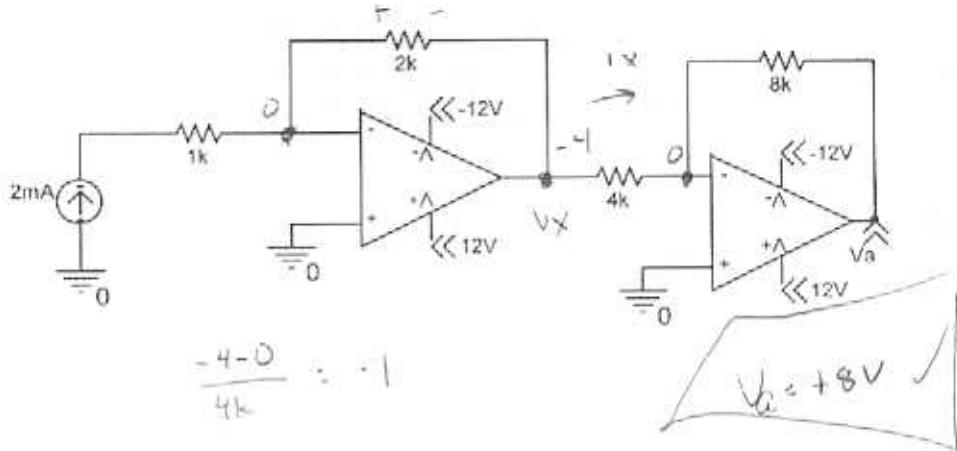


Problem 1 (25 points)

In the circuit below, find V_a . DO NOT IGNORE THE EFFECTS OF THE RAIL VOLTAGES.



$$V_{P1} = V_{N1} = 0$$

$$\frac{-4 - 0}{4k} = -1$$

$$V_x = 0 - (2k)(2mA) = -4V$$

$$I_X = \frac{-4 - 0}{4k} = -1mA$$


$$V_{P2} = V_{N2} = 0$$

$$V_a = 0 - (8k)(-1mA) = +8V$$

$V_a = 8V$

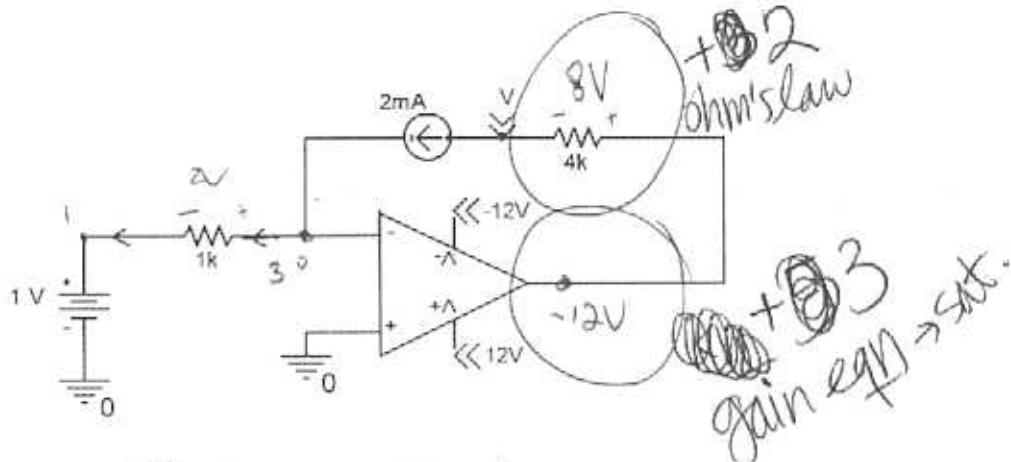Problem 4 (12 points)

In the circuit below, find V. DO NOT IGNORE THE EFFECTS OF THE RAIL VOLTAGES!



~~Guess~~ $v_n = v_p = 0$ Wrong

$v_n = 3$

$A(v_p - v_n) = \frac{v_n + 8}{A(0 - 3)} \rightarrow -\infty \rightarrow v_{ov+} = 12V$

~~-12~~ $V + 8V = -12$

$V = -20$

+3 KVL

