

April 18th 2015
 BRAT M.

EE100 Stereo Amplifier Left side schematic

NOTE: RIGHT SIDE IS EXACTLY THE SAME


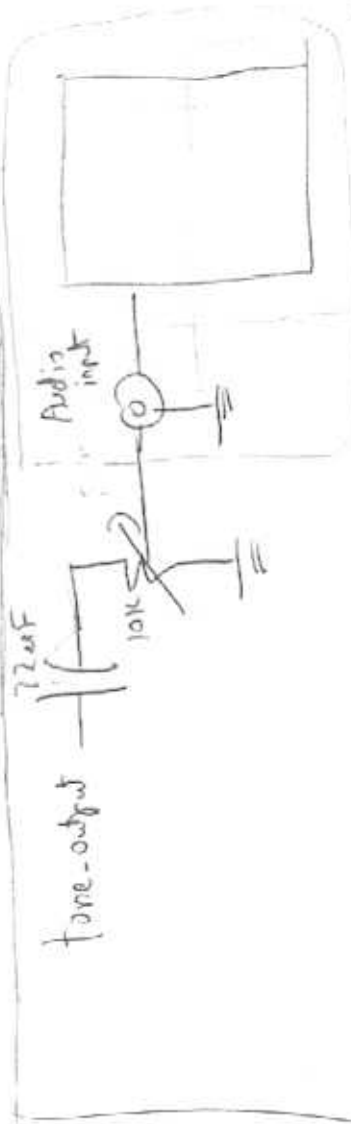
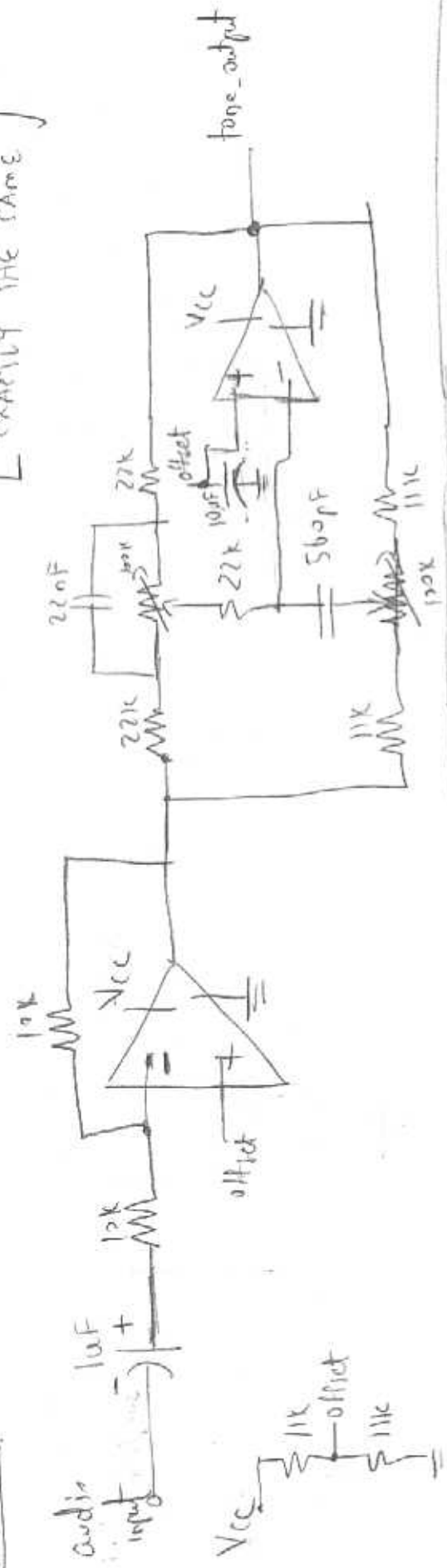


Figure 8 on p.204 of your reader.

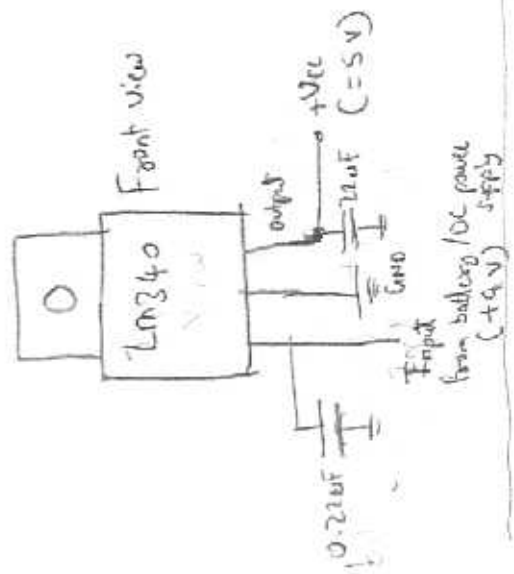

Notes:

- (1) I changed the voltage follower into an inverting amplifier. This is for better performance. Thanks Tho!
- (2) We couldn't get the LM2940CT-5.0, so we are giving you the LM340. Google search for datasheet, pinout is shown above.