
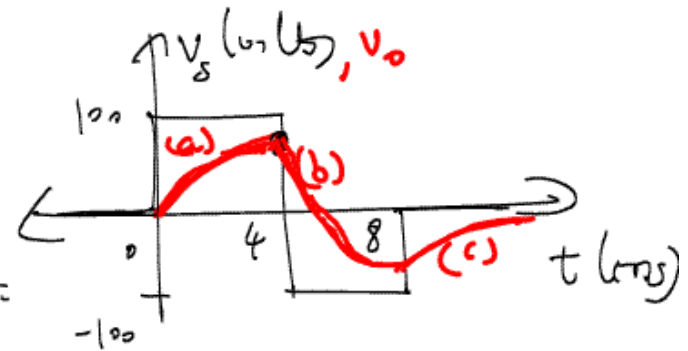


# Find, Final Office Hours

Question - p 7.82

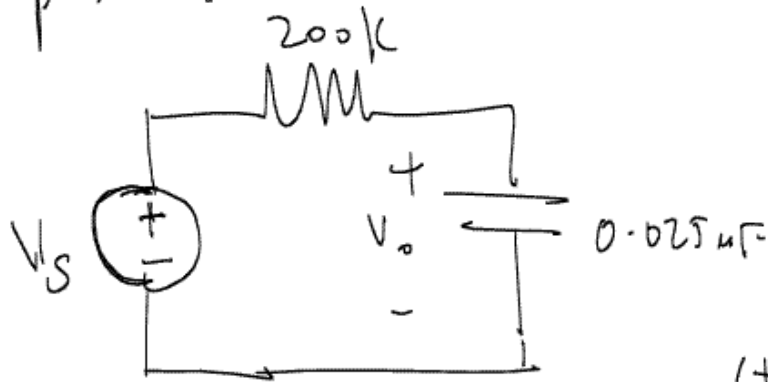

$$V_o(t) = V_{of} + (V_{oi} - V_{of}) e^{-\frac{(t-t_{oi})}{\tau}}$$

$$\tau = RC = 200\text{k}\Omega \cdot \frac{25}{1000}\mu\text{F}$$

$$= 5\text{ms}$$

Region (a):  $V_{oi} = 0$

$$V_{of} = \lim_{t \rightarrow \infty} V_o(t) = 100\text{V}$$

$$V_o(t_{\text{switching}} = 4\text{ms}) = ?$$



$$\Rightarrow V_o(t_{\text{switch}} = 4\text{ms}) = 100 + (0 - 100) e^{-\frac{(4\text{ms} - 0)}{5\text{ms}}}$$

$$\downarrow$$



$$V_o(t_{\text{switch}}) = 55\text{V}$$

Load lines:

"Load line equation"

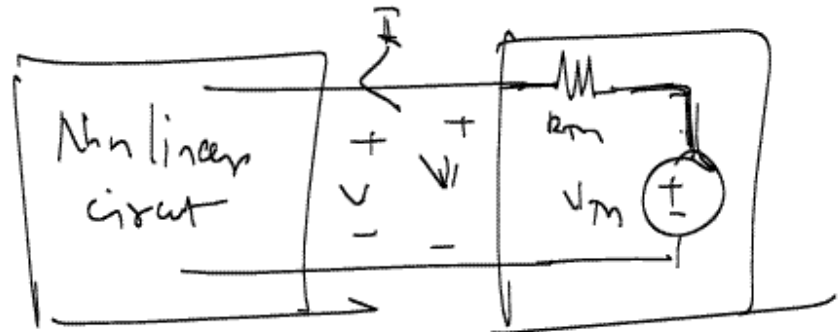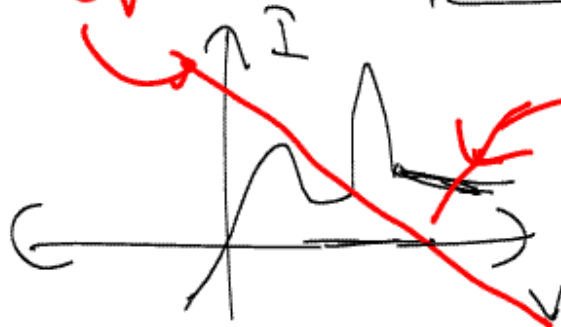

$$I = \frac{V - V_M}{R_M}$$

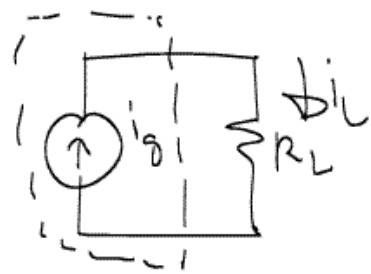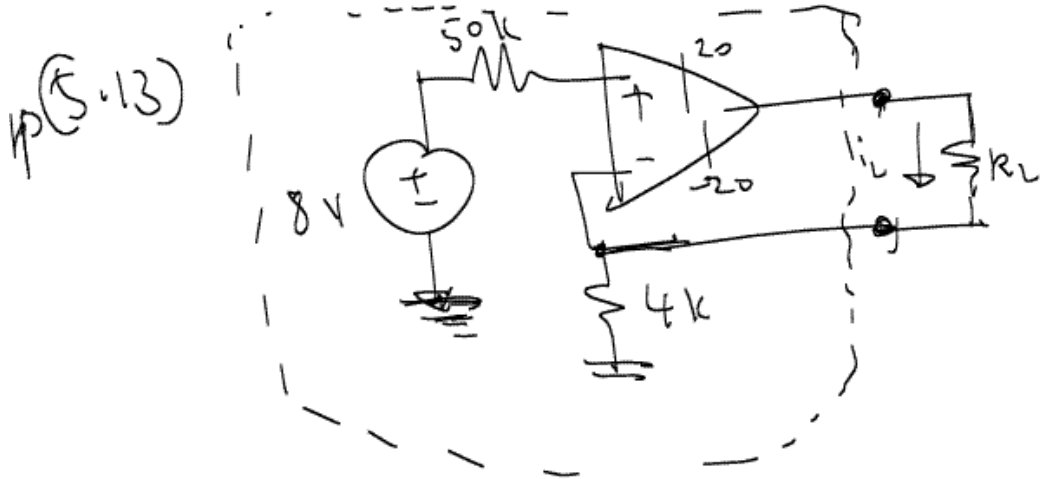


any value you want

point of the problem: ideally,  $i_s$  can be  $\infty$  but in reality, the op-amp saturates.

part (c): if  $R_L = 16k$ ,  
 $i_L = ?$

Assume:  $V_p = V_n$

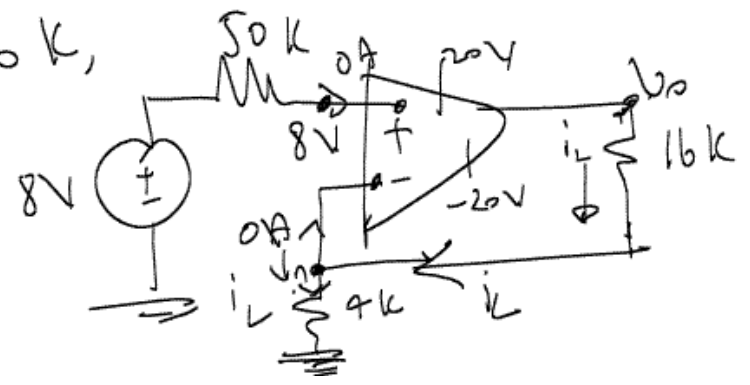

$$\therefore V_n = 8V \Rightarrow i_L = \frac{8}{4k} = 2 \text{ mA}$$

$$\text{But, } V_o = V_n + (i_L)(16k) \leftarrow \left( i_L = \frac{V_o - V_n}{16k} \right)$$

$$\Rightarrow 40V > 20V$$

$\Rightarrow$  op-amp saturates  $\Rightarrow V_n \neq 8V \Rightarrow i_L \neq 2 \text{ mA}$

Note: Find

$$V_n: \frac{20 - V_n}{10k} = \frac{V_n}{4k}$$

$$\Rightarrow 4V_n = 20 - V_n$$

$$\Rightarrow \boxed{V_n = 4V}$$

Notice  $V_o = A(V_p - V_n) = 10^6(8 - 4) \rightarrow 4 \times 10^6 > 20$   
 $\Rightarrow V_o = 20$


$\therefore$  op-amp is not acting as a constant current source, because

$V_n = 4V$ ,  $i_L$  is only 1 mA.

Evil Find problem:

Find  $i_x$

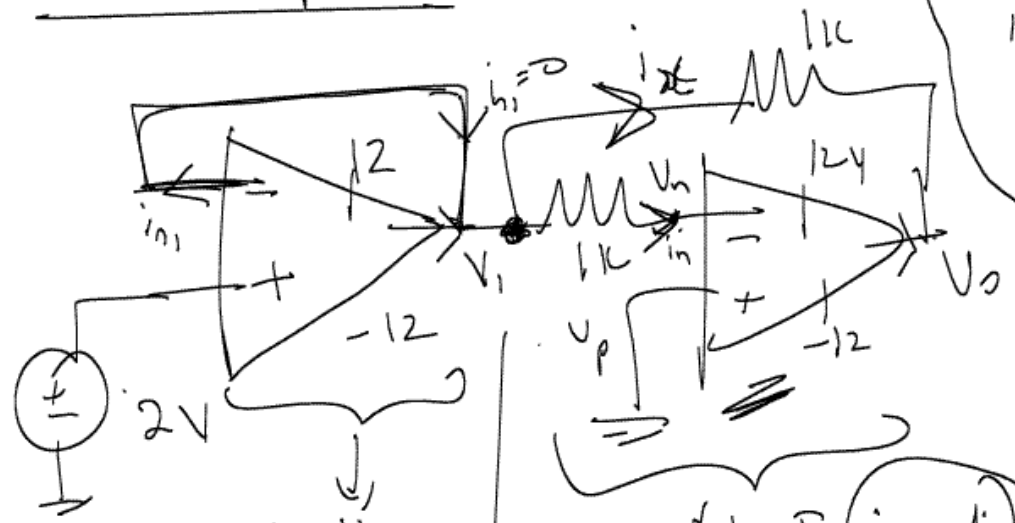NOT LIKE THIS,  
it is conceptual,  
NOT tricky



voltage follower

$V_1 = 2V$ ,




$V_0 = ?$


NOT inverting amplifiers

Assume  $V_n = V_p$

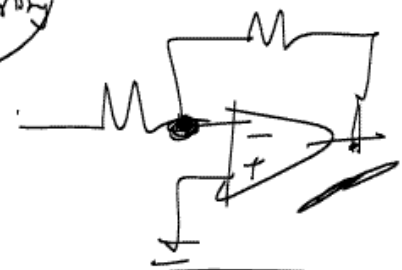$\Rightarrow V_n = 0 \Rightarrow i_n \neq 0, i_n = \frac{V_1 - V_n}{1k} = \frac{2 - 0}{1k} = 2mA$



Note:  $i_o$  usually  $\neq 0$

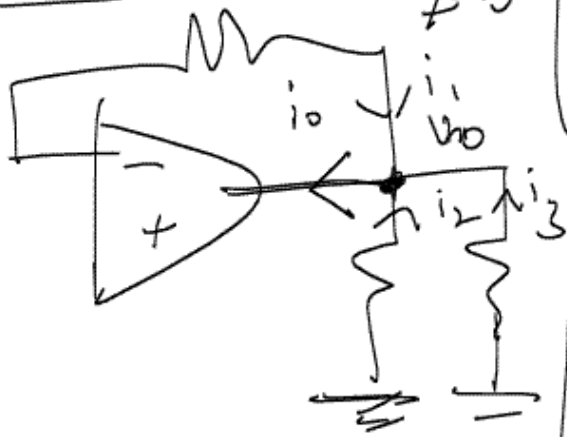

Only way to find  
 $i_o$ : KCL @  $v_o$   
 $i_o = i_1 + i_2 + i_3$

But,  $i_n = i_p = 0 \leftarrow$  ALWAYS TRUE!

$\therefore$  if  $i_n = 0 \Rightarrow v_n = v_p = 2V$

Ok, what's  $v_o$ ?

You can't use,  $i_d = \frac{v_n - v_o}{R_c}$


Since you don't know  $i_d$ .

Therefore,  $v_o = A(v_p - v_n)$

$$= 10^6(0 - 2) < 0$$


$$\Rightarrow \boxed{v_o = -12}$$

Diodes:

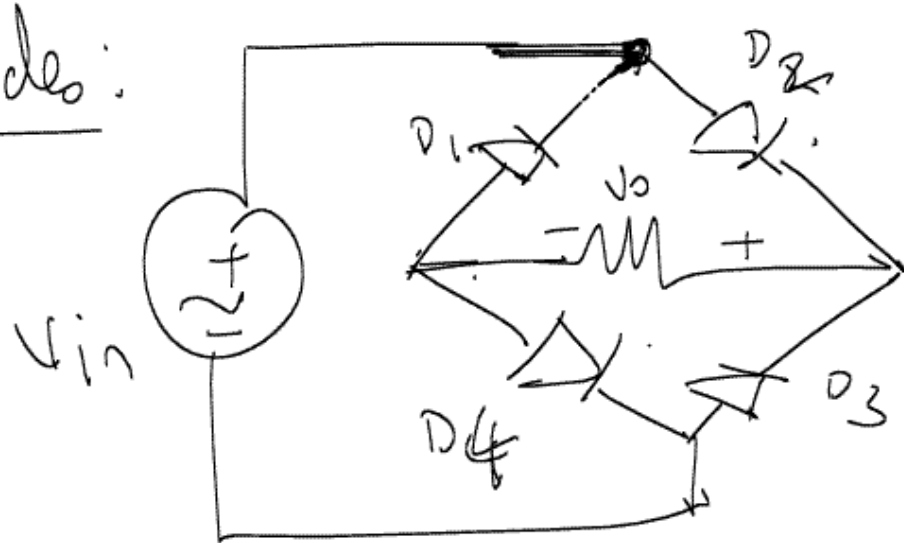


Bridge  
rectifier  
(refer to  
Justin notes,  
eg 5)

$v_{in}(t) = \sin(\omega t)$


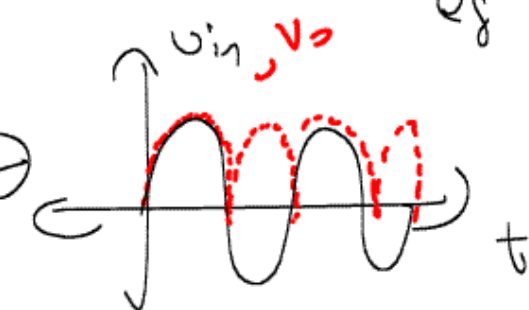


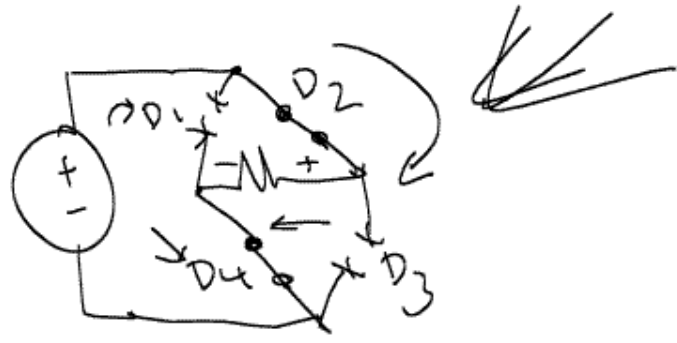if  $v_{in} > 0$ ,  $D_2$  &  $D_4$  are on!





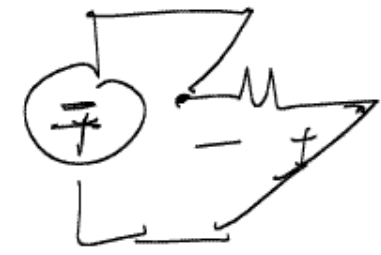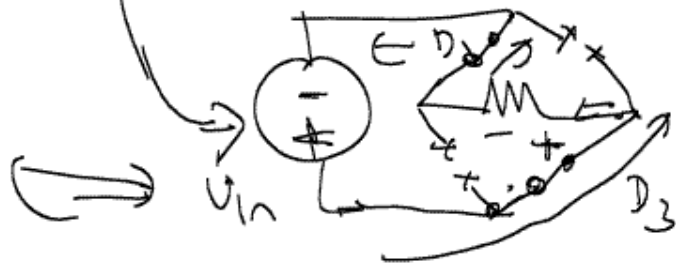If  $V_{in} < 0$ ,  $D_1$  &  $D_3$  are on








@  $\underline{V}_A$ :  $i_1 + I_{AA} \cos(\omega t + 37^\circ) = I_{BB} \cos(\omega t) + i_2$

@  $\underline{V}_B$ :  $I_{BB} \cos(\omega t) + i_2 = i_3$

(3) Write unknown currents in terms of unknown node voltages:

$$i_1 = C \frac{dv_C}{dt} = C \frac{d}{dt} (V_{AA} \cos(\omega t) - V_A)$$

$$i_2 = \frac{1}{L} \int (V_A - V_B)$$

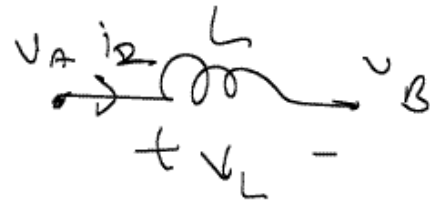

$$V_L = L \frac{di_2}{dt}$$

not necessary





$$\begin{aligned} \underline{V}_A: \quad C \frac{d}{dt} (V_{AA} \cos(\omega t) - V_A) + I_{AA} \cos(\omega t + 37^\circ) \\ = I_{BB} \cos(\omega t) + \frac{1}{L} \int (V_A - V_B) \end{aligned}$$

$$i_2 \text{ (D)} = \frac{1}{L} \int V_L dt$$

limits unnecessary

$$\underline{v_B}: \quad I_{B3} \cos(\omega t) + \frac{1}{L} \int (v_A - v_B) = \frac{v_B + v_{B3} \cos(\omega t + 58^\circ)}{R_2}$$

Review problem 14:

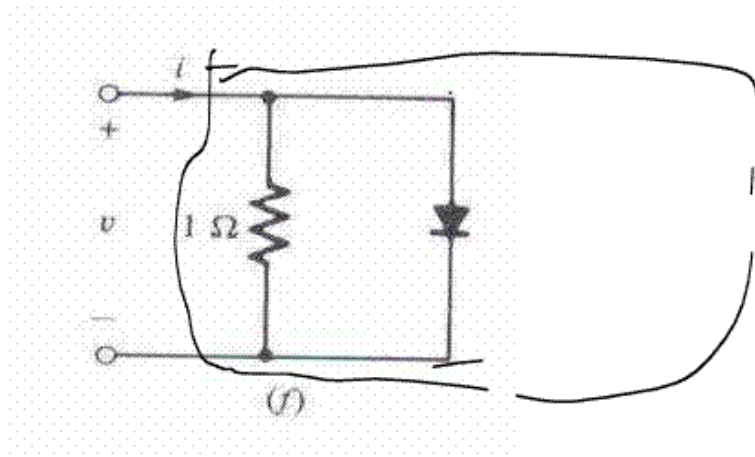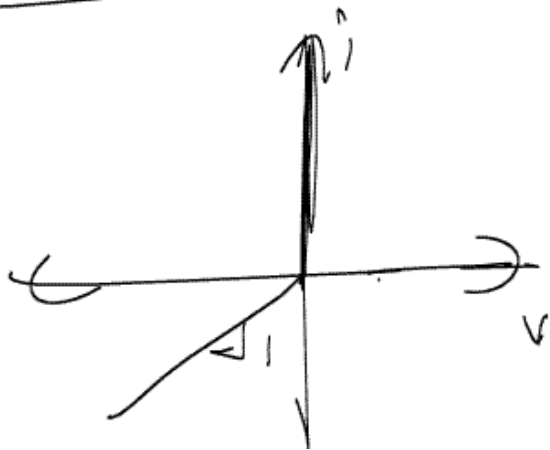

$e^{j\omega t}$

Q:.) What if you have a dependent source?






I h e v e n i s:

$$i_x = \frac{20i_x}{20} \Rightarrow i_x = i_x$$



$$v = 20v_x$$

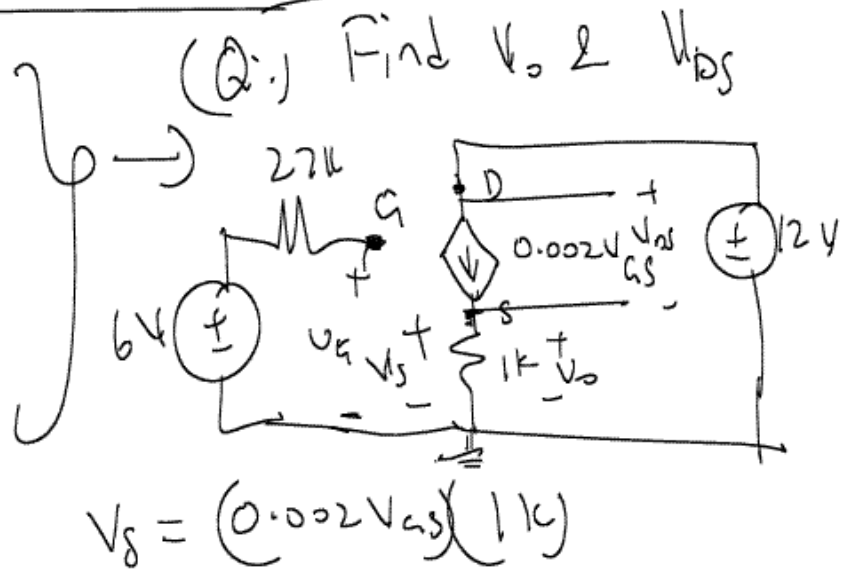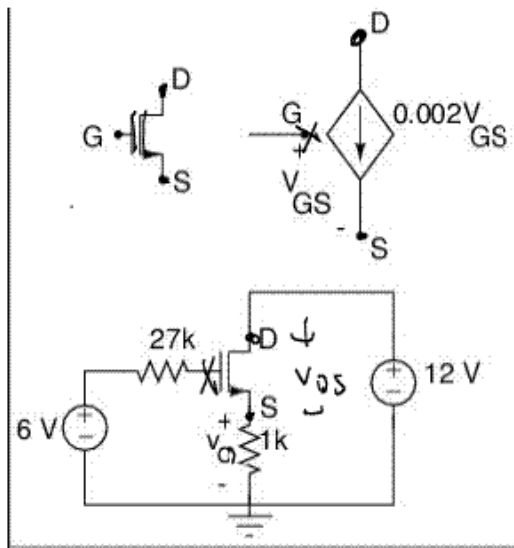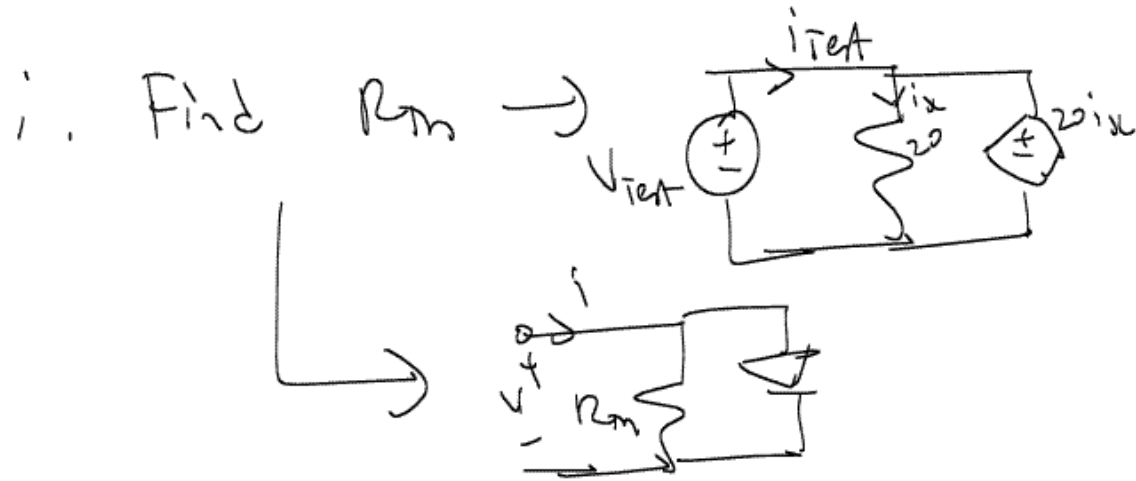begs the question:  
How do we set  
an i-v graph for  
a dependent source?



$$V_S = [0.002 (V_A - V_S)] (11\%)$$

$$\Rightarrow V_S = [0.002 (6 - V_S)] (11\%)$$

$$\Rightarrow V_S = ?, \quad V_{0S} \Rightarrow \text{use } \frac{1}{100} \quad (V_S = V_0)$$

---