

UNIVERSITY OF CALIFORNIA, BERKELEY
Department of Electrical Engineering and Computer Sciences

EE 100
Intro. To Electronics Engineering

Summer 2004
Bharath Muthuswamy

FINAL EXAM
August 2004
Time Allotted: 3 hours

NAME: Solomon, _____
(print) Last First

STUDENT ID#: _____

I WILL NOT CHEAT ON THIS EXAM. Signature: _____

Note(s):

1. You will receive [3 pts] for filling out the information above.
2. This is a **CLOSED BOOK** exam. However, you may use two 8.5 x 11" of notes (both sides) and a calculator.
3. **SHOW YOUR WORK** on this exam. **MAKE YOUR METHODS CLEAR TO THE GRADER** so you can receive partial credit.
4. **WRITE ANSWERS CLEARLY IN THE SPACES** (lines or boxes) **PROVIDED.**
5. Remember to specify units on answers whenever appropriate.

SCORE: This page: _____ / 3

1: _____ / 7 → Arhwin

2: _____ / 20] Best

3: _____ / 20]



4: _____ / 10 → Jim

5: _____ / 25] Justin

6: _____ / 15]

TOTAL: _____ / 100

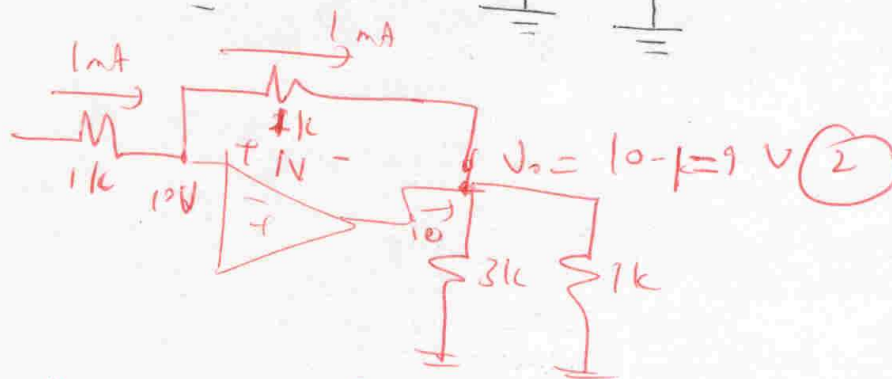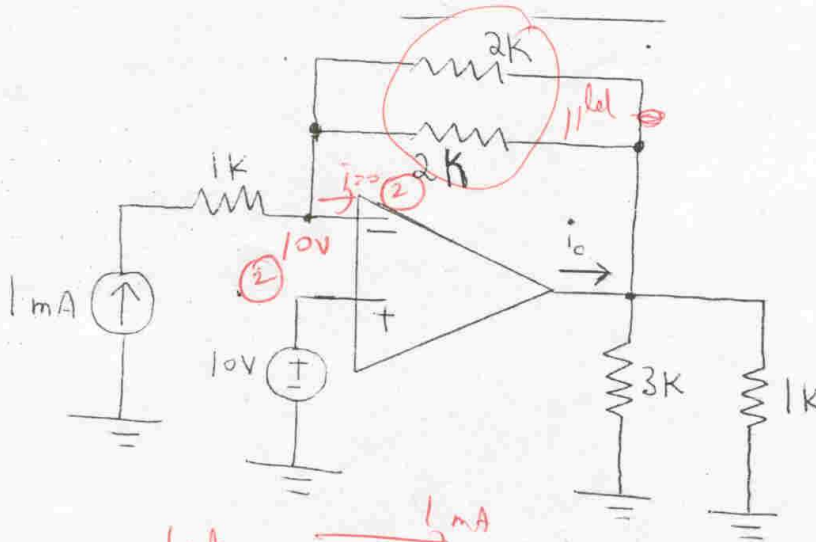1. (7 points) In the circuit below, assume the op-amp is ideal (ignore the effects of rail voltages). Find i_o .




$$i_o \neq 1\text{mA} = \frac{V_o}{3\text{k}} + \frac{V_o}{1\text{k}} \quad (1)$$

$$\text{Total} = (2) + (2) + (2) = 7$$

$$\Rightarrow i_o = 12 - 1 \Rightarrow i_o = 11\text{mA}$$

$$i_o = \underline{11\text{mA}}$$

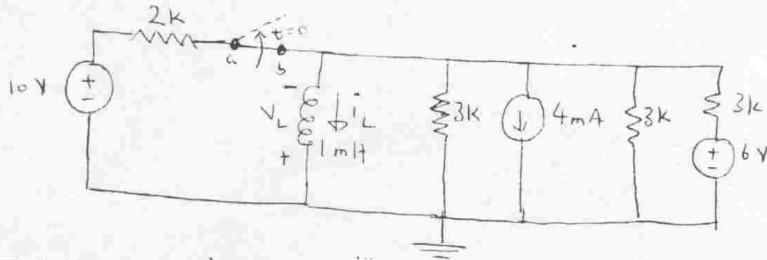
2. (20 points) In the circuit below, the switch has been closed for a long time before opening at $t = 0$.



- Find: (a) $i_L(t=0^-)$ (5 points)
 (b) $i_L(t=0^+)$ (5 points)
 (c) $v_L(t=0^+)$ (5 points)
 (d) τ (5 points)

(b) $i_L(t=0^+) = i_L(t=0^-)$
 5 point

$\Rightarrow i_L(t=0^+) = 3 \text{ mA}$

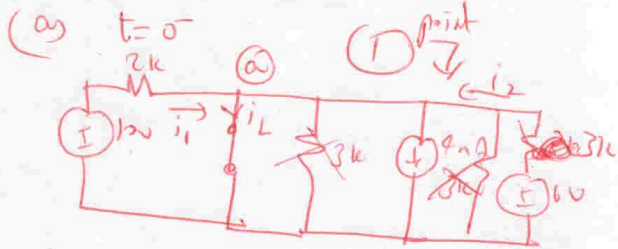

$i_1 = \frac{10 \text{ V}}{2 \text{ k}\Omega} = 5 \text{ mA}$

$i_2 = \frac{6 \text{ V}}{3 \text{ k}\Omega} = 2 \text{ mA}$

(c) $t=0^+$




2 points

$\therefore v_L = (5 \text{ mA})(1 \text{ k}\Omega)$

$v_L(t=0^+) = 5 \text{ V}$

1 point

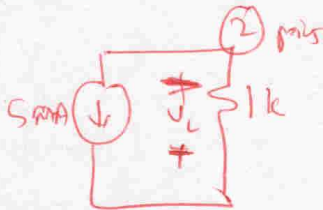

Resistors shorted out \Rightarrow 1 point
 Final answer: KCL @ node a: $i_1 + i_2 = i_L + 4$
 $\Rightarrow i_L = 3 \text{ mA}$

$i_L(t=0^-) = 3 \text{ mA}$

$i_L(t=0^+) = 3 \text{ mA}$

$v_L(t=0^+) = 5 \text{ V}$

$\tau = 1 \mu\text{s}$



(d) $\tau = \frac{L}{R} = \frac{1 \text{ mH}}{1 \text{ k}\Omega} \Rightarrow 1 \mu\text{s}$

2 points

2 points

1 point

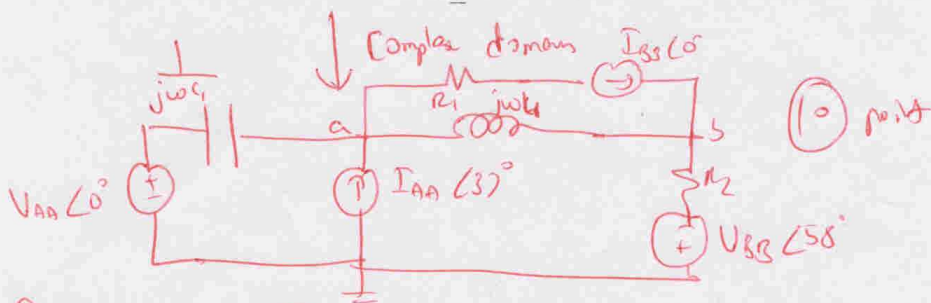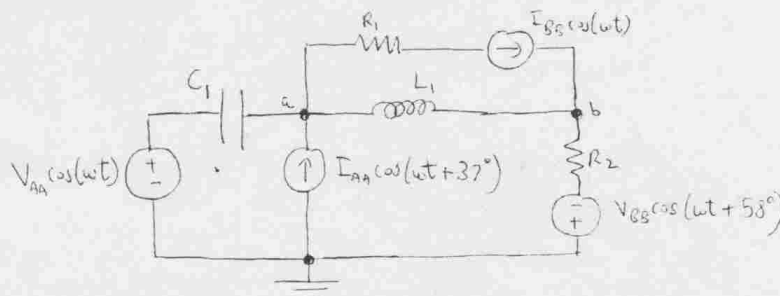3. (20 points) In the circuit below, use the **NODE VOLTAGE** method to write 2 equations (**IN THE COMPLEX DOMAIN**) sufficient to solve for V_a and V_b (the phasor voltages at nodes a and b respectively). Your equations will obviously be in terms of the impedances and the independent AC source values. To receive credit, you must write your answer in the box below. **DO NOT SOLVE OR SIMPLIFY THE EQUATIONS!**



@ a:
$$\frac{V_{AA} \angle 0^\circ - \bar{V}_a}{\frac{1}{j\omega C_1}} + I_{AA} \angle 37^\circ = I_{BB} \angle 0^\circ + \frac{\bar{V}_a - \bar{V}_b}{j\omega L_1}$$
 (5) point

Write your equations here:



$$\frac{(V_{AA} \angle 0^\circ - \bar{V}_a)}{\frac{1}{j\omega C_1}} + I_{AA} \angle 37^\circ = I_{BB} \angle 0^\circ + \frac{\bar{V}_a - \bar{V}_b}{j\omega L_1}$$

$$I_{BB} \angle 0^\circ + \frac{\bar{V}_a - \bar{V}_b}{j\omega L_1} = \frac{\bar{V}_b + V_{BB} \angle 58^\circ}{R_2}$$

@ b:
$$I_{BB} \angle 0^\circ + \frac{\bar{V}_a - \bar{V}_b}{j\omega L_1} = \frac{\bar{V}_b + V_{BB} \angle 58^\circ}{R_2}$$
 (5) points

ok to mix & match!

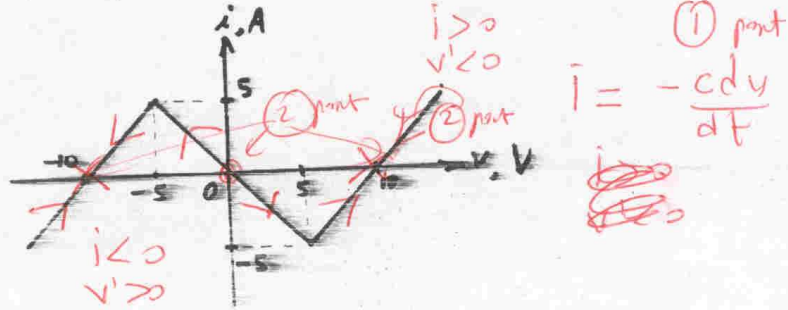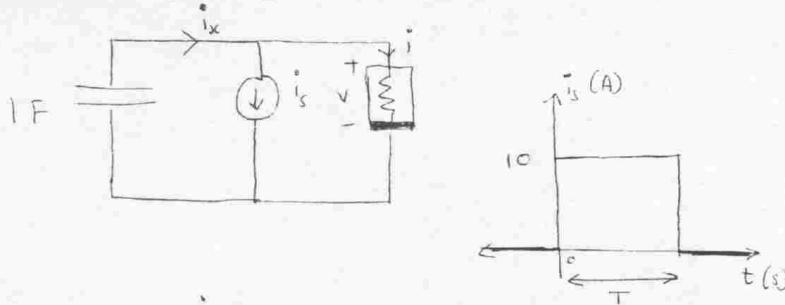4. (10 points) The circuit below is to be used as a flip-flop. The i-v characteristic of the nonlinear resistor is given along with a current square pulse as input.



- (a) Determine the equilibrium points, classify them as stable or unstable and determine the dynamic route. (5 points) *(assume $i_s = 0$) ← correct!*
- (b) If the amplitude of the current pulse is 10 A as shown above, calculate the minimum T required to move from the right equilibrium point to the left equilibrium point. Use $\ln(2) = 0.69$. (5 points)

Handwritten solution:

$T = t_1 + t_2 = 2 \ln(2) = 1.385$ (2) point


$i_x = i_s + i$ (3) point

Stable equilibrium point(s): (10, 0); (-10, 0)


Unstable equilibrium point(s): (0, 0)

T = 1.385

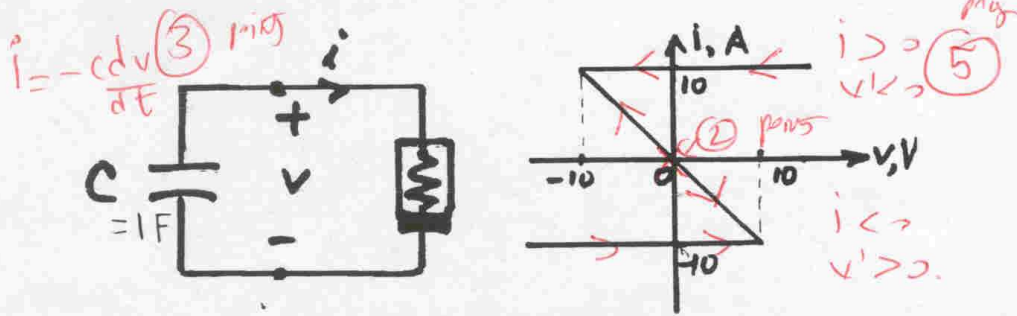5. (25 points) Consider the oscillator circuit and the i-v characteristic of the nonlinear resistor shown below. $C = 1F$.



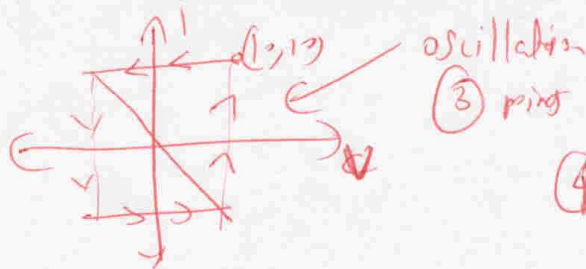- (a) Find the equilibrium points, classify them as stable or unstable and determine the dynamic route. (10 points)
- (b) Assuming $v(0) = 10$ V and $i(0) = 10$ A, find the period of oscillation. Plot $i(t)$ and $v(t)$ for two periods and indicate the maximum and minimum values of current and voltage in the graphs. (15 points)



④ points:

$$i = -C \frac{dv}{dt}$$

$$\Rightarrow 10 = -1F \cdot \frac{10 - 0}{t_1 - 0}$$


$$\Rightarrow t_1 = 2 \text{ sec} = t_L$$

$$\therefore T = 4 \text{ sec}$$

Stable equilibrium point(s): None


Unstable equilibrium point(s): (0, 0)

Period of Oscillation = 4 sec

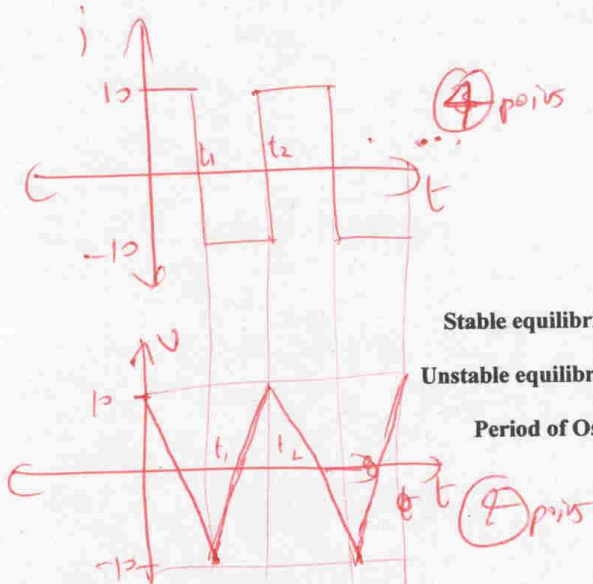

6. (15 points)

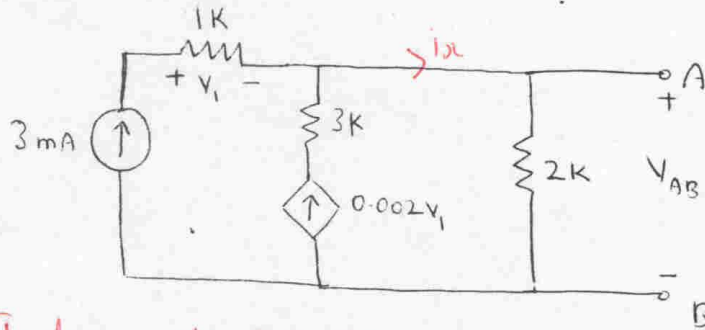
(a) Find the Thevenin equivalent of the following circuit at terminals AB (3 points):



Justin: points distoo??


$$\begin{aligned}
 V_{oc} &= i_x \cdot 2k \\
 &= (0.002v_1 + 3mA) 2k \\
 &= [0.002 \cdot (3mA)(1k) + 3mA] 2k = 18V
 \end{aligned}$$
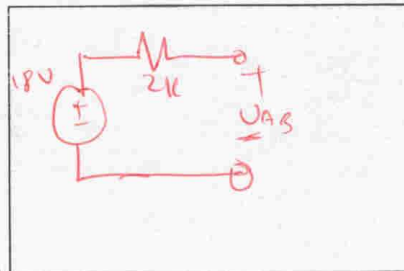
$$\begin{aligned}
 R_{th} &= \frac{V_{oc}}{I_{sc}} = \frac{V_{oc}}{i_x} \\
 &= \frac{18V}{9mA} \\
 &= 2k
 \end{aligned}$$




Draw Thevenin eq. in the box:

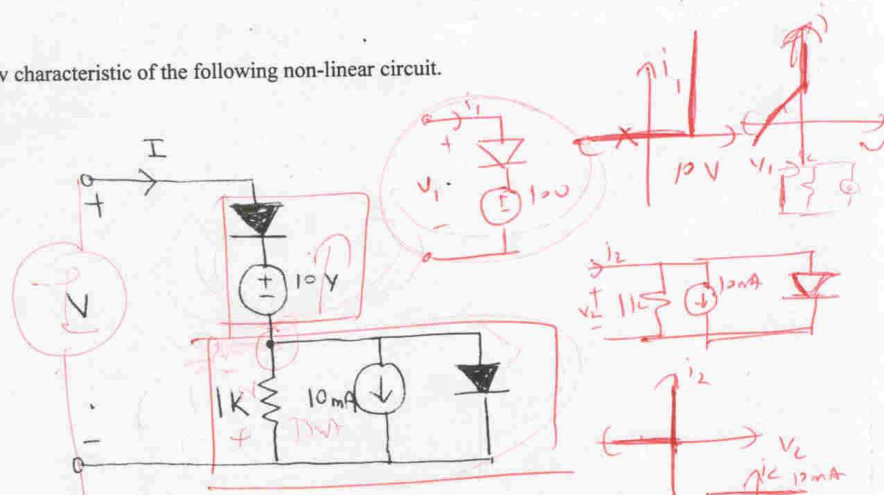
(b) Plot the i-v characteristic of the following non-linear circuit.



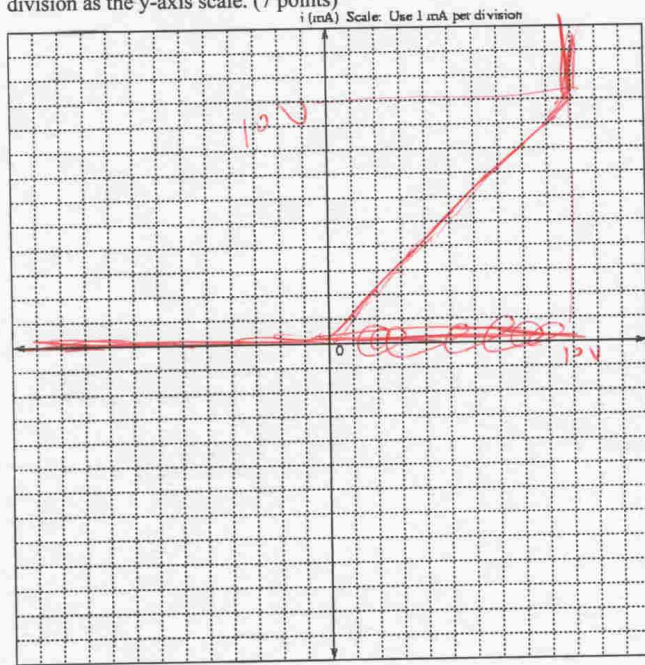
Use the grid shown below. Use 1 V per division as the x-axis scale and 1 mA per division as the y-axis scale. (7 points)



V (volts)
Scale:
Use: 1 V per division

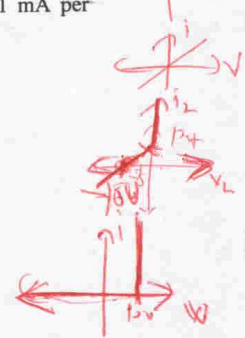

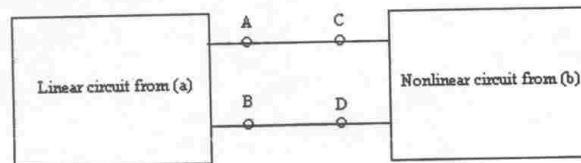(c) Suppose we connect the circuits in (a) and (b) such that node A is connected to node C and node B is connected to node D, as shown below. Using the graph from (b) and load line data from (a) solve for the operating point of the circuit. (3 points)



Operating Point = 6V, 6mA

(d) Is power being absorbed or delivered by the non-linear portion of the circuit at the operating point? How much power? (2 points)

Power = 36mW absorbed