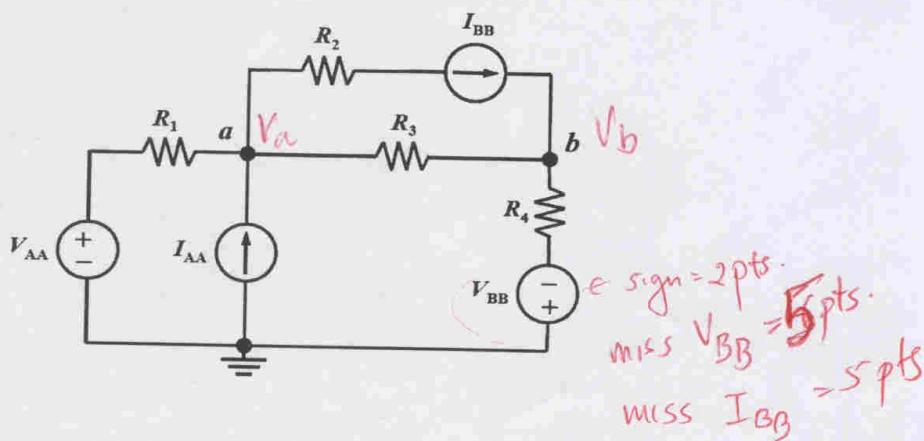


EE100 Summer 2004 Midterm Solutions

1. (25 points) In the circuit below, use the **NODE VOLTAGE** method to write 2 equations sufficient to solve for V_a and V_b (the voltages at nodes a and b respectively). Your equations will obviously be in terms of the resistances and the independent source values. To receive credit, you must write your answer in the box below. **DO NOT SOLVE THE EQUATIONS!**




$$\frac{V_a - V_{AA}}{R_1} + \frac{V_a - V_b}{R_3} + I_{BB} = I_{AA}.$$

$$\frac{V_b + V_{BB}}{R_4} + \frac{V_b - V_a}{R_3} = I_{BB}.$$

(1)

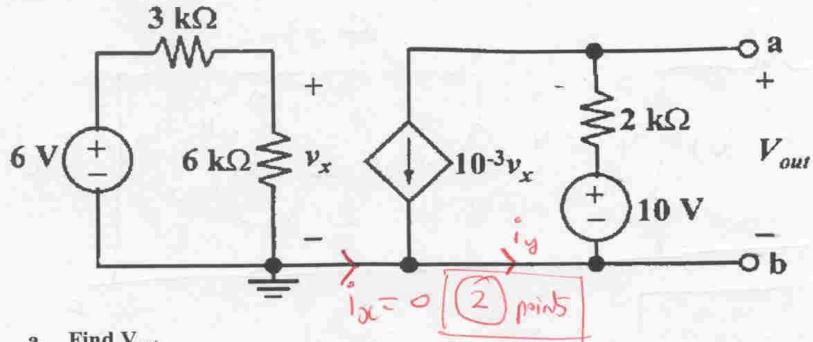2. (25 points). Consider the following circuit:



a. Find V_{out}

$$v_x = \left(\frac{6 \text{ k}}{6 \text{ k} + 3 \text{ k}} \right) 6 \text{ V} \quad (\text{voltage divider})$$

$$= 4 \text{ V} \quad (4 \text{ points})$$

(12) point

$$i_y = 10^{-3} v_x = 4 \cdot 10^{-3} = 4 \text{ mA} \quad (2 \text{ points})$$



$$V_{out} = 10 - (2 \text{ k})(4 \text{ mA}) = 2 \text{ V} \quad (4 \text{ points})$$

$$V_{out} = \underline{\hspace{2cm}} 2 \text{ V} \underline{\hspace{2cm}}$$

b. Draw the Thevenin equivalent with respect to terminals ab

$$\text{Now, } V_{out} = V_{oc} = 2 \text{ V}$$

R_{Th} : Kill all independent sources.

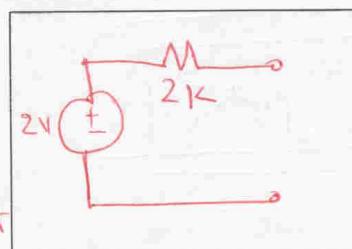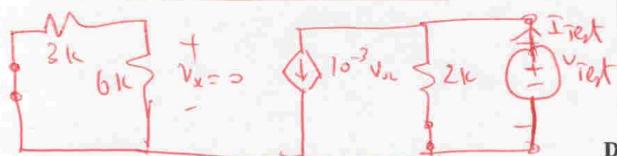


Draw Thevenin equivalent in the box

Apply v_{test} (circuit has only dependent sources & resistors) (13) points

Since $v_{oc} = 0 \Rightarrow R_{Th} = 2 \text{ k} \quad (P.T.O \rightarrow)$

(2)

R_m: (2) Finding I_{sc}

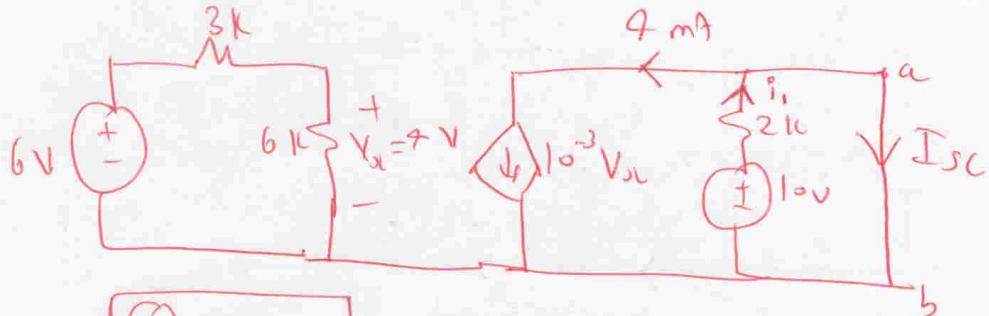

(6) points: correct direction for I_{sc}

(7) points:

$$i_1 \neq 0$$

(6) points


$$I_{sc} = i_1 - 4 = \frac{10}{2\Omega} - 4 \text{ mA} = 1 \text{ mA}$$

(1) point

Total:

(13) points

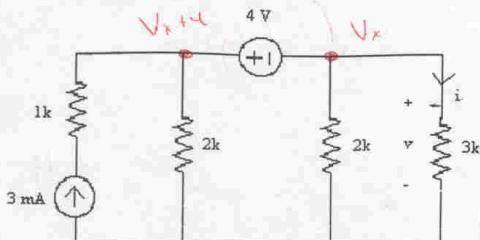3. (25 points). Find v and i in the circuit below.



Nodal


$$\frac{V_x}{3} + \frac{V_x}{2} + \frac{V_x + 4}{2} = 3$$

$$2V_x + 3V_x + 3V_x + 12 = 18$$

$$8V_x = 6 \Rightarrow i = \frac{\frac{3}{4}V}{3k} \Rightarrow i = 1/4 \text{ mA}$$

$$V_x = 3/4 \text{ V}$$


Source Transform

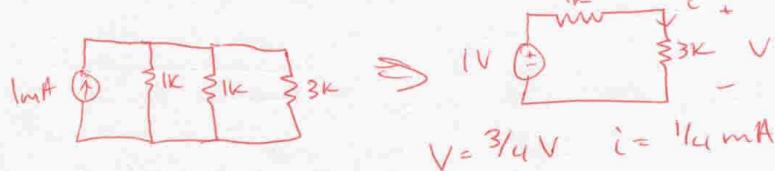

$$V = 3/4 \text{ V} \quad i = 1/4 \text{ mA}$$


$$v = \frac{3/4}{4} \text{ V}$$

$$i = \frac{1}{4} \text{ mA}$$

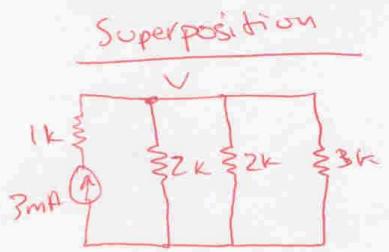

$$3\text{mA} = \frac{V}{2} + \frac{V}{2} + \frac{V}{3}$$

$$V = 2.25\text{ V}$$

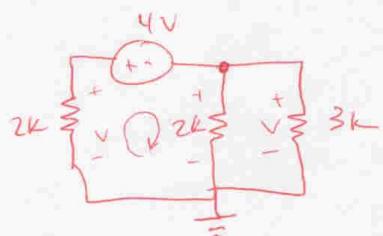


$$\frac{V}{2} + \frac{V}{3} + \frac{V+4}{2} = 0$$

$$V = -1.5\text{ V}$$

$$V_{\text{total}} = .75\text{ V}$$

$$\therefore i = \frac{V}{R} = .25\text{ mA}$$

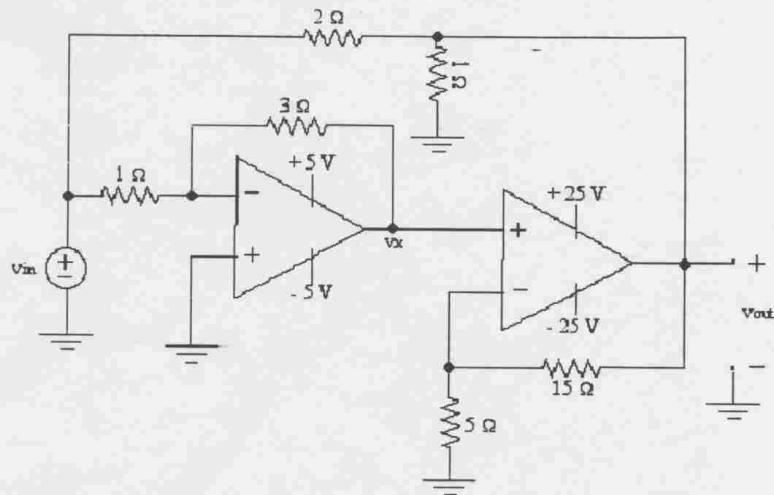4. (22 points) Consider the following dual op-amp circuit. Each op-amp has a separate power supply. Assume the open loop gain for both op-amps is infinite ($A = \infty$).



a.) Overall, is the above circuit an inverting or non-inverting amplifier?

(1) *Inverting \rightarrow non-inverting*
Inverting Write your answer here: INVERTING

(5) b.) Assuming op-amp 1 is working in the linear region; find the closed loop gain of op-amp 1.

$$\frac{v_x}{v_{in}} = \underline{-3}$$

(5) c.) Assuming both op-amps are working in the linear region, find the overall closed loop gain

$$\frac{v_{out}}{v_{in}} = \underline{-12}$$

(4) d.) If $v_{in} = 3$ V, find v_{out} .
 $v_{out} = \underline{-20 \text{ V}}$

(4) e.) If $v_{in} = -4$ V, find v_{out} .
 $v_{out} = \underline{+20 \text{ V}}$

(2) f.) If $v_{in} = 1$ V, find v_{out} .
 $v_{out} = \underline{-12 \text{ V}}$

PROBLEM 4 EXTRA WORKSPACE

B.)

$$\frac{V_{in}-0}{1} = \frac{0-V_x}{3} \Rightarrow V_{in} = -\frac{V_x}{3} \Rightarrow \boxed{\frac{V_x}{V_{in}} = -3}$$

C.)

$$\frac{V_o - V_x}{15} = \frac{V_x}{5} \Rightarrow \frac{V_o}{V_x} = 15 \left(\frac{1}{5} + \frac{1}{15} \right) = 3+1 \Rightarrow \frac{V_o}{V_x} = 4$$

$$V_x = -3V_{in} \quad V_o = 4V_x \Rightarrow V_o = 4(-3V_{in}) \Rightarrow \boxed{\frac{V_o}{V_{in}} = -12}$$

D.) Op-Amp 1: $V_{in} = 3V \rightarrow V_x = -9 \Rightarrow V_x = -5V$
RAIL

Op-Amp 2: $V_x = -5 \Rightarrow \boxed{V_o = -20V}$

E.) Op-Amp 1: $V_{in} = -4V \rightarrow V_x = 12$ RAIL $\Rightarrow V_x = 5V$

Op-Amp 2: $V_x = 5V \quad \boxed{V_o = 20V}$

F) $\frac{V_{out}}{V_{in}} = -12 \rightarrow V_{out} = -12(V) \rightarrow \boxed{V_{out} = -12V}$