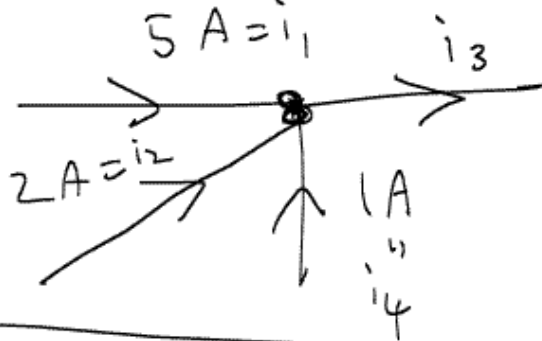


Discussion Notes - 1

Ex 1: KCL (Kirchoff's Current Law) Find i_3




$$i_3 = 8 \text{ A (KCL)} \quad \text{--- ①}$$

$$\text{KCL: } i_1 + i_2 + i_4 = i_3$$

Current entering = Current leaving } KCL

Fig 2'

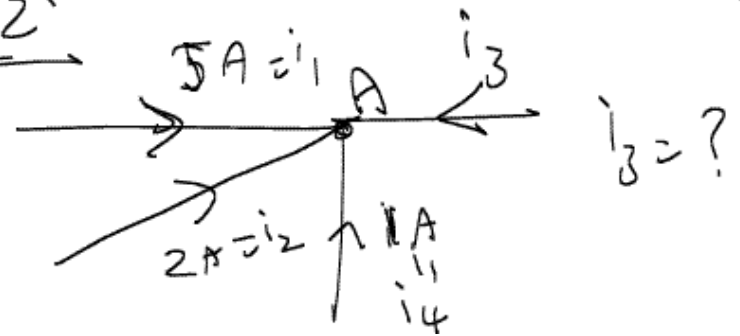


$$\text{KCL: } i_1 + i_2 + i_4 + i_3 = 0$$

$$\Rightarrow i_3 = -(i_1 + i_2 + i_4)$$

$$\boxed{i_3 = -8A} \quad \text{--- (2)}$$

Compare (1) & (2), magnitude of i_3 is the same (8A) but sign is different. This is because, in Eq 2, all currents are drawn as entering the point A, which is not physically possible. Therefore i_3 in Eq 2 is -ve because i_1, i_2 & i_4 are fixed! (negative)


Eg 3: (KVL)

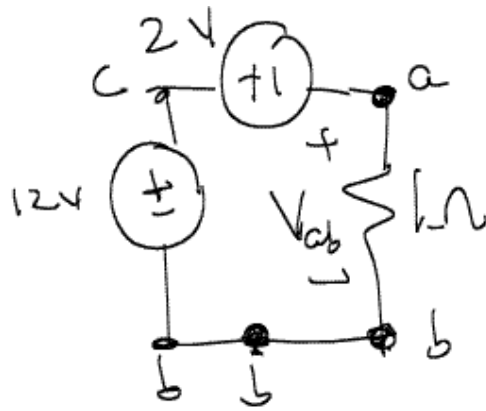

$$V_{cb} = ? = 10 \text{ or } 14$$


KVL: $\sum (\text{voltages around a loop}) = 0$

Note: (1) $c = 22?$

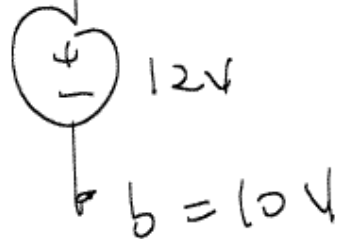

$$V_{cb} = 12 \text{ V}$$

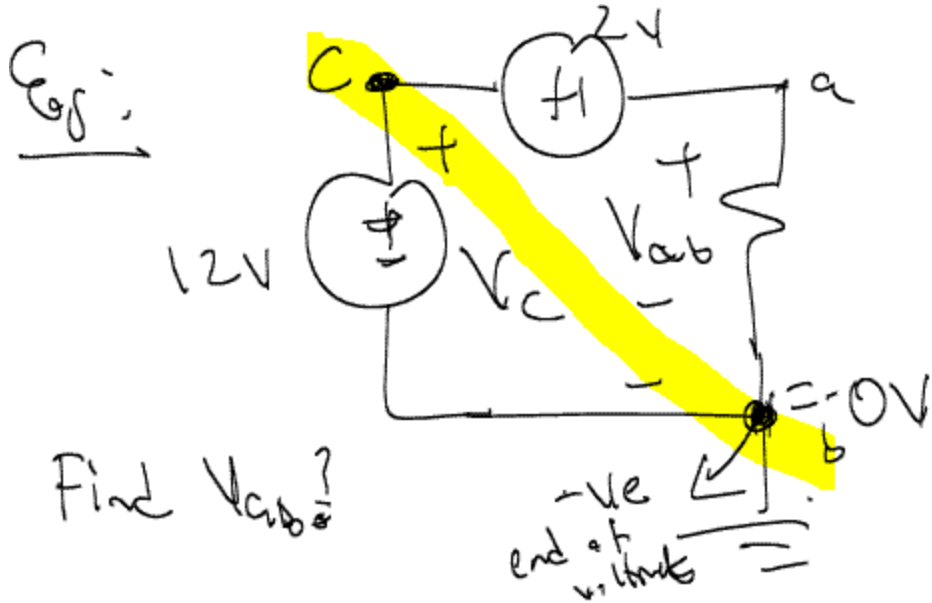(2) GND ∞ ref really does not matter in the sense that potential differences are important



$$V_{cb} = 12 \text{ V}$$

$$\Rightarrow V_c - V_b = 12 \text{ V}$$

$$\Rightarrow \boxed{V_c = 12 \text{ V}}$$


Now, $V_{ca} = 2 \text{ V}$

$$\Rightarrow \underline{V_c - V_a = 2 \text{ V}} \Rightarrow V_a = V_c - 2$$

$$\Rightarrow \boxed{V_a = 10 \text{ V}}$$

$$V_{ab} = V_a - V_b = 10 \text{ V}$$

But, suppose:

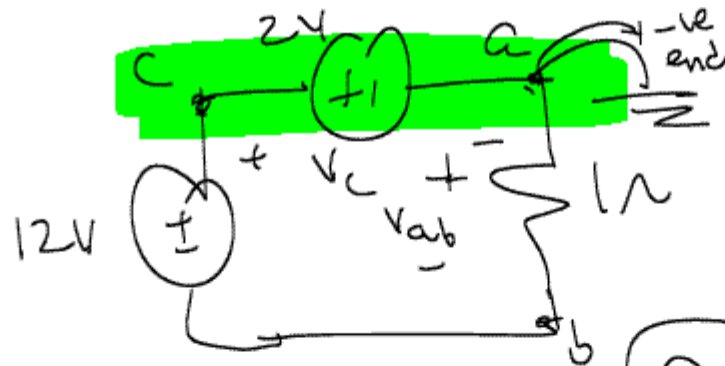

What is V_{ab} now?

$$V_c - V_a = 2V \quad (1)$$

$$V_c - V_b = 12V \quad (2)$$

$$(1) \Rightarrow V_c = 2V \quad [V_a = 0V]$$


$$V_c - V_b = 12V \Rightarrow V_b = V_c - 12$$

$$V_b = -10V$$

$$V_{ab} = V_a - V_b = 0 - (-10) = 10V$$

Notice V_{as} did not change !!!, because of

KVL:

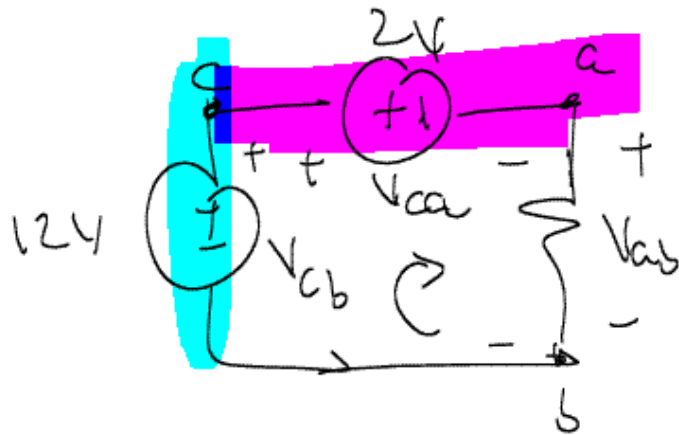

Note: V_{cb} means
 plus at c &
 minus at b i.e..
 $V_{cb} \triangleq V_c - V_b$

going clockwise from b:


$$+V_{cs} - V_{ca} - V_{ab} = 0$$

$$\begin{aligned} V_{ab} &= V_{cb} - V_{ca} \\ &= 12 - 2 = 10 \text{ V} \end{aligned}$$

→ rise in potential
 → drop in potential
 } convention

Note: If my convention was "opposite": $-12 + 2 + V_{ab} = 0$
 $\Rightarrow \boxed{V_{ab} = 10V}$

Ex:

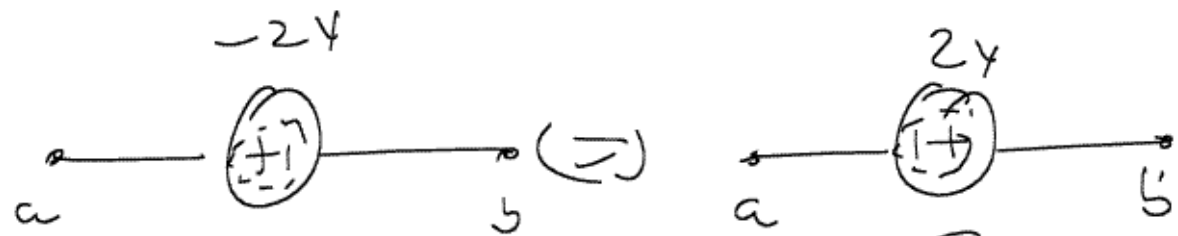

$$V_a - V_b = -2$$

$$\Rightarrow V_b - V_a = +2$$

