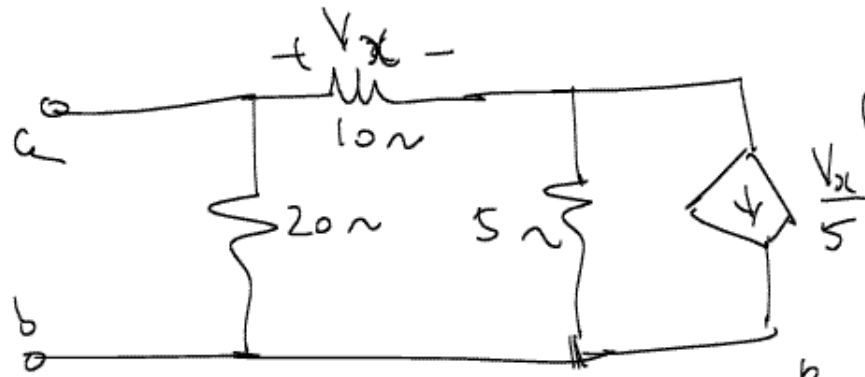


# EE 100 Discussion 2


(Q. 1) Example of Thevenin/Norton with dependent sources

Ex:





(Q:) Find Thevenin equivalent at ab

(A:)

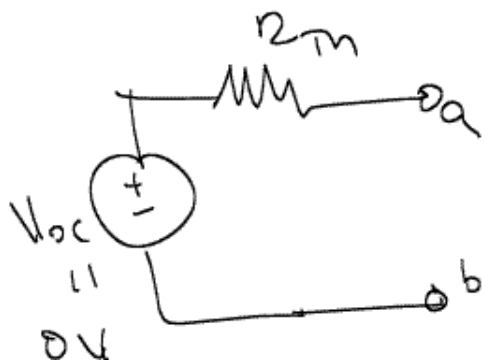


$\Leftrightarrow$

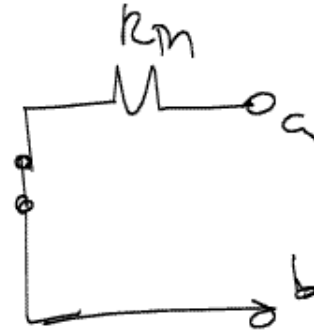

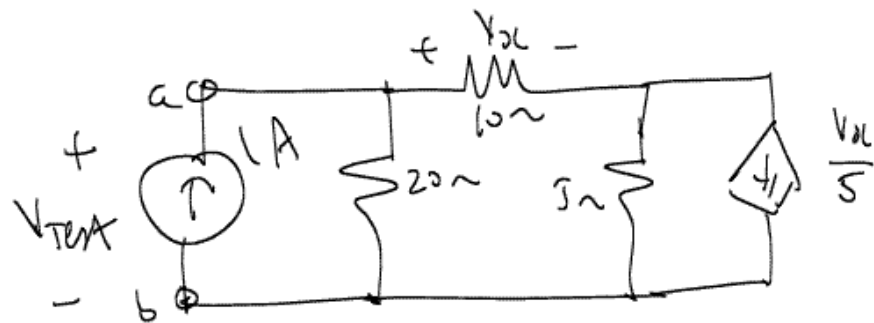


Note:


To pick direction of test source:

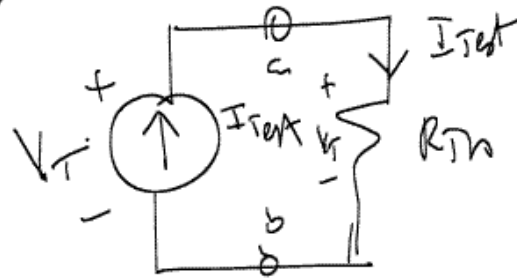

Nodal Analysis:

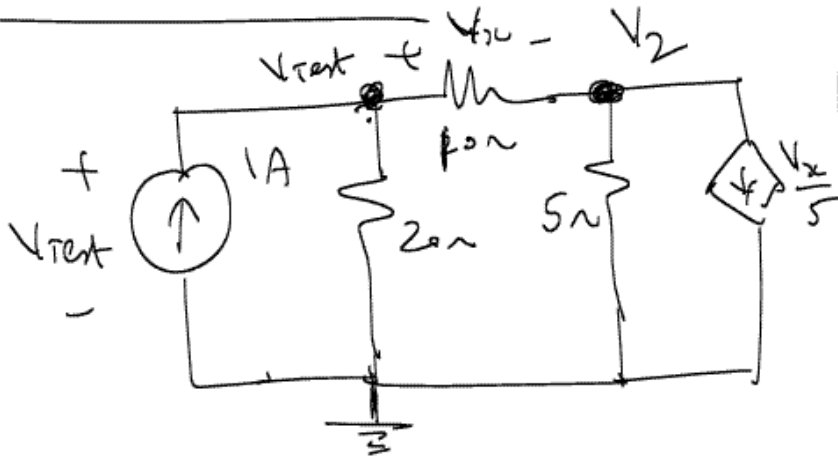

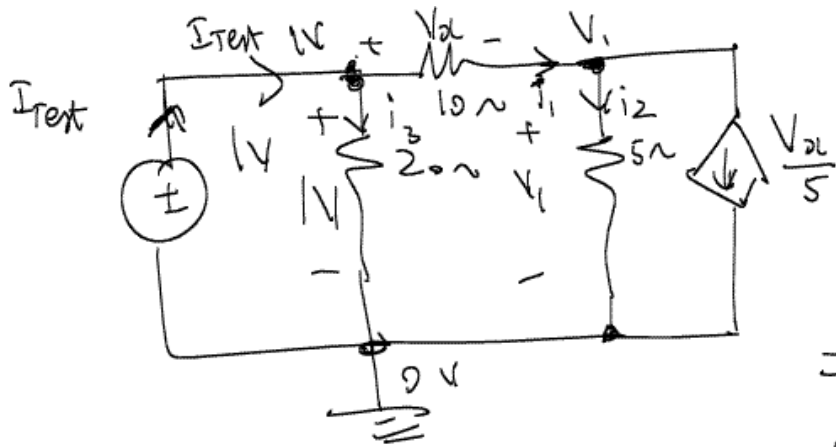Notice we have two unknown node voltages, but lets back track. Lets pick a test voltage source:



KCC @  $V_1$ .

$$i_1 = i_2 + \frac{V_x}{5}$$

$$\Rightarrow \frac{V_x}{10} = \frac{V_1}{5} + \frac{V_x}{5}$$

$$1 - V_1 = V_x$$

$$\Rightarrow V_1 = 1 - V_x$$

$$\therefore \frac{V_x}{10} = \frac{1 - V_x}{5} + \frac{V_x}{5}$$

$$\Rightarrow \frac{V_x}{10} = \frac{1}{5}$$

$$\Rightarrow \boxed{V_x = 2V}$$

Goal

$$I_{\text{Test}} = ?$$

$$I_{\text{Test}} = i_3 + i_1$$

$$I_{\text{Test}} = \frac{1}{20} + i_1$$

$$\therefore I_{\text{Test}} = \frac{1}{20} + \frac{V_x}{10}$$

$$= \frac{1}{20} + \frac{2}{10}$$


$$\Rightarrow I_{\text{TEST}} = \frac{1}{20} + \frac{9}{20}$$


$$I_{\text{TEST}} = \frac{1}{4} \text{ A}$$

$$\therefore R_m = \frac{V_{\text{TEST}}}{I_{\text{TEST}}} = \frac{1}{\frac{1}{4}} = 4 \Omega$$


(c:) Thevenin / Norton at different terminals in a circuit

Q:

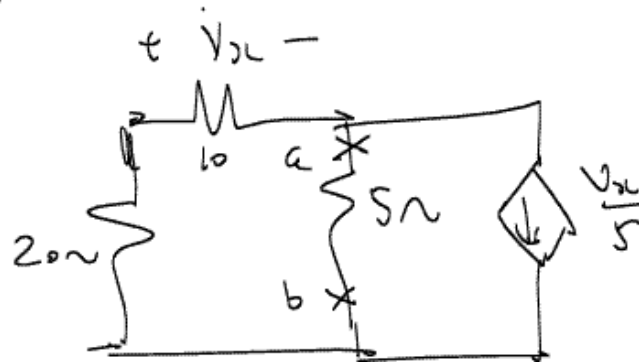

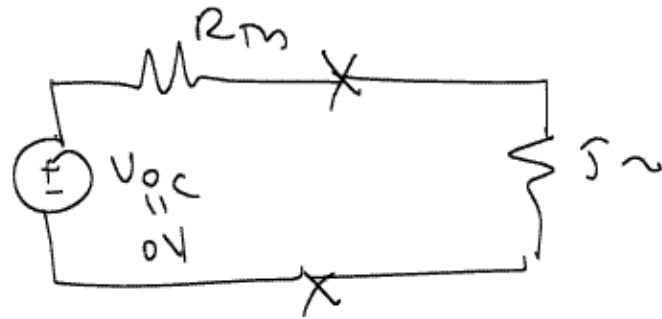

$R_m = ?$

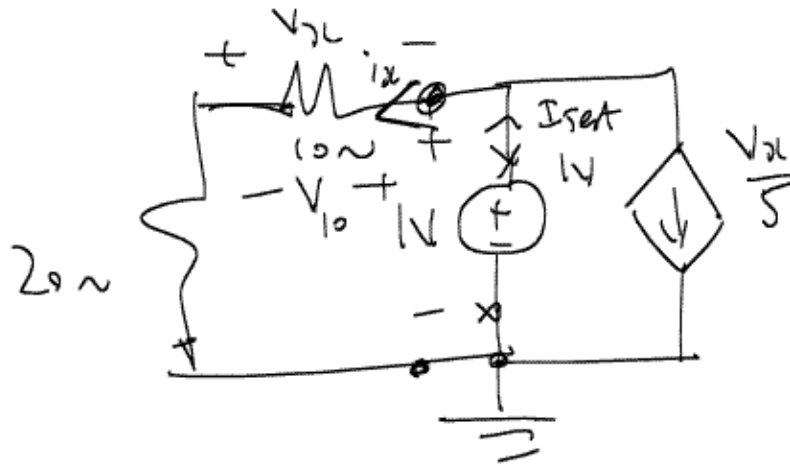

$$V_x = -\frac{10}{30} \text{ V}$$


(Q:)  $I_{TEA} = ?$

$$V_{10} = 1\text{V} \cdot \frac{10}{10 + 20}$$

(Voltage divider)

$$V_{10} = \frac{10}{30} \text{ V}$$



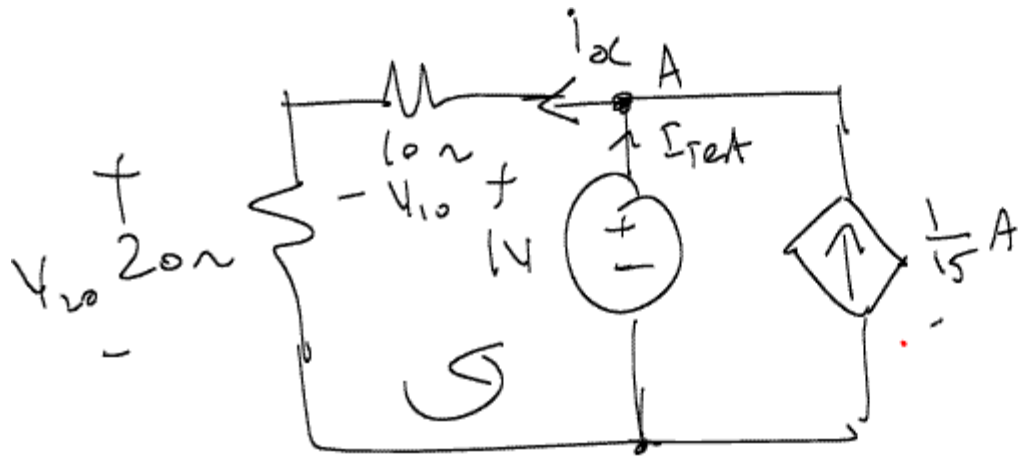

$$I_{\text{dependent}} = \frac{V_{20}}{5} = \frac{-\cancel{10} \cdot \frac{1}{15}}{5} = -\frac{1}{15} \text{ A}$$

$$I_{\text{Test}} + \frac{1}{15} = i_x \quad (\text{KCL at node A})$$

$$I_{\text{Test}} = \frac{V_{10}}{10} - \frac{1}{15}$$

$$= \frac{1}{30} - \frac{1}{15} = \frac{-1}{30} = -33.33 \text{ mA}$$

$$D_{ops}, R_m \ll \infty \Rightarrow R_{Th} = \frac{V_{Test}}{I_{Test}} = \frac{1}{-\frac{1}{30}} = \underline{\underline{-30\Omega}}$$

Verified in PSpice: (ask me in office how to explain this)

