
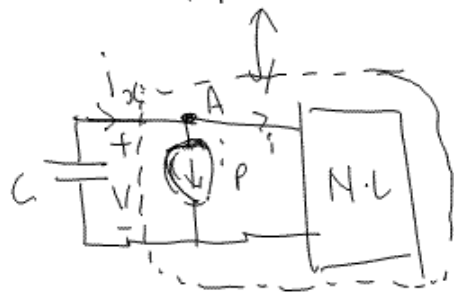
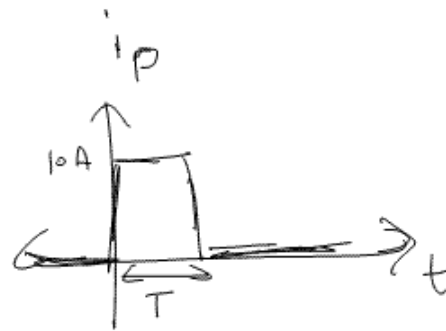


EE100 Discussion #7

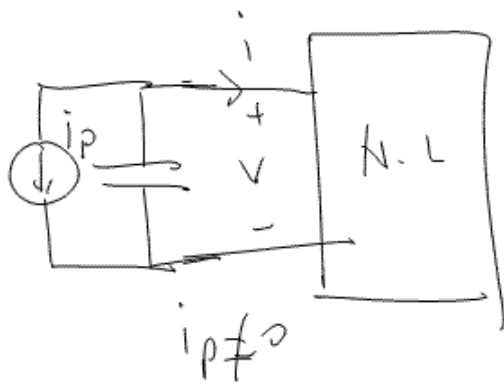
(Q.1) Related to Flip-Flops (#3 Form Sp05 MT II)



$$i_x = i + i_p$$

(KCL @ A)

$$\Rightarrow i_x = i + 10$$

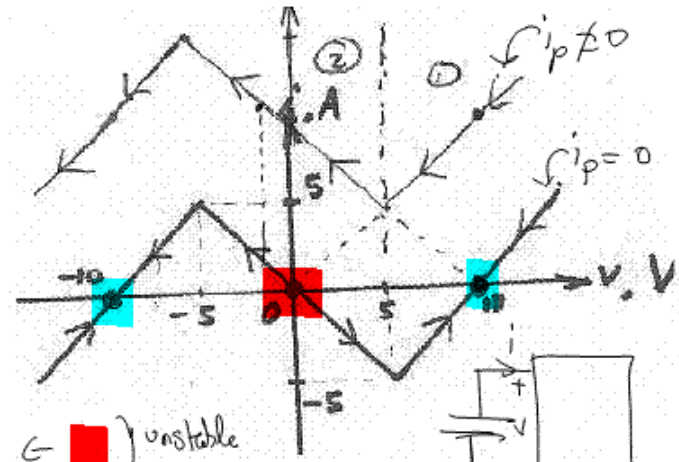

$(0,0) \leftarrow$ ■ unstable



$(10,0), (-10,0) \leftarrow$ ■ stable $i_c = -C \frac{dv}{dt}$ $i_p = 0$

(Q.1) $\tau < 0$

(3) Consider the circuit shown in figure P6.23 (a) where N is described by the i-v characteristic shown in figure P6.23 (b).

i. Sketch the dynamic route.

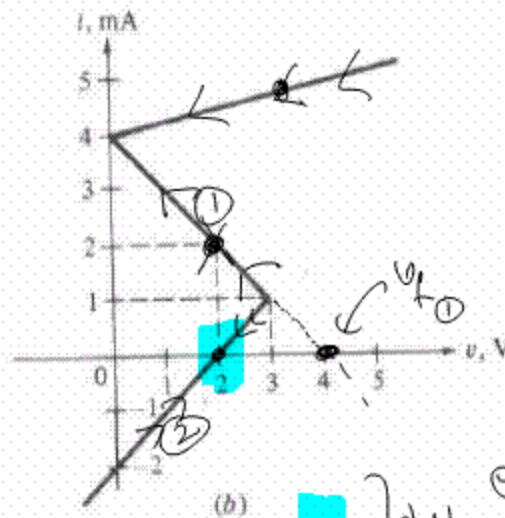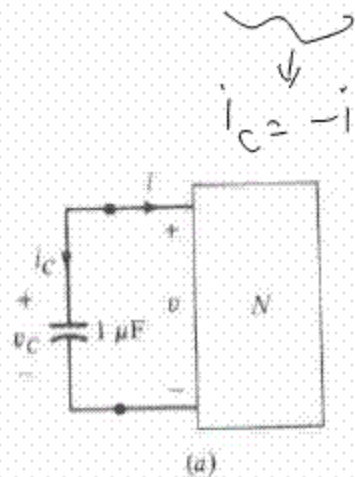ii. If $v_c(0) = 2$ V and $i_c(0) = -2$ mA; calculate and sketch $i(t)$ and $v(t)$ for $t \geq 0$.



$$i = -C \frac{dv}{dt}$$

$$\left. \begin{array}{l} i > 0 \\ v < 0 \end{array} \right\} \begin{array}{l} i < 0 \\ v > 0 \end{array}$$

$$\frac{dv}{dt} = 0 \Rightarrow \boxed{1=0}$$

Figure P6.23

$$v(t) = V_f + (v_i - V_f) e^{-t/\tau}$$

$$= V_f + (v_i - V_f) e^{t/\tau} \quad (\tau < 0)$$

Q:)



POINT! Nmos is always saturated!

Note: $V_{GS} = V_{DS}$ because of feedback.


Now, if Nmos is saturated: (Triode)

$$\begin{aligned} V_{DS} &\geq V_{GS} - V_{T0} & \Bigg| & \Bigg| & V_{DS} \leq V_{GS} - V_{T0} \\ \Rightarrow V_{GS} &\geq V_{GS} - V_{T0} & \Bigg| & \Bigg| & \Rightarrow V_{GS} \leq V_{GS} - V_{T0} \\ & & & & \text{impossible!} \end{aligned}$$

Q:.) Find V_o

$$\left(\frac{\omega}{L} = 1 \quad k_p = 50 \frac{\mu A}{V^2} \right)$$

$$V_{i0} = 1V \quad 5V$$

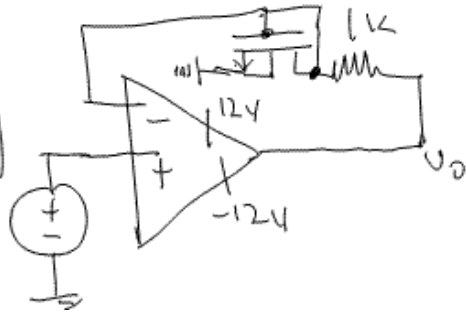

Two things

- ↳ (1) mode of operation of the Nmos
- ↳ (2) Is op-amp railing?


(A1): NMOS is always saturated (gate connected to drain)

(A2): Assume op-amp is linear.

$\therefore V_p = V_n = 5V$

$\therefore V_G = V_D = 5V$

Since NMOS is saturated:

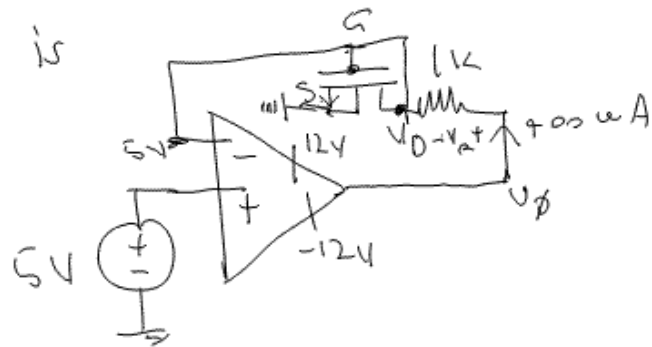

$$I_{DS} \approx K (V_{GS} - V_{T0})^2$$

$$= \frac{1}{2} (k_p) \left(\frac{W}{L}\right) (V_{GS} - V_{T0})^2$$

$$= \frac{1}{2} \cdot 50 \frac{\mu A}{V^2} (5 - 1)^2$$

$$\approx 400 \mu A$$

$$\hat{\therefore} V_o = V_p = V_R + V_D \Rightarrow V_o = (I_{DS})(1k) + 5V \Rightarrow \boxed{V_o = 5.4V}$$