

EE100 office hours - July 6<sup>th</sup> 2005

Question 1:

midterm  
review form  
EE100  
Summer 04  
- ignore b  
d c

http://inst.eecs.berkeley.edu/~ee100/ee100\_spring\_05/webpage/ee100\_fall\_04/webpage/ee100\_summer

File Edit Go To Favorites Help

Address http://inst.eecs.berkeley.edu/~ee100/ee100\_spring\_05/webpage/ee100\_fall\_04/webpage/ee100\_summer/exams/midterm\_review\_problems.pdf

Save a Copy Search Select 118% Go Want to create online forms?

5.) See the circuit below:

a.) Find the open circuit voltage, the short circuit current, and the equivalent resistance from the a-b terminals.


b.) Let  $V_s = 24$  V and  $R_a = 10$  k $\Omega$ . If the power delivered by the voltage source is 12 mW and the power delivered by the current source is 170 mW, find a value for:

- $R_s$
- $g_m$
- $R_b$

c.) From a and b, draw the Thévenin and Norton equivalent circuits, using the proper numerical values.

Done 14 4 2 of 5 Unknown Zone

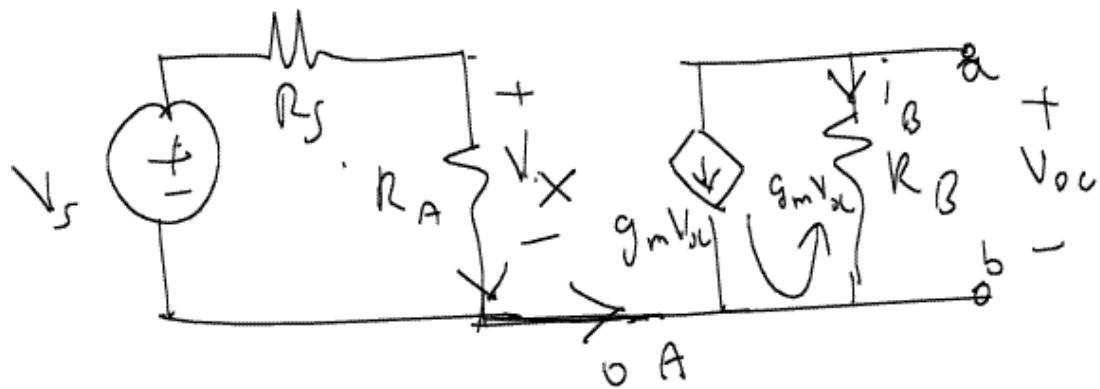start offcourseQuestions http://inst.eecs.berkeley.edu/~ee100/ee100\_spring\_05/webpage/ee100\_fall\_04/webpage/ee100\_summer/exams/midterm\_review\_problems.pdf Java(TM) - Windows 7... 5:38 PM



$$(a) \quad V_{oc} = i_B R_B$$


$$= (-g_m V_x) R_B$$

$$V_{oc} = (-g_m R_B) \left[ \frac{V_s R_A}{R_A + R_s} \right]$$

$$V_x = \left( \frac{R_A}{R_A + R_s} \right) V_s$$

(Voltage divider)

$I_{SC} = ?$

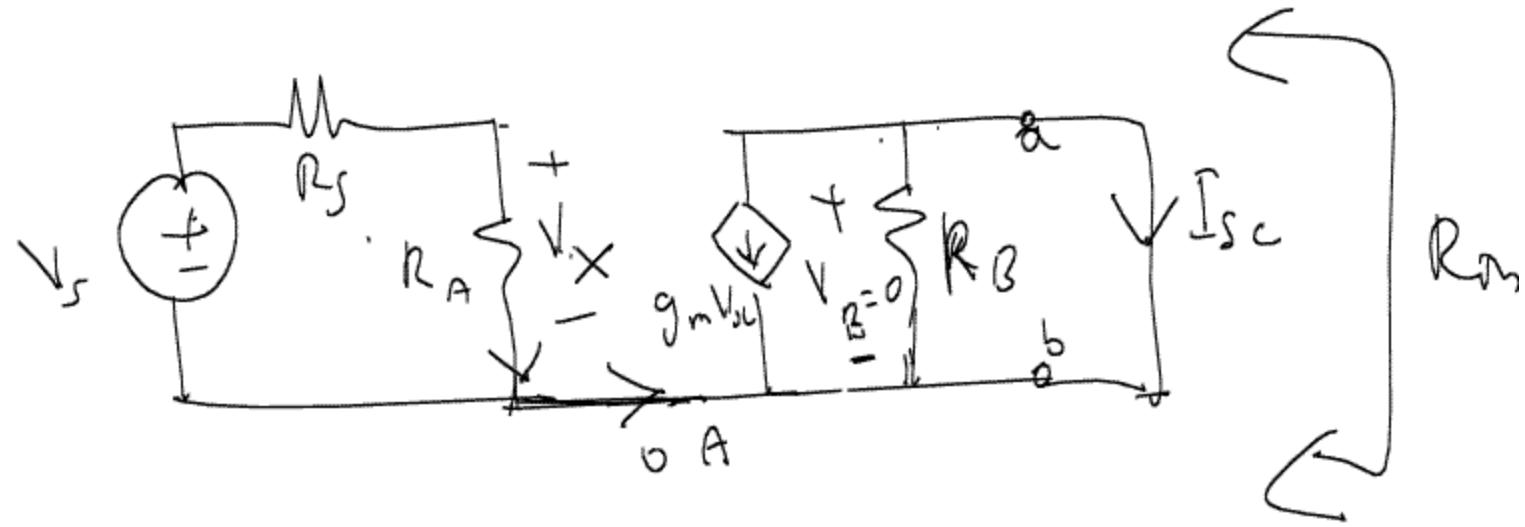

$$I_{SC} = -g_m V_x$$


$$I_{SC} = -g_m \left[ \frac{R_A}{R_A + R_S} V_s \right]$$

As an aside, 
$$R_m = R_B = \frac{V_{oc}}{I_{sc}}$$

Example: This was going to be the hard problem  
on the test (worth 5 points)

Find & sketch  $v_c(t)$

[All elements are ideal]

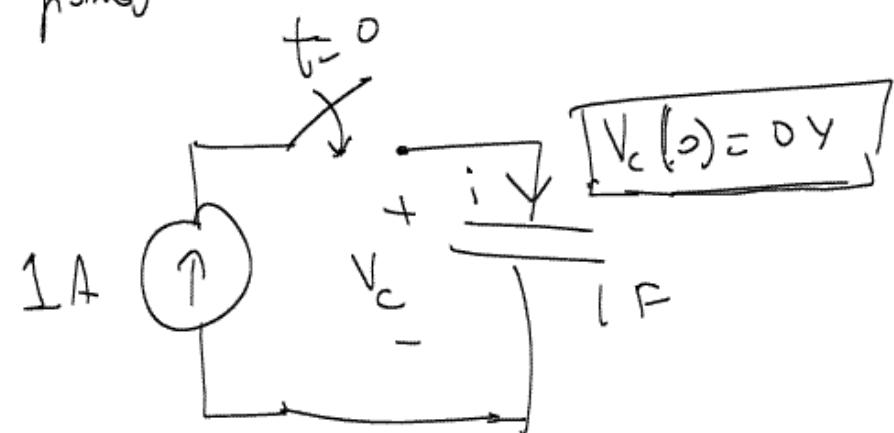


Sol: You can't use:  $V_c(t) = V_{cf} + (V_{ci} - V_{cf}) e^{-t/\tau}$ , because  $\tau$  is undefined!

$\therefore$  Go back to first principles:  $i = C \frac{dv}{dt} \Rightarrow i = C \frac{dv}{dt}$

$$\Rightarrow \frac{dv}{dt} = i$$

$$v(t) = t$$

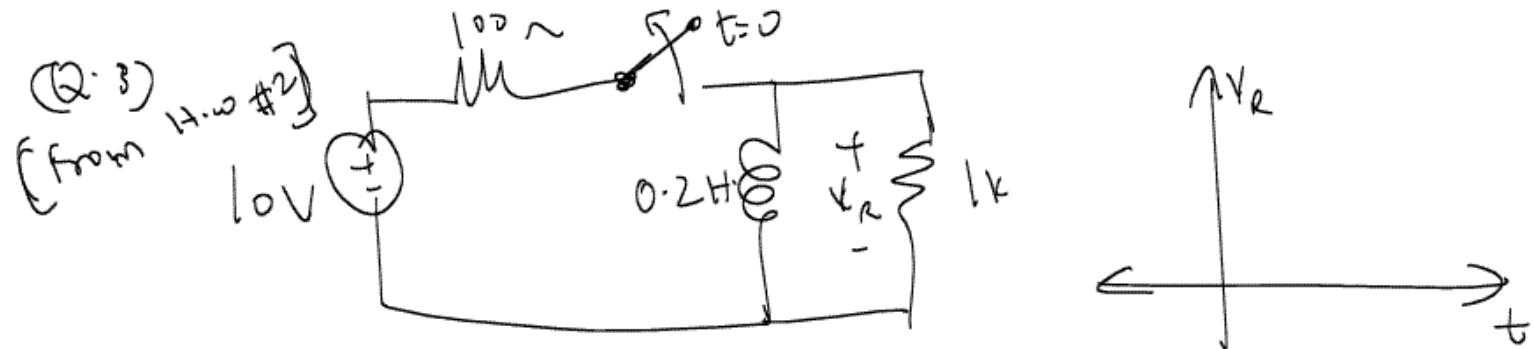

(Q.4) Find  $V_R$  & sketch  $v_R$


$$V_R(t) = V_{R_f} + (V_{R_i} - V_{R_f}) e^{-t/\tau}$$



$V_L(0^-) = 0 \text{ V}$   
(inductor is short circuited)

$$i_L(0^-) = \frac{10 \text{ V}}{100 \text{ mH}}$$

$$i_L(0^-) = 100 \text{ mA}$$

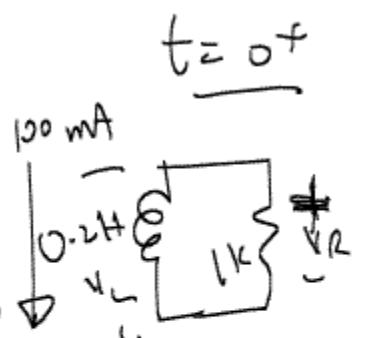

$$V_R(0^+) = ?$$

Notice the direction of the 100mA current:

$$V_R(0^+) = -(1\text{k})$$

(100mA)

$$V_L(0^+) = -100 \text{ V}$$

$t \rightarrow \infty$

$$V_R(t \rightarrow \infty) = 0 \text{ V}$$

(because inductor is fully discharged)

$$\tau = \frac{L}{R} = \frac{0.2 \text{ H}}{1\text{k}} = 0.2 \text{ ms}$$

$$V_R(t) = -100 e^{-\frac{t}{0.2 \text{ ms}}} \text{ V}$$

(Q.) Are  $R_1$  &  $R_2$  in series or parallel?

