
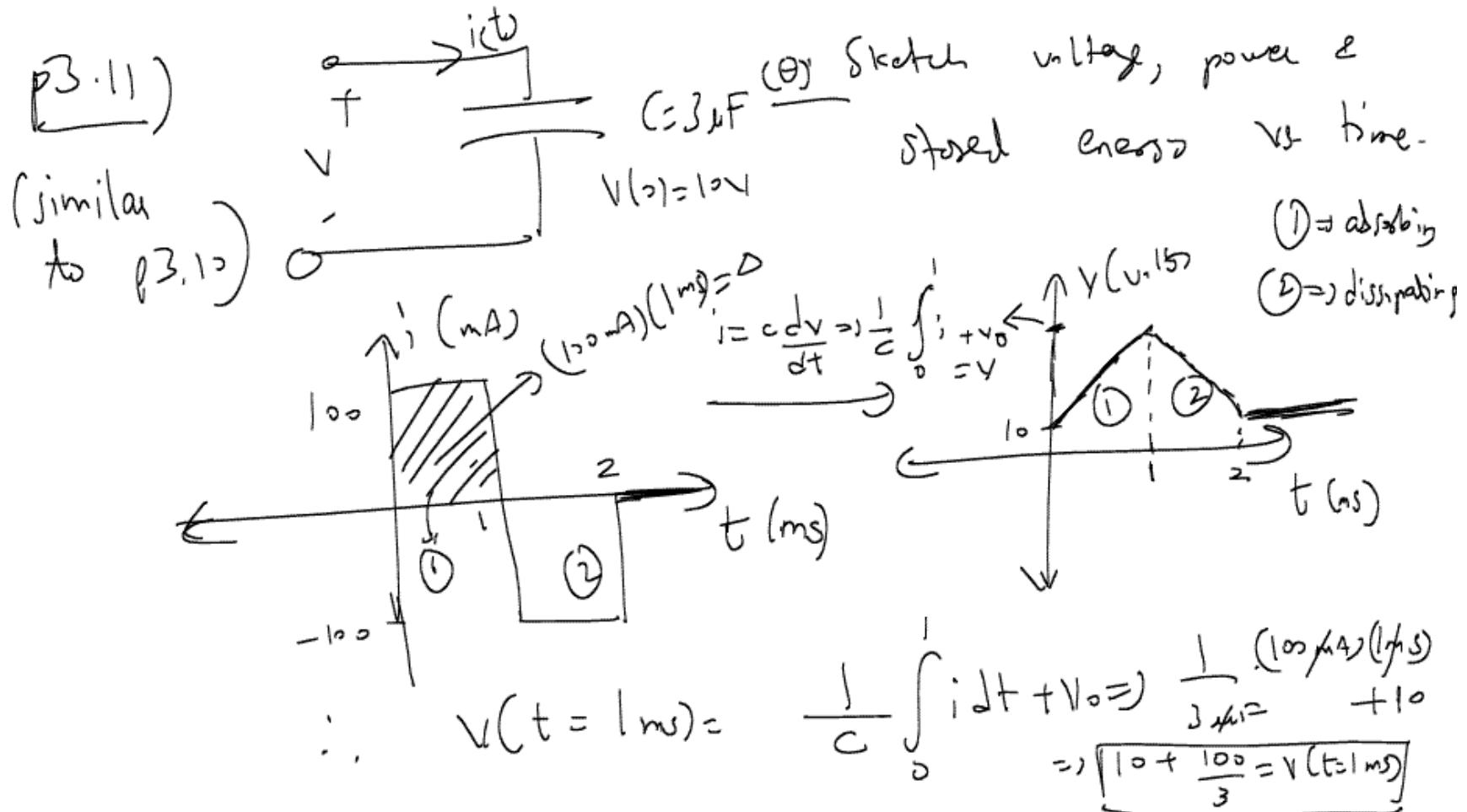


EE100 Wednesday June 29th 2005

(Office hour
notes)

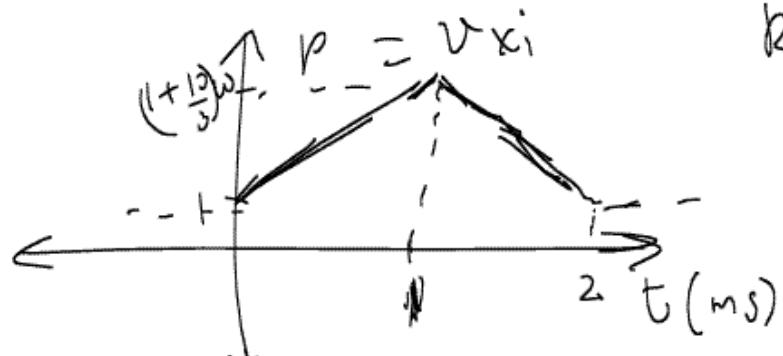



Region ①: $i_1(t) = 100 \text{ mA}$

$v_1(t) = ?$

$\frac{\Delta v}{\Delta t} ① = \frac{(120 - 100)}{1 - 0} = 100 \text{ V/s}$

$\therefore v_1(t) = \frac{100}{3}t + 10 \text{ volts}$


$\therefore P_1(t) = v_1(t) \cdot i_1(t) = \frac{100 \text{ mV}}{2} t + 1000 \text{ mW}$

$$\boxed{P(t) = \frac{10}{3}t + 1000 \text{ mW}}$$

→ Copy from now!

p 4-2)

$$t \leq 0$$

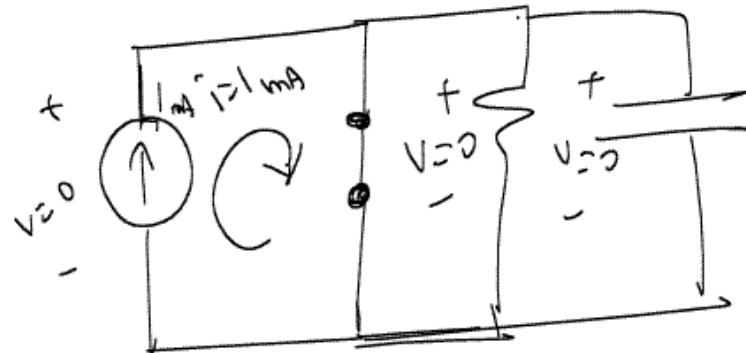

N.t.: Check ^{EE450} online exams on <http://hkn.eecs.berkeley.edu>.
for good practice problems.

Example


Fall 2000 midterms);
problem 3:

(Ca)


Problem #3

Initial Conditions
 In each of the problems below, find the value of the current or voltage just after the switch moves ($i = 0+$). (What is requested is just a numerical value, Not an equation or function of time.)

a.

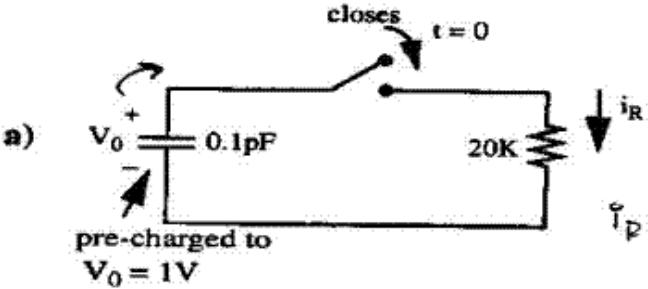

$i_R = ?$

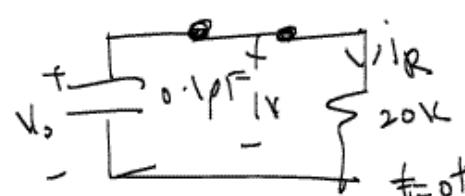


$V_0 = 1V = V(t=0^+)$
 $(t=0^-)$

$i_R(t=0^+) = \frac{1}{20k} = \frac{1}{20 \times 10^3} = 50 \mu A$

Voltage across a capacitor can't change instantaneously

b.



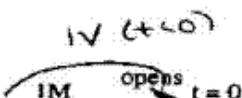


$i_R = 50 \mu A$

Done

start OfficeHourQuestions <--course, exam #, ... June29th - Windows ... cory.eecs.berkeley.e... Internet 6:05 PM



(b) (slight variation):

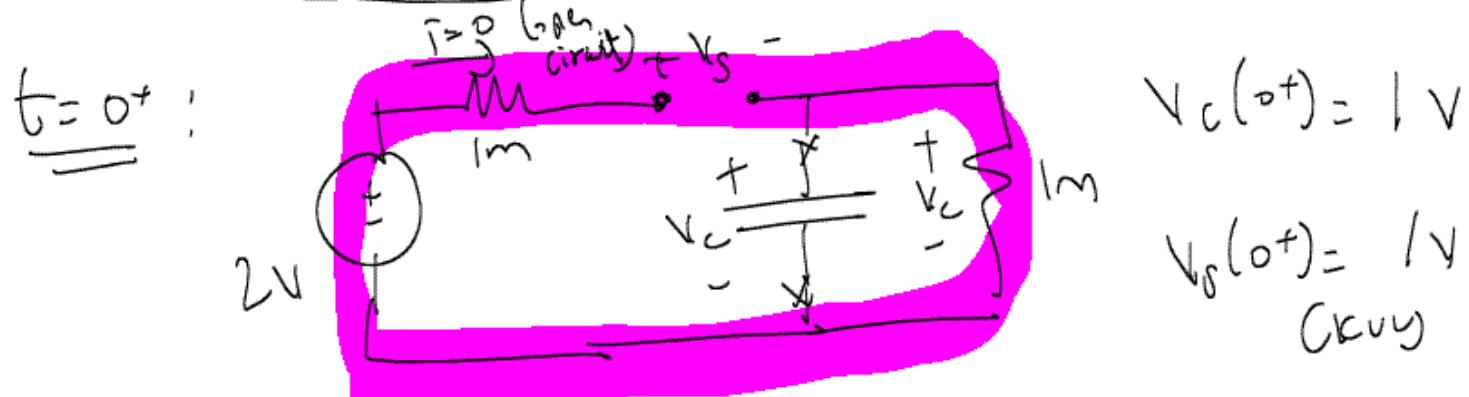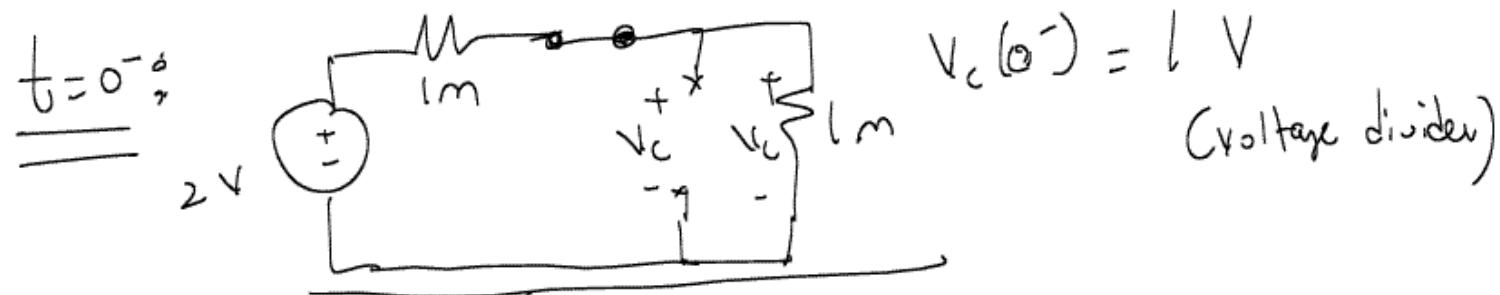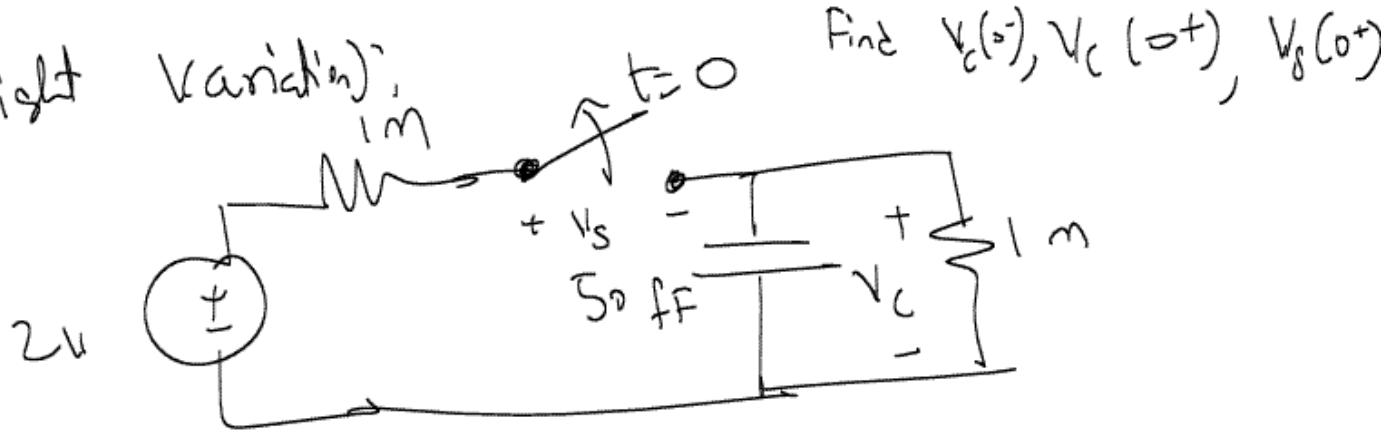

KVL

$$2 - (0)(1m) - V_S - V_C = 0$$
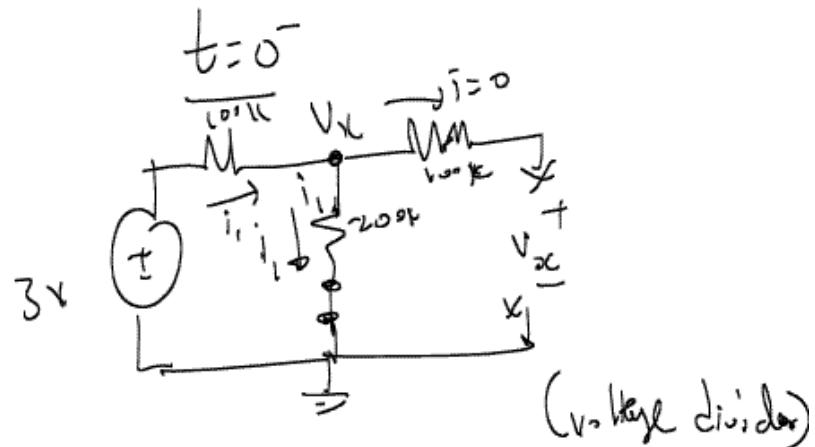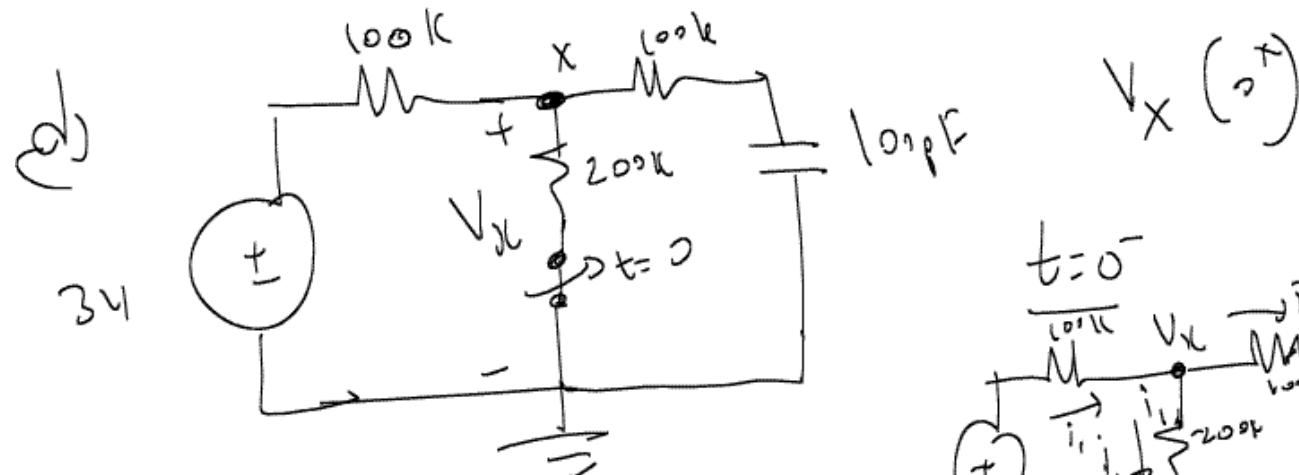
$$\Rightarrow \boxed{V_S = 2 - 1 = 1 \text{ V}}$$




$$V_x(0^-) = \frac{200k}{300k} \cdot 3 = 2 \text{ V}$$

$t = 0^+$

Note $\rightarrow V_{RL} \neq V_C$ at $t = 0^+$ 3V

because $i \neq 0$

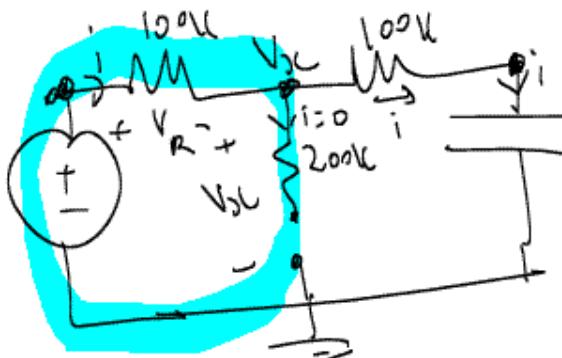

$$V_C = 2V$$

KVL $3 - V_R - V_{RL} = 0 \Rightarrow V_{RL} = 3 - V_R$


$$= 3 - i(100\Omega)$$

$$= 3 - \left(\frac{3-2}{200\Omega}\right) \cdot 100\Omega$$

$$= 3 - 0.5 = 2.5V$$

$V_{RL}(0^+) = 2.5V$



(Q.) What happens?

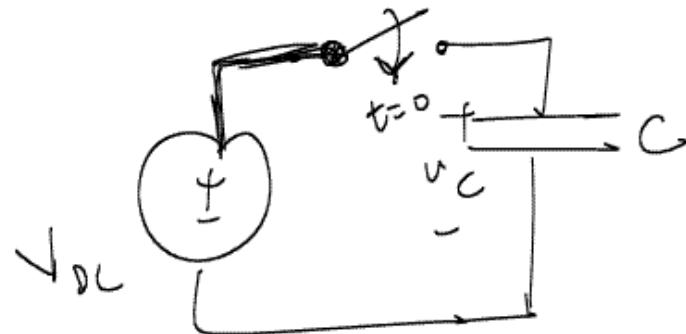


I deally: Bad! V_C cannot change instantaneously!!!


(Q.) 2.66

Find Thevenin & Norton equivalent:

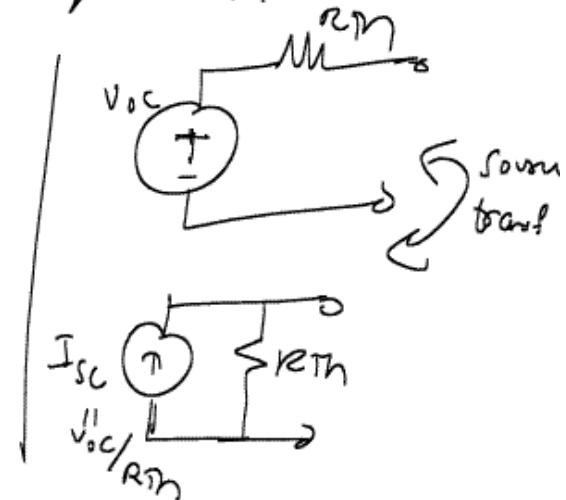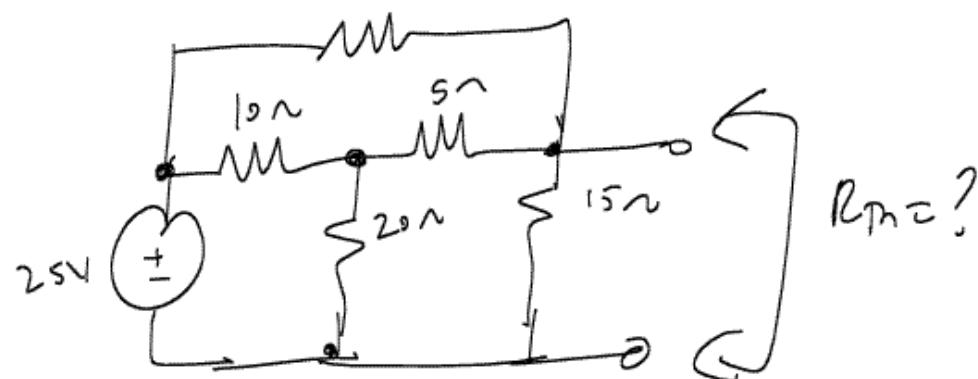

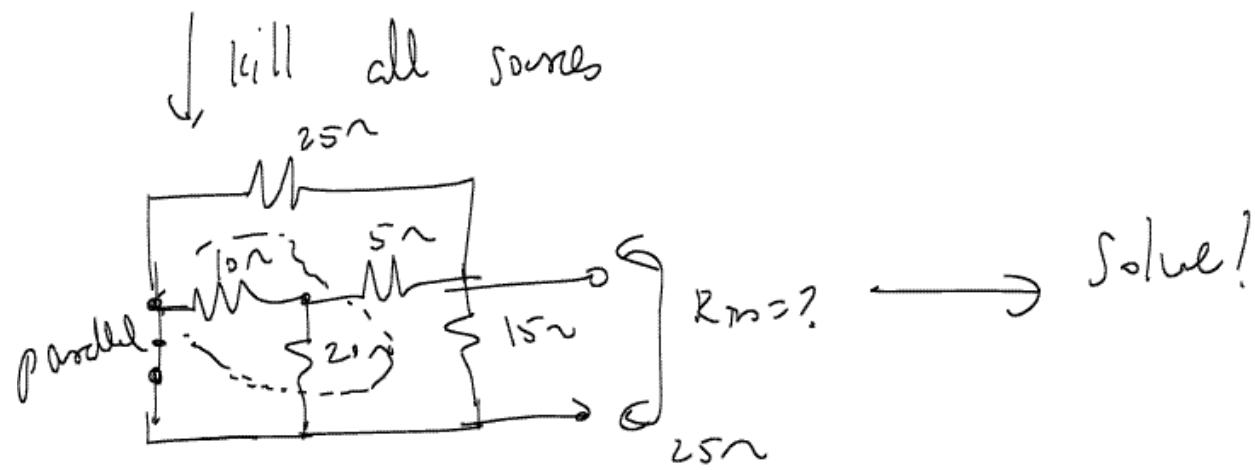

$$V_{oc} = ?$$

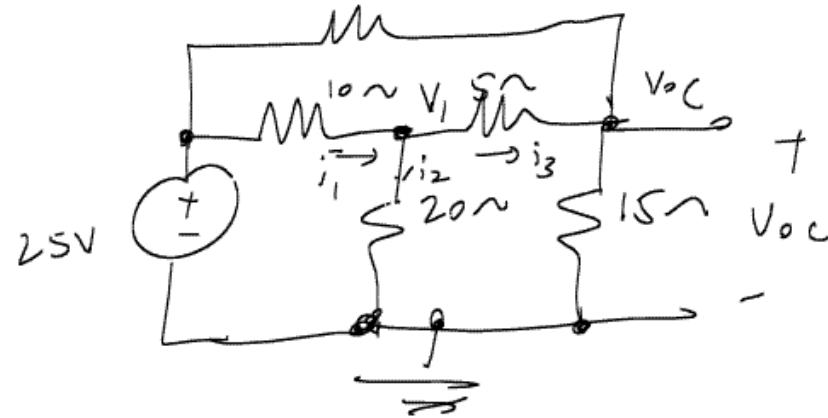


CCCL @ V_i : $i_1 = i_2 + i_3 \Rightarrow \frac{25 - V_i}{10} = \sum i + \frac{V_i - V_{oc}}{5}$

Setup KCL at V_{AB} & then solve!

More example problems: Refer to old exams & review problems from EE10 website (eg: Click on "EE10 Spring 2005 website" on EE10 homepage & click on Exams).

E8:

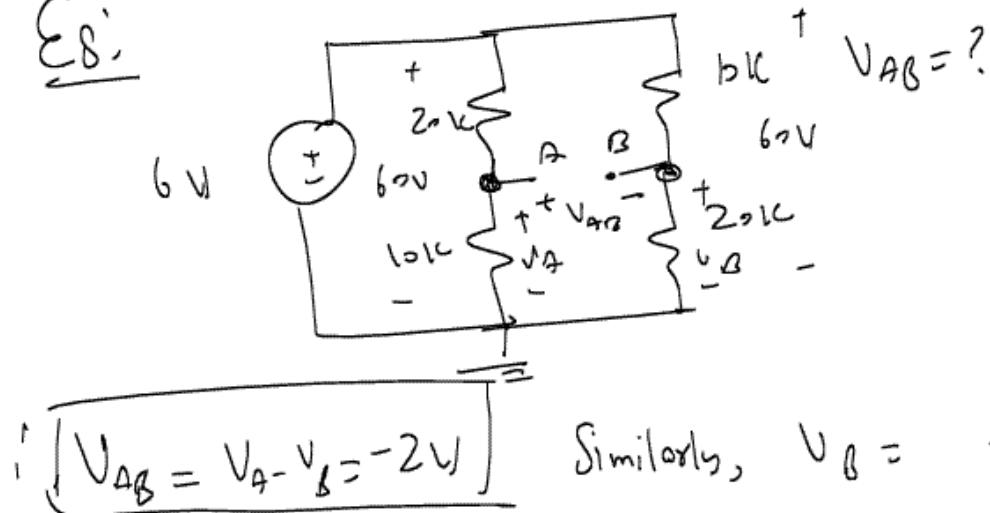


$$V_A = \frac{90k}{10+20k} \cdot 6V \quad (\text{Voltage divider})$$

$$= 2V$$

$$\boxed{V_{AB} = V_A - V_B = -2V}$$

Similarly, $V_B = \frac{20k}{30k} \cdot 6V = 4V$

e.g:

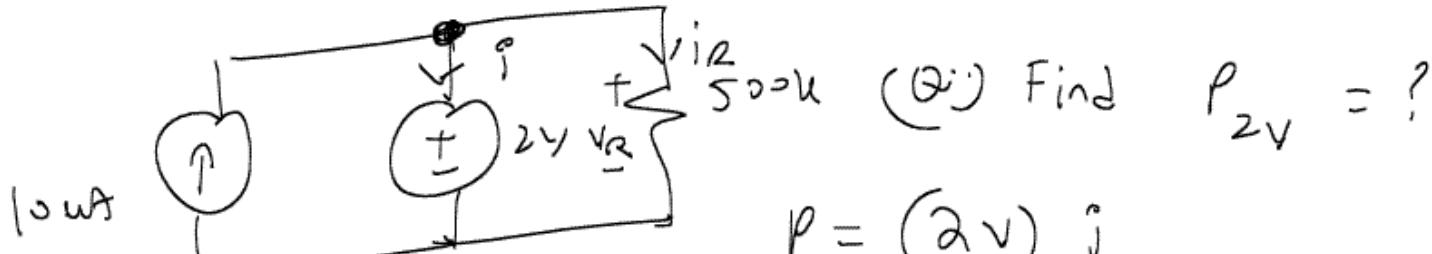


$$P = \underbrace{(2V)}_V i$$

$$10 \mu A = i + i_R \quad (\text{KCL})$$

$$= i + \frac{2 = V_R}{500 \Omega} \Rightarrow 10 \mu A = i + 4 \mu A$$

$$\Rightarrow i = \underline{6 \mu A}$$

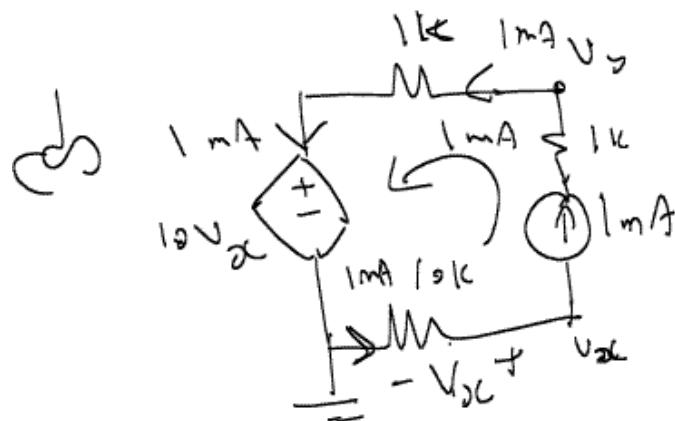
$$\therefore P = (2V) (6 \mu A) = \boxed{\underline{+12 \mu W = P}}$$



$$V_{xL} = - \underbrace{(1mA)}_{\text{current enters negative terminal}} \underbrace{(10k)}_{\text{at } V_{xL} \text{ across } 10k}$$

$$\Rightarrow \boxed{V_{xL} = -10V}$$

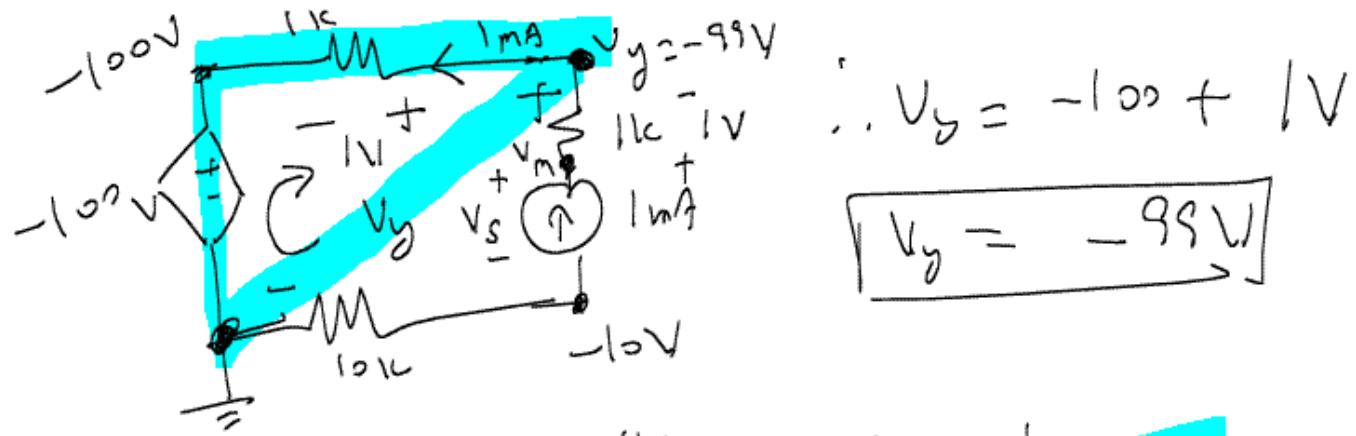(Invention, current enters negative terminal at V_{xL} across $10k$)



$$\boxed{V_y = -99V}$$


Note: KVL around "loop" marked by

Expt: Find V_s ? Now, $V_s = V_m - (-10V)$

$$= (-99 + 1V) + 10$$

$$= -98 + 10 \Rightarrow \boxed{V_s = -88V}$$

(Q.) Chap. 9 material. p. 4.1b

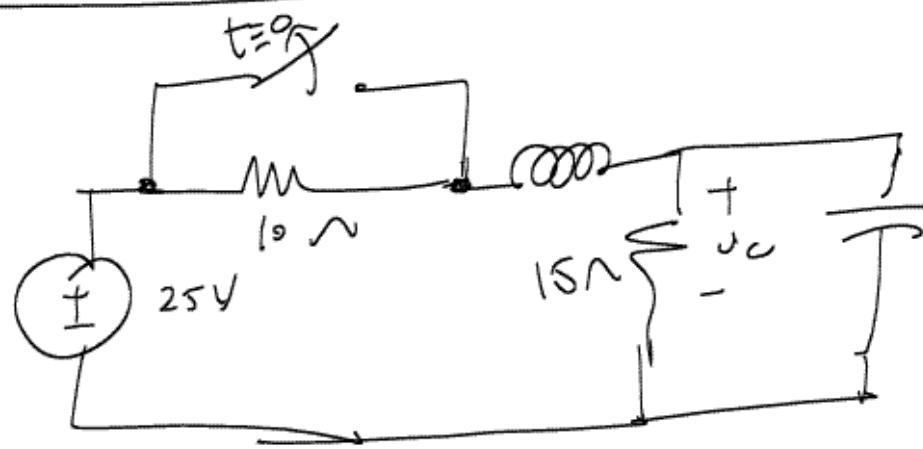

|+int: for $t < \infty$
 $\rightarrow t \rightarrow \infty$

Steady state!

