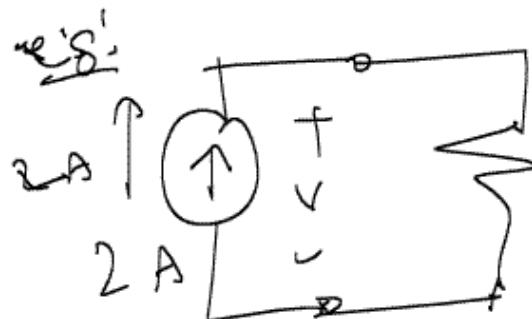





FEEL02 lecture 2 - Part II (After book)

(2) Independent Current Sources:

Note: Current sources are
a little weird!





loop most
be complete

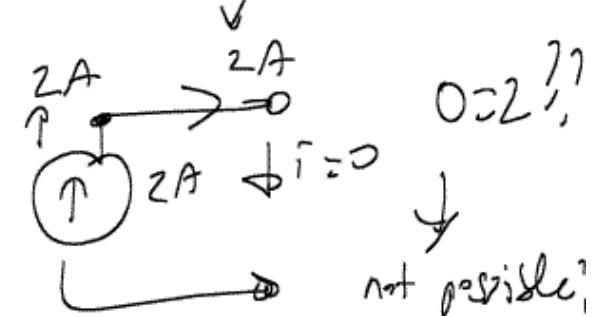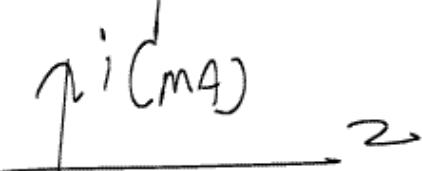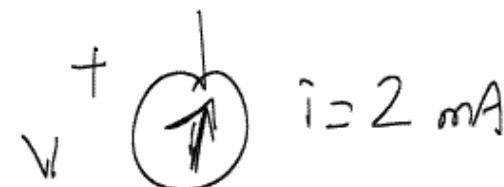

This brings up open circuits & short-circuits

Warning  Watch out for these concepts \Rightarrow potential pitfalls.

Q:

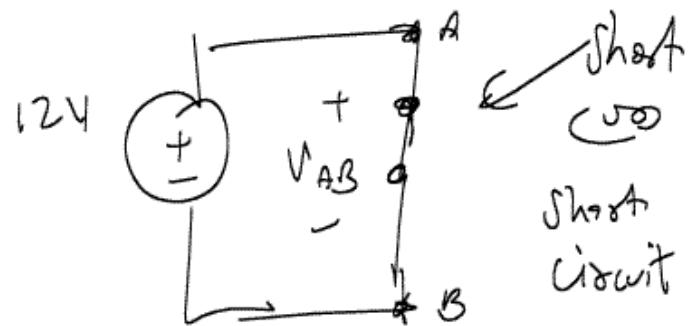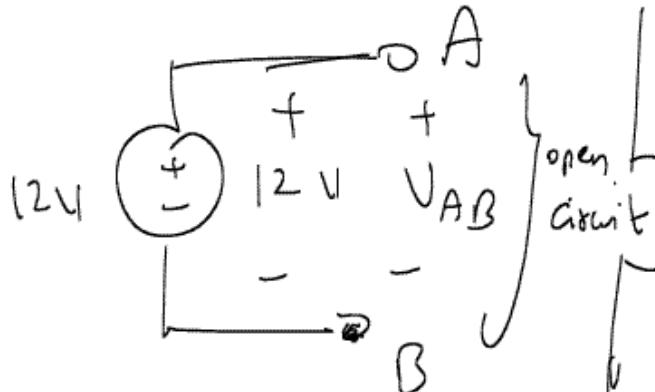

Given

$$V_{AB} - 12 = 0$$

$$\Rightarrow \boxed{V_{AB} = 12 \text{ V}}$$


 $V_{AB} = 0$ (short circuit)

 $i = \frac{12}{R}$] $\rightarrow \infty$

CORRECT: $V_{AB} = 12 \Rightarrow 0 \neq 12$

Again: watch out for open circuit & short circuit solutions \Rightarrow tricks!

e.g:-

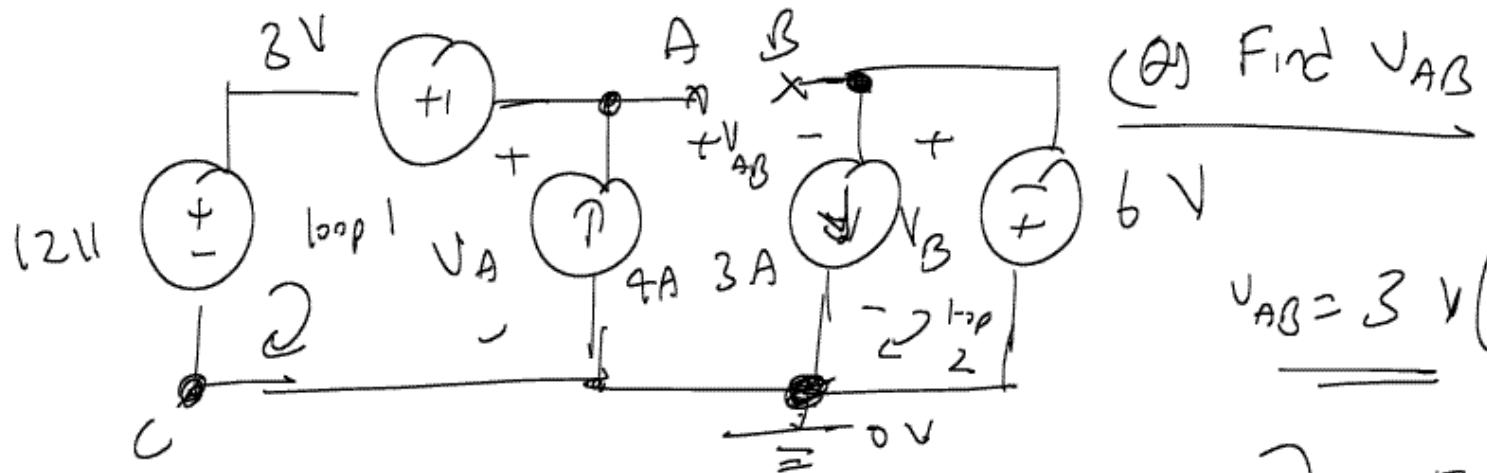

Note: $V_{AB} \Rightarrow + \text{ at } A, - \text{ at } B$] FE
i.e., in the solution above $V_{AB} = V_A - V_B$ Correction


KVL around loop 2: $V_B + 6 = 0 \Rightarrow V_B = -6 \text{ V}$

KVL around loop 1: $12 - 3 - V_A = 0 \Rightarrow V_A = 9 \text{ V}$


$\therefore V_{AB} = V_A - V_B = 15 \text{ V}$

Summary:

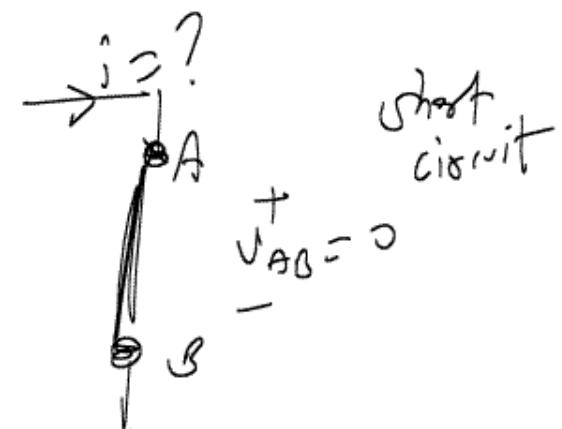$i = 0$
open circuit
 $v_+ = ?$
 $v_- = ?$



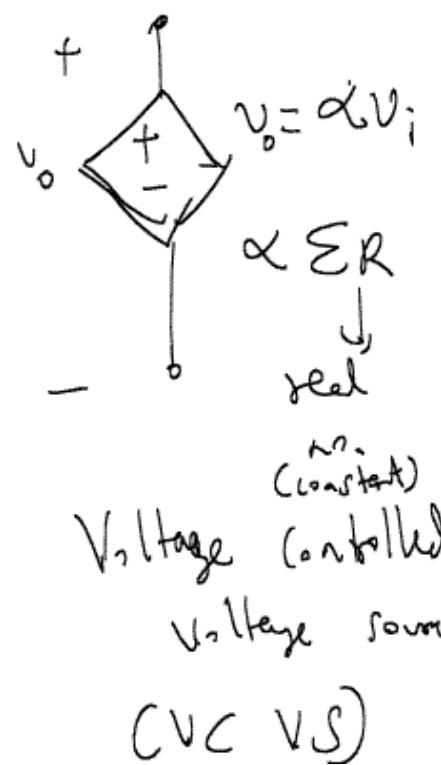Dependent sources: Sources (voltage or current) whose output depends on a current or voltage elsewhere in the circuit. Far type:



$v_1 = \beta i_2$

(CCVS)

$[\beta] = \frac{V}{A}$

$i_1 + i_2 = \gamma i_3$

(CCCS)


$[\gamma] = \text{none}$

$i_3 = \Delta V_4$

(VCCS)

$[\Delta] = \frac{A}{V}$

e8:

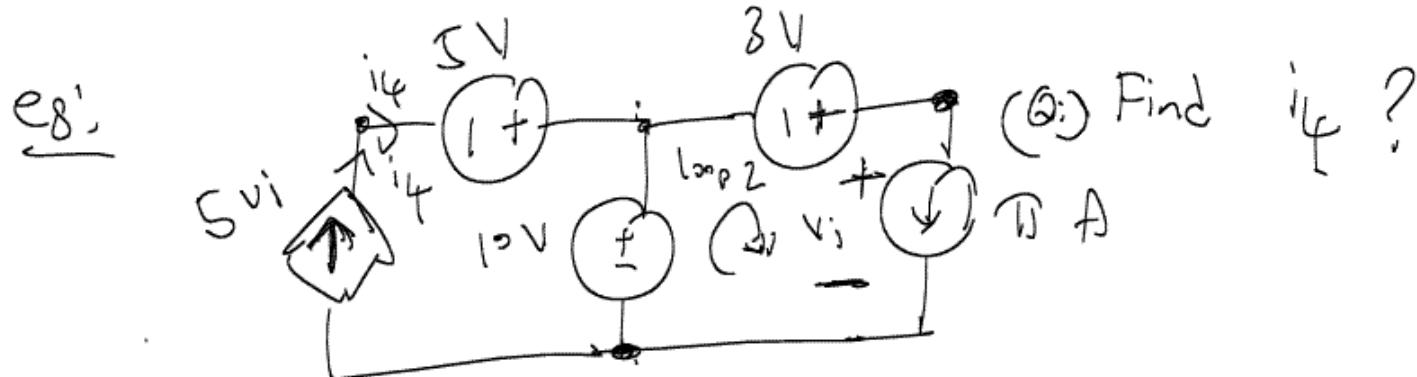

(Q:) Find i_4 ?

(A:) $i_4 = 5v_i$ kvl around loop 2:

$$i_4 = 65 \text{ A}$$

$$10 + 3 - v_i = 0 \Rightarrow v_i = 13 \text{ V}$$


Resistors:
 $\begin{cases} - \\ + \end{cases} \xrightarrow{i} \begin{cases} + \\ - \end{cases} \xrightarrow{R} \Leftrightarrow v = -iR$

Symbols:
 $\begin{cases} - \\ + \end{cases} \xrightarrow{i} R \Leftrightarrow v = -iR$

R


$\begin{cases} + \\ - \end{cases}$

$v = iR$
(Ohm's law)

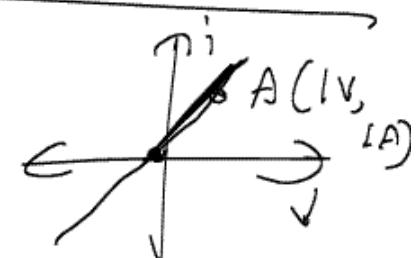

Notice: Resistors always absorb energy!

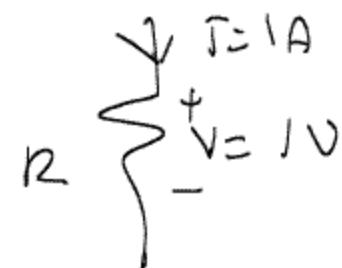Ex: If $V=1\text{ V}$, $i=1\text{ A}$, $R=1\text{ }\Omega$



Ex: If $V=-1\text{ V}$, $i=-1\text{ A}$,

$$V = -1\text{ V} \quad R \quad (\Rightarrow) \quad V = iR \Rightarrow (-1\text{ V}) = (-1\text{ A})R$$
$$\Rightarrow \boxed{R = 1\text{ }\Omega}$$

$$(\text{oo}) \quad \begin{array}{c} + \\ V = -iV \\ - \end{array} \quad \left\{ \begin{array}{l} \Rightarrow V = -iR \\ I A \end{array} \right.$$

$$\frac{\text{physically}}{R = \frac{\rho L}{A}} \quad \left. \begin{array}{l} \text{load} \\ p = ? \end{array} \right\} \Rightarrow (-iV) = - (IA) R \quad \Rightarrow \boxed{R = 1 \Omega}$$


Note: power can be expressed in terms of
R for a resistor: $p = vi$

$$\begin{array}{c} i \rightarrow \\ \left. \begin{array}{l} + \\ V \\ - \end{array} \right\} R \end{array} \Rightarrow p = (iR)i = i^2 R$$

Now, we will do circuits, circuits, circuits, ...

Ex (Pl. 50) p. 43

Find V_x

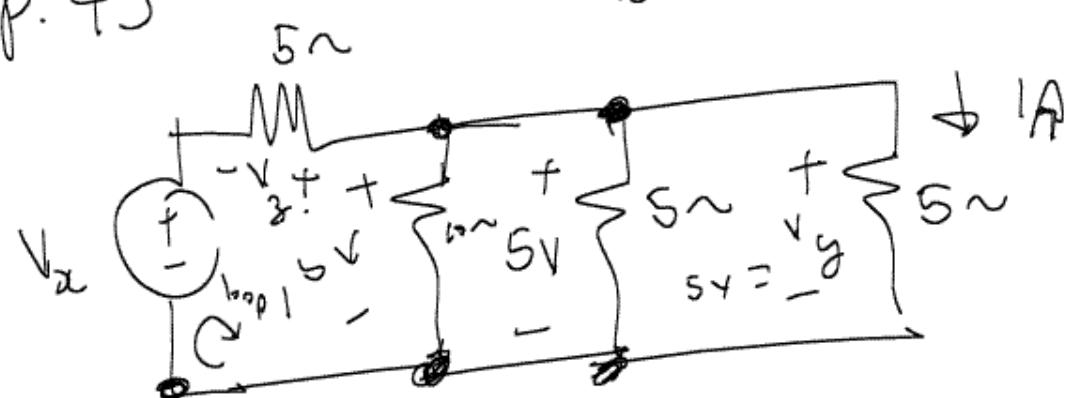

Use kvl, kcl & ohm's law to find V_x ,

[Do NOT use resistors in parallel and/or series]


Step 1: Use Ohm's law on rightmost resistor!

$$V_y + \underbrace{\begin{matrix} \downarrow \\ 5\Omega \end{matrix}}_{\text{in parallel}} I_A = V_y = (I)(5) = 5 \text{ V}$$

Step 2: Use parallel elements idea to set voltage across 10Ω as 5 V

Step 3: KVL around loop 1: $V_{2L} + V_3 - 5 = 0$

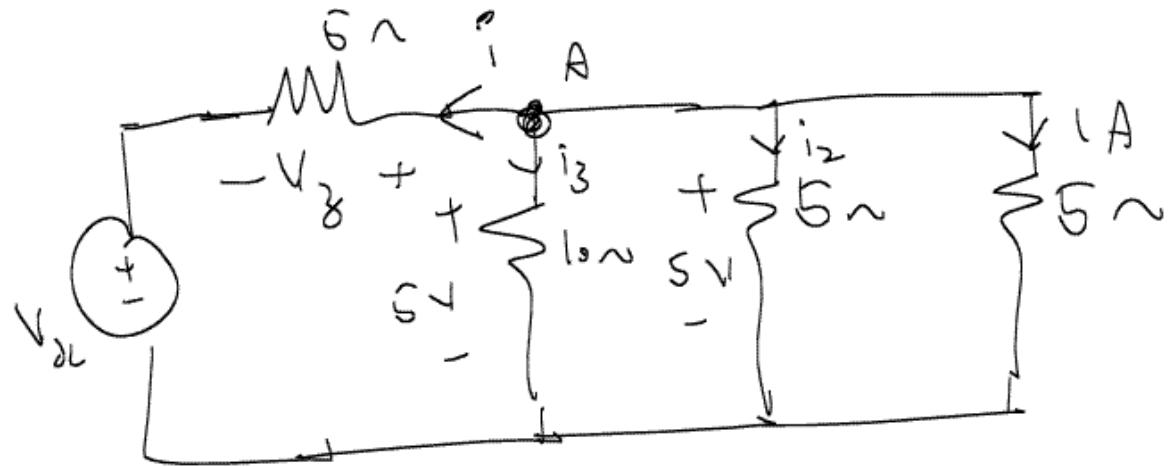We still need $V_2 \Rightarrow$ Ohm's law.




Step 4: Use KCL at node A: $i + i_3 + i_2 + 1 = 0$

$$i_2 = \frac{5V}{5\Omega} \quad (\text{Ohm's law}) = 1A$$


$$i_3 = \frac{5V}{10\Omega} \quad (\text{Ohm's law}) = 0.5A$$
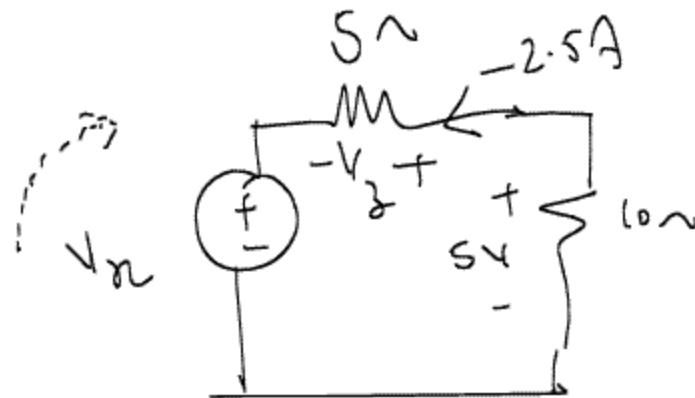
$$\therefore i = -(1 + 1 + 0.5) \Rightarrow i = -2.5A$$



$$V_y = iR \quad (\text{Ohm's law})$$
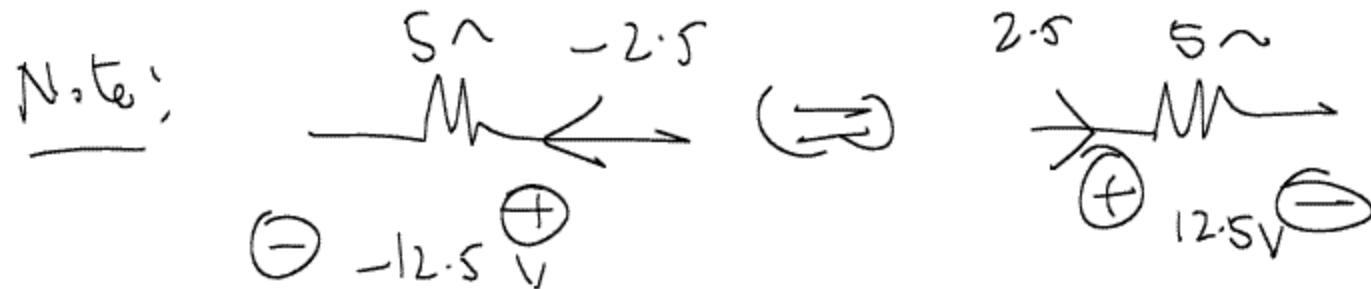
$$= (-2.5) (5) = \underline{\underline{-12.5V}}$$



$$\therefore V_x + V_y - 5 = 0 \Rightarrow \boxed{V_{oc} = 17.5 \text{ V}}$$

Next time → [D Chapter 2] READ!

(2) Intro to PSpICE

(Office hours)

START HWK #1, USE OH for
questions