# EECS 100/43 Lab 7 Strain Gauge

## 1. Objective

In this lab, you will build an op-amp amplifier circuit for a strain gauge.

## 2. Equipment

- a. Breadboard
- b. Wire cutters
- c. Wires
- d. Oscilloscope
- e. Function Generator
- f. Power supply
- g. LMC6482 op-amp
- h. Strain gauge bridge on your lab bench
- i. Various connectors for the power supply, function generator and oscilloscope
- j. Resistors (you will pick their values depending on your strain gauge)

## 3. Theory

## a. System Block Diagram

In this lab you will design a strain gauge system that you can interface to digital systems (like microcontrollers). Figure 1 shows the expected block diagram of your strain gauge system.



Figure 1. Strain Gauge block diagram

# YOU NEED TO READ THIS LAB AHEAD OF TIME SO THAT YOU CAN COME PREPARED IN LAB. IF YOU DON'T YOU WILL NOT BE ABLE TO FINISH THE LAB IN 3 HOURS!

Let us examine the blocks in figure 1 (excluding the scope).

## b. Strain Gauge

A nice description of strain gauges is in **Chapter 5** of your book. Thus, **READ**:

1. p. 155 in your book (**Practical Perspective**).

## 2. pp. 165 – 166 in your book (Section 5.6: The Difference Amplifier Circuit)

We will not be using the 4-pair strain gauge model in your book. Rather (for simplicity) we will be using only one strain gauge and build a Wheatstone bridge network out of discrete resistors. The Wheatstone bridge is also described in your book. Hence, **READ pp. 71 – 72** (Section 3.6: Measuring Resistance – The Wheatstone Bridge) in your book.

When you deflect the strain gauge, the resistance of the strain gauge changes by a very small amount (around 0.5% to 1%). First, you need to convert the resistance measurement into a voltage output and then amplify this voltage. This is the purpose of your Sensor Interface block in figure 1.

## c. Sensor Circuit

Figure 2 below shows a MultiSim screen shot of your sensor circuit. It contains two amplifiers: a difference amplifier followed by a non-inverting amplifier for additional gain.



Figure 2. The sensor interface circuit

Figure 3 shows a screen shot of the completed system in MultiSim. I also assumed a theoretical "rest" resistance of the strain gauge to be 119.4 ohms. The actual resistance in lab will vary depending on your strain gauge. Now, answer your prelab questions.



**Figure 3.** The completed Strain Gauge interface. Rstrain is the resistance of the strain gauge. For the simulation above, I have assumed the strain gauge is at rest.

Date/Author	Revision Comments
Summer 2007/Bharathwaj Muthuswamy	Typed up source documentation, organized
	lab report, typed up solutions.
Summer 2008/Bharathwaj Muthuswamy,	Modified original lab for use as a stand-
Ronnie Bajwa	alone lab. Incorporated Ronnie's idea to
	use potentiometer to adjust zero offset.

# 4. REVISION HISTORY