


## npn BJT Amplifier Stages: Common-Emitter (CE)

### 1. Bias amplifier in high-gain region

Note that the source resistor  $R_S$  and the load resistor  $R_L$  are removed for determining the bias point; the small-signal source is ignored, as well.

Use the load-line technique to find  $V_{BIAS} = V_{BE}$  and  $I_C = I_{SUP}$ .
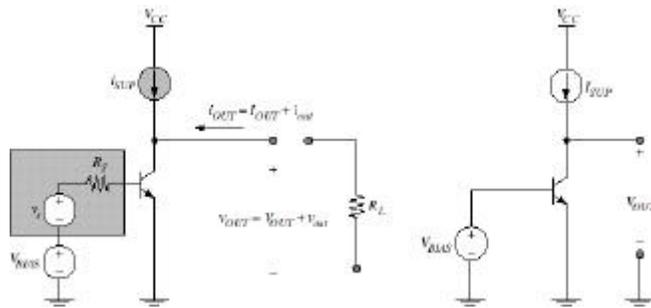
### 2. Determine two-port model parameters



## Small-Signal Model of CE Amplifier


- The small-signal model is evaluated at the bias point; we assume that the current gain is  $\beta_o = 100$  and the Early voltage is  $V_{An} = 25$  V:

$$g_m = I_C / V_{th} \text{ (at room temperature)}$$

$$r_\pi = \beta_o / g_m = 10 \text{ k}\Omega$$


$$r_o = V_{An} / I_C = 100 \text{ k}\Omega$$

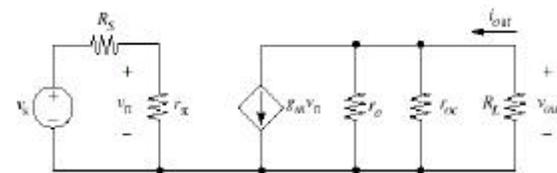- Substitute small-signal model for BJT;  $V_{CC}$  and  $V_{BIAS}$  are short-circuited for small-signals


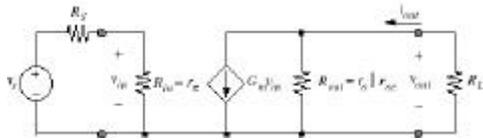
## Two-Port Model: CE Amplifier


- Use transconductance amplifier form for model (*not* mandatory)
- $R_{in} = r_{\pi}$ ,  $R_{out} = r_o \parallel r_{oc}$ ,  $G_m = g_m$  by inspection



- Compare with CS amplifier
  - inferior input resistance
  - superior transconductance
  - about the same output resistance (assuming  $r_o$  dominates)
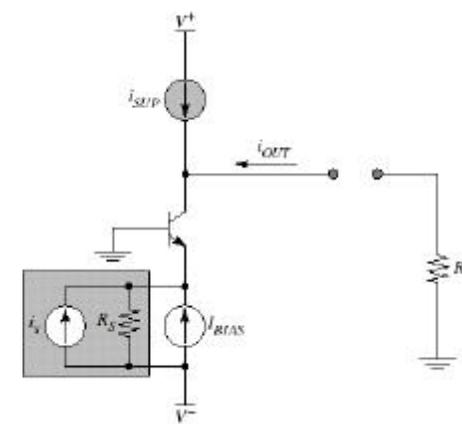
## Common-Base Amplifier

Input current is applied to the emitter (with a bias current source) and the output current is taken from the collector




## Common Base Two-Port Model

- See text for details of nodal analysis

$$R_{in} \cong 1/g_m, R_{out} \cong r_{oc} \parallel [r_o(1 + g_m(r_{\pi} \parallel R_S))], A_i = -\beta_o / (1 + \beta_o) \cong -1$$

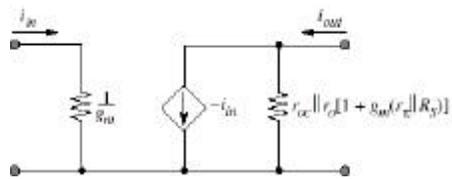- CB stage is an excellent current buffer



Comparison with the CG stage:


note the effect of the source resistance on the output resistance

if  $R_S$  is much greater than  $r_{\pi}$ , then the output resistance is approximately:

$$R_{out} \approx r_{oc} \parallel [\beta r_o]$$

## Common-Collector Amplifier

- Circuit configuration

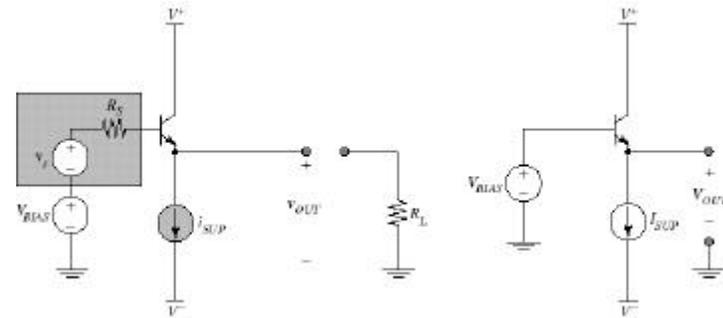

- Biasing: if transistor is "on" (i.e., not cutoff), then


$$V_{BIAS} - V_{OUT} = 0.7 \text{ V. Plot --}$$

Alternative name ... emitter follower

## Common Collector Two-Port Model

- Two-port model:

presence of  $r_\pi$  makes the analysis more involved than for a common drain

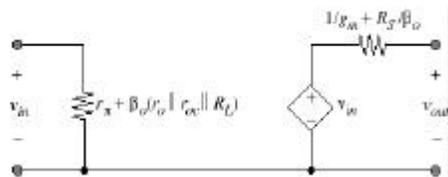

Note 1: both the input and the output resistances depend on the load and source resistances, respectively (note typo in Fig. 8.47 in text)

Note 2: this model is approximate and can give erroneous results for extremely low values of  $R_L$ . However, it is very convenient for hand analysis.


Comparison with CD stage:

CC's input resistance: high but not infinity

CC's output resistance: generally lower (but watch out for large  $R_S$ )

## Summary of BJT Single-Stage Amplifiers

Why no pnp's?

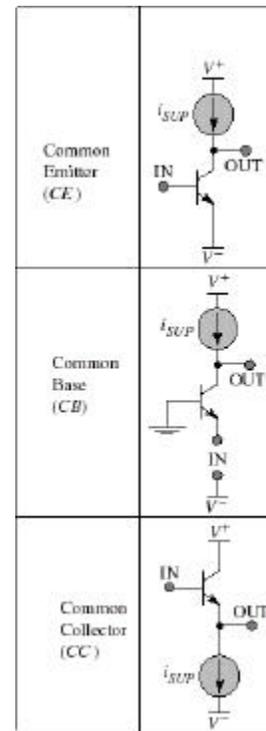

## Single-Stage MOS and BJT Amplifier


Amplifier Type	Transistor Type		
	NMOS	PMOS	BJT
Common Source/ Common Emitter (CS/CE)			
Common Gate/ Common Base (CG/CB)			
Common Drain/ Common Collector (CD/CC)			

## DC Voltage and Current Sources

- Output characteristics of a BJT or MOSFET look like a family of current sources ... how do we pick one?

specify the gate-source *voltage*  $V_{GS}$  in order to select the desired current level for a MOSFET ( specify  $V_{BE}$  exactly for a BJT)

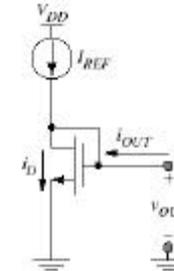how do we generate a precise voltage? ... we use a current source to set the current in a "diode-connected" MOSFET



(wait a minute ... where do we find  $I_{REF}$ ? Assume that one is available!)

$$i_D = I_{REF} + i_{OUT} \cong \left(\frac{W}{2L}\right) \mu_n C_{ox} (v_{OUT} - V_{Th})^2$$

## DC Voltage Sources


- Solving for the output voltage

$$v_{OUT} = V_{Tn} + \sqrt{\frac{I_{REF} + i_{OUT}}{\left(\frac{W}{2L}\right)\mu_n C_{ox}}}$$

If  $I_D = 100 \mu\text{A}$ ,  $\mu_n = 50 \mu\text{AV}^{-2}$ ,  $(W/L) = 20$ ,  $V_{Tn} = 1 \text{ V}$ , then


$$V_{OUT} = 1.45 \text{ V for } I_{OUT} = 0 \text{ A.}$$

- Stack up two diode-connected MOSFETs

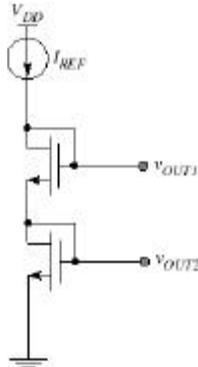
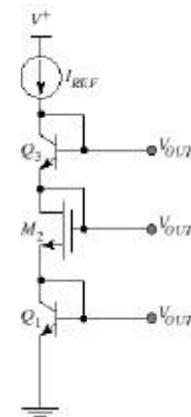
## Totem Pole Voltage Sources


- Define a series of bias voltages between the positive and the negative supply voltages.



- In practice, output currents are small (or zero), so that the DC bias voltages are set by  $I_{REF}$
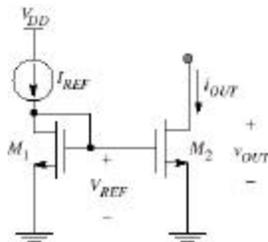
## MOSFET Current Sources

- Bias the n-channel MOSFET with a MOSFET DC voltage source!



- Intuitively,  $V_{REF}$  is set by  $I_{REF}$  and determines the output current of  $M_2$

$$V_{REF} = V_{Tn} + \sqrt{\frac{I_{REF}}{\left(\frac{W}{2L}\right)_1 \mu_n C_{ox}}} = V_{GS1} = V_{GS2}$$

Substituting into the drain current of  $M_2$  (and neglecting  $(1 + \lambda_n V_{DS2})$  term)

$$i_{OUT} = i_{D2} = \left(\frac{W}{2L}\right)_2 \mu_n C_{ox} (V_{GS2} - V_{Tn})^2$$

## MOSFET Current Sources (cont.)


- Output current is scaled from  $I_{REF}$  by a geometrical ratio:

$$i_{OUT} = i_{D2} = \left(\frac{W}{2L}\right)_2 \mu_n C_{ox} \left( V_{Tn} + \sqrt{\frac{I_{REF}}{\left(\frac{W}{2L}\right)_1 \mu_n C_{ox}}} - V_{Tn} \right)^2$$


$$I_{OUT} = \left( \frac{(W/L)_2}{(W/L)_1} \right) I_{REF}$$
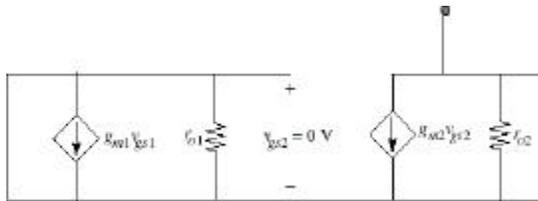
## MOSFET Current Source Equivalent Circuit

- Small-signal model: source resistance is  $r_{o2}$  by inspection



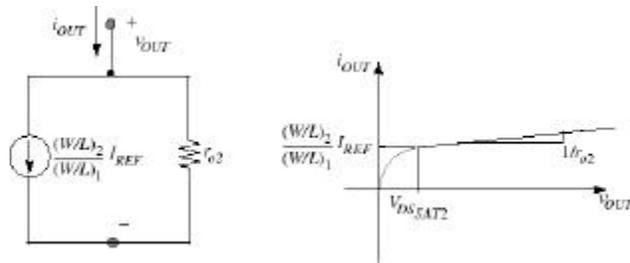
- Combine output resistance with DC output current for approximate equivalent circuit ... actual  $i_{OUT}$  vs.  $v_{OUT}$  characteristics are those of  $M_2$  with  $V_{GS2} = V_{REF}$



The model is only valid for  $v_{DS} = v_{OUT} > v_{DS(SAT)} = V_{GS} - V_{Tn}$
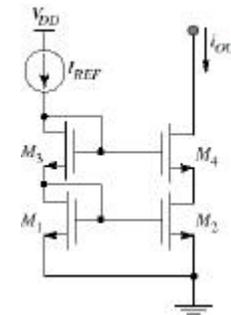
## The Cascode Current Source

- In order to boost the source resistance, we can study our single-stage building blocks and recognize that a common-gate is attractive, due to its high output resistance




- Adapting the output resistance for a common gate amplifier, the cascode current source has a source resistance of

$$r_{oc} = (1 + g_{m4}r_{o2})r_{o4} \approx g_{m4}r_{o4}r_{o2}$$

- Penalty for cascode: needs larger  $V_{OUT}$  to function
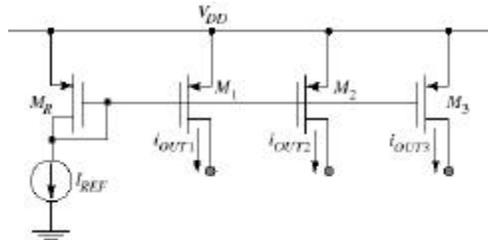
## MOSFET Current “Mirrors”

- n-channel current source *sinks* current to ground ... how do we *source* current from the positive supply? Answer: p-channel current sources...?



- By mixing n-channel and p-channel diode-connected devices, we can produce current sinks and sources from a reference current connected to  $V_{DD}$  or ground.

## Two-Port Parameters for Single-Stage Amplifiers

Amplifier Type	Controlled Source	Input Resistance $R_{in}$	Output Resistance $R_{out}$
Common Emitter	$G_m = g_m$	$r_\pi$	$r_o \parallel r_{oc}$
Common Source	$G_m = g_m$	infinity	$r_o \parallel r_{oc}$
Common Base	$A_i = -1$	$1 / g_m$	$r_{oc} \parallel [(1 + g_m(r_\pi \parallel R_S)) r_o]$ , for $g_m r_o \gg 1$
Common Gate	$A_i = -1$	$1 / g_m, (v_{sb} = 0)$ -otherwise- $1 / (g_m + g_{mb})$	$r_{oc} \parallel [(1 + g_m R_S) r_o], (v_{sb} = 0)$ -otherwise- $r_{oc} \parallel [(1 + (g_m + g_{mb}) R_S) r_o]$ both for $r_o \gg R_S$
Common Collector	$A_v = 1$	$r_\pi + \beta_o(r_o \parallel r_{oc} \parallel R_L)$	$(1 / g_m) + R_S / \beta_o$
Common Drain	$A_v = 1$ if $v_{sb} = 0$ , -otherwise- $g_m / (g_m + g_{mb})$	infinity	$1 / g_m$ if $v_{sb} = 0$ , -otherwise- $1 / (g_m + g_{mb})$


Note: appropriate two-port model is used, depending on controlled source

## Sinusoidal Function Review

Sinusoidal functions are important in analog signal processing

$$v(t) = v \cos(\omega t + \phi)$$

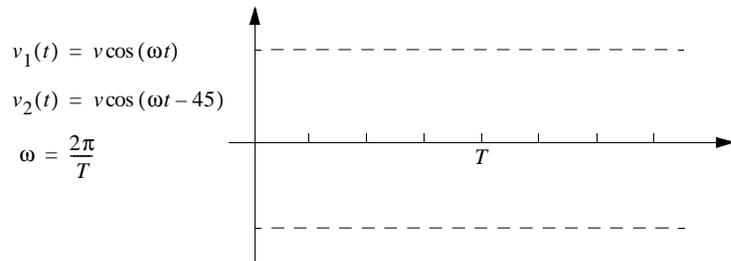amplitude (half of peak-to-peak)      frequency (radian) ...  $\omega = 2\pi f = 2\pi (1/T)$       phase (degrees or radians)




1. EECS 20/120: periodic functions can be represented as sums of sinusoids functions at different frequencies.
2. The response of a circuit to a sinusoidal input signal, as a function of the frequency, leads to insights into the behavior of the circuit.
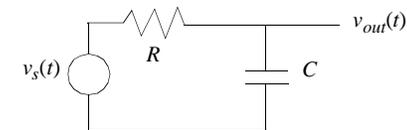
## Frequency Response

**Key concept:** small-signal models for amplifiers are *linear* and therefore, cosines and sines are solutions of the linear differential equations which arise from  $R$ ,  $C$ , and controlled source (e.g.,  $G_m$ ) networks.

- The problem: finding the solutions to the differential equations is **TEDIOUS** and provides little insight into the behavior of the circuit!



## Phasors

It is much more efficient to work with *imaginary exponentials* as “representing” the sinusoidal voltages and currents ... since these functions are solutions of linear differential equations and

$$\frac{d}{dt}(e^{j\omega t}) = j\omega(e^{j\omega t})$$

How to connect the exponential to the measured function  $v(t)$ ? Conventionally,  $v(t)$  is the real part of the of the imaginary exponential

$$v(t) = v \cos(\omega t + \phi) \rightarrow \operatorname{Re}(ve^{j(\omega t + \phi)}) = \operatorname{Re}(ve^{j\phi} e^{j\omega t})$$

where  $v$  is the amplitude and  $\phi$  is the phase of the sinusoidal signal  $v(t)$ .

The **phasor**  $V$  is defined as the complex number

$$V = ve^{j\phi}$$

Therefore, the measured function is related to the phasor by

$$v(t) = \operatorname{Re}(Ve^{j\omega t})$$

## Circuit Analysis with Phasors

- The current through a capacitor is proportional to the derivative of the voltage:

$$i(t) = C \frac{d}{dt} v(t)$$

We assume that all signals in the circuit are represented by sinusoids. Substitution of the phasor expression for voltage leads to:

$$v(t) \rightarrow Ve^{j\omega t} \quad \dots \quad Ie^{j\omega t} = C \frac{d}{dt} (Ve^{j\omega t}) = j\omega CVe^{j\omega t}$$


which implies that the ratio of the phasor voltage to the phasor current through a capacitor (the **impedance**) is

$$Z(j\omega) = \frac{V}{I} = \frac{1}{j\omega C}$$

- Implication: the phasor current is *linearly proportional* to the phasor voltage, making it possible to solve circuits involving capacitors and inductors as rapidly as resistive networks ... as long as all signals are sinusoidal.

## Phasor Analysis of the Low-Pass Filter

- Voltage divider with impedances --

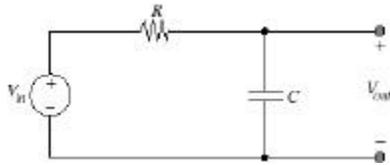

Replacing the capacitor by its impedance,  $1/(j\omega C)$ , we can solve for the ratio of the phasors  $V_{out}/V_{in}$

$$\frac{V_{out}}{V_{in}} = \frac{1/j\omega C}{R + 1/j\omega C}$$

multiplying by  $j\omega C/j\omega C$  leads to

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

## Frequency Response of LPF Circuits

The phasor ratio  $V_{out}/V_{in}$  is called the transfer function for the circuit

How to describe  $V_{out}/V_{in}$ ?

complex number ... could plot  $\text{Re}(V_{out}/V_{in})$  and  $\text{Im}(V_{out}/V_{in})$  versus frequency  
 polar form translates better into what we measure on the oscilloscope ... the magnitude (determines the amplitude) and the phase

- “Bode plots”:

magnitude and phase of the phasor ratio:  $V_{out}/V_{in}$

range of frequencies is very wide (DC to  $10^{10}$  Hz, for some amplifiers)  
 therefore, plot frequency axis on log scale

range of magnitudes is also very wide:  
 therefore, plot magnitude on log scale

Convention: express the magnitude in decibels “dB” by

$$\left| \frac{V_{out}}{V_{in}} \right|_{dB} = 20 \log \left| \frac{V_{out}}{V_{in}} \right|$$

phase is usually expressed in degrees (rather than radians):

$$\angle \frac{V_{out}}{V_{in}} = \text{atan} \left[ \frac{\text{Im}(V_{out}/V_{in})}{\text{Re}(V_{out}/V_{in})} \right]$$

## Complex Algebra Review

\* Magnitudes:

$$\frac{|Z_1|}{|Z_2|} = \frac{|Z_1|}{|Z_2|} = \frac{\sqrt{X_1^2 + Y_1^2}}{\sqrt{X_2^2 + Y_2^2}}, \text{ where}$$

$$Z_1 = X_1 + jY_1 \quad Z_2 = X_2 + jY_2$$

\* Phases:

$$\angle \frac{Z_1}{Z_2} = \angle Z_1 - \angle Z_2 = \text{atan} \frac{Y_1}{X_1} - \text{atan} \frac{Y_2}{X_2}$$

\* Examples: