 


Common-Source Amplifier

- “Common” means “grounded” or more generally, “connected to a DC supply”



What is going on with the load resistor R_L ?

DC level of the output voltage is NOT zero ... but


A “typical load” does not draw much if any DC current ... because it is non-linear and the load resistor is the load’s small-signal model!

What is a “typical load”?

DC Bias Point of the Common-Source Amplifier

For biasing, we

 1. ignore the small-signal source v_s and its small-signal resistance: $R_S \rightarrow 0 \Omega$
2. ignore the load resistor (since it’s a small-signal resistance, too): $R_L \rightarrow \text{inf. } \Omega$




Where to set V_{OUT} ?

Graphical “Load-Line” Analysis

The current through R_D must equal the drain current.


$$I_D = \frac{V_{DD} - V_{OUT}}{R_D} = I_{R_D}$$

What does this equation mean?

 

Small-Signal Model of CS Amplifier

 - Substitute parameters at operating point selected so that $V_{OUT} \approx V_{DD}/2$



- Find two-port parameters of this amplifier:
“natural” to use the transconductance form


$$R_{in} =$$

$$R_{out} =$$

$$G_m =$$

Two-Port Model of Common-Source Amplifier

 - Attach the source and load to find output current as a function of the source voltage




Infinite input resistance is ideal for a voltage input

Output resistance increases with R_D increasing, but DC drain current I_D will decrease and g_m will decrease with $I_D^{1/2}$

Current-Source Supplies

 - A current source to supply current, rather than a resistor, allows a high DC current for the device with a large incremental (small-signal) resistance




The plot of i_{SUP} vs. v_{SUP} is: (note that v_{SUP} must be positive)




Common-Source with Current Source Supply

 
- R_D is replaced with idealized current source with internal resistance



 
- For DC bias analysis, the small-signal source (with R_S) and the load resistor R_L are eliminated, along with the internal resistance r_{oc} of the current source



 Graphical Analysis of CS Amplifier with Current-Source Supply




 The region of input bias voltage V_{BIAS} for which the current source and the MOSFET are in their constant-current regions is *extremely* small



Common-Source/Current-Source Supply Models

 
- The small-signal model is identical to the resistor supply, except that the current source's internal resistance r_{oc} replaces R_D



Tradeoffs are different from case of resistor load since I_D is now decoupled from the small-signal current supply resistance r_{oc}

p-Channel Common-Source Amplifier

 
- Source of p-channel is tied to positive supply; current supply sinks I_{SUP} to ground or to lower supply



- DC bias:
Eliminate small-signal sources; control voltage is $V_{SG} = V_{DD} - V_{BIAS}$

p-Channel CS Small-Signal Model

 - p-channel MOSFET small-signal model has the source at the top



Transform this into a circuit with v_{gs} as the control voltage


Common Gate Amplifiers

- Input signal is applied to the *source*, output is taken from the *drain*

- Summary:

current gain is about unity, input resistance is low, output resistance is high

 a CG stage is a current “buffer” ... it takes a current at the input that may have a relatively small Norton equivalent resistance and replicates it at the output port, which is a good current source due to the high output resistance.




Biasing is very easy ... $I_{BIAS} = -I_{SUP}$

Note that the source can be tied to the bulk if the device is in a well.

Common-Gate Current Gain A_i

 - Small-signal circuit, with output shorted (according to the two-port procedure to find A_i)




Analysis: $i_{out} = i_d$ and $i_d = -i_g - i_s = -i_s = -i_t$

Solving for the short-circuit gain:

$$A_i = \frac{i_{out}}{i_t} = -1$$

Common-Gate Input Resistance R_{in}

 - Apply test current, with load resistor R_L present at the output



- Add the currents at the input node and set equal to the test current:

$$i_t = -g_m v_{gs} + g_{mb} v_t + \left(\frac{v_t - v_{out}}{r_o} \right)$$

- The output voltage = $-i_{out} (r_{oc} \parallel R_L) = -(-i_t)(r_{oc} \parallel R_L)$ (why?)

$$i_t = g_m v_t + g_{mb} v_t + \left(\frac{v_t - (r_{oc} \parallel R_L) i_t}{r_o} \right)$$

Input Resistance (Cont.)

- Solve for the ratio of the test voltage to the test current

$$R_{in} = \frac{v_t}{i_t} = \frac{1 + (r_{oc} \parallel R_L)/r_o}{g_m + g_{mb} + (1/r_o)}$$

the input resistance is a function of the load resistance R_L ...

- Evaluate the relative sizes of the terms:

g_m is around 500 μS

g_{mb} is around 50 μS

$1/r_o$ is around 5 μS or less, so neglect versus $g_m + g_{mb}$

current supply is usually good enough that $r_{oc} \parallel R_L \cong R_L$

$$R_{in} = \frac{v_t}{i_t} = \frac{1 + R_L/r_o}{g_m + g_{mb}}$$


What about ratio of R_L and r_o ? It depends ...

IF $R_L \ll r_o$, then we get a simpler form of the

$$R_{in} \cong \frac{1}{g_m + g_{mb}} \approx \frac{1}{g_m} \quad (\text{for } r_{oc}, r_o \gg R_L)$$

Common-Gate Output Resistance R_{out}

 - Test circuit: leave source resistance R_S of small-signal source current in place; remove r_{oc} for analysis and put it back in at the end ...



- Circuit analysis exercise:

it helps to note that $v_s = i_t R_S$

- Kirchhoff's current law at the source resistor node: sum currents leaving node

$$\frac{v_s}{R_S} - g_m v_{gs} - (-g_{mb} v_s) + \frac{v_s - v_t}{r_o} = 0$$

$$v_s \left(\frac{1}{R_S} + g_m + g_{mb} + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

- Substituting $v_t = i_t R_S$ and solving for the output resistance = $(v_t / i_t) \parallel r_{oc}$

$$R_{out} = r_{oc} \parallel \left((R_S [r_o/R_S + g_m r_o + g_{mb} r_o + 1]) \right)$$

... quite a mess

Common-Gate Output Resistance (Cont.)

- The output resistance is a function of the source resistance R_S
see Appendix to Chapter 8 for an analysis of the error in using the two-port approach for the common-gate amplifier

- Evaluate the relative sizes of the terms:

g_m is around $500 \mu\text{S}$

g_{mb} is around $50 \mu\text{S}$

r_o is around $200 \text{ k}\Omega$

$g_m r_o = (0.5)(200) = 100 \gg 1$

- Simplifying


$$R_{out} \cong r_{oc} \parallel [(r_o + (g_m r_o + g_{mb} r_o) R_S)] = r_{oc} \parallel [r_o (1 + (g_m + g_{mb}) R_S)]$$

If we neglect the backgate generator ($g_{mb} \ll g_m$)

$$R_{out} \cong r_{oc} \parallel [r_o (1 + (g_m R_S))]$$

- The output resistance of the common-gate can be *very* large ... on the order of 100 times r_o ... if the current supply's resistance is large enough not to limit it.

Common-Gate Two-Port Model

 


Design tradeoffs:

Ideal current buffer has $R_{in} = 0 \Omega$: need to increase g_m to approach this goal

Also, an ideal current buffer has $R_{out} = \text{infinity } \Omega$:

increase $g_m r_o$... and use a good current supply with a large r_{oc}


P-Channel Common Gate Amplifier

 

Small-signal model is identical to n-channel version

Common-Drain Amplifier

 - Also called a “source follower” for reasons that will become clear shortly



For DC bias, neglect small signal source (and its resistance) and the small-signal load resistance; $i_{SUP} = I_{SUP}$


Note that

$$V_{OUT} = V_{BIAS} - V_{GS}$$

The DC gate-source voltage is:

DC Transfer Curve

 
p-well CMOS process means that the source and bulk can be shorted ... not true for an n-well process.



The threshold voltage V_{Tn} is not a constant, since the source-bulk voltage V_{SB} increases as V_{OUT} increases:

$$V_{Tn} = V_{TO_n} + \gamma_n \left[\sqrt{(V_{OUT} - V^-) - 2\phi_p} - \sqrt{2\phi_p} \right]$$

DC Transfer Curve for Common-Drain Amps

 


Simple idea: slope of transfer curve is the voltage gain ... about 1

The common-drain is a *voltage buffer*

$$A_v = \frac{dv_{OUT}}{dv_{BIAS}} \approx 1$$

Common-Drain Open-Circuit Voltage Gain

 For finding A_v exactly, remove the source and its resistance and the load resistance ... apply a test voltage and find the output voltage



KCL at source node:


$$\frac{v_{out}}{r_{oc} \parallel r_o} - g_m(v_t - v_{out}) - (-g_{mb}v_{out}) = 0$$

$$v_{out} \left(\frac{1}{r_{oc} \parallel r_o} + g_m + g_{mb} \right) = g_m v_t$$

$$A_v = \frac{v_{out}}{v_t} = \frac{g_m}{g_m + g_{mb} + \left(\frac{1}{r_{oc} \parallel r_o} \right)} \approx \frac{g_m}{g_m + g_{mb}}$$

Output Resistance of Common-Drain Amplifier

 - Leave the source resistance attached while exercising the output with a test voltage



KCL at the source node ... remove $r_o \parallel r_{oc}$ and put it back in

$$i_t + g_m(0 - v_t) + (-g_{mb}v_t) = 0$$


$$R_{out} = (r_o \parallel r_{oc}) \parallel \left(\frac{v_t}{i_t} \right) = (r_o \parallel r_{oc}) \parallel \left(\frac{1}{g_m + g_{mb}} \right) = \frac{1}{[1/(r_o \parallel r_{oc})] + g_m + g_{mb}}$$

Typically, $r_o \parallel r_{oc} \gg g_m + g_{mb}$

$$R_{out} \cong \frac{1}{g_m + g_{mb}}$$

Common-Drain Small-Signal Model

 Input resistance is infinite: open-circuit from gate-source



If source and bulk can be shorted (possible for a MOSFET in a well), then the gate is essentially 1 (since backgate generator has zero v_{sb} controlling it.)

Output resistance is ideally zero for a voltage-output amplifier: typical values


$$g_m = 500 \mu\text{S}$$

$$g_{mb} = 50 \mu\text{S}$$

$$R_{out} = \frac{1}{g_m + g_{mb}} \approx 2 \text{ k}\Omega$$

The output resistance can be reduced by increasing the transconductance ... (W/L) can be made huge in order to drive R_{out} toward zero.

Summary of MOSFET Two-Port Models

 

Assessment of MOS Amplifiers

Common-source is the only stage that provides gain

Common-gate can buffer a poor current source into a nearly ideal one

Common-drain can buffer a poor voltage source into a nearly ideal one

We need more than one stage to approach an ideal amplifier (of any of the 4 types)