

EE105 – Fall 2014

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)




Lecture14-Frequency Response

1



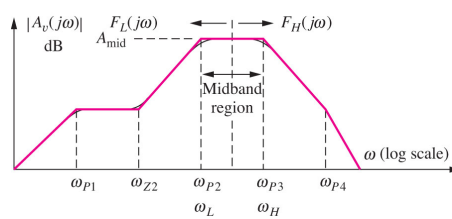Amplifier Frequency Response Transfer Function Analysis



$$F_L(s) = \frac{(s + \omega_{Z1}^L)(s + \omega_{Z2}^L) \cdots (s + \omega_{Zk}^L)}{(s + \omega_{P1}^L)(s + \omega_{P2}^L) \cdots (s + \omega_{Pk}^L)}$$

$$F_H(s) = \frac{\left(1 + \frac{s}{\omega_{Z1}^H}\right) \left(1 + \frac{s}{\omega_{Z2}^H}\right) \cdots \left(1 + \frac{s}{\omega_{Zl}^H}\right)}{\left(1 + \frac{s}{\omega_{P1}^H}\right) \left(1 + \frac{s}{\omega_{P2}^H}\right) \cdots \left(1 + \frac{s}{\omega_{Pl}^H}\right)}$$

$$A_v(s) = \frac{N(s)}{D(s)} = \frac{a_0 + a_1s + a_2s^2 + \cdots + a_ms^m}{b_0 + b_1s + b_2s^2 + \cdots + b_ns^n}$$

$$A_v(s) = A_{mid} F_L(s) F_H(s)$$

A_{mid} is the midband gain between the lower and upper cutoff frequencies ω_L and ω_H .

$$|F_H(j\omega)| \rightarrow 1 \text{ for } \omega \ll \omega_{Zj}^H, \omega_{Pj}^H, j = 1 \dots l$$

$$\therefore A_L(s) \cong A_{mid} F_L(s)$$

$$|F_L(j\omega)| \rightarrow 1 \text{ for } \omega \gg \omega_{Zj}^L, \omega_{Pj}^L, j = 1 \dots k$$

$$\therefore A_H(s) \cong A_{mid} F_H(s)$$




Lecture14-Frequency Response

2



Low Frequency Dominant Pole Approximation

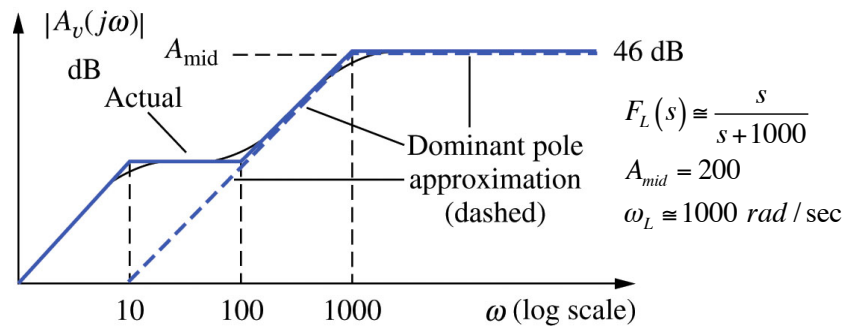- A **Dominant Pole** exists if one of the low frequency poles is much larger than the others.
 - In the graph below case $\omega = 1000$ rad/sec is a dominant pole. All other poles and zeros are at low enough frequencies that they do not affect the lower cutoff frequency ω_L .



Lower Cutoff Frequency Calculations

If there is no dominant pole at low frequencies, the poles and zeros interact to determine the lower cutoff frequency ω_L .

For example, suppose:

$$A_L(s) = A_{mid} F_L(s) = A_{mid} \frac{(s + \omega_{z1})(s + \omega_{z2})}{(s + \omega_{p1})(s + \omega_{p2})}$$

$$\text{For } s = j\omega_L, |A_L(j\omega_L)| = \frac{A_{mid}}{\sqrt{2}}$$

$$\frac{1}{\sqrt{2}} = \frac{(\omega_L^2 + \omega_{z1}^2)(\omega_L^2 + \omega_{z2}^2)}{(\omega_L^2 + \omega_{p1}^2)(\omega_L^2 + \omega_{p2}^2)}$$

$$\frac{1}{2} = \frac{\omega_L^4 + (\omega_{z1}^2 + \omega_{z2}^2)\omega_L^2 + \omega_{z1}^2\omega_{z2}^2}{\omega_L^4 + (\omega_{p1}^2 + \omega_{p2}^2)\omega_L^2 + \omega_{p1}^2\omega_{p2}^2}$$

Lower cutoff frequency ω_L will be greater than all the individual pole zero frequencies.

$$\therefore \omega_L \approx \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$

In general, for n poles and n zeros,

$$\omega_L \approx \sqrt{\sum_n \omega_{pn}^2 - 2 \sum_n \omega_{zn}^2}$$



Dominant Pole Example

- **Problem:** Find midband gain, $F_L(s)$ and f_L for

$$A_L(s) = 2000 \frac{s \left(\frac{s}{100} + 1 \right)}{(0.1s + 1)(s + 1000)}$$

- **Analysis:** Rearranging the given transfer function into standard form,

$$A_L(s) = 200 \frac{s(s+100)}{(s+10)(s+1000)} = A_{mid} F_L(s) \rightarrow A_{mid} = 200 \quad F_L(s) = \frac{s(s+100)}{(s+10)(s+1000)}$$

Zeros: $s = 0$ and $s = -100$ Poles: $s = -10$ and $s = -1000$

The poles and zeros are all widely separated. $\therefore A_L(s) \cong 200 \frac{s}{s+1000}$

The dominant pole is at $\omega = 1000$ and $f_L \cong \frac{1000}{2\pi} = 159 \text{ Hz}$.

The more exact calculation is $f_L = \frac{1}{2\pi} \sqrt{10^2 + 1000^2 - 2 \times 0^2 - 2 \times 100^2} = 158 \text{ Hz}$



High-Frequency Dominant Pole

- The lowest of all high frequency poles is called the dominant high-frequency pole.

$$A_H(s) \cong A_{mid} F_H(s)$$

$$F_H(s) \cong \frac{1}{1 + (s/\omega_{p3})} \quad \omega_H \cong \omega_{p3}$$

$$\frac{1}{\sqrt{2}} = \sqrt{\frac{1 + \left(\frac{\omega_H}{\omega_{z1}}\right)^2}{1 + \left(\frac{\omega_H}{\omega_{p1}}\right)^2} \frac{1 + \left(\frac{\omega_H}{\omega_{z2}}\right)^2}{1 + \left(\frac{\omega_H}{\omega_{p2}}\right)^2}}$$

- If there is no dominant pole at high frequencies, the poles and zeros interact to determine ω_H .

$$A_H(s) = A_{mid} F_H(s) = A_{mid} \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$\text{For } s = j\omega_H, |A_{mid}(j\omega_H)| = \frac{A_{mid}}{\sqrt{2}}$$


$$\frac{1}{\omega_H} \cong \sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} - \frac{2}{\omega_{z1}^2} - \frac{2}{\omega_{z2}^2}}$$

For the general case of n poles and n zeros,

$$\frac{1}{\omega_H} \cong \sqrt{\sum_n \frac{1}{\omega_{pn}^2} - 2 \sum_n \frac{1}{\omega_{zn}^2}}$$



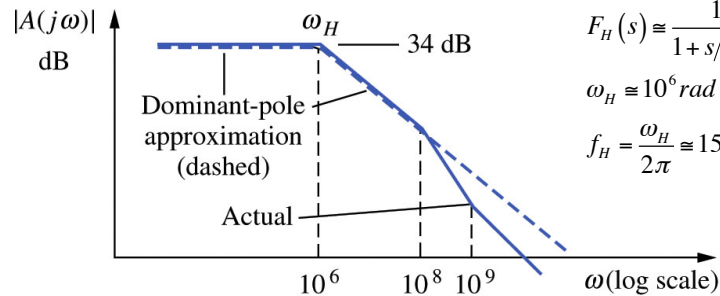High Frequency Dominant Pole Approximation



$$A_H(s) = A_{mid} F_H(s)$$

$$A_{mid} = 200$$



$$F_H(s) \approx \frac{1}{1 + s/10^6} = \frac{10^6}{s + 10^6}$$

$$\omega_H \approx 10^6 \text{ rad/sec}$$

$$f_H = \frac{\omega_H}{2\pi} \approx 159 \text{ kHz}$$



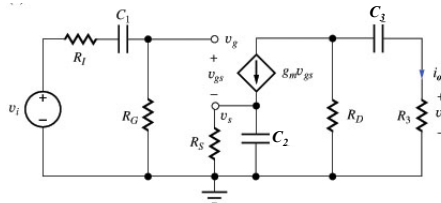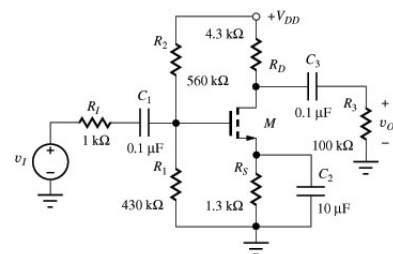Low-Frequency Poles and Zeros Direct Calculation: C-S Amplifier



$$V_o(s) = I_o(s) R_3 = -g_m V_{gs}(s) \frac{R_D}{R_D + (1/sC_3) + R_3} R_3$$

$$V_o(s) = -g_m (R_D \parallel R_3) \frac{s}{s + \frac{1}{C_3(R_D + R_3)}} V_{gs}(s)$$

$$V_{gs}(s) = \frac{sC_1 R_G}{sC_1(R_G + R_S) + 1} V_i(s)$$

$$\text{Node Eq. at Source: } g_m(V_g - V_s) = \frac{V_s}{R_S} + sC_2 V_s$$

$$V_{gs}(s) = V_g - V_s = \frac{s + \frac{1}{R_S C_2}}{s + \frac{1}{\left(\frac{1}{g_m} \parallel R_S\right) C_2}} V_g(s)$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = A_{mid} F_L(s)$$

$$A_{mid} = -g_m (R_D \parallel R_3) \frac{R_G}{R_I + R_G}$$



Low-Frequency Poles and Zeros Direct Calculation: C-S Amplifier (cont.)

$$F_L(s) = \frac{s^2 \left(s + \frac{1}{R_S C_2} \right)}{\left[s + \frac{1}{(R_I + R_G) C_1} \right] \left[s + \frac{1}{(1/g_m \parallel R_S) C_2} \right] \left[s + \frac{1}{(R_D + R_3) C_3} \right]}$$

The three zero locations are: $s = 0, 0, -1/R_S C_2$

The three pole locations are: $s = -\frac{1}{(R_I + R_G) C_1}, -\frac{1}{(1/g_m \parallel R_S) C_2}, -\frac{1}{(R_D + R_3) C_3}$

Each independent capacitor in the circuit contributes one pole and one zero. Series capacitors C_1 and C_3 contribute the two zeros at $s = 0$ (dc), blocking propagation of dc signals through the amplifier. The third zero due to the parallel combination of C_2 and R_S occurs at frequency where signal current propagation through the MOSFET is blocked (output voltage is zero).

