

EE105 – Fall 2014

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)




Lecture16-High Frequency Transistor Model

1



BJT Unity-Gain and Beta-Cutoff Frequencies

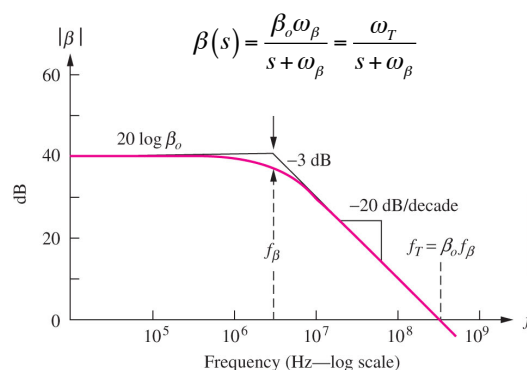- The current gain of the transistor decreases as the frequency increases and can be modeled by a single-pole transfer function.



$$\beta(s) = \frac{\beta_o \omega_\beta}{s + \omega_\beta} = \frac{\omega_T}{s + \omega_\beta}$$

The "beta-cutoff frequency" of the BJT is called f_β :

$$|\beta(j\omega_\beta)| = \frac{\beta_o}{\sqrt{2}} \quad (-3 \text{ dB pt.})$$

The "unity-gain frequency" is referred to as f_T :

$$|\beta(j\omega_T)| = 1 \quad (0 \text{ dB})$$

The two frequencies are related:

$$\omega_T = \beta_o \omega_\beta$$




Lecture16-High Frequency Transistor Model

2



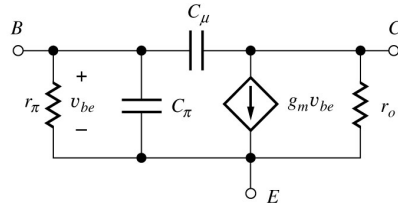Frequency-Dependent Transistor Models Hybrid-Pi Model for the BJT



C_μ is the capacitance of the reverse-biased collector-base diode:

$$C_\mu = \frac{C_{\mu o}}{\sqrt{1 + (V_{CB}/\phi_{jc})}}$$

The frequency dependence of the BJT in forward-active region can be modeled by adding capacitors C_μ and C_π to the hybrid-pi model.

C_π models the change in base minority carrier charge as the base-emitter voltage of the transistor changes:

$$C_\pi = g_m \tau_F$$

where τ_F is the forward base transit-time of the transistor, the time a carrier takes to cross the base region. For BJT,

$$\tau_F = \frac{Q}{i_T} = \frac{W_B^2}{2D_n}, \quad \text{where}$$

W_B is the base width,

D_n is the diffusion coefficient




Lecture16-High Frequency Transistor Model

3



Beta-cutoff Frequency (ω_β) of BJT

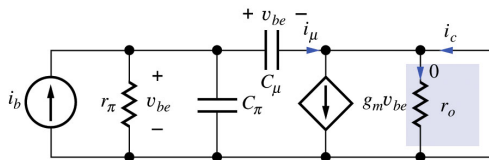

We calculate the cutoff frequency for the short-circuit current gain using the circuit model given here.

$$\beta(s) = I_c(s)/I_b(s)$$

$$I_c(s) = (g_m - sC_\mu)V_{be}(s)$$

$$V_{be}(s) = I_b(s) \frac{r_\pi}{s(C_\pi + C_\mu)r_\pi + 1}$$

$$\beta(s) = \beta_o \frac{1 - sC_\mu/g_m}{s(C_\pi + C_\mu)r_\pi + 1}$$

The right-half plane transmission zero $\omega_z = +g_m/C_\mu$ occurring at high frequency (above ω_T) can be neglected.

$$\therefore \beta(s) \cong \frac{\beta_o}{s(C_\pi + C_\mu)r_\pi + 1} = \frac{\beta_o}{(s/\omega_\beta) + 1}$$

where $\omega_\beta = 1/(r_\pi(C_\pi + C_\mu))$ is the beta-cutoff frequency




Lecture16-High Frequency Transistor Model


4



Unity-gain Frequency (ω_T) of BJT

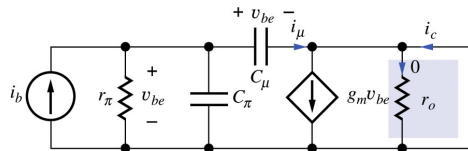

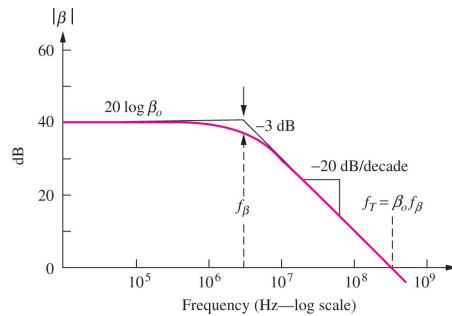We can rearrange the current gain expression to expose the unity-gain frequency ω_T of the transistor.



$$\beta(s) \approx \frac{\beta_o}{\left(\frac{s}{\omega_\beta} + 1\right)} = \frac{\beta_o \omega_\beta}{s + \omega_\beta} = \frac{\omega_T}{s + \omega_\beta}$$

$$\omega_\beta = \frac{1}{r_\pi (C_\pi + C_\mu)}$$

$$\omega_T = \beta_o \omega_\beta = \frac{g_m}{C_\pi + C_\mu}$$

$$f_T = \frac{\omega_T}{2\pi}$$





Lecture16-High Frequency Transistor Model

5



High-frequency Model for the MOSFET

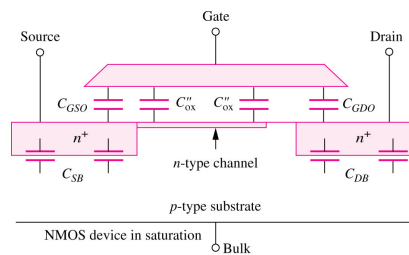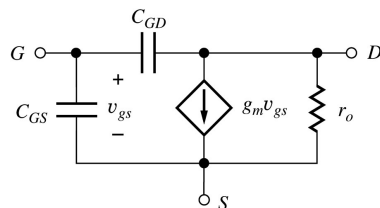At frequencies above dc, the input resistance and current gain of the MOSFET is no longer infinite. The pi-model for the MOSFET includes the gate-source and gate-drain capacitors C_{GS} and C_{GD} .



$$C_{GS} = \frac{2}{3} C_{GC} + C_{GSO} W \quad C_{GD} = C_{GDO} W \quad \text{where} \quad C_{GC} = C_{OX}^* WL$$




Lecture16-High Frequency Transistor Model

6



Unity-gain Frequency for the MOSFET

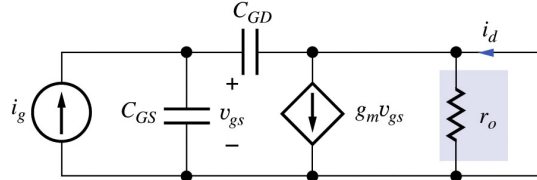The short-circuit current gain and unity-gain frequency of the MOSFET are calculated in a manner similar to the BJT.



$$\beta(s) = \frac{I_d(s)}{I_g(s)}$$

$$\omega_T = \frac{g_m}{C_{GS} + C_{GD}}$$

$$\beta(s) = \frac{g_m}{s(C_{GS} + C_{GD})} \left(1 - s \frac{C_{GD}}{g_m} \right)$$

$$\beta(s) \approx \frac{g_m}{s(C_{GS} + C_{GD})} = \frac{\omega_T}{s}$$

$$\omega_T \approx \frac{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})}{(2/3) C_{ox} WL} = \frac{3}{2} \mu_n \frac{(V_{GS} - V_{TN})}{L^2}$$




Lecture16-High Frequency Transistor Model

7



Limitations of High-frequency Models

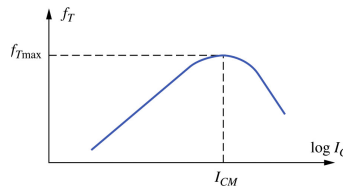- Above $0.3 f_T$, behavior of simple pi-models begins to deviate significantly from the actual device.
- Also, ω_T depends on operating current as shown below and is not constant as assumed in the earlier slides.
- For given BJT, a collector current I_{CM} exists that yields f_{Tmax} .



- For the FET in saturation, C_{GS} and C_{GD} are independent of Q-point current, so

$$\omega_T \propto g_m \propto \sqrt{I_D}$$




Lecture16-High Frequency Transistor Model

8



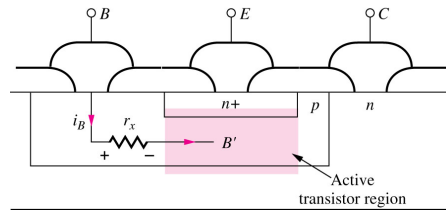Bipolar Transistor Model Base Resistance r_x



Base current enters the BJT through the external base contact and traverses a high resistance region before entering active area. Resistor r_x models the voltage drop between the base contact and the active area of the BJT.

