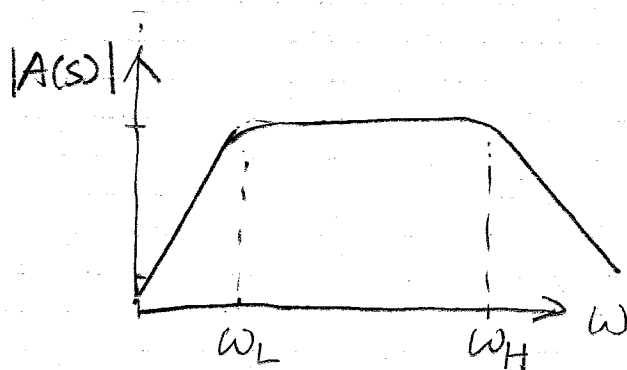


High Frequency Response of CE Amplifiers




$$A(s) = A_{mid} F_L(s) F_H(s)$$

The low frequency response $F_L(s)$ is primarily determined by the bypass and coupling capacitors.

The high frequency response $F_H(s)$ is primarily determined by the intrinsic capacitances of the transistors, such as


$$\begin{cases} C_{\pi}, C_{\mu} \text{ in BJT} & \text{(typically in pF)} \\ C_{gs}, C_{gd} \text{ in MOS} & \text{(typically } < \text{ nF)} \end{cases}$$

Common-Emitter (CE) amplifier

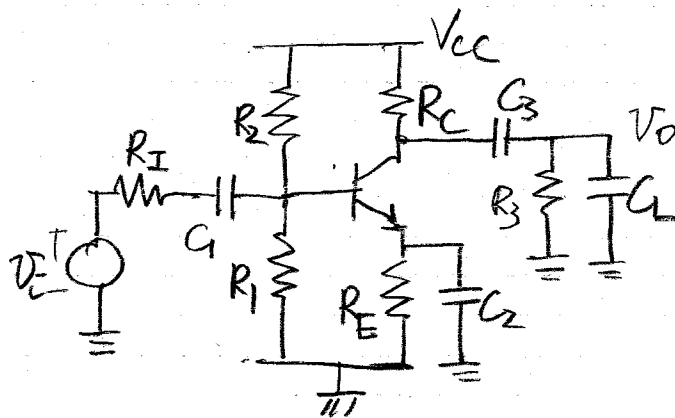

High-frequency equivalent ckt

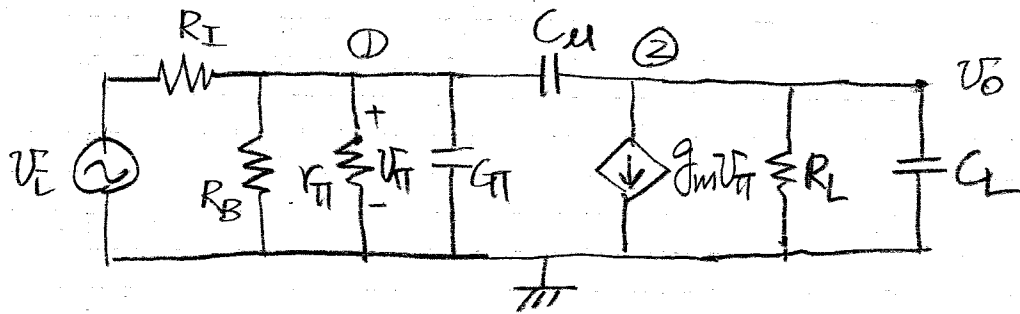- ① Replace C_1, C_2, C_3 by short ckt
- ② Use high-frequency hybrid- π model for BJT



$$R_B = R_I \parallel R_2$$

$$R_L = r_o \parallel R_C \parallel R_3$$

(I) Brute Force solution

Solve the ckt by KVL, KCL

$$\text{KCL @ ①: } \frac{V_\pi - V_E}{R_I} + \frac{V_\pi}{R_B \parallel r_\pi} + V_\pi s C_\pi + (V_\pi - V_O) s C_\mu = 0 \quad (3)$$

$$\text{KCL @ ②: } (V_O - V_\pi) s C_\mu + g_m V_\pi + \frac{V_O}{R_L} + s C_L V_O = 0 \quad (4)$$

$$\text{From (4) } V_O (s C_\mu + s C_L + \frac{1}{R_L}) = -V_\pi (g_m - s C_\mu)$$

$$\text{From (3) } V_\pi \left(\frac{1}{R_I \parallel R_B \parallel r_\pi} + s C_\pi + s C_\mu \right) = V_O s C_\mu + \frac{V_E}{R_I}$$

$$\text{Let } R_I \parallel R_B \parallel r_\pi = R'$$

$$\Rightarrow V_O \left(\frac{1}{R_L} + s(C_\mu + C_L) \right) = \frac{-(g_m - s C_\mu) \left(s C_\mu V_O + \frac{V_E}{R_I} \right)}{\frac{1}{R'} + s(C_\pi + C_\mu)}$$

$$\Rightarrow A(s) = \frac{V_O}{V_E} = -g_m R_L \frac{R'}{R_I} \frac{(1 - s \frac{C_\mu}{g_m})}{f(s)}$$

$$f(s) = 1 + s [R' (C_\pi + C_\mu + g_m R_L C_\mu) + R_L (C_\mu + C_L)] + s^2 [R_L R' (C_\mu C_\pi + C_L C_\pi + C_L C_\mu)]$$

$$F_H(s) = \frac{1 + \frac{s}{\omega_z}}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

$$\text{RHP zero} \approx \omega_z = \frac{g_m}{C_{eq}} > \omega_T = \frac{g_m}{C_u + C_T}$$

much higher than ω_T ($\because C_T \gg C_u$)
 \Rightarrow ignore

Assume there is a dominant pole.

$$\begin{aligned} D(s) &= (1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}}) \\ &= 1 + s(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}) + \frac{s^2}{\omega_{p1}\omega_{p2}} \end{aligned}$$

$$\omega_{p2} \gg \omega_{p1}$$

$$\frac{1}{\omega_{p2}} \ll \frac{1}{\omega_{p1}}$$

$$D(s) \approx 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}} = 1 + A_1 s + A_2 s^2$$

$$\Rightarrow \omega_{p1} = \frac{1}{A_1} = \left[R'(C_T + (1 + g_m R_L)C_u) + R_L(C_u + C_L) \right]^{-1}$$

$$\omega_{p2} = \frac{1}{A_2/A_1} = \frac{A_1}{A_2} = \frac{R'(C_T + (1 + g_m R_L)C_u) + R_L(C_u + C_L)}{R_L R' (C_u C_T + C_L C_T + C_L C_u)}$$

Need to verify $\omega_{p2} \gg \omega_{p1}$

If we assume $C_T \gg C_u, C_L$

$$\omega_{p2} \approx \frac{R'(1 + g_m R_L)C_u}{R_L R' C_T C_u} \approx \frac{g_m}{C_T} > \omega_T = \frac{g_m}{C_u + C_T}$$

The dominant pole ω_{p1}

$$\frac{1}{\omega_{p1}} = R' C_T + R'(1 + g_m R_L)C_u + R_L(C_u + C_L)$$

: Sum of RC times.

Open-Circuit Time Constant (OCTC) Method
Approximation to quickly find dominant pole
in high frequency response.

$$F_H(s) = \frac{(1 + \frac{s}{\omega_{z1}})(1 + \frac{s}{\omega_{z2}})(\dots)}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})(\dots)} = \frac{1 + a_1 s + a_2 s^2 + \dots}{1 + b_1 s + b_2 s^2 + \dots}$$

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{i=1}^{n_p} T_{pi}$$

Through network theory, one can prove

$$\sum_{i=1}^{n_p} T_{pi} = \sum_j R_{j0} G_j$$

G_j = capacitors in H.F. circuit


R_{j0} : resistances measured at terminals
of G_j , with other capacitors
open-circuited,
and all independent voltage sources
short-circuited,
all independent current sources
open-circuited.

Now use dominant pole approximation:


$$b_1 \approx \frac{1}{\omega_H}$$

$$\omega_H = \frac{1}{b_1} = \frac{1}{\sum_j R_{j0} G_j}$$


OCTC analysis of CE amplifier

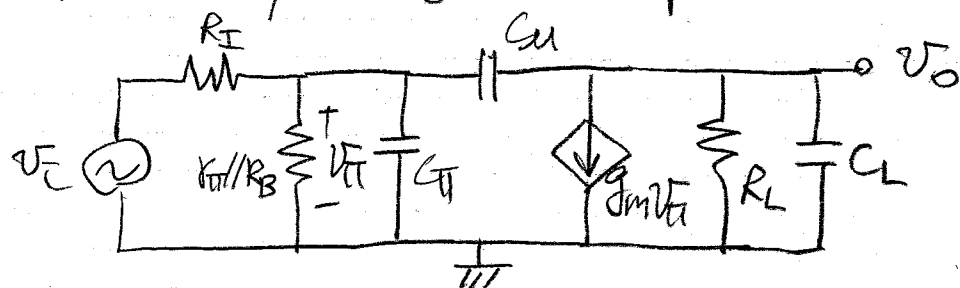
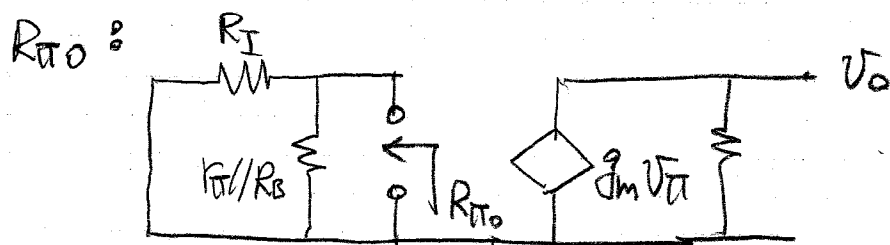
$$\omega_H = \frac{1}{R_{\pi 0} C_{\pi} + R_{u0} C_{\mu} + R_{L0} C_L}$$


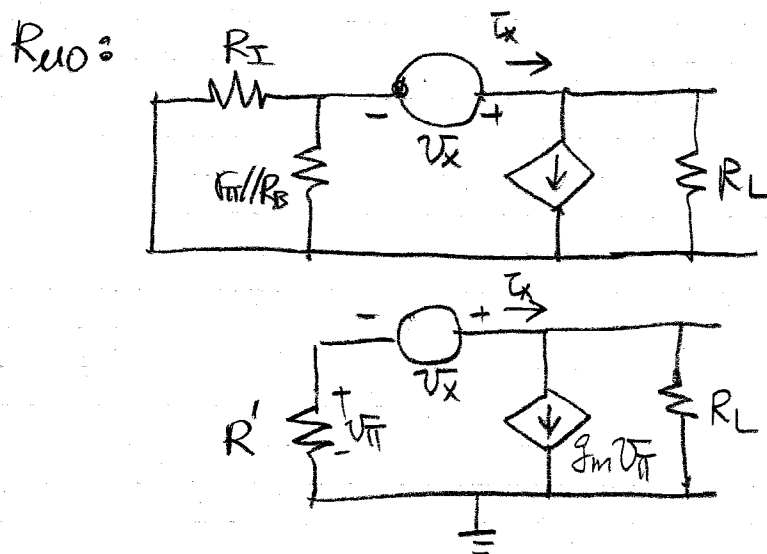
$$R_{\pi 0} = r_{\pi} // R_B // R_I = R'$$




$$v_{\pi} = -i_x R'$$

$$\text{KCL: } i_x = g_m v_{\pi} + (v_{\pi} + v_x) / R_L$$

$$i_x = \frac{1}{R_L} (1 + g_m R_L) v_{\pi} + \frac{v_x}{R_L}$$

$$[R_L + R' (1 + g_m R_L)] i_x = v_x$$

$$R_{u0} = R_L + R' (1 + g_m R_L)$$

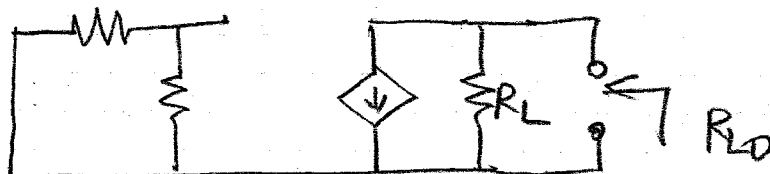R_{Lo} :


$$v_T = 0 \quad g_m v_T = 0$$

$$R_{Lo} = R_L$$

$$\Rightarrow \omega_H = \frac{1}{R' C_{\pi} + (R_L + R'(1 + g_m R_L)) C_{e1} + R_L C_L}$$

Same as brute force solution!
But much easier to analyze.


Miller Effect

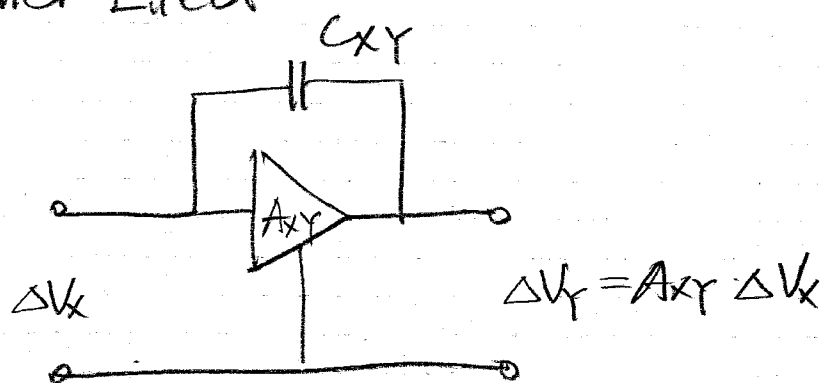

$$C = \frac{\Delta Q}{\Delta V}$$

$$\Delta Q = C_{xy} (\Delta V_x - \Delta V_y) = C_{xy} (1 - A_{xy}) \cdot \Delta V_x$$

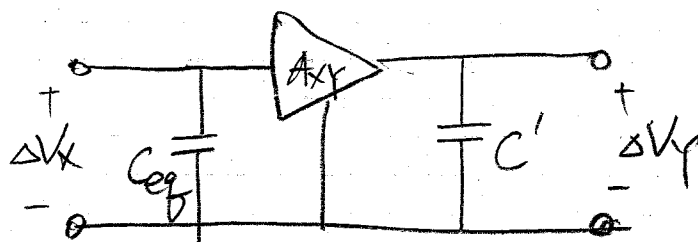Can be considered as an equivalent capacitance on the input side:





$$C_{eq} = (1 - A_{xy}) C_{xy} \Rightarrow \text{called "Miller Capacitance"}$$

On the output side

$$\Delta Q = C_{xy} (\Delta V_y - \Delta V_x) = C_{xy} (1 - \frac{1}{A_{xy}}) \cdot \Delta V_y$$

$$\Rightarrow C' = (1 - \frac{1}{A_{xy}}) C_{xy}$$

CE Amplifier

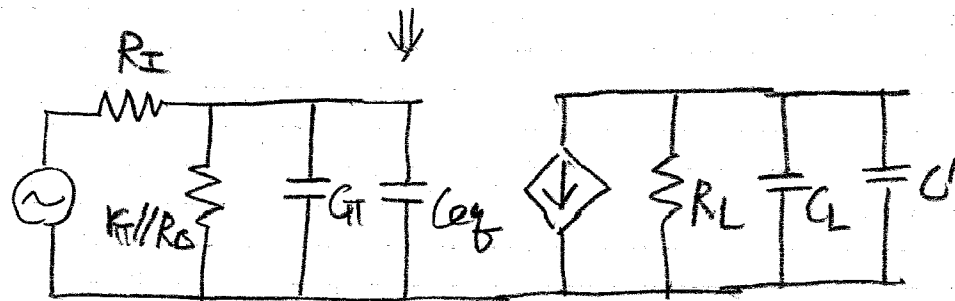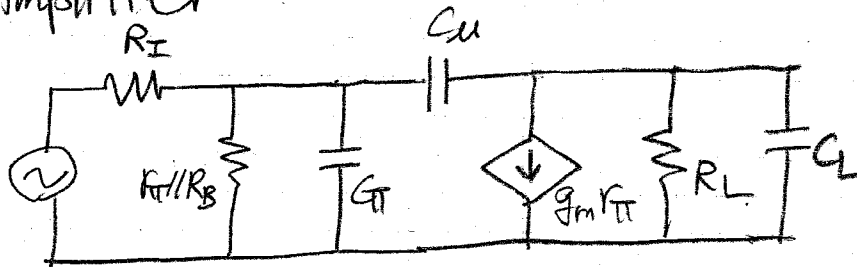

$$C_{eq} = (1 - A_{xy}) C_{\mu} = (1 - (-g_m R_L)) C_{\mu} \\ = (1 + g_m R_L) C_{\mu}$$

$$C' = (1 - \frac{1}{A_{xy}}) C_{\mu} = (1 + \frac{1}{g_m R_L}) C_{\mu} \approx C_{\mu}$$

$$A(s) = \frac{Y_{\pi} // R_B}{R_I + Y_{\pi} // R_B} (-g_m R_L) \cdot \frac{1}{[1 + sR'(C_{\pi} + C_{eq})][1 + sR_L(C_L + C')]}$$

$$R' = R_I // Y_{\pi} // R_B$$

Dominant pole

$$\omega_H = \frac{1}{R'(C_{\pi} + C_{eq}) + R_L(C_L + C')}$$

$$= \frac{1}{R'(C_{\pi} + (1 + g_m R_L) C_{\mu}) + R_L(C_L + C_{\mu})}$$

Same as brute force
OCTC