

EE105 – Fall 2014

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)



Lecture21-Multistage Amplifiers

1



Terminal Gain and I/O Resistances of BJT Amplifiers

Common Emitter (CE)	Common Collector (CC)	Common Base (CB)
 (b)	 (c)	 (d)
$A_{V,I} = -\frac{g_m R_L}{1 + g_m R_E}$ $R_i = r_\pi + (\beta + 1)R_E$ $R_o = [r_o(1 + g_m R_E)]$ $A_{I,I} = \beta$ <p>Without degeneration: Simply set $R_E = 0$</p>	$A_{V,I} = \frac{R_L}{\frac{g_m}{R_E} + R_L}$ $R_i = r_\pi + (\beta + 1)R_L$ $R_o = \frac{r_\pi + R_{th}}{1 + \beta} \approx \frac{1}{g_m} + \frac{R_{th}}{\beta}$ $A_{I,I} = \beta + 1$	$A_{V,I} = g_m R_L \beta$ $R_i = \frac{1}{g_m}$ $R_o = [r_o(1 + g_m R_E)]$ $A_{I,I} \approx 1$

For the gain, R_i , R_o of the whole amplifier, you need to include voltage/current dividers at input and output stages


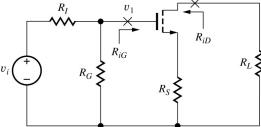
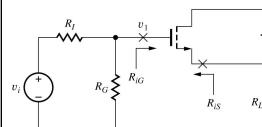


Lecture21-Multistage Amplifiers

2

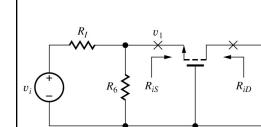

Terminal Gain and I/O Resistances of MOS Amplifiers

Common Source (CS)	Common Drain (CD)	Common Gate (CG)
 <p>(a)</p>	 <p>(b)</p>	 <p>(c)</p>
$A_{V,I} = -\frac{g_m R_L}{1 + g_m R_S}$ $R_i = \infty$ $R_o = [r_o(1 + g_m R_E)]$ $A_{I,I} = \infty$ Without degeneration: Simply set $R_S = 0$	$A_{V,I} = \frac{R_L}{\frac{1}{g_m} + R_L}$ $R_i = \infty$ $R_o = \frac{1}{g_m}$ $A_{I,I} = \infty$	$A_{V,I} = g_m R_L$ $R_i = \frac{1}{g_m}$ $R_o = [r_o(1 + g_m R_E)]$ $A_{I,I} \approx 1$

For the gain, R_i , R_o of the whole amplifier, you need to include voltage/current dividers at input and output stages



Summary of Single-Transistor Amplifiers

BJT	Ideal Voltage Amplifiers	Common Emitter	Common Emitter with Deg.	Common Collector	Common Base
R_i	∞	Moderate	Large	Large	Small
R_o	0	Large	Very Large	Small	Large
A_V	∞	Large	Moderate	~ 1	Large
f_H	∞	Small	Moderate	Large	Large

MOS	Ideal Voltage Amplifiers	Common Source	Common Source with Deg.	Common Drain	Common Gate
R_i	∞	Very Large	Very Large	Large	Small
R_o	0	Large	Very Large	Small	Large
A_V	∞	Moderate	Small	~ 1	Moderate
f_H	∞	Small	Moderate	Large	Large




Need for Multistage Amplifiers

- Typical spec for a general purpose operational amplifier
 - Input resistance $\sim 1\text{M}\Omega$
 - Output resistance $\sim 100\Omega$
 - Voltage gain $\sim 100,000$
- No single transistor amplifier can satisfy the spec
- Cascading multiple stages of amplifiers to meet the spec
- Usually
 - An input stage to provide required input resistance
 - A middle stage(s) to provide gain
 - An output stage to provide required output resistance
- It is important to note that the input resistance of the follow-on stage becomes the load of the previous stage




A 3-Stage ac-coupled Amplifier Circuit

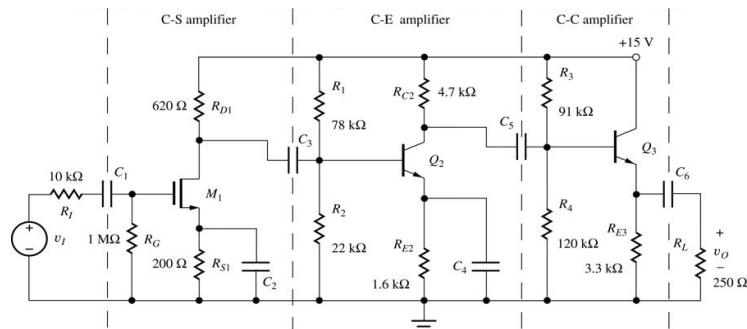

- MOSFET M_1 operating in the C-S configuration provides high input resistance and moderate voltage gain.
- BJT Q_2 in a C-E configuration, the second stage, provides high gain.
- BJT Q_3 , an emitter-follower gives low output resistance and buffers the high gain stage from the relatively low value of load resistance.




A 3-Stage ac-coupled Amplifier Circuit

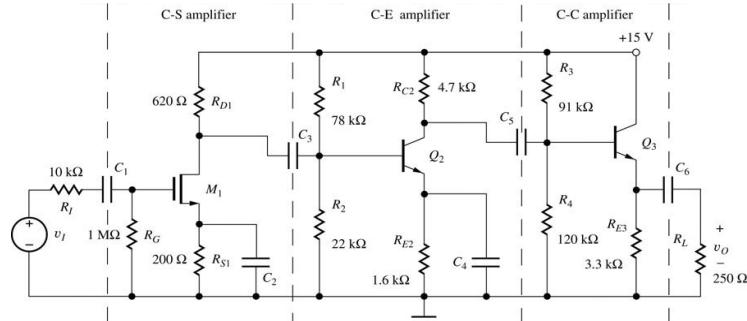

- Input and output of overall amplifier is ac-coupled through capacitors C_1 and C_6 .
- Bypass capacitors C_2 and C_4 are used to get maximum voltage gain from the two inverting amplifiers.
- Interstage coupling capacitors C_3 and C_5 transfer ac signals between amplifiers but provide isolation at dc and prevent Q-points of the transistors from being affected.
- In the ac equivalent circuit, bias resistors are replaced by $R_{B2} = R_1 \parallel R_2$ and $R_{B3} = R_3 \parallel R_4$



dc Equivalent Circuit

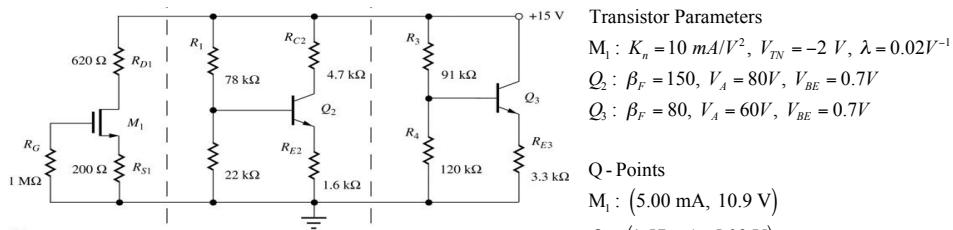

At dc, the capacitors isolate each individual transistor stage from the others. Thus, the bias point for each transistor may be found using the single transistor analysis methods already discussed.

Transistor Parameters

$M_1 : K_n = 10 \text{ mA/V}^2, V_{TN} = -2 \text{ V}, \lambda = 0.02 \text{ V}^{-1}$
 $Q_2 : \beta_F = 150, V_A = 80 \text{ V}, V_{BE} = 0.7 \text{ V}$
 $Q_3 : \beta_F = 80, V_A = 60 \text{ V}, V_{BE} = 0.7 \text{ V}$

Q-Points


$M_1 : (5.00 \text{ mA}, 10.9 \text{ V})$
 $Q_2 : (1.57 \text{ mA}, 5.09 \text{ V})$
 $Q_3 : (1.99 \text{ mA}, 8.36 \text{ V})$

Small-Signal Parameters

$M_1 : g_{m1} = 10.0 \text{ mS}, r_{o1} = 12.2 \text{ k}\Omega$
 $Q_2 : g_{m2} = 62.8 \text{ mS}, r_{\pi 2} = 2.39 \text{ k}\Omega, r_{o2} = 54.2 \text{ k}\Omega$
 $Q_3 : g_{m3} = 79.6 \text{ mS}, r_{\pi 3} = 1.00 \text{ k}\Omega, r_{o3} = 34.4 \text{ k}\Omega$



ac and Small-Signal Equivalent Circuits

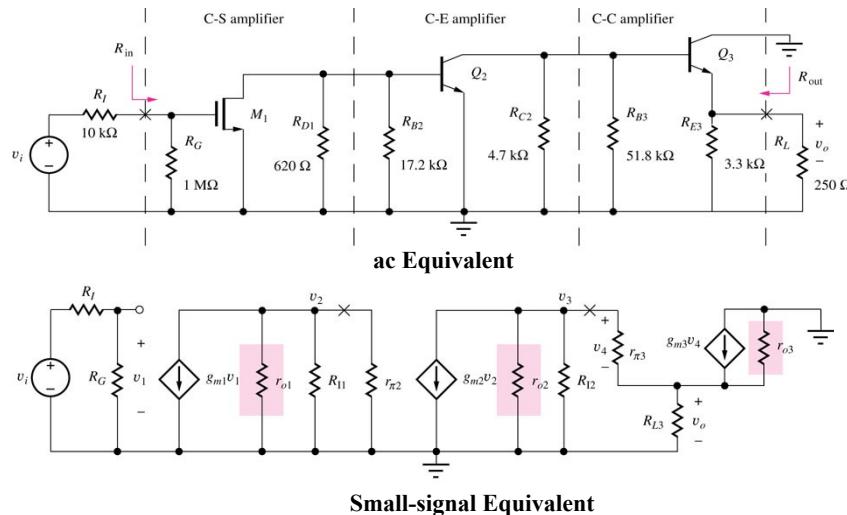

Cal

Lecture21-Multistage Amplifiers

9



Input Resistance and Voltage Gain

$$A_v = A_{vt3} A_{vt2} A_{vt1} \frac{R_{in}}{R_f + R_{in}}$$

$$A_{vt1} = \frac{V_2}{V_1} = -g_{m1} R_{L1} = -0.01S(0.478k\Omega) = -4.78$$

$$V_1 = V_i \frac{R_{in}}{R_f + R_{in}} = V_i \frac{1M\Omega}{10k\Omega + 1M\Omega} = 0.990V_i$$

$$R_{in} = 620\Omega \parallel 17.2k\Omega = 598\Omega$$

$$R_{L1} = R_{f1} \parallel R_{m2} = 598\Omega \parallel r_{\pi2} = 598\Omega \parallel 2390\Omega = 478\Omega$$

$$R_{in} = R_G = 1M\Omega$$

$$R_{in3} = R_{f3} \parallel R_{m3} = R_{f3} \parallel [r_{\pi3} + (\beta_{o3} + 1)R_{L3}] = 3.54k\Omega$$

$$A_{vt2} = \frac{V_3}{V_2} = -g_{m2} R_{L2} = -62.8S(3.54k\Omega) = -222$$

$$A_{vt3} = \frac{V_o}{V_3} = \frac{(\beta_{o3} + 1)R_{L3}}{r_{\pi3} + (\beta_{o3} + 1)R_{L3}} = 0.950$$

$$A_v = A_{vt3} A_{vt2} A_{vt1} \frac{R_G}{R_f + R_G} = +998$$


Cal

Lecture21-Multistage Amplifiers

10



Output Resistance

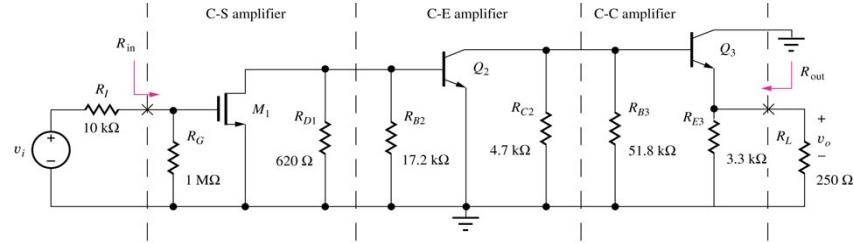

$$R_{o3} = \frac{r_\pi + R_{th}}{1 + \beta} \approx \frac{1}{g_m} + \frac{R_{th}}{\beta}$$


$$R_{th} = R_{I2} \parallel r_{o2} = 4.31\text{k}\Omega \parallel 54.2\text{k}\Omega = 4\text{k}\Omega$$

$$R_{o3} = \frac{1}{79.6mS} + \frac{4\text{k}\Omega}{80} = 12.6\Omega + 50\Omega = 62.6\Omega$$

$$R_{out} = R_{E3} \parallel R_{o3} = 3.3\text{k}\Omega \parallel 62.6\Omega = 61.3\Omega$$



Current and Power Gain

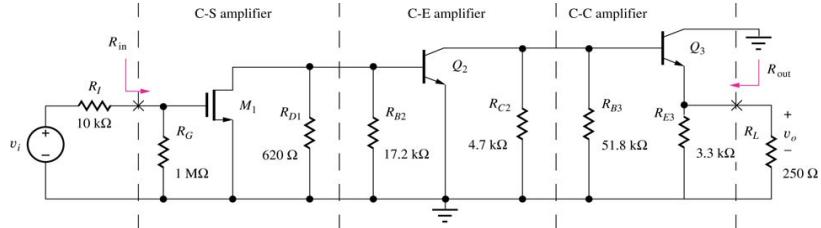

The input signal current delivered to the amplifier from source v_i is

$$i_i = \frac{v_i}{R_I + R_{in}} = 9.90 \times 10^{-7} v_i$$

and the signal current delivered to the load resistor is

$$i_o = \frac{v_o}{R_L} = \frac{A_v v_i}{250\Omega} = \frac{998 v_i}{250\Omega} = 3.99 v_i$$


$$\text{Current Gain: } A_i = \frac{i_o}{i_i} = 4.03 \times 10^6 \quad (132 \text{ dB})$$

$$\text{Voltage Gain: } A_v = \frac{v_o}{v_i} = 9.98 \times 10^2 \quad (60 \text{ dB})$$

$$\text{Power Gain: } A_p = \frac{P_o}{P_i} = \left| \frac{v_o i_o}{v_i i_i} \right| = A_v A_i = 4.02 \times 10^9 \quad (96 \text{ dB})$$



Input and Output Signal Range

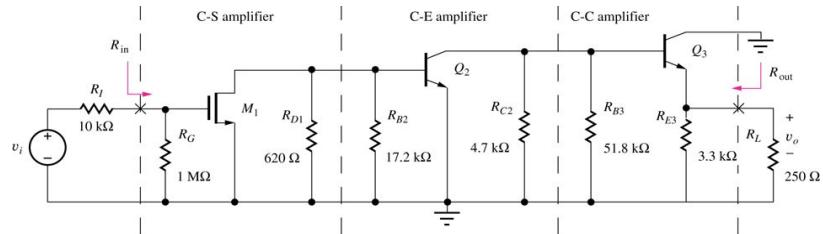

$$\text{For the first stage: } |v_i| \leq 0.2(V_{GS} - V_{TN}) \rightarrow |v_i| \leq \frac{0.2(-1+2)V}{0.99} = 0.202 \text{ V}$$

$$\text{For the second stage: } |v_{be2}| = |v_2| = |A_{v1}v_i| \leq 5 \text{ mV}$$

$$|v_1| \leq \frac{5 \text{ mV}}{A_{v1}} = \frac{5 \text{ mV}}{4.78} = 1.05 \text{ mV} \rightarrow |v_i| \leq \frac{1.05 \text{ mV}}{0.99} = 1.06 \text{ mV}$$

$$\text{For the third stage: } v_{be3} \approx \frac{v_3}{1 + g_m R_{L3}} = \frac{A_{v1} A_{v2} (0.990 v_i)}{1 + g_m R_{L3}} \leq 5 \text{ mV}$$

$$|v_i| \leq \frac{1 + g_m R_{L3}}{A_{v1} A_{v2} (0.990)} 5 \text{ mV} = 92.7 \mu\text{V}$$

$$\text{Overall: } |v_i| \leq \min(202 \text{ mV}, 1.06 \text{ mV}, 92.7 \mu\text{V}) = 92.7 \mu\text{V}$$

$$|v_o| \leq A_v (92.7 \mu\text{V}) = 998 (92.7 \mu\text{V}) = 92.5 \text{ mV}$$


Cal

Lecture21-Multistage Amplifiers

13



SPICE Simulation Circuit

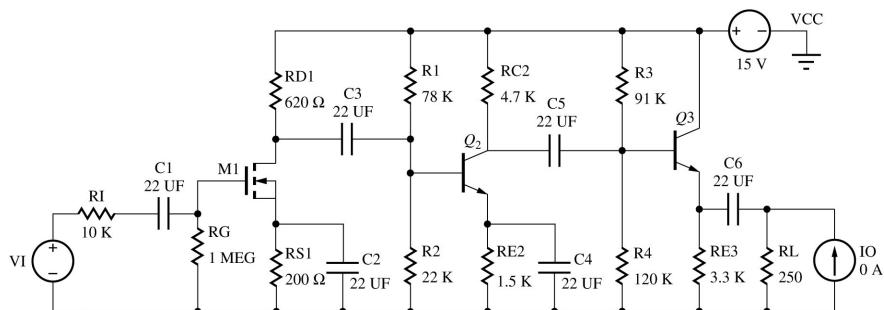


Cal

Lecture21-Multistage Amplifiers


14



SPICE Simulation Results

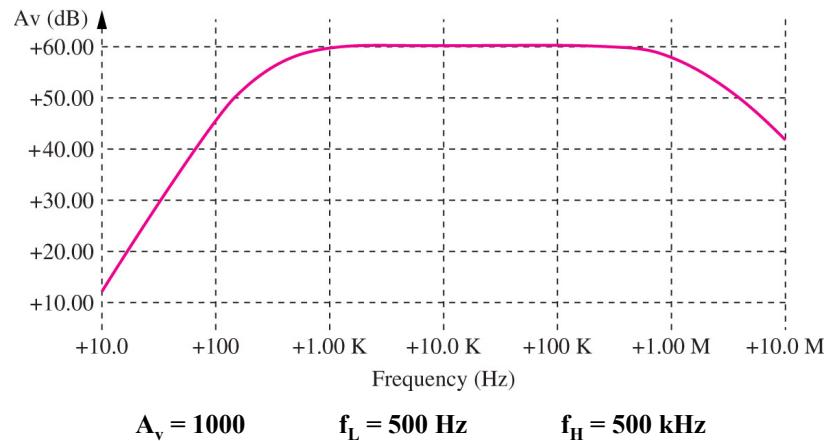


SPICE Simulation Results

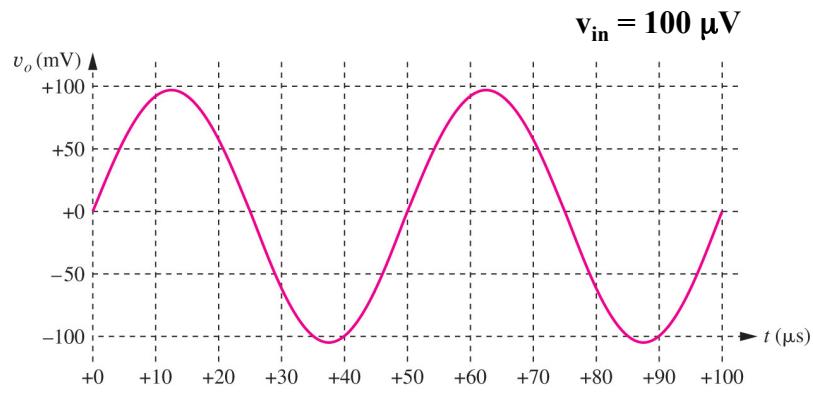

Simulation with undistorted output and gain of 1000.



SPICE Simulation Results

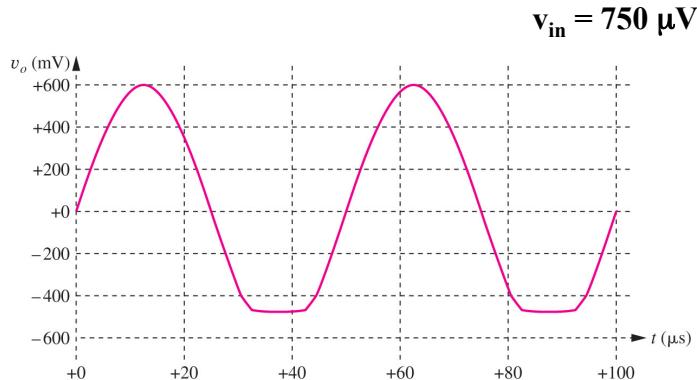

Distorted output with amplitude exceeding output voltage capability of amplifier.



Short-Circuit Time Constant Estimate for f_L


An estimate for the lower cutoff frequency for an amplifier with multiple coupling and bypass capacitors is given by the sum of the reciprocals of the "short-circuit" time constants:

$$f_L \cong \frac{1}{2\pi} \sum_{i=1}^n \frac{1}{R_{iS} C_i}$$

where R_{iS} is the resistance at the terminals of the i th capacitor with all the other capacitors shorted.



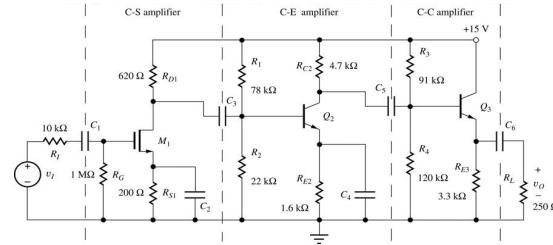Short-Circuit Time Constant Estimate for f_L



$$C_1: R_{1S} = R_j + R_G = 1.01 \text{ M}\Omega$$

$$C_2: R_{2S} = R_{S1} \| R_{1S1} = R_{S1} \left\| \frac{1}{g_m1} \right\| = 200\Omega \left\| \frac{1}{0.01S} \right\| = 66.7 \Omega$$

$$C_3: R_{3S} = R_{D1} + R_{I1} \| R_{iB2} = R_{D1} + R_{I1} \| r_{\pi2} = 620\Omega + 17.2k\Omega \| 2.39k\Omega = 2.72 \text{ k}\Omega$$

$$C_4: R_{4S} = R_{E2} \| R_{iE2} = R_{E2} \left\| \frac{r_{\pi2} + R_{th2}}{\beta_{o2} + 1} \right\| = 1.5k\Omega \left\| \frac{2.39k\Omega + 17.2k\Omega}{0.620k\Omega} \right\| = 19.2 \Omega$$

$$C_5: R_{5S} = R_C + R_{I2} \| R_{iB3} = R_L + R_{I2} \| r_{\pi3} (1 + g_{m3} R_{L3})$$

$$R_{5S} = 4.7k\Omega + 51.8k\Omega \| 1.0k\Omega [1 + 0.0796S(232\Omega)] = 18.9 \text{ k}\Omega$$

$$C_6: R_{6S} = R_L + R_{E3} \| R_{iE3} = R_L + R_{E3} \left\| \frac{r_{\pi3} + R_{th3}}{\beta_{o3} + 1} \right\|$$

$$R_{6S} = 250\Omega + 3.3k\Omega \left\| \frac{1.0k\Omega + 51.8k\Omega \| 4.7k\Omega }{81} \right\| = 315 \Omega$$



Short-Circuit Time Constant Estimate for f_L

$$f_L \approx \frac{1}{2\pi} \left[\frac{1}{1.01M\Omega(22\mu F)} + \frac{1}{66.7\Omega(22\mu F)} + \frac{1}{2.72k\Omega(22\mu F)} + \frac{1}{19.2\Omega(22\mu F)} \right. \\ \left. + \frac{1}{18.9k\Omega(22\mu F)} + \frac{1}{315\Omega(22\mu F)} \right] = 511 \text{ Hz}$$

