

Common-Emitter Amplifier – ω_{H} Open-Circuit Time Constant (OCTC) Method

At high frequencies, impedances of coupling and bypass capacitors are small enough to be considered short circuits. Open-circuit time constants associated with impedances of device capacitances are considered instead.

$$\omega_{H} \cong \frac{1}{\sum_{i=1}^{m} R_{io} C_{i}}$$

where R_{io} is resistance at terminals of *i*th capacitor C_i with all other capacitors open-circuited. For a C-E amplifier, assuming $C_L = 0$

$$R_{\pi 0} = r_{\pi 0}$$

Lecture23-Amplifier Frequency Response 2













Constant of the equivalence of the equiva



Lecture23-Amplifier Frequency Response 10



















Frequency Response Multistage Amplifier: High-Frequency Poles

High-frequency pole at the gate of $\rm M_1$: Using our equation for the C-S input pole:

$$f_{P_{1}} = \frac{1}{2\pi} \frac{1}{R_{h1} \left[C_{GD1} \left(1 + g_{m} R_{L1} \right) + C_{GS1} + \frac{R_{L1}}{R_{h1}} (C_{GD1} + C_{L1}) \right]}$$

$$R_{L1} = R_{I12} \left\| (r_{x2} + r_{x2}) \right\| r_{o1} = 598\Omega \left\| (250\Omega + 2.39k\Omega) \right\| 12.2k\Omega = 469 \ \Omega$$

$$C_{L1} = C_{x2} + C_{\mu 2} \left(1 + g_{m2} R_{L2} \right)$$

$$R_{L2} = R_{I23} \left\| R_{in3} \right\| r_{o2} = R_{I23} \left\| (r_{x3} + r_{x3} + (\beta_{o3} + 1) (R_{E3} \| R_{L})) \right\| r_{o2} = 3.33 \ k\Omega$$

$$C_{L1} = C_{x2} + C_{\mu 2} \left(1 + g_{m2} R_{L2} \right) = 39 \ pF + 1pF \left[1 + 67.8mS (3.33k\Omega) \right] = 266 \ pF$$

$$f_{P_{1}} = \frac{1}{2\pi} \frac{1}{9.9k\Omega \left[1pF \left[1 + 0.01S (3.33k\Omega) \right] + 5pF + \frac{469\Omega}{9.9k\Omega} (1pF + 266pF) \right]} = 689 \ kHz$$
We Lecture 23-Amplifier Frequency Response 20



Frequency Response Multistage Amplifier: High-Freq. Poles (cont.)

High-frequency pole at the base of Q_3 : Again, due to the pole-splitting behavior of the C-E second stage, we expect that the pole at the base of Q_3 will be set by equation 17.96:

$$f_{p3} \cong \frac{g_{m2}}{2\pi [C_{\pi 2}(1 + \frac{C_{L2}}{C_{\mu 2}}) + C_{L2}]}$$

The load capacitance of Q₂ is the input capacitance of the C-C stage.

$$\begin{split} C_{L2} &= C_{\mu 3} + \frac{C_{\pi 3}}{1 + g_{m 3} \left(R_{E3} \parallel R_L\right)} = 1 pF + \frac{50 pF}{1 + 79.6 mS(3.3 k\Omega \parallel 250 \Omega)} = 3.55 \ pF \\ f_{p 3} &\simeq \frac{67.8 mS[1 k\Omega / (1 k\Omega + 250 \Omega)]}{2 \pi [39 \ pF(1 + \frac{3.55 pF}{1 pF}) + 3.55 pF]} = 47.7 \ MHz \end{split}$$

Lecture23-Amplifier Frequency Response 22



