

EE105 – Fall 2014

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)




Lecture24-Digital Circuits-CMOS
Inverters

1



The Ideal Inverter

 The ideal inverter has the following voltage transfer characteristic (VTC) and is described by the following symbol



V_+ and V_- are the supply rails, and V_H and V_L describe the high and low logic levels at the output




Lecture24-Digital Circuits-CMOS
Inverters

2




Logic Level Definitions

 

- An inverter operating with power supplies at V_+ and 0 V can be implemented using a switch with a resistive load
- The switch could be a mechanical device such as a wall switch or relay, a vacuum tube, or an MOS or bipolar transistor




NMOS Inverter with a Resistive Load

 

- Resistor R is used to “pull” the output high.
- M_S is the switching transistor used to force the output low.
- The size of R and the W/L ratio of M_S are the design factors that need to be chosen.



 NMOS Inverter with a Resistive Load Load Line Visualization



Q-pts for V_L and V_H on the NMOS device output (i_D - v_{DS}) characteristics.

Load line equation:

$$v_{DS} = V_{DD} - i_D R$$




Lecture24-Digital Circuits-CMOS
Inverters


5



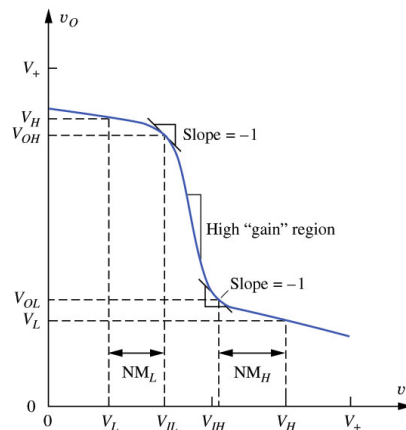Logic Level Definitions Voltage Levels (cont.)



 Note that for the voltage transfer characteristic (VTC) of the nonideal inverter, there is now an undefined logic state.



Noise Margin:
 $NM_H = V_{OH} - V_{IH}$
 $NM_L = V_{IL} - V_{OL}$



Lecture24-Digital Circuits-CMOS
Inverters

6



Logic Level Definitions Voltage Levels

- V_L – The nominal voltage corresponding to a low-logic state at the output of a logic gate for $v_i = V_H$
- V_H – The nominal voltage corresponding to a high-logic state at the output of a logic gate for $v_i = V_L$
- V_{IL} – The maximum input voltage that will be recognized as a low input logic level
- V_{IH} – The maximum input voltage that will be recognized as a high input logic level
- V_{OH} – The output voltage corresponding to an input voltage of V_{IL}
- V_{OL} – The output voltage corresponding to an input voltage of V_{IH}




Logic Gate Design Goals

- An ideal logic gate is highly nonlinear and attempts to quantize the input signal to two discrete states. In an actual gate, the designer should attempt to minimize the undefined input region while maximizing noise margins.
- The input should produce a well-defined output, and changes at the output should have no effect on the input.
- Voltage levels at the output of one gate should be compatible with the input levels of a following gate.
- The gate should have sufficient fan-out and fan-in capabilities.
- The gate should consume minimal power (and area for ICs) and still operate under the design specifications.



 Dynamic Response of Logic Gates Propagation Delay



- Propagation delay describes the amount of time between the input reaching the 50% point and the output reaching the 50% point.

$$V_{50\%} = \frac{V_H + V_L}{2}$$

- The high-to-low propagation delay, τ_{PHL} , and the low-to-high propagation delay, τ_{PLH} , are usually not equal, but can be combined as an average value:

$$\tau_P = \frac{\tau_{PHL} + \tau_{PLH}}{2}$$



Dynamic Response of Logic Gates Power-Delay Product

- The power-delay product (PDP) is a metric that describes the amount of energy (Joules) required to perform a basic logic operation and is given by the following equation where P is the average power dissipated by the logic gate:

$$PDP = P\tau_P$$



Review of Boolean Algebra

A	Z
0	1
1	0

NOT
Truth Table
 $Z = \overline{A}$

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR
Truth Table

$$Z = A + B$$

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND
Truth Table

$$Z = AB$$

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

NOR
Truth Table

$$Z = \overline{A + B}$$




A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

NAND
Truth Table

$$Z = \overline{AB}$$



   Logic Gate Symbols and Boolean Expressions




CMOS Technology

- Complementary MOS, or CMOS, needs both PMOS and NMOS devices for the logic gates to be realized
- The concept of CMOS was introduced in 1963 by Wanlass and Sah, but it did not become common until the 1980's as NMOS microprocessors were dissipating as much as 50 W and an alternative design technique was needed
- CMOS dominates digital IC design today



CMOS Inverter Circuit

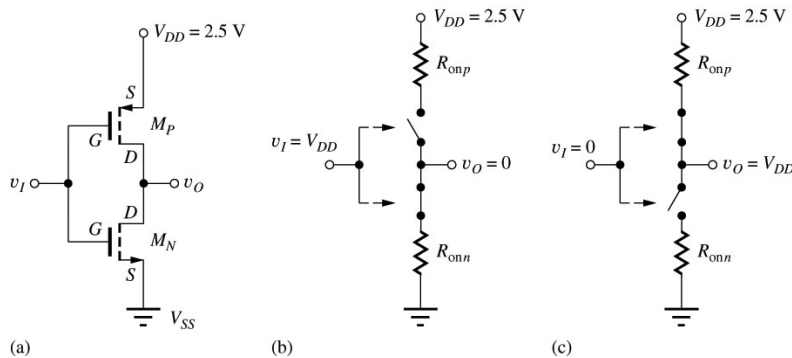


- When v_I is pulled high (to V_{DD}), the PMOS transistor is turned off, while the NMOS device is turned on pulling the output down to V_{SS}
- When v_I is pulled low (to V_{SS}), the NMOS transistor is turned off, while the PMOS device is turned on pulling the output up to V_{DD}




CMOS Inverter Fabrication

 - The CMOS inverter consists of a PMOS device stacked on top of an NMOS device, but they need to be fabricated on the same wafer
- To accomplish this, the technique of “n-well” implantation was developed as shown in this cross-section of a CMOS inverter



 CMOS Inverter Static Characteristics: $v_I = V_L$




- For $v_I = V_L \leq V_{TN}$, M_N is off, and M_P is on. Therefore $V_H = V_{DD}$, $I_D = 0$, and there is no static power dissipation.



CMOS Inverter

Static Characteristics: $v_I = V_H$

 


- For $v_I = V_H = V_{DD}$, $V_L = 0$ V, and $I_D = 0$ A which means that there is no static power dissipation



CMOS Inverter

Voltage Transfer Characteristics

 Regions of Operation of Transistors in a Symmetrical CMOS Inverter



The VTC shown is for a CMOS inverter that is symmetrical ($K_p = K_n$).



CMOS Inverter Noise Margins (cont.)

$$K_R = \frac{K_N}{K_P} \quad NM_L = V_{IL} - V_{OL} \quad NM_H = V_{OH} - V_{IH}$$

$$V_{IH} = \frac{2K_R(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{K_R - 1}$$


$$V_{OL} = \frac{(K_R + 1)V_{IH} - V_{DD} - K_R V_{TN} - V_{TP}}{2K_R}$$

$$V_{IL} = \frac{2\sqrt{K_R}(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{K_R - 1}$$

$$V_{OH} = \frac{(K_R + 1)V_{IL} + V_{DD} - K_R V_{TN} - V_{TP}}{2}$$




CMOS Inverter Propagation Delay Estimate

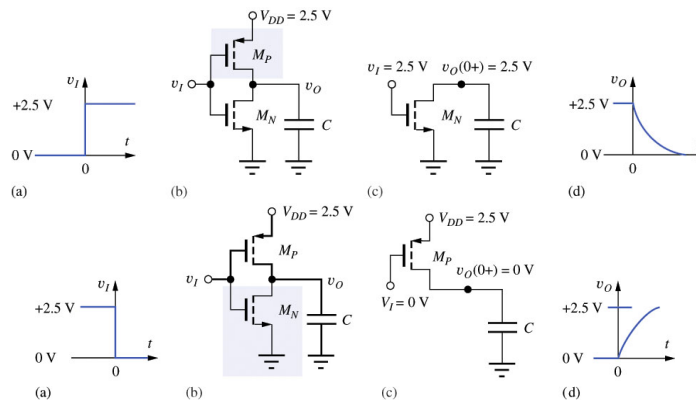

- The two modes of capacitive charging/discharging that contribute to propagation delay



CMOS Inverter Rise and Fall Times

 

RC charging (or discharging) is exponential:

$$\Delta v(t) = \Delta V \exp\left(-\frac{t}{RC}\right)$$

$$\text{At 10\%, } 0.1 = \exp\left(-\frac{t_1}{RC}\right)$$

$$\text{At 90\%, } 0.9 = \exp\left(-\frac{t_2}{RC}\right)$$

$$\text{Fall time: } t_f = t_2 - t_1 = RC \ln\left(\frac{0.9}{0.1}\right) = 2.2RC$$

$$\text{At 50\%, } 0.5 = \exp\left(-\frac{\tau_{PHL}}{RC}\right) \Rightarrow \tau_{PHL} = 0.69RC$$

Therefore, $t_f \approx 3\tau_{PHL}$

Similarly, $t_r \approx 3\tau_{PLH}$



CMOS Inverter Propagation Delay Estimate (cont.)

$$\tau_{PHL} = R_{onN} C \left\{ \ln \left[4 \left(\frac{V_H - V_{TN}}{V_H + V_L} \right) - 1 \right] + \frac{2V_{TN}}{V_H - V_{TN}} \right\}$$

$$R_{onN} = \frac{1}{K_n (V_H - V_{TN})}$$

$$\tau_p = \frac{\tau_{PHL} + \tau_{PLH}}{2} = \tau_{PHL} = 1.2R_{onN}C$$

- If it is assumed the inverter is “symmetrical” with $(W/L)_p = 2.5(W/L)_n$, then $\tau_{PLH} = \tau_{PHL}$



CMOS Inverter Performance Scaling


- State-of-the-art short gate length technologies are hard to analyze
- Scaling can be used to properly set W/L for a given load capacitance relative to reference gate simulation with a reference load.

$$\tau_P = \left(\frac{W/L}{(W/L)'} \right) \times \left(\frac{C_L'}{C_{Lref}} \right) \times \tau_{Pref} \quad \text{OR} \quad \left(\frac{W}{L} \right)' = \left(\frac{W}{L} \right) \times \left(\frac{\tau_{Pref}}{\tau_P} \right) \times \left(\frac{C_L'}{C_{Lref}} \right)$$

- Scaling allows us to calculate a new geometry (W/L)' in terms of a target load and delay.



CMOS Logic Dynamic Power Dissipation

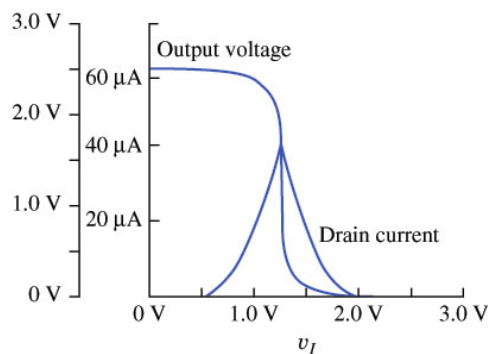

- There are two components that add to dynamic power dissipation:
 - Capacitive load charging at a frequency f given by: $PD = CV_{DD}^2 f$
 - The current that occurs during switching which can be seen in the figure




CMOS Logic Power-Delay Product

- The power-delay product is given as:

$$PDP = P_{av} \tau_p$$

$$P_{av} = CV_{DD}^2 f = CV_{DD}^2 \frac{1}{T}$$

 - The figure shows a symmetrical inverter switching waveform




$$T \geq t_r + t_a + t_f + t_b = \frac{2t_r}{0.8} = \frac{2(2\tau_p)}{0.8} = 5\tau_p$$

$$PDP \geq \frac{CV_{DD}^2}{5\tau_p} \tau_p = \frac{CV_{DD}^2}{5}$$




CMOS Logic NOR Gate

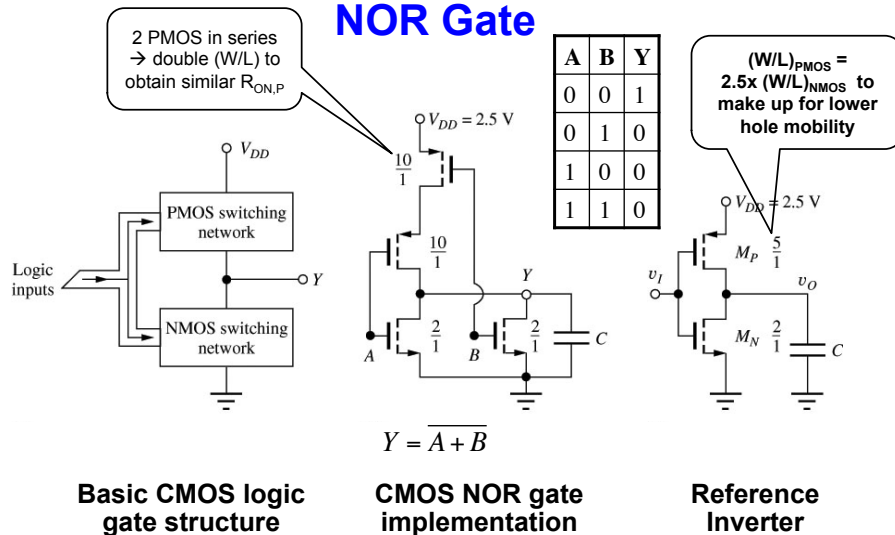


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

CMOS Logic NAND Gates

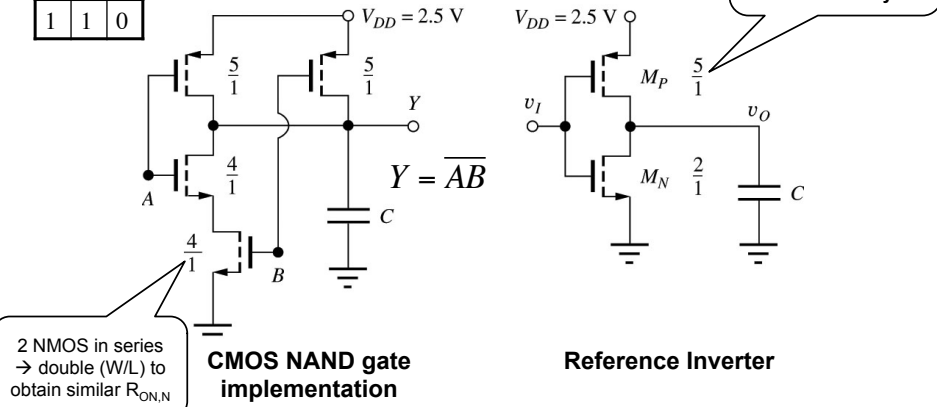

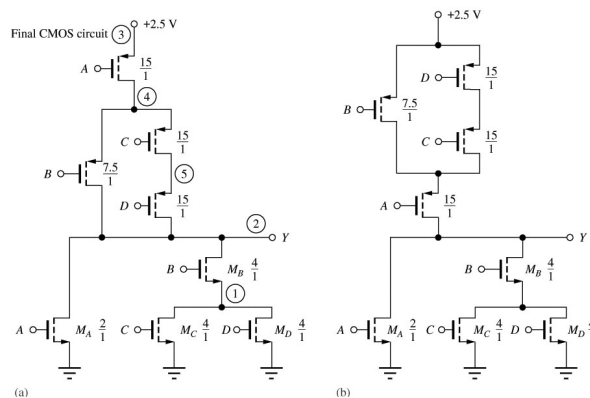Complex CMOS Logic Gate Design Example (cont.)



Two equivalent forms of the final circuit

- From the PMOS graph, the PMOS network can now be drawn for the final CMOS logic gate while once again considering the longest PMOS path for sizing

