

EE105 – Fall 2015

Microelectronic Devices and Circuits

Current Sources

Prof. Ming C. Wu

wu@eecs.berkeley.edu




511 Sutardja Dai Hall (SDH)

Krishna Settaluri


kset@berkeley.edu



Load Impedance

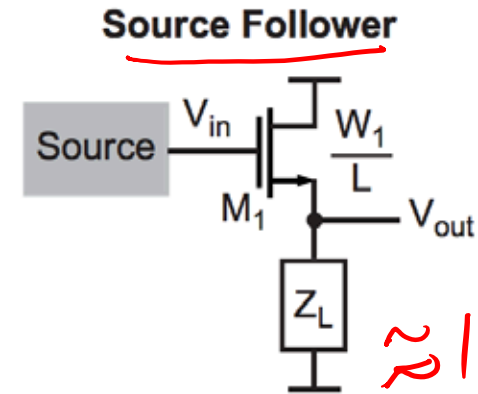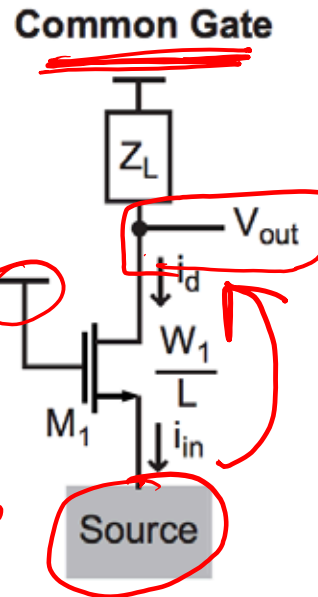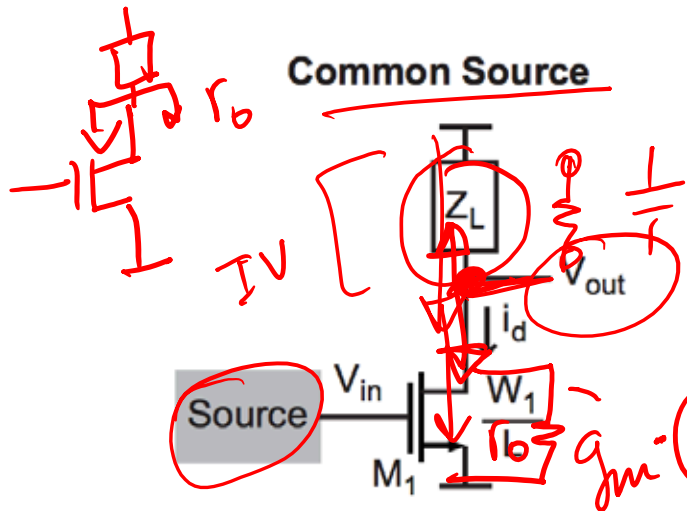


Common Source with Source Degeneration

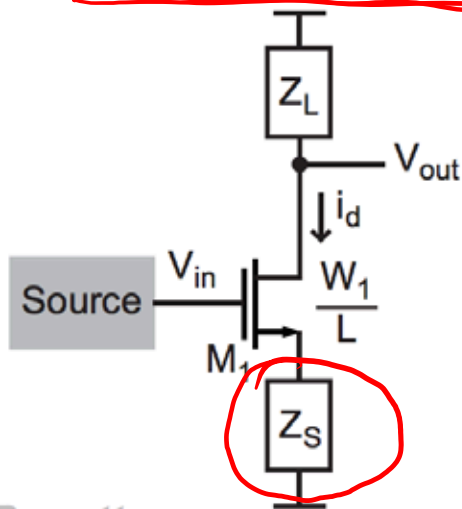

- To achieve high gain (or low attenuation in the case of a source follower), it is very desirable to achieve high load impedance, Z_L
 - Unfortunately, using a simple resistor of high value has issues
 - What are these issues?

Issue: Headroom Limitations

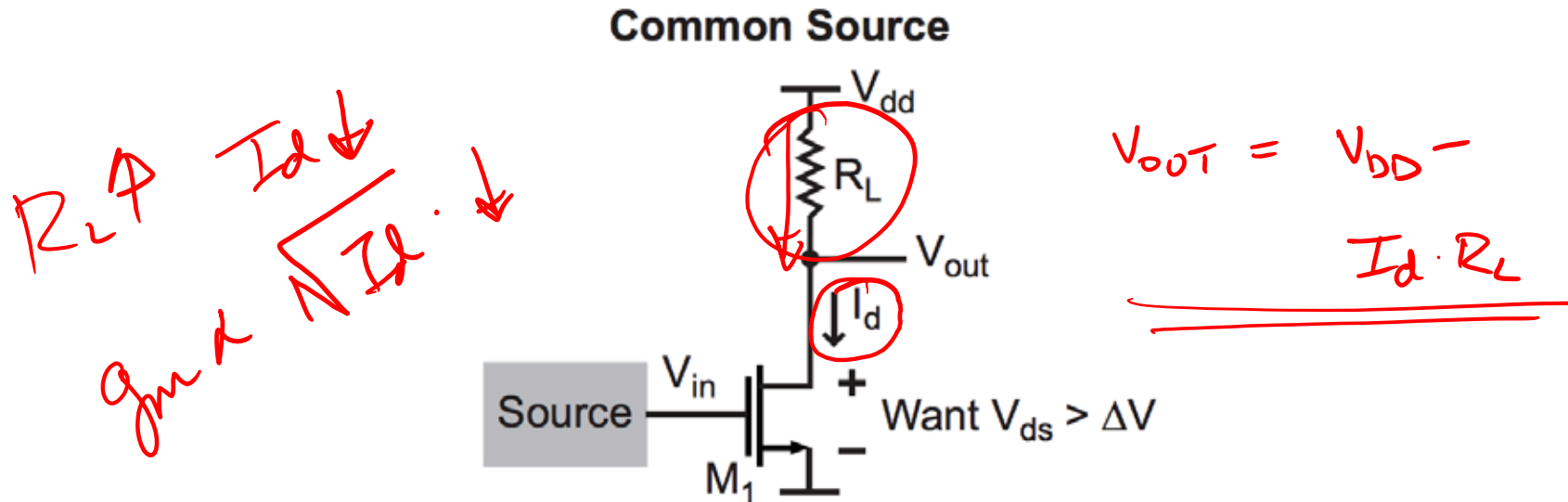


- The bias current of the device is a direct function of R_L

$$I_d = \frac{V_{dd} - V_{ds}}{R_L}$$

- V_{dd} is $< 3.6V$ for most modern CMOS processes
- V_{ds} must be greater than ΔV to maintain device saturation

Large R_L implies small I_d
(implies small g_m , poor frequency response, etc.)


Achieving High Gain

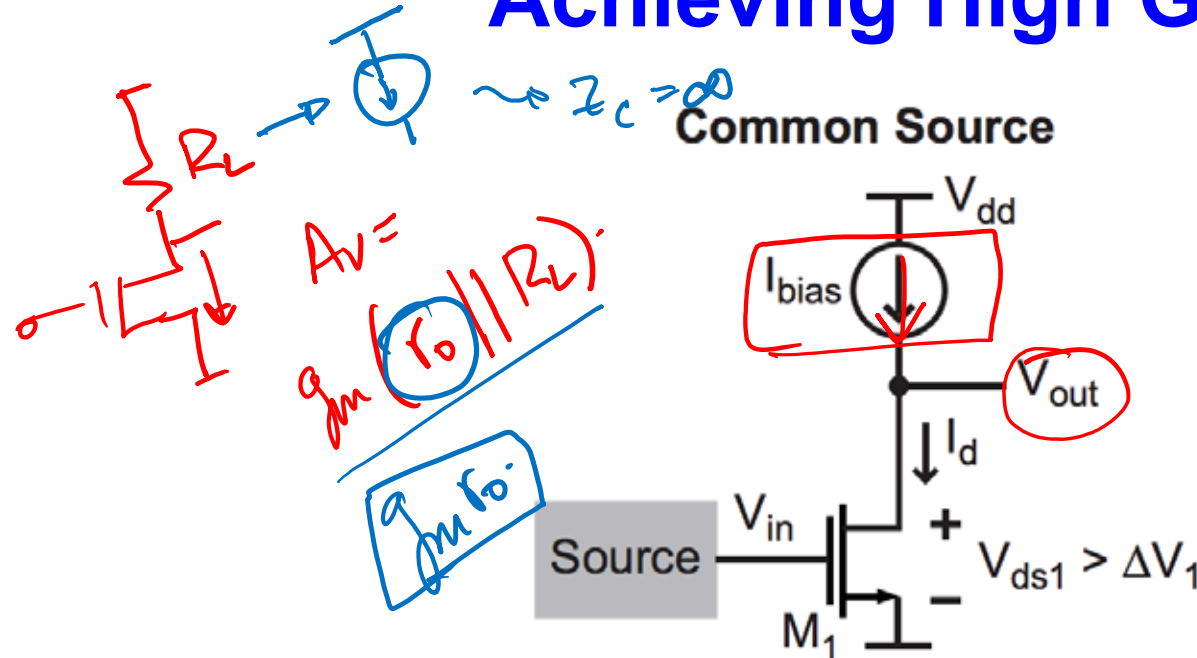

- Replacement of resistor load with a current source yields the highest possible DC gain out of the amplifier
 - Current source determines I_d of device
- We can make current sources out of transistors
 - Generally smaller area than polysilicon resistors


What is the small signal gain of the above circuit?

Diode Connected Device

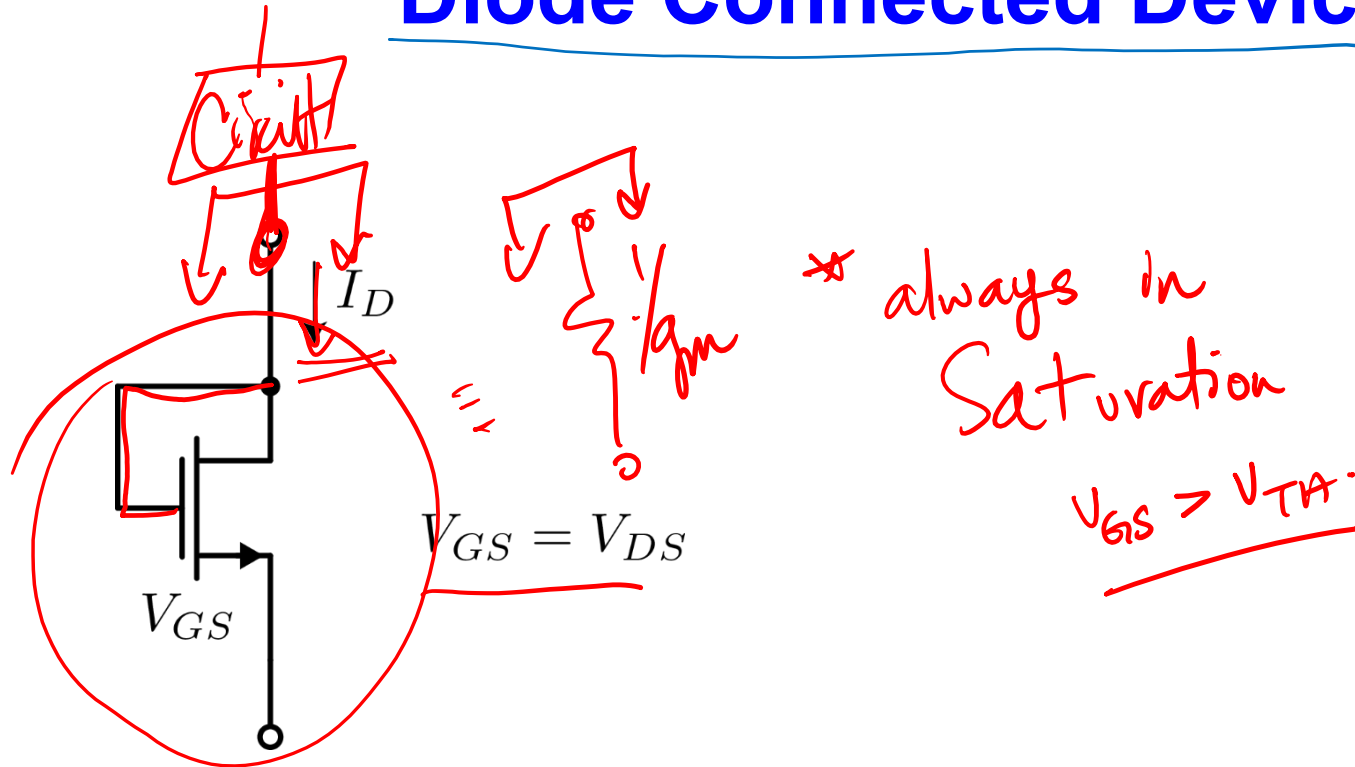


- How do we build current sources?
- Let's start with a "diode connected" device
- A MOS device with gate and drain shorted operates like a diode (but not exponential)

Diode Connected -- SS Model

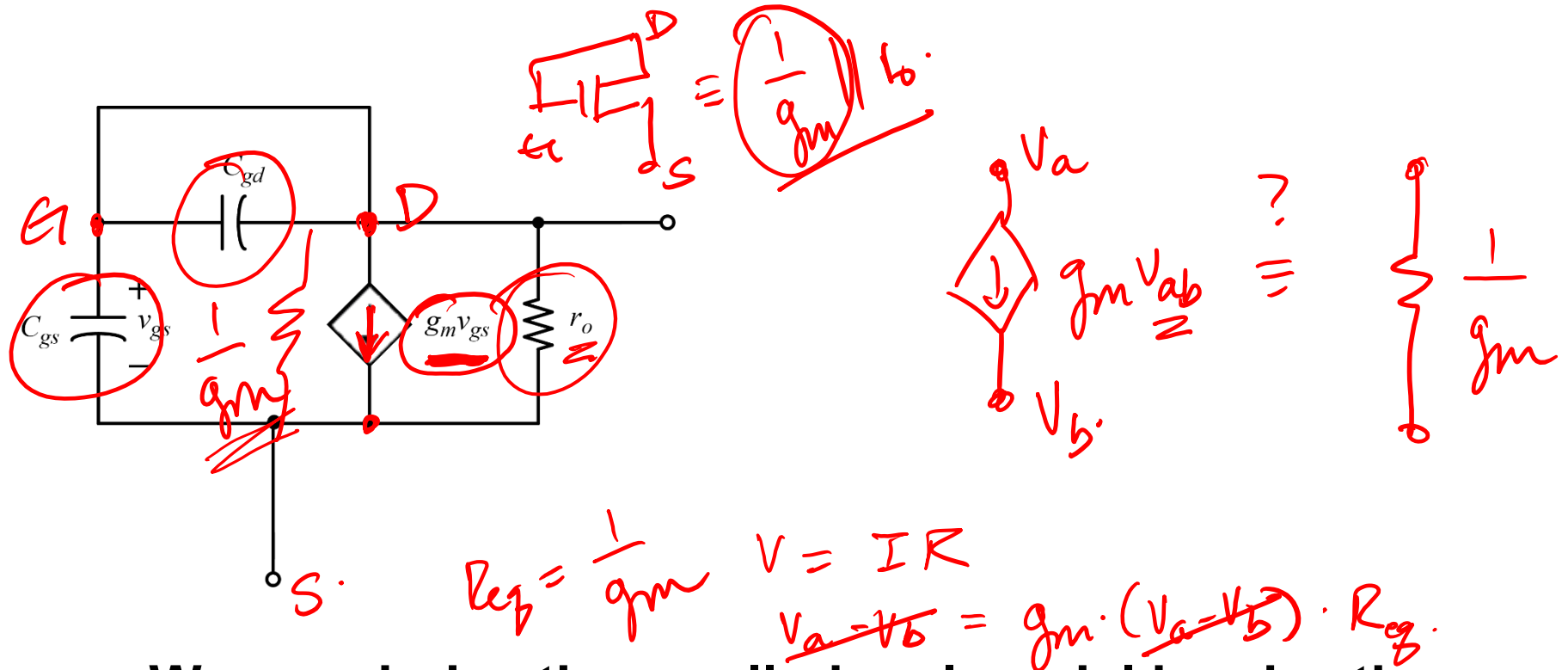


- We can derive the small-signal model by shorting out the hybrid-pi model
- Note that a Gm generator with it's controlling terminals connected to the Gm is more simply a ...?

The Integrated “Current Mirror”

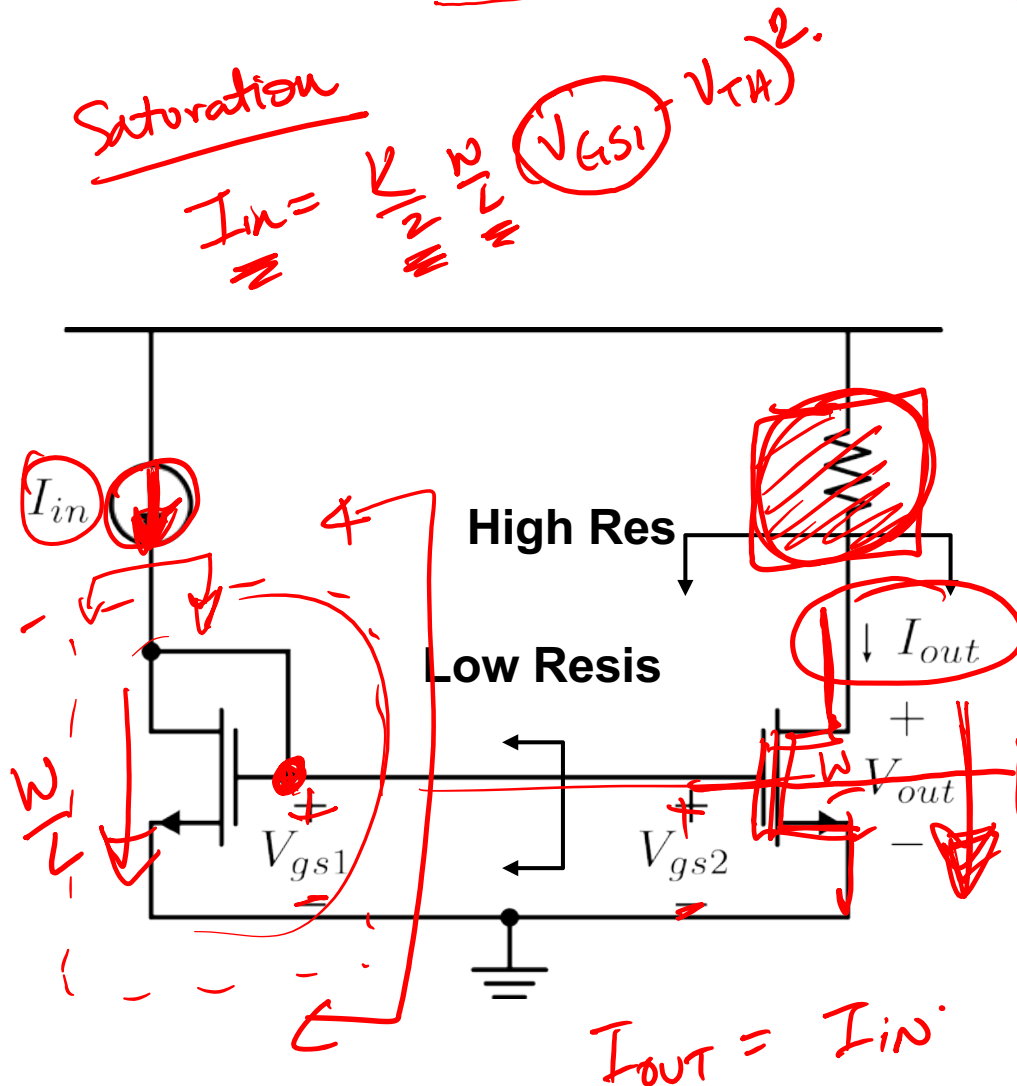

- M_1 and M_2 have the same V_{GS}
- If we neglect CLM ($\lambda=0$), then the drain currents are equal
- Since λ is small, the currents will nearly mirror one another even if V_{out} is not equal to V_{GS1}
- We say that the current I_{REF} is mirrored into i_{OUT}
- Notice that the mirror works for small and large signals!

Multiplication Ratio

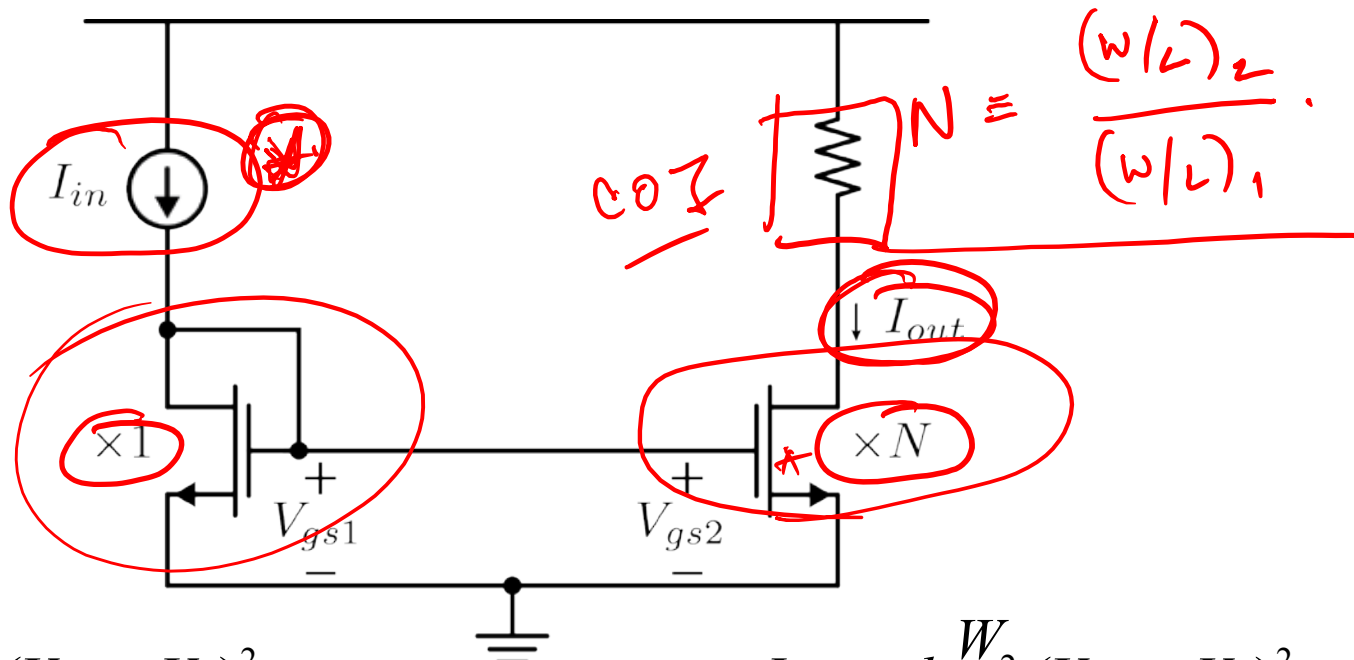

$$I_{IN} = k \frac{W_1}{L_1} (V_{GS1} - V_T)^2$$

$I_{IN} = \frac{k}{2} \frac{W_1}{L_1} (V_{GS1} - V_{TH})^2$

$$I_{OUT} = k \frac{W_2}{L_2} (V_{GS2} - V_T)^2$$

$V_{GS2} = V_{GS1}$


$V_{GS1} = \sqrt{\frac{2 I_{IN}}{k} \frac{L_1}{W_1}} + V_{TH}$

$I_{OUT} = \frac{k}{2} \cdot N \cdot \frac{W}{L} (V_{GS1} - V_{TH})^2$

$$I_{OUT} = k \frac{W_2}{L_2} (V_{GS2} - V_T)^2 = I_{IN} \frac{W_2 / L_2}{W_1 / L_1} = N I_{IN}$$


$I_{OUT} = N I_{IN}$

Current Mirror as Current Source

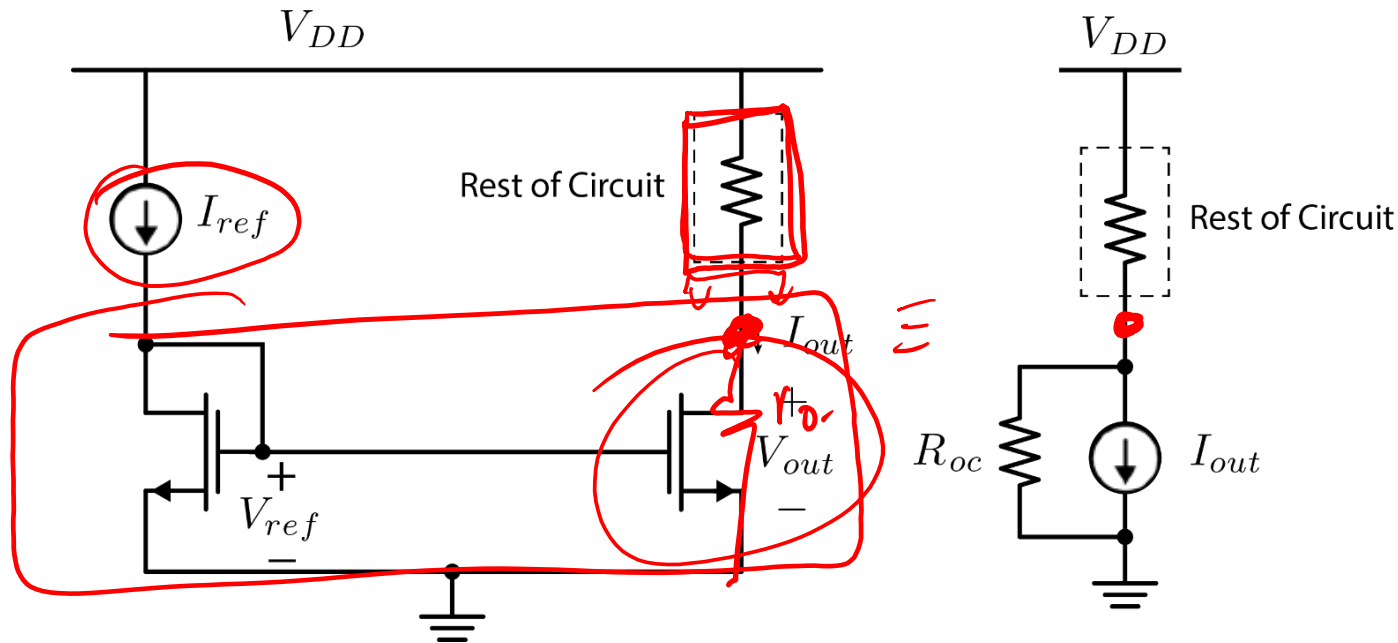

- The output current of M_2 is only weakly dependent on v_{OUT} due to high output resistance of FET
- M_2 acts like a current source to the rest of the circuit
- For good current source behavior, what is the minimum v_{OUT} ?

Small-Signal Resistance of I -Source

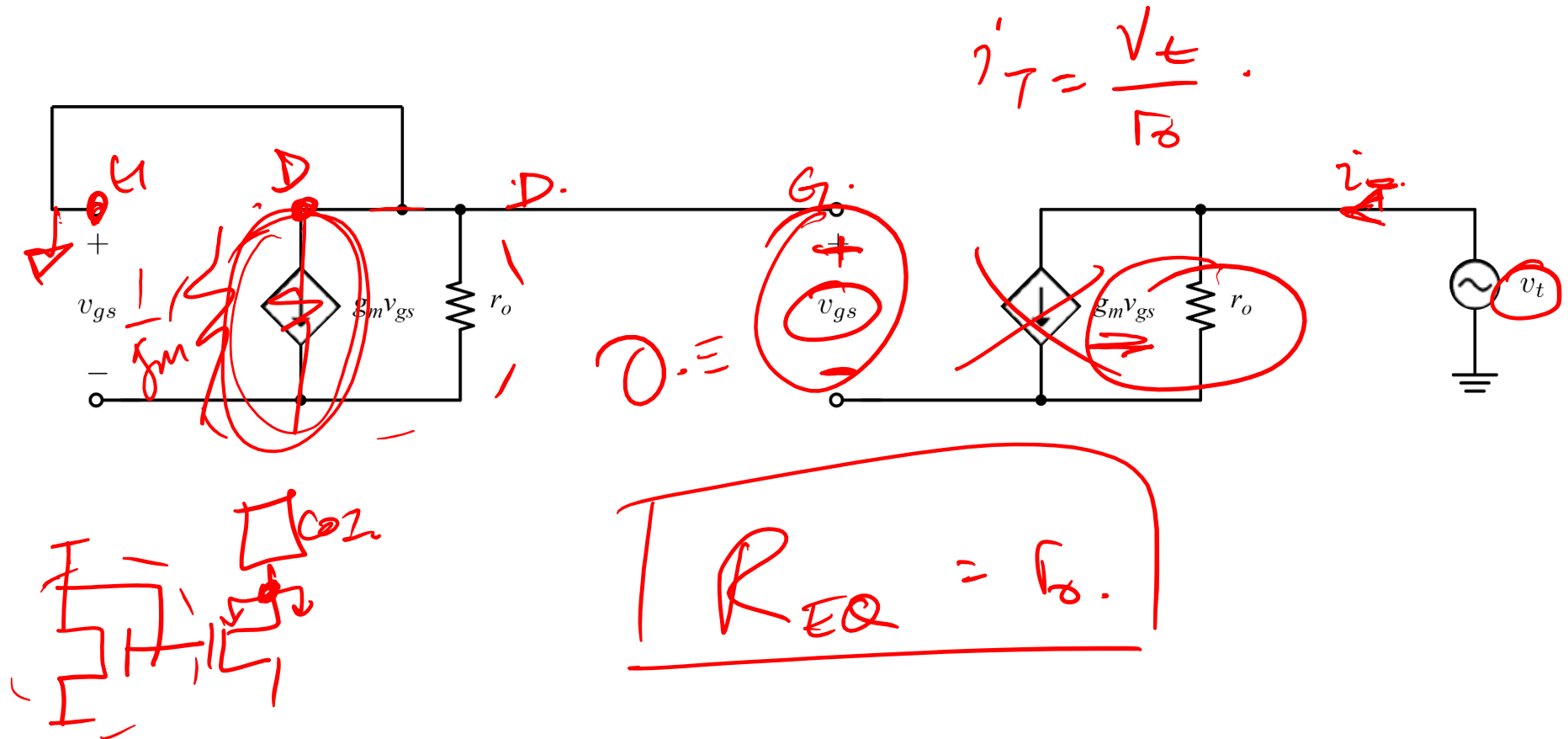


Improved Current Sources


Goal: increase $R_{o(ut)}$

Approach: look at *amplifier* output resistance results ... to see topologies that boost resistance
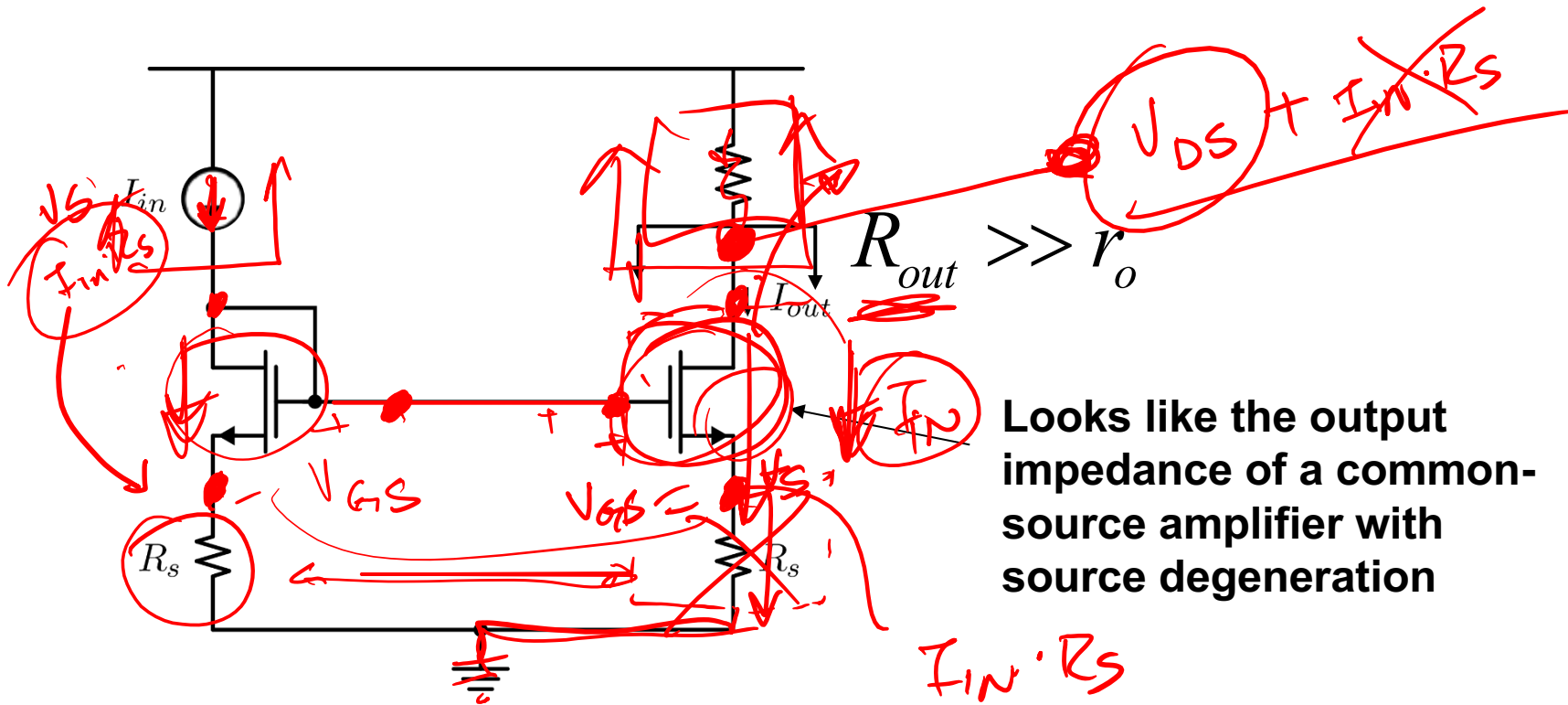
$$\text{diode symbol} = \square \approx \text{huge.}$$



Effect of Source Degeneration

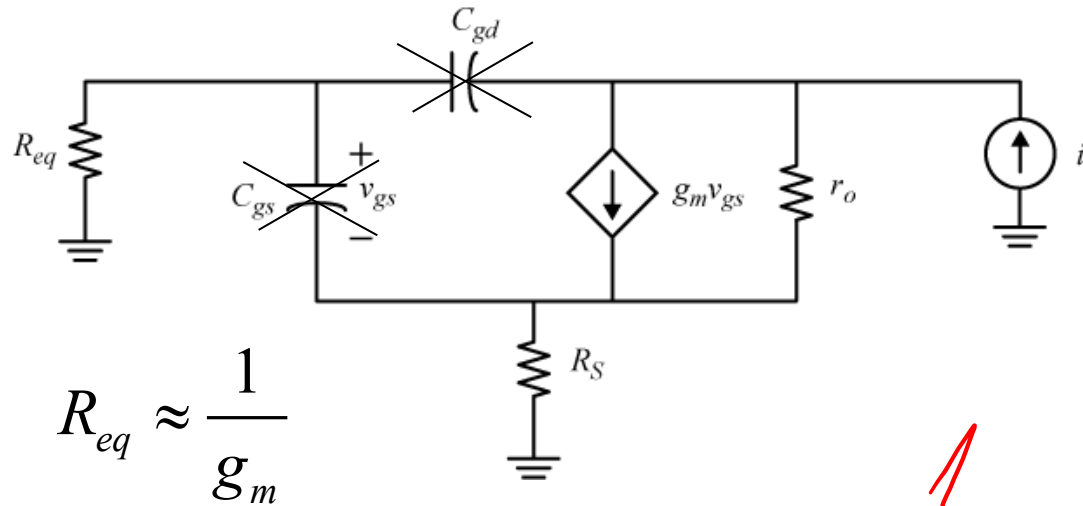

$$v_t = (i_t - g_m v_{gs}) r_o + v_{R_S}$$

$$v_{gs} \approx -v_{R_S}$$

$$v_{R_S} = i_t R_S$$


$$v_t = (i_t + g_m R_S i_t) r_o + i_t R_S$$

$$R_o = \frac{v_t}{i_t} \approx (1 + g_m R_S) r_o$$

- Equivalent resistance loading gate is dominated by the diode resistance ... assume this is a small impedance
- Output impedance is boosted by factor $(1 + g_m R_S)$

Improved Current Sources


How would you scale the output current?

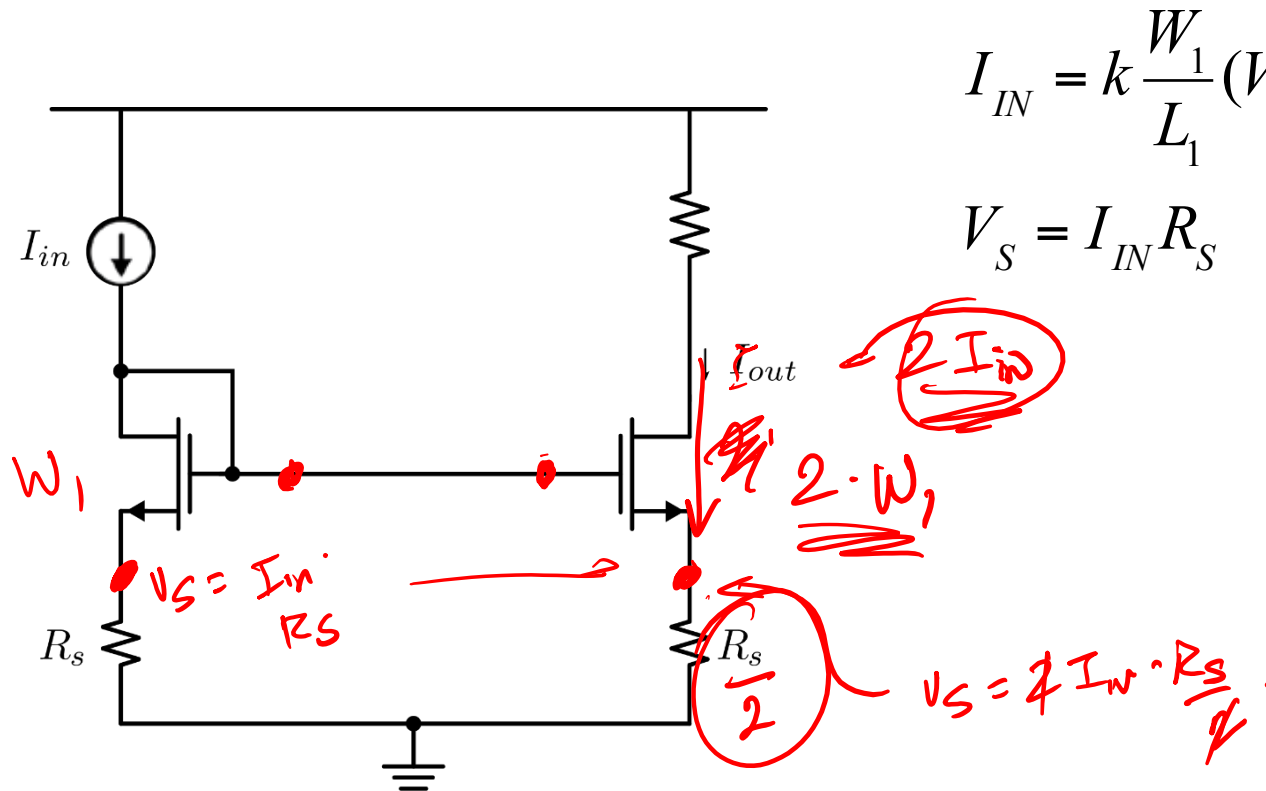

$$I_{IN} = k \frac{W_1}{L_1} (V_G - V_S - V_T)^2$$

$$V_S = I_{IN} R_S$$

Cascode (or Stacked) Current Source

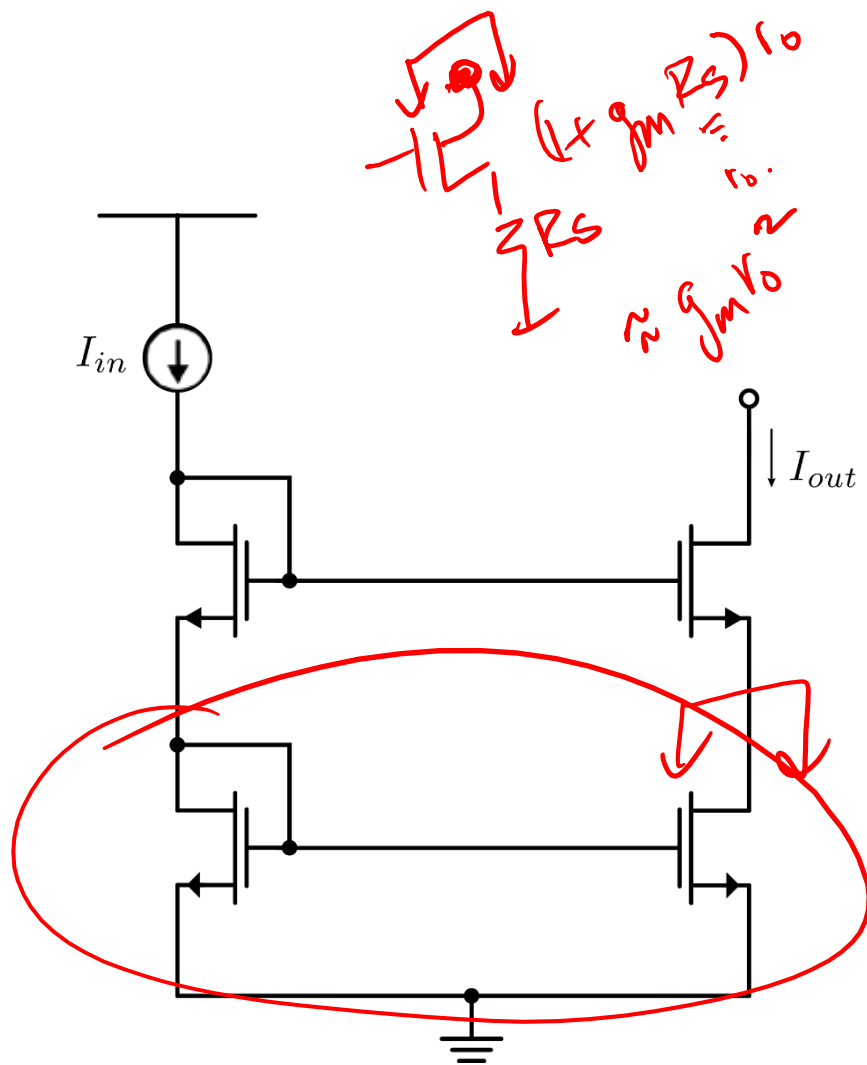

Insight: $V_{GS2} = \text{constant}$ AND $V_{DS2} = \text{constant}$

Small-Signal Resistance R_o :


$$R_o \approx (1 + g_m R_S) r_o$$

$$R_o \approx (1 + g_m r_o) r_o$$

$$R_o \approx g_m r_o^2 \gg r_o$$

Drawback of Cascode I-Source

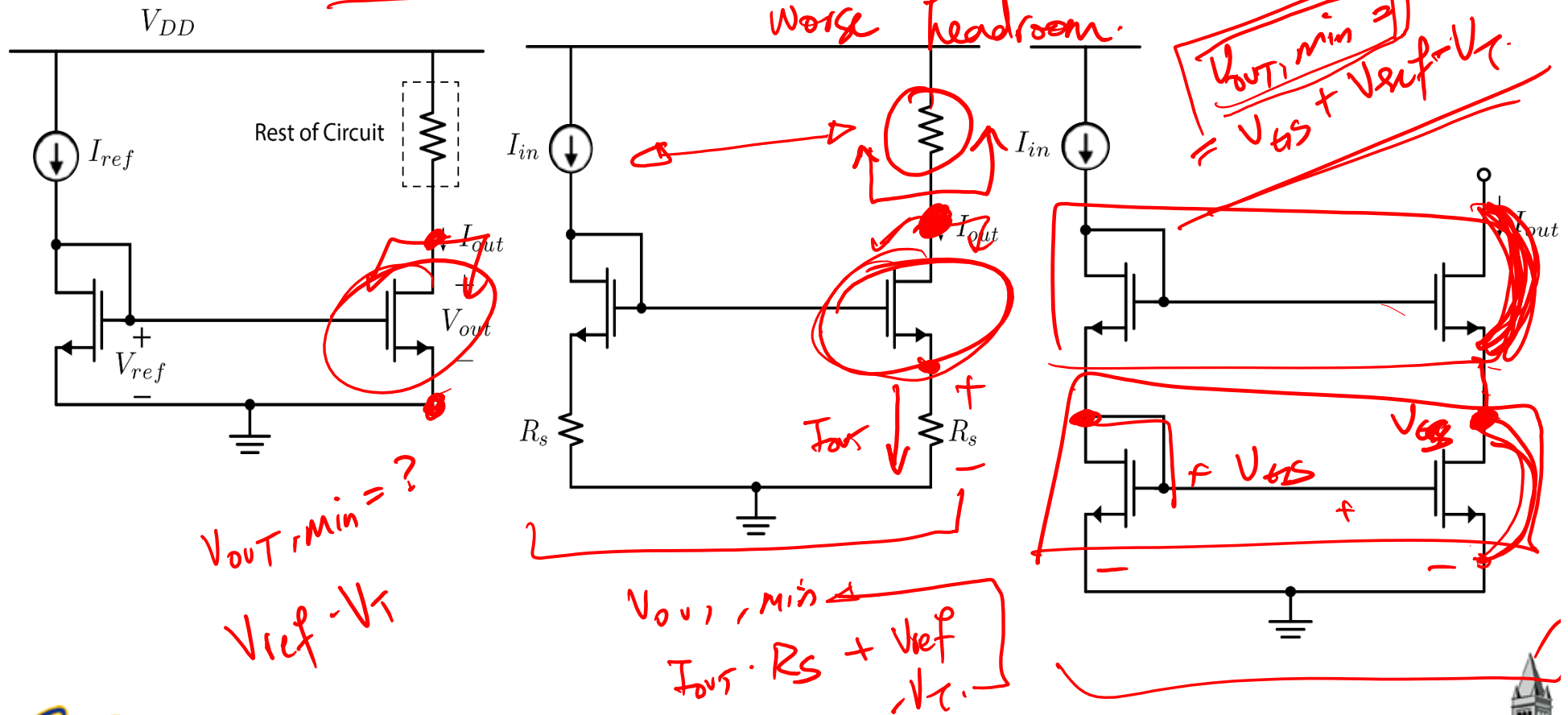What is the minimum output voltage to keep all transistors in saturation?





Drawback of Cascode /-Source

Minimum output voltage to keep both transistors in saturation:


$$V_{OUT,MIN} = V_{DS4,MIN} + V_{DS2,MIN}$$
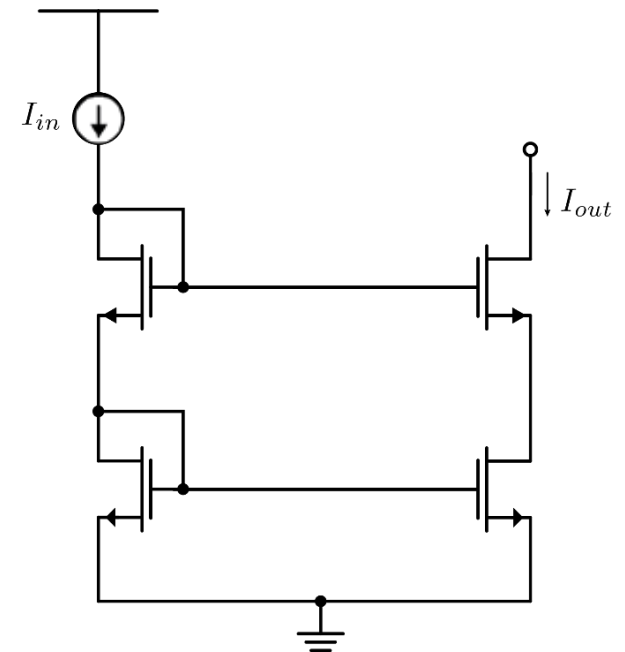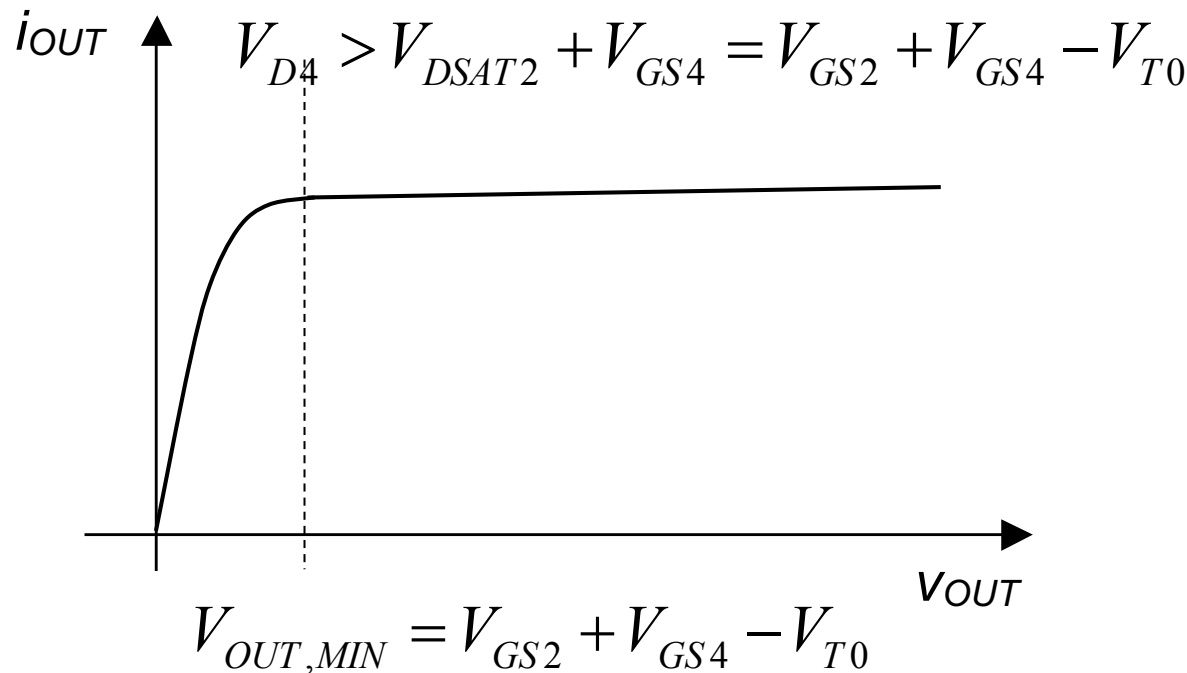
$$V_{DS2,MIN} > V_{GS2} - V_{T0} = V_{DSAT2}$$




Current Sinks and Sources

Sink: output current goes to ground

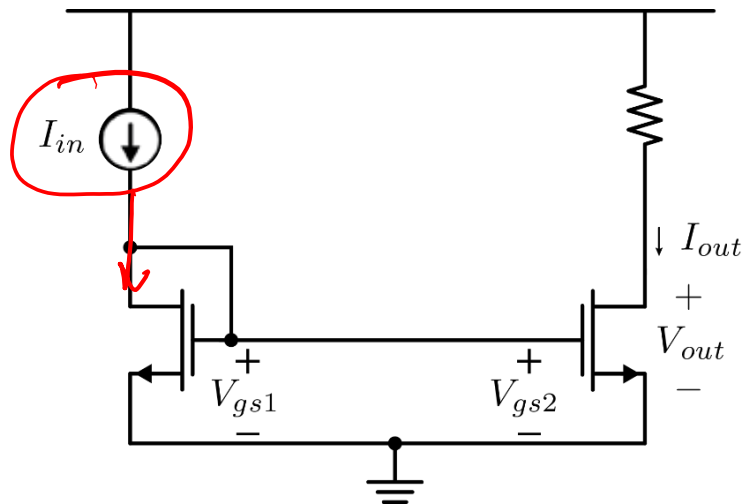


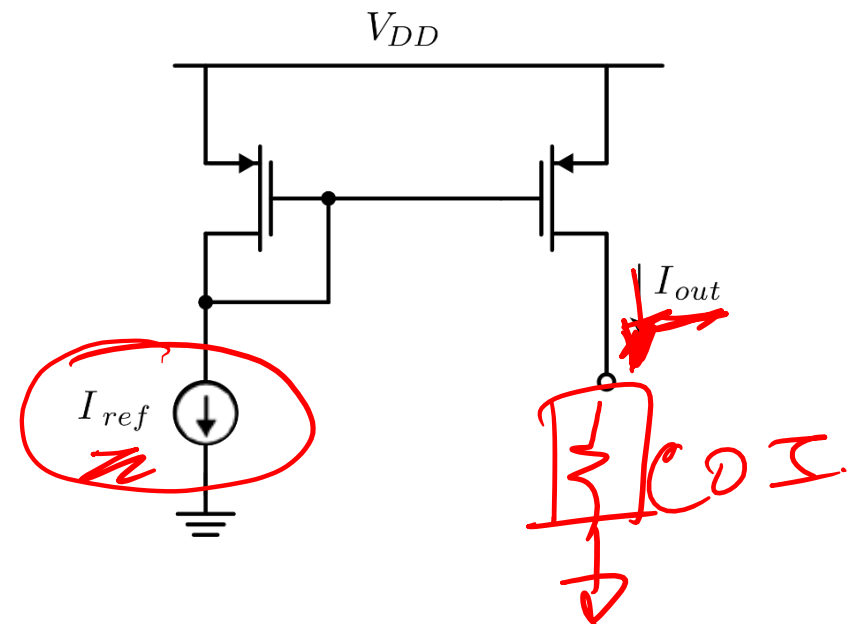Source: output current comes from voltage supply




Current Mirrors

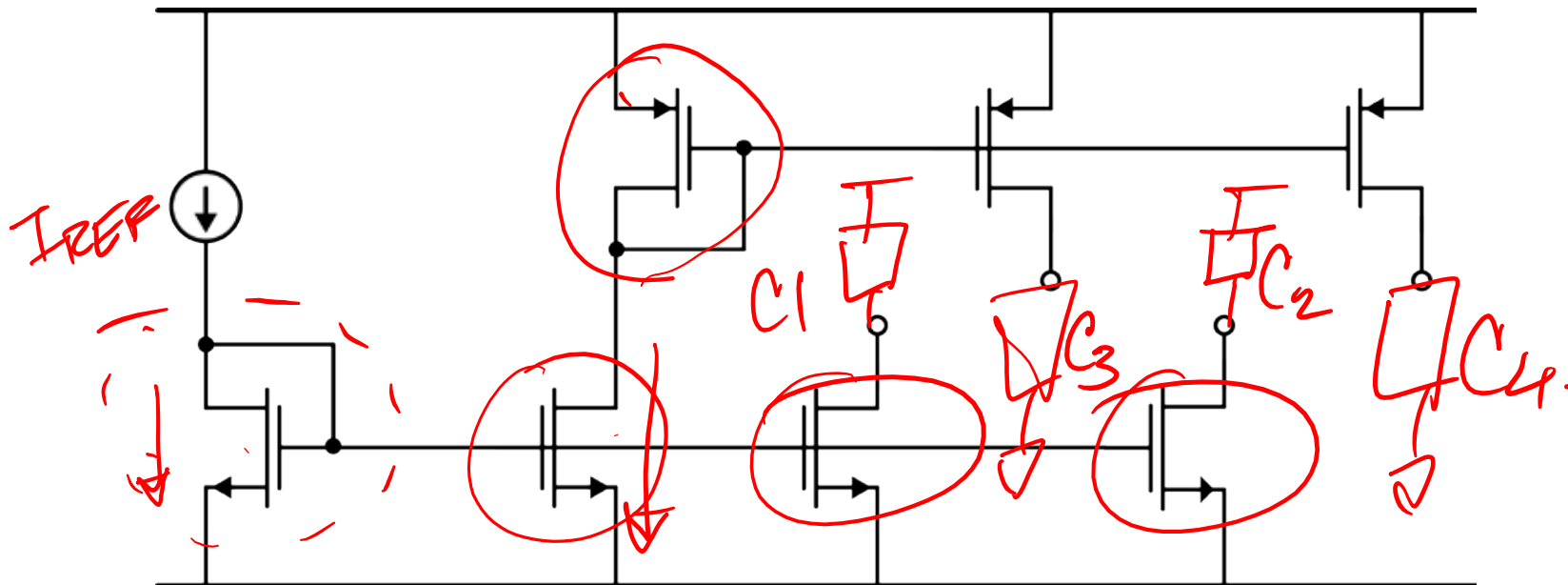
Idea: we only need one reference current to set up all the current sources and sinks needed for a multistage amplifier.



Example: Common-Drain Amplifier

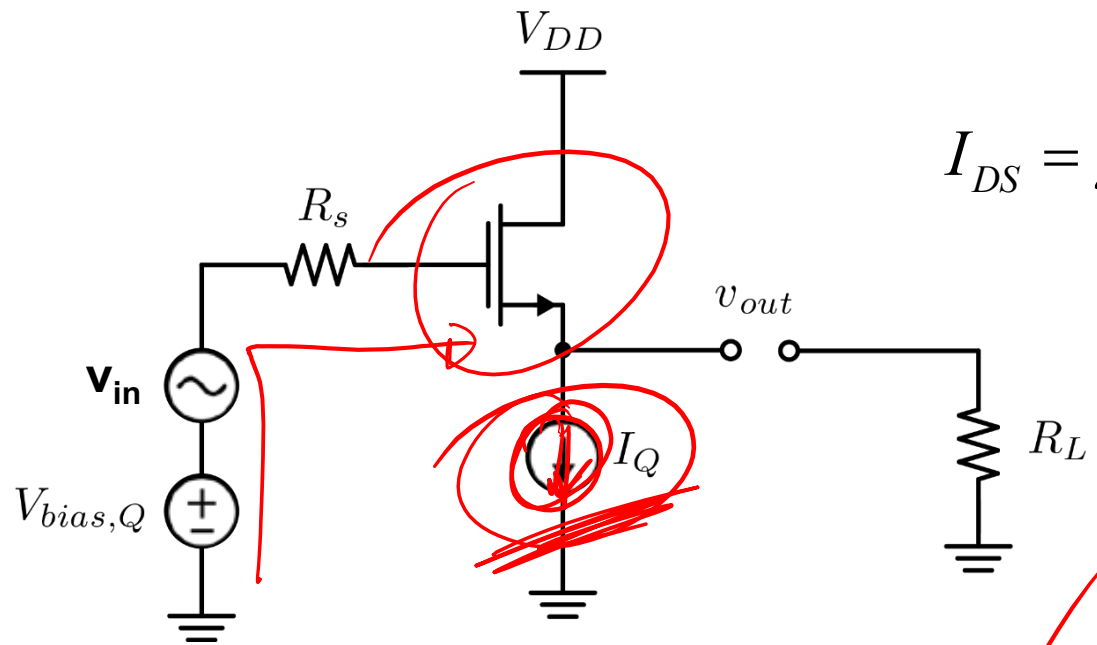

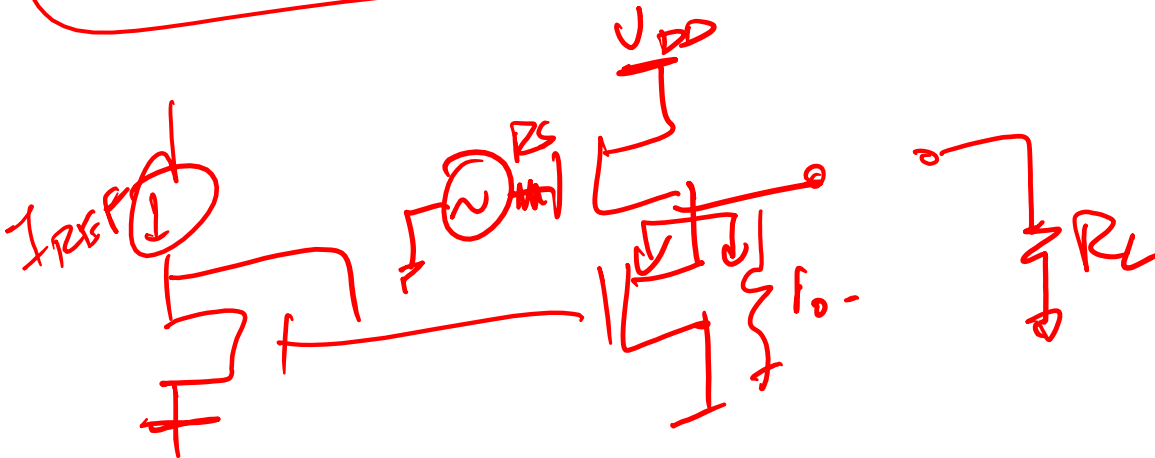
$$I_{DS} = \mu C_{ox} \frac{W}{L} \frac{1}{2} (V_{GS} - V_T)^2$$




Common Drain AC Schematic

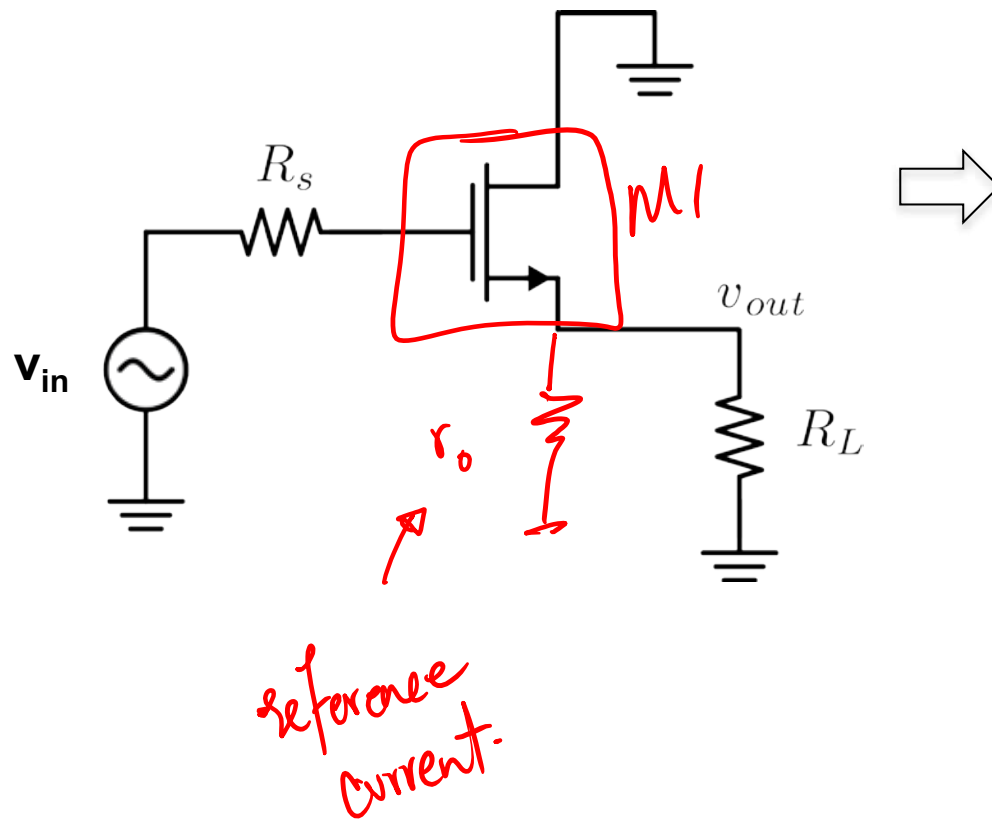How does a REAL current source fit in to the small-signal model?



CD Voltage Gain With Real I-Source

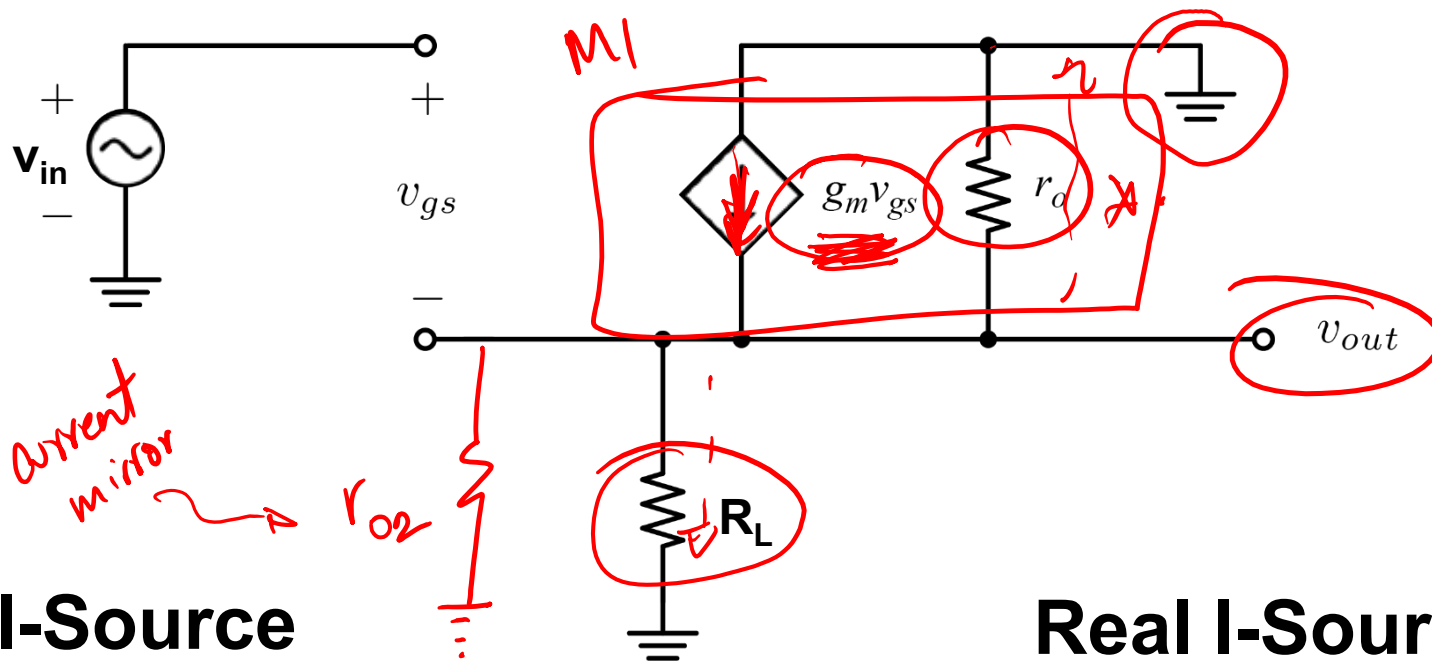

Ideal I-Source

Real I-Source


$$\frac{v_{out}}{R_L \parallel r_o} = g_m v_{gs}$$

$$v_{out} = g_m v_{gs} \cdot R_L \parallel r_o$$

$$\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out}) \cdot R_L \parallel r_o$$

$$v_{out} = g_m v_{gs} \cdot [R_L \parallel r_o \parallel r_{o2}]$$

CD Voltage Gain (Cont.)

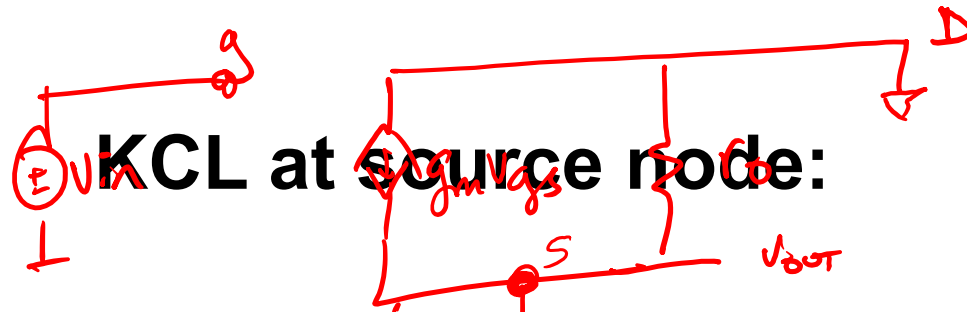

Current out. \rightarrow v_{o2}

Voltage gain: $\frac{v_{out}}{v_{in}} = \frac{g_m (v_{in} - v_{out})}{g_m + \frac{1}{R_L \parallel r_o \parallel r_{o2}}} = 0$

$\frac{v_{out}}{v_{in}} = \frac{g_m}{g_m + \frac{1}{R_L \parallel r_o \parallel r_{o2}}}$