

Lecture 20: Small-Signal Analysis

- Announcements:
- HW#6 online and due Friday Oct. 12 via Gradescope
- Lab#4 (the experimental part) online very soon
- I hear that those who did not have access to 125 Cory now have access
- Midterm 1 Exams coming back today
 - ↳ I will hand them out with solutions in the last 15 minutes
 - ↳ Will show you Z-scores on Wednesday

-
- Lecture Topics:
 - ↳ Small Signal Analysis
 - Linearizing Non-Linear Elements
 - DC and Small-Signal AC Components
 - Taylor Series Approximation


-
- Last Time:
 - Going through biasing for discrete MOS transistors
 - Now, continue with this ...

For practical amplification requirements: compromise:

- ① $V_{BB} \approx \frac{1}{3} V_{CC}$
 - ② $V_{CE} \approx \frac{1}{3} V_{CC}$
 - ③ $V_{R_E} = I_E R_E \approx \frac{1}{3} V_{CC}$
 - ④ $0.1 I_E < I_{BIAS} < I_E$
- } Good starting pt.
 ... but not rules!
 ↓
 must adjust for a given design

MOS Biasing

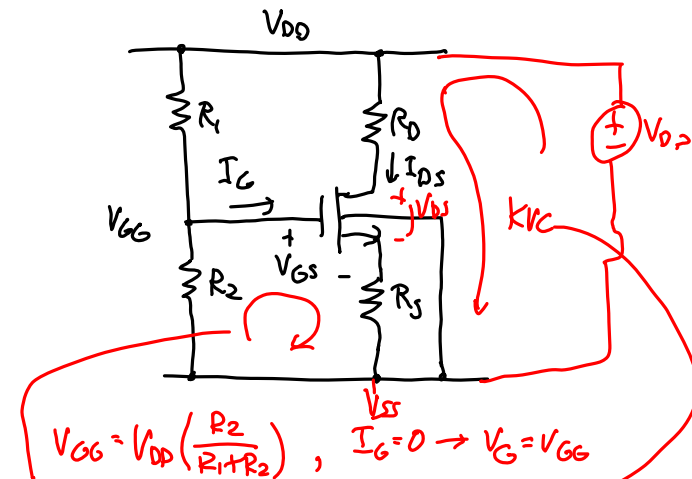⇒ can use a similar biasing strategy for discrete MOS ckt's.



$V_{GS} = V_{DD} \left(\frac{R_2}{R_1 + R_2} \right), I_G = 0 \rightarrow V_G = V_{GS}$

KVL: $V_{GS} = V_{GS} + I_{DS} R_S$ (2)

→ $V_{DD} = I_{DS} R_D + V_{DS} + I_{DS} R_S + V_{SS}$ (1)

To find the DC operating point: (by hand)

① Assume saturation:

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$\omega V_t = f(V_{SB}) = V_{t0} + \gamma (\sqrt{2\phi_f - V_{SB}} - \sqrt{2\phi_f})$$

$$\Rightarrow \text{using (2): } V_{GS} = V_{GS} + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 R_S \quad (3)$$

② Solve for V_{OS} assuming $V_t = V_{t0}$.

③ $V_S = V_{GS} - V_{GS} \rightarrow V_{SB} = V_S - V_{SS} \rightarrow$ find $V_t(V_{SB}) = V_t'$

④ Plug $V_t' = V_t(V_{SB})$ into (3) \rightarrow Get V_{GS}'

⑤ Back to ③ \rightarrow iterate to convergence

⋮

⑥ Check operating pt. \rightarrow saturated?

if yes \rightarrow done


if no \rightarrow assume linear & start over

\Rightarrow tedious, but effective for discrete (i.e., off-chip) MOS ckt.

\Rightarrow on-chip, we generally use current mirrors...

- For discrete (off-chip) circuits, avoid transistors
 - \hookrightarrow Discrete transistors are more expensive than discrete resistors
- For integrated (on-chip) circuits, avoid resistors
 - \hookrightarrow Resistors take up much more space than transistors, and space is money
 - \hookrightarrow Use lots of transistors and few if any resistors

Current Mirror \leftarrow for on-chip


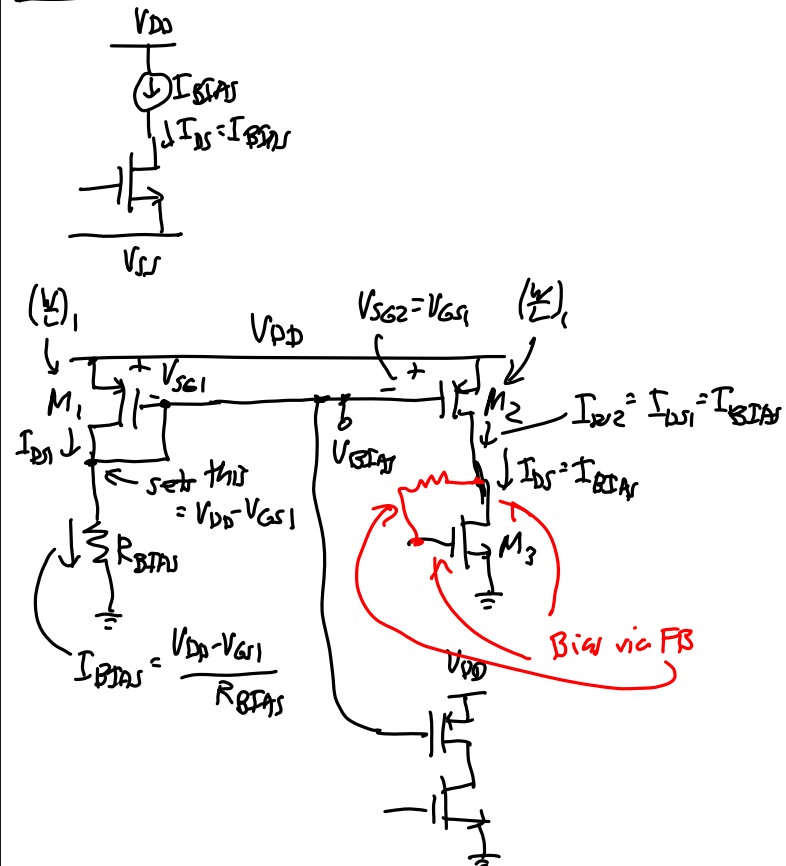


Small-Signal Analysis



- A method to solve nonlinear problems by linearizing them around a specific coordinate

→ Bias Pt.

Linear Resistor

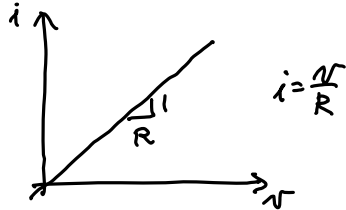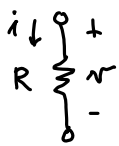


Non-linear Resistor

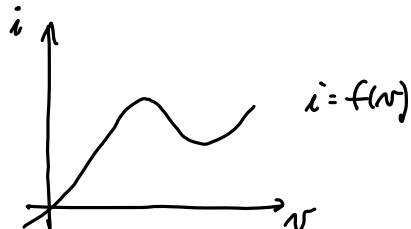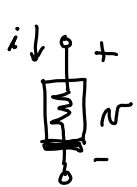

- As we've seen, transistors are nonlinear devices
- We've already experienced difficulty solving for DC operating points for nonlinear transistors
- So solving circuits with more complex inputs, e.g., sinusoids or sums of them, will become even more difficult
- Need some way to simplify these problems → Small-Signal Analysis
- Take a two-terminal nonlinear resistor circuit as an example:

Example. Two-Terminal Non-Linear Ckt.

⇒ First, look at a linear ckt:

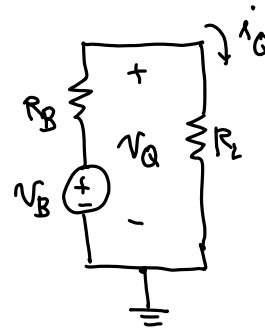


$$v_Q = v_B - i_Q R_B$$

$$v_Q = i_Q R_L$$

Solve two simultaneous linear equations:

$$v_Q = \left(\frac{R_L}{R_L + R_B} \right) v_B$$

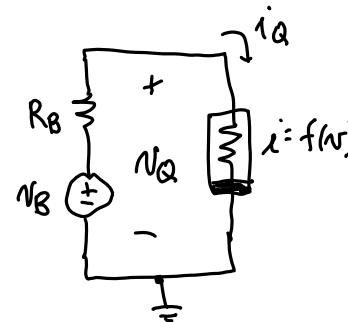⇒ With non-linear ckt., things become more difficult:



$$v_Q = v_B - i_Q R_B$$

$$i_Q = f(v_Q)$$

Must solve two simultaneous equations

$$v_Q = v_B - f(v_Q) R_B$$


Not easy to solve!

Generally, can't get into closed form.

$$\left[\text{e.g., } i = f(v) = 2v^2 + v^3 \rightarrow v_Q = v_B - (2v_Q^2 + v_Q^3) R_B \right]$$

- Need a convenient method to solve this nonlinear circuit, i.e., need some way to linearize it
- Such linearization is possible for analog circuits when the signals can break down into DC and small-signal AC components

Signal Nomenclature

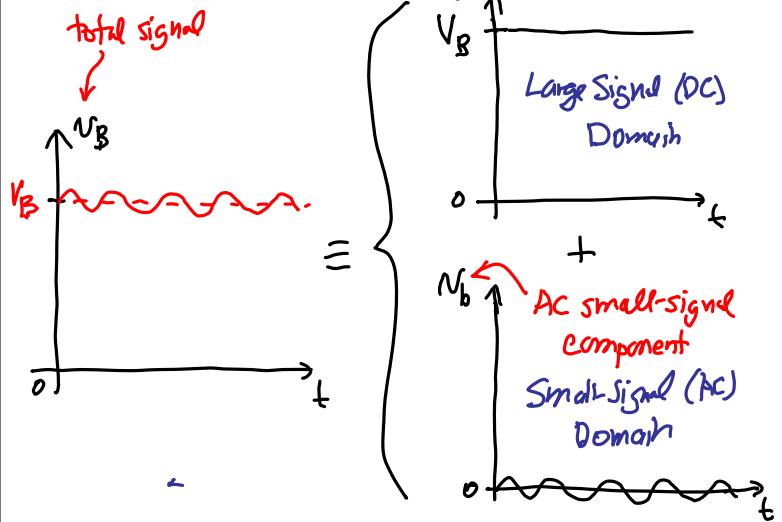


$v_B \triangleq V_B + n_b$
Total Signal
 lower case variable
 upper case subscript
 or
 upper case variable
 lower case subscript

DC Component
 upper case variable
 upper case subscript

AC Small-Signal
 lower case variable
 lower case subscript

Using this notation:

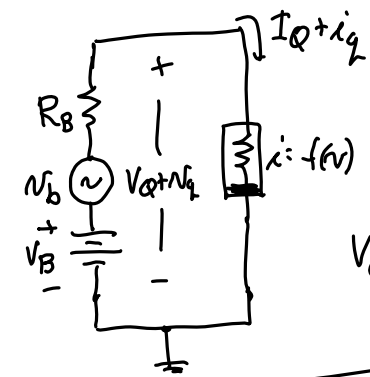

$$V_Q + n_q = V_B + n_b - f[V_Q + n_q] R_B$$

For this: Use Taylor Series approx. for $f(v)$ around $V = V_Q$.

Review Taylor Series:

⇒ function $f(x)$ can be approximated for points near $x=a$ by:

$$f(x) = f(a) + f'(a)(x-a) + \frac{f''(a)}{2!}(x-a)^2 + \dots + \frac{f^{(n)}(a)}{n!}(x-a)^n + \dots$$

1st derivative: $\left. \frac{df}{dx} \right|_{x=a}$

$\approx f(a) + f'(a)(x-a)$ for $(x-a) = \text{small}$
 linear! easy to solve!
 total signal = bias point + small-signal

$$V_Q + n_q = V_B + n_b - f[V_Q] R_B - f'(V_Q) n_q R_B$$

$$V_Q + N_Q = V_B + N_B - I_Q R_B - \frac{R_B}{R_{SS}} N_Q$$

↑

Evaluate
nonlinear fn
 $I_Q = f(V_Q)$

↑

$$R_{SS} = \frac{1}{\frac{\partial f}{\partial V_Q}} = \text{Small-signal resistance}$$