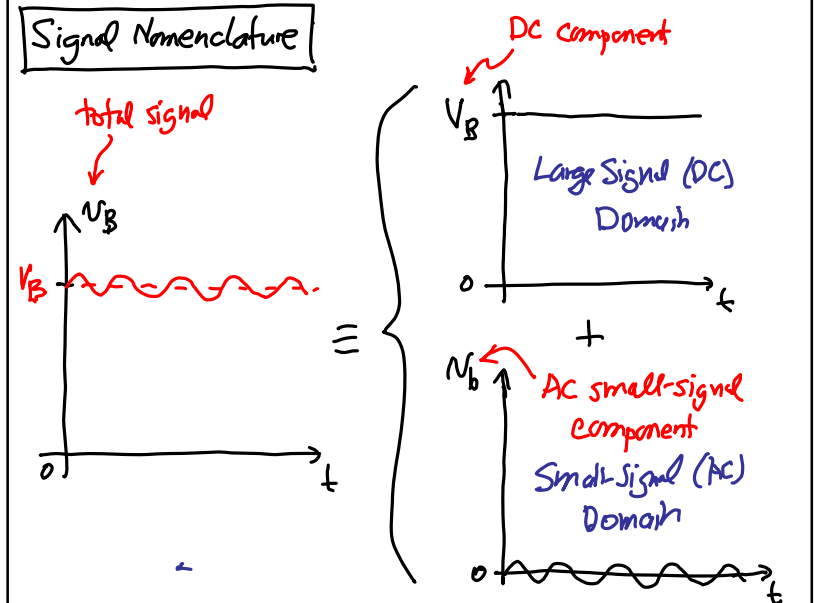


Lecture 21: Transistors As Amplifiers

- Announcements:
- HW#6 online and due Friday Oct. 12 via Gradescope
- Passed Midterm 1 Exams with solutions handed back last time
  - ↳ Remaining midterms coming back in lab section
  - ↳ Will discuss grading next time
- Lab#5 online (this is your first project)
  - ↳ Due Tuesday, Oct. 30, 5 p.m.
- 
- Lecture Topics:
  - ↳ Small Signal Analysis
    - Linearizing Non-Linear Elements
    - DC and Small-Signal AC Components
    - Taylor Series Approximation
  - ↳ Transistors As Amplifiers
  - ↳ Small-Signal Model for the BJT
- 
- Last Time:
- Discussing how Taylor series leads to the small-signal method for solving nonlinear problems
- Now, continue with this ...

- Need a convenient method to solve this nonlinear circuit, i.e., need some way to linearize it
- Such linearization is possible for analog circuits when the signals can break down into DC and small-signal AC components




$$V_B \cong V_B + v_b$$

Total Signal  
 lower case variable  
 upper case subscript  
 or  
 upper case variable  
 lower case subscript

DC Component  
 upper case variable  
 upper case subscript

AC Small-Signal  
 lower case variable  
 lower case subscript

Using this notation:

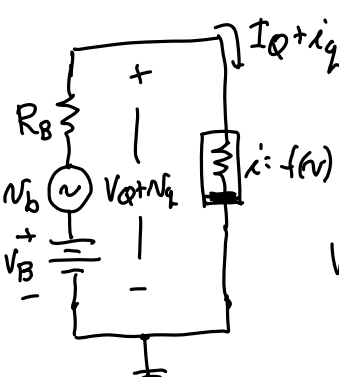

$$V_Q + N_q = V_B + N_b - f[V_Q + N_q] R_B$$

For this: Use Taylor Series approx. for  $f(v)$  around  $v = V_Q$ .

Review Taylor Series:

⇒ function  $f(x)$  can be approximated for points near  $x=a$  by:

$$f(x) = f(a) + f'(a)(x-a) + \frac{f''(a)}{2!}(x-a)^2 + \dots + \frac{f^{(n)}(a)}{n!}(x-a)^n + \dots$$

1st derivative:  $\frac{df}{dx} \Big|_{x=a}$   $\left\{ \frac{di}{dv} \Big|_{v=V_Q} \right\}$  *Small-signal*

≈  $f(a) + f'(a)(x-a)$  for  $(x-a) = \text{small}$

linear! easy to solve!

total signal bias point

$$V_Q + N_q = V_B + N_b - f[V_Q] R_B - f'(V_Q) N_q R_B$$


$$V_Q + N_q = V_B + N_b - \frac{I_Q R_B}{\pi} - \frac{R_B N_q}{R_{SS} \pi}$$

Evaluate nonlinear fn  $I_Q = f(V_Q)$

$$R_{SS} = \frac{1}{\frac{df}{dv} \Big|_{V_Q}} = \Delta \text{ Small-signal resistance}$$

⇒ can split this into equations → two ckt.

DC Components:  $V_Q = V_B - I_Q R_B$

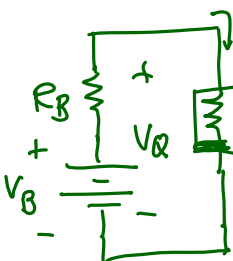


DC Circuit

must deal w a nonlinear calculation ... but only one!

Want:  $(V_Q, I_Q)$  operating pt.


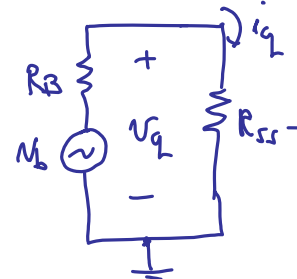
Small-Signal AC Components:  $N_q = N_b - \frac{R_B N_q}{R_{SS}} \leftarrow \text{linear!}$



Small-Signal Ckt.


All linear analysis!

$$R_{SS} = \frac{1}{\frac{df}{dv} \Big|_{V_Q}}$$

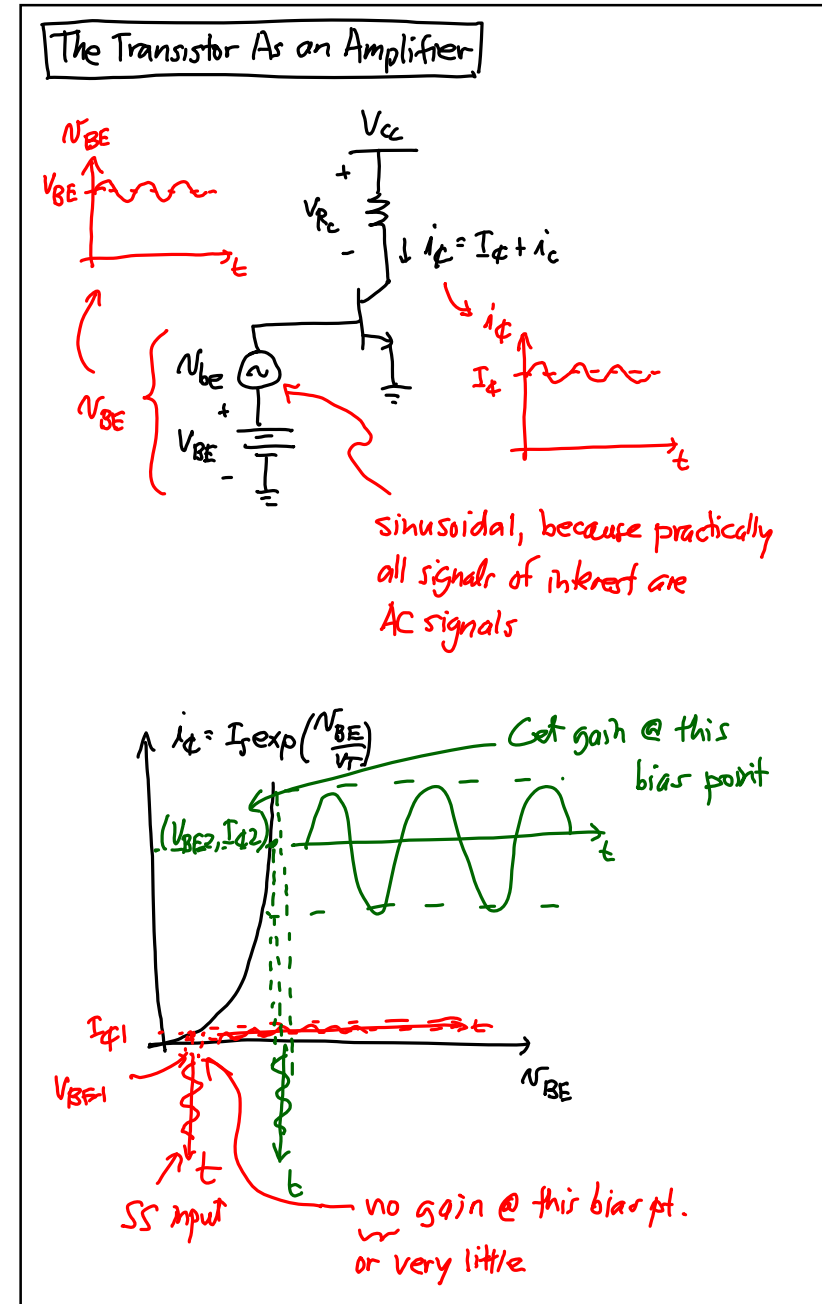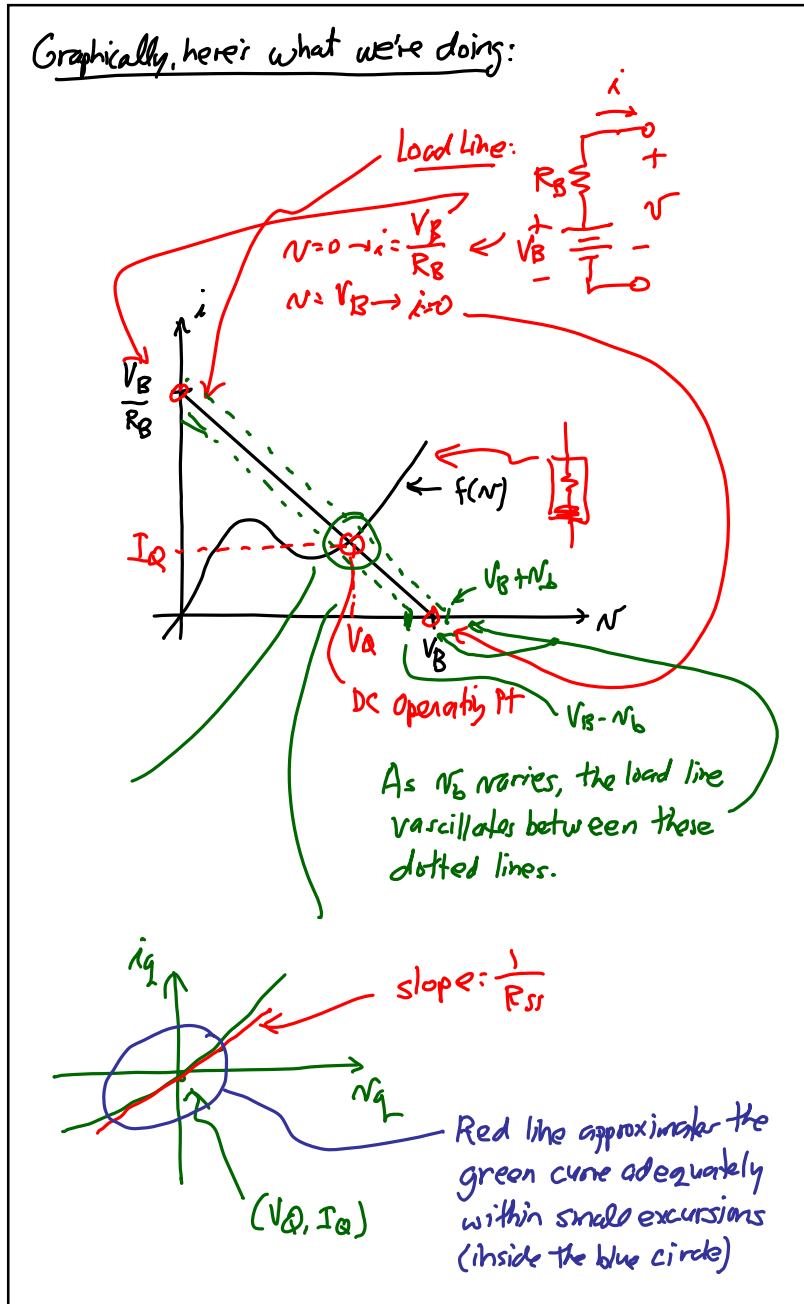

- So far, we have shown how to obtain the small-signal circuit model for a two-terminal nonlinear resistor
- How about for three-terminal transistors?
- Look back to our general amplifier networks
- Any of the networks apply ... but the most popular one is the y-parameter model:



Y-Parameter Model

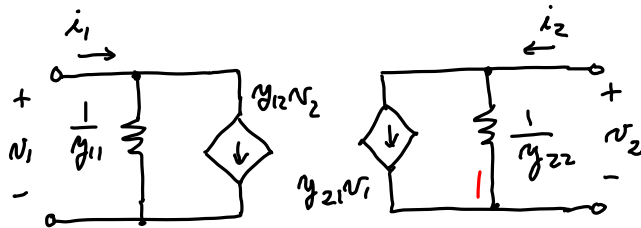

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} \quad y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

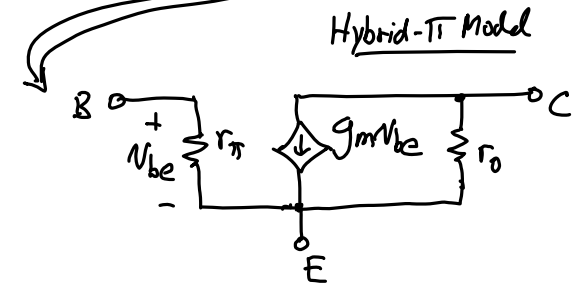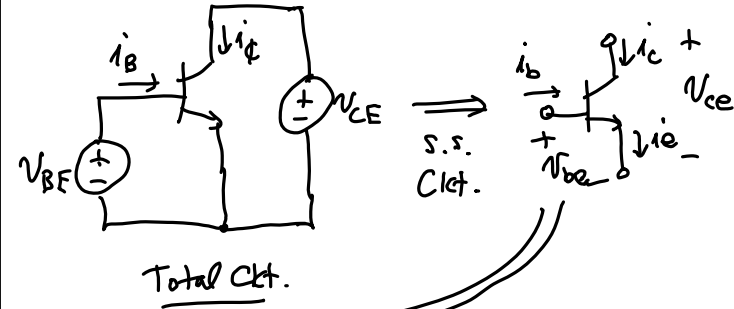Small-Signal Models for Forward-Active BJTs



$$\left. \begin{aligned} v_{be} \uparrow \rightarrow i_b \uparrow &\Rightarrow r_{\pi} = \frac{v_{be}}{i_b} \\ v_{be} \uparrow \rightarrow i_c \uparrow &\Rightarrow g_m = \frac{i_c}{v_{be}} \\ v_{ce} \uparrow \rightarrow i_c \uparrow &\Rightarrow r_o = \frac{v_{ce}}{i_c} \end{aligned} \right\} \text{Each of these determined by the bias pt.}$$