

Lecture 22: Small-Signal Modeling

- Announcements:
- HW#7 online
- Lab#5 online (this is your first project)
 - ↳ Due Tuesday, Oct. 30, 5 p.m.
- Z scores today (at end of class)



 • Lecture Topics:

- ↳ Hybrid- π Model for the npn BJT
- ↳ T Model
- ↳ Pnp Transistor Hybrid- π Model
- ↳ Saturated NMOS Hybrid- π Model

 • Last Time:

- Introduced the BJT Hybrid- π Model
- Now, continue by deriving its elements ...

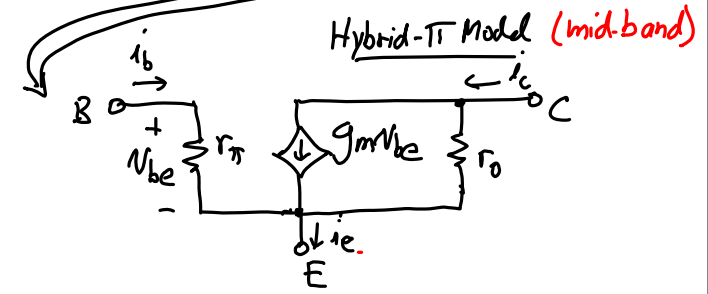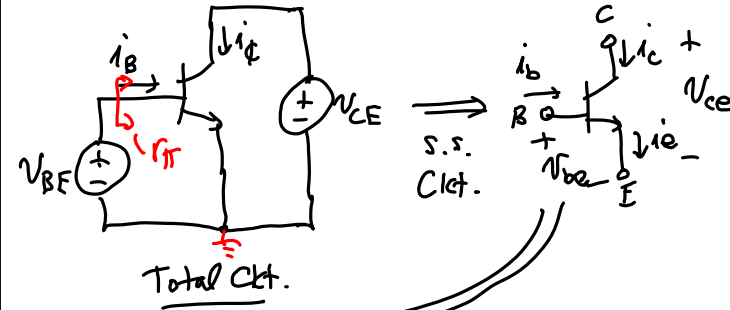Small-Signal Models for Forward-Active BJTs



$$\begin{aligned}
 V_{be} \uparrow &\rightarrow i_b \uparrow \Rightarrow r_{\pi} = \frac{V_{be}}{i_b} \\
 V_{be} \uparrow &\rightarrow i_c \uparrow \Rightarrow g_m = \frac{i_c}{V_{be}} \\
 V_{ce} \uparrow &\rightarrow i_c \uparrow \Rightarrow r_o = \frac{V_{ce}}{i_c}
 \end{aligned}
 \left. \vphantom{\begin{aligned} V_{be} \uparrow &\rightarrow i_b \uparrow \\ V_{be} \uparrow &\rightarrow i_c \uparrow \\ V_{ce} \uparrow &\rightarrow i_c \uparrow \end{aligned}} \right\} \text{Each of these determined by the bias pt.}$$

Determine the Small-Signal Elements

$g_m = \frac{i_c}{v_{be}}$

$i_Q = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$

$I_Q + i_c = I_S \exp\left(\frac{v_{BE}}{V_T}\right) \exp\left(\frac{v_{be}}{V_T}\right)$

$= I_Q \exp\left(\frac{v_{be}}{V_T}\right)$

large signal DC collector current

$v_{BE} = V_{BE} + v_{be}$

For $v_{be} \ll V_T$, can use Taylor series approximation:
 $e^x \approx 1 + x$ for small x

$I_Q + i_c = I_Q \left(1 + \frac{v_{be}}{V_T}\right) = I_Q + \frac{I_Q}{V_T} v_{be}$

This is the condition that should be satisfied to have a "small-signal"

$\frac{i_c}{v_{be}} = g_m = \frac{I_Q}{V_T}$ ← fn. of I_Q
comes from the DC operating pt. (Q-pt.) ← quiescent

Typical: $I_Q = 1 \text{ mA}$

$g_m = \frac{1 \text{ mA}}{25 \text{ mV}} = 0.04 \text{ } \Omega^{-1}$

$r_{\pi} = \frac{v_{be}}{i_b}$

$r_{\pi} = \frac{v_{be}}{i_b}$

$r_{\pi} = \frac{v_{be}}{i_b} = \frac{v_{be}}{\frac{i_c}{\beta}} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_Q}{V_T}} = r_{\pi}$

again, for a DC operating pt.

Typical: $\beta = 100$
 $r_{\pi} = \frac{100}{0.04} = 2.5 \text{ k}\Omega$

$r_o = \frac{v_{ce}}{i_c}$

$r_o = \frac{v_{ce}}{i_c}$

$$i_{\phi} = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$


$$r_o = \left[\frac{\partial i_{\phi}}{\partial V_{CE}} \bigg|_{Q_{pt.}} \right]^{-1} = \left[I_s \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \bigg|_{V_{BE}=V_{BE}} \right]^{-1}$$

I_{ϕ}

$r_o = \frac{V_A}{I_{\phi}}$

Typical: $V_A = 100V$
 $r_o = \frac{100}{1m} = 100k\Omega$
 Large, so often we neglect!

Hybrid- π Model Summary (for npn BJT)

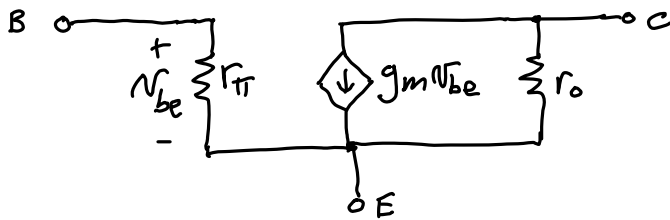

$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$


$$g_m = \frac{I_{\phi}}{V_T}$$

$$r_o = \frac{V_A}{I_{\phi}}$$

Remarks:

- g_m is independent of device specifics, i.e., β , I_s
- Depends only on temperature (via V_T) and biasing (I_C)
- Small-signal model valid for $v_{be} \ll V_T$

What about emitter resistance?

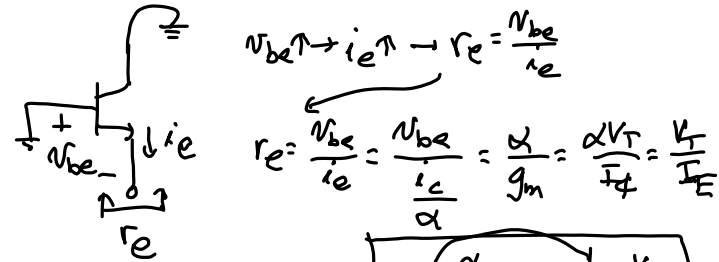


$$r_e = \frac{v_{be}}{i_e} = \frac{v_{be}}{i_c} = \frac{v_{be}}{g_m v_{be}} = \frac{1}{g_m} = \frac{V_T}{I_E}$$

$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_E}$

Why is this not included in the hybrid- π model?

↳ well... it is!

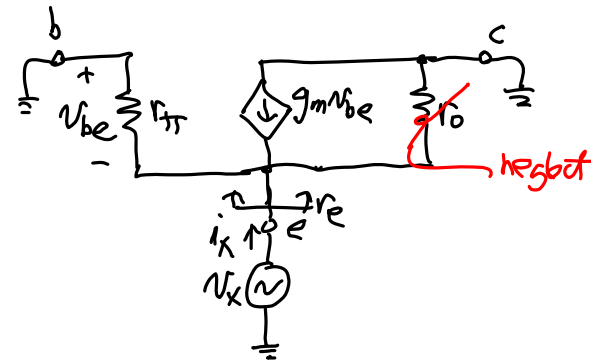

$$i_x = -\frac{v_{be}}{r_{\pi}} - g_m v_{be}$$


$$(v_x = -v_{be}) \Rightarrow i_x = v_x \left(\frac{1}{r_{\pi}} + g_m \right)$$

$$r_e = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_{\pi}} + g_m} = \frac{r_{\pi}}{1 + g_m r_{\pi}} = \frac{r_{\pi}}{1 + \beta} = \frac{\beta}{g_m(1 + \beta)}$$

$$r_e = \frac{\alpha}{g_m} \checkmark$$

- To explicitly show the emitter resistance in the small-signal model, use the T-model:

T-Model (Common Base Model)

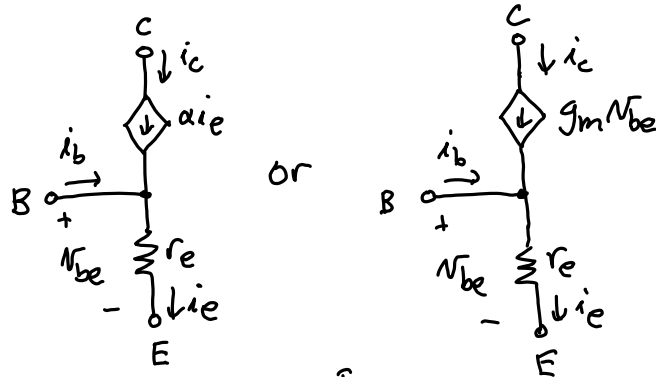

where (as before): $g_m = \frac{I_E}{V_T}$
 $r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$