
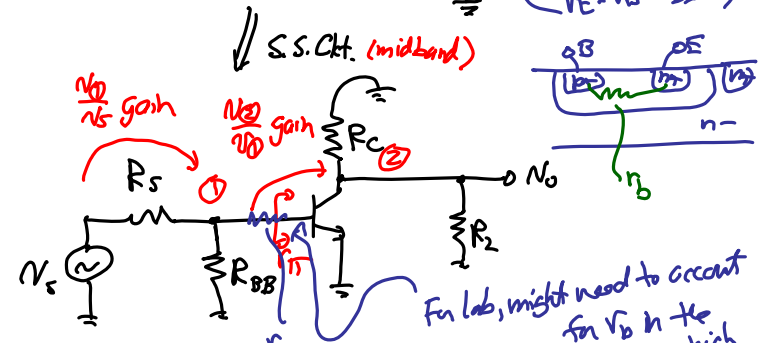


Lecture 28: Inspection Analysis & Miller Effect

- **Announcements:**
- HW#9 online and due Friday via Gradescope
- Extend Lab#5 due date by one week
 ↳ Now due Tuesday, Nov. 6, 5 p.m.
- Hopefully, you watched Monday's video lecture
- -----
- **Lecture Topics:**
- ↳ Intro. to Inspection Analysis
- ↳ C.E. Design Project Hints
- ↳ Other Amplifier Configurations
- ↳ Generally-Loaded Transistor
- -----
- **Last Time:**
- Started introduction to inspection analysis
- Now continue with this ...

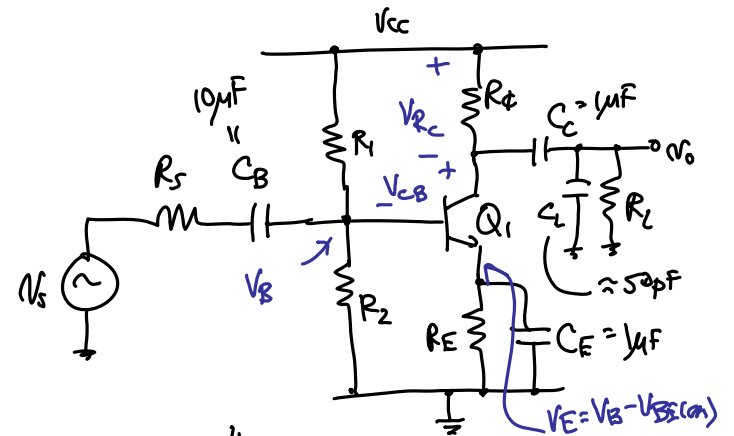Intro. to Inspection Analysis (w/ Lab#5 hints)





⇒ get gains from node-to-node, then combine. high freq.
 ⇒ account for load resistance for each gain calculation for each stage

1st Stage:

$$\frac{V_{(1)}}{V_s} = \frac{r_{\pi} || R_{BB}}{R_s + r_{\pi} || R_{BB}}$$

Hybrid- π model

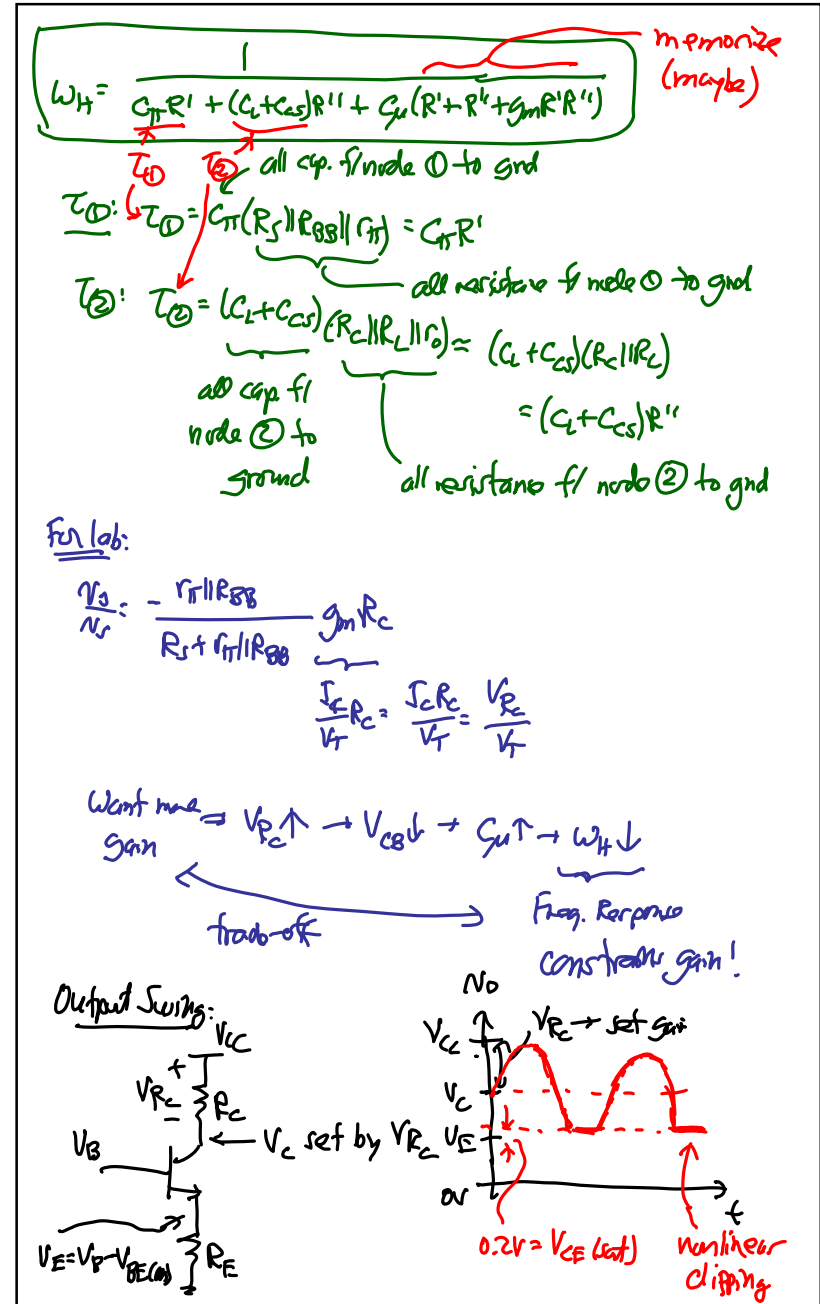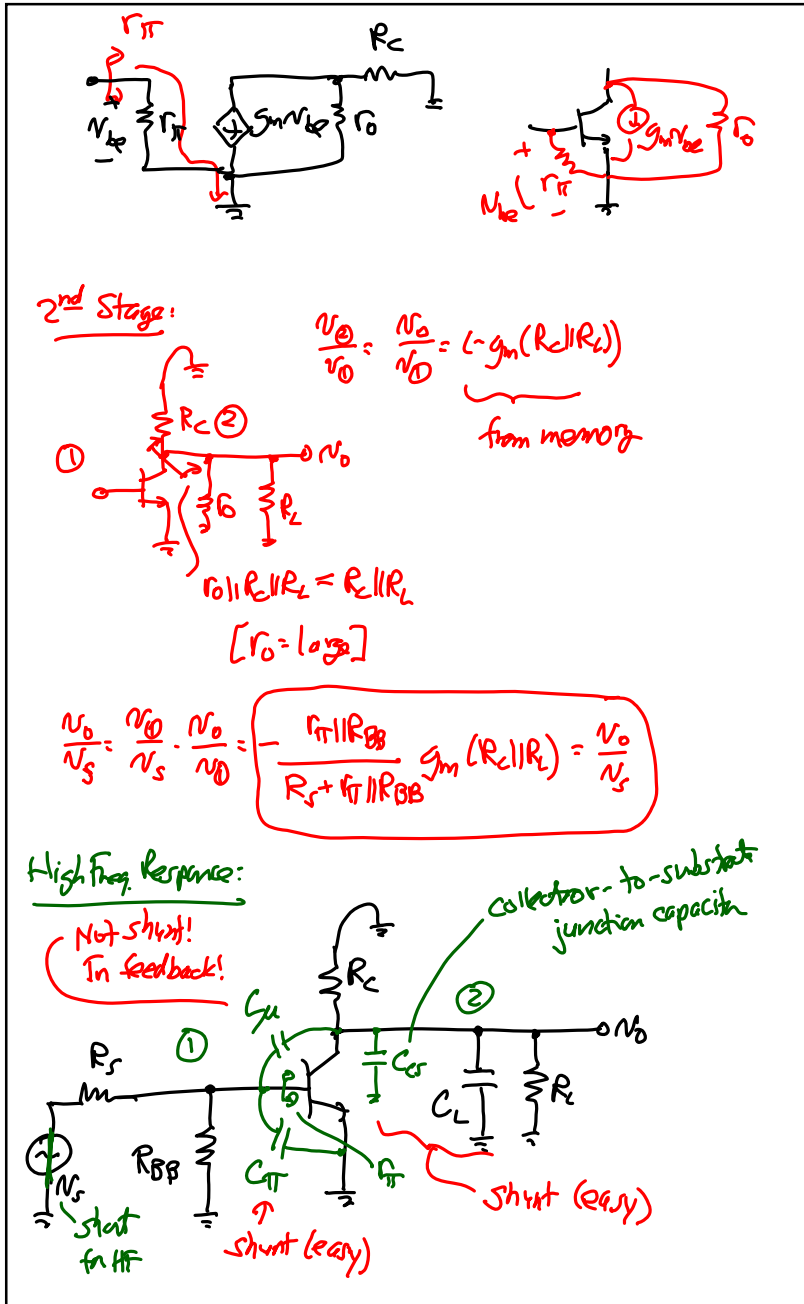

The Miller Effect

⇒ useful to transform a ckt. w/ feedback into a simpler ckt. w/ feedback

Formal Derivation - $k = \text{gain}$

Find Y_1 : (equate i_1 for both ckt.)

(original)	(Miller)
$i_1 = Y(N_1 - N_2)$	$i_1 = Y_1 N_1$
$= Y(N_1 - kN_1)$	$Y_1 = Y(1-k)$
$= Y(1-k)N_1$	

Find Y_2 : (equate i_2 for both ckt.)

(original)	(Miller)
$i_2 = (N_2 - N_1)Y$	$i_2 = Y_2 N_2$
$[N_1 = \frac{1}{k}N_2] \rightarrow = (N_2 - \frac{1}{k}N_2)Y$	$Y_2 = Y(1 - \frac{1}{k})$
$= (1 - \frac{1}{k})Y N_2$	

⇒ no longer have FB → easy... $C_M(1 - \frac{1}{k}) = C_M$
BTG

C.F. Inspection Analysis for HF Using the Miller Effect

Miller X-form

gain = $-g_m(R_C || R_L)$

$C_M = C_{CE}(1 + g_m(R_C || R_L))$

$C_{M2} = C_{CB}$

$\tau_D = [C_M + C_{CE}(1 + \frac{g_m(R_C || R_L)}{R_i})](R_S || R_B || R_i)$

$\tau_C = \frac{C_L + C_{CS} + C_M}{R_C || R_L}$

$\omega_H = \frac{1}{\tau_D + \tau_C}$

→ All terms from previous analysis captured here!
 (same answer... no need to deal w/ FB)